

P.No 1 :-

Name : Hazrat Bilal

ID : 14622

Paper : Electronic Circuit Design


Instructor : Sir Mujtaba Ihsan

Dep : BE (E)

Marks :- 30

101

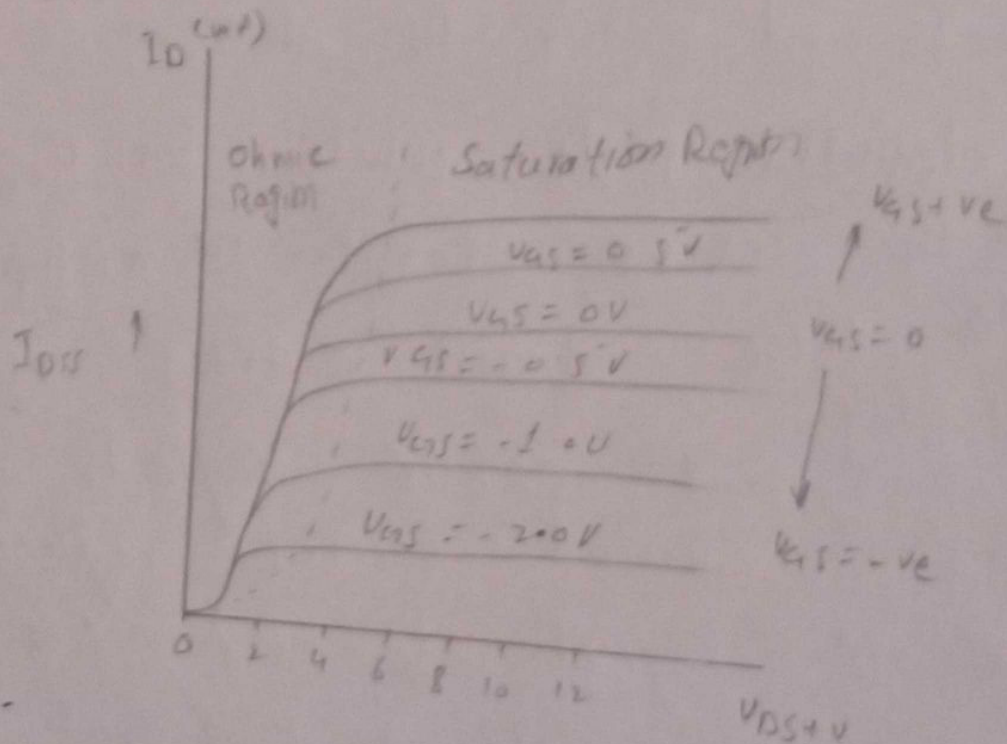a) :- Explain the drain characteristic curve of D.MOSFET given below.



Solution :-

Explanation of characteristics curve of D.MOSFET:-

Typical drain characteristics for various levels of gate-source voltage of an N-channel MOSFET are shown in the fig. The upper curve are for positive V_{GS} and the lower curve are for negative V_{GS} . The bottom drain curve is for $V_{GS} = V_{GS(OFF)}$. For a specified drain-source voltage V_{DS} , $V_{GS(OFF)}$ is the gate-source voltage at which drain current reduce

P. No 3
to a certain specified negligibly small value as shown in fig.

This voltage corresponds to the pinch off voltage V_p of JFET. For V_{GS} between $V_{GS(DEF)}$ and zero, the device operates in depletion-mode while for V_{GS} exceeding zero the device operates in enhancement mode. These drain curves again display an ohmic region, a constant-current source region and cut-off region. MOSFET has two major applications a constant current source and a voltage variable source.


Q No 2:-

b):- Sketch the hybrid model and write equation for the transistor in common emitter configuration.

Answer:- The hybrid model is a popular circuit model used for analyzing the small signal behavior of bipolar junction


and field effect transistor. Sometime it is also called Giacoleto model because it was introduced by L.J. Giacoleto in 1969.

Sketch is below:-

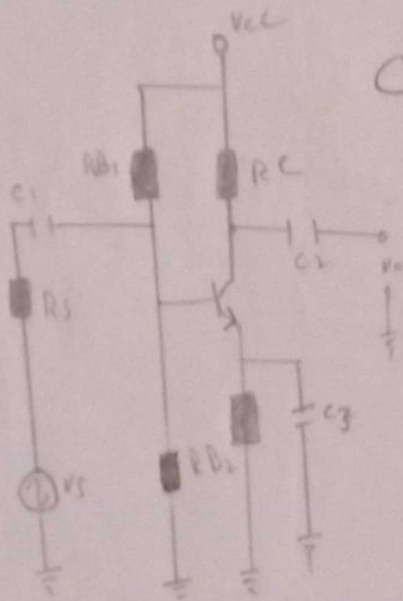

Common Emitter

Equivalent Circuit

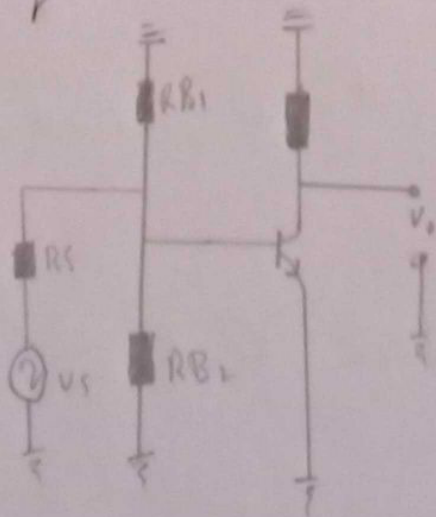

The hybrid model is suitable for small signals at mid band and describes the action of the transistor

P. No 5:

Two equations can be derived from circuit diagram, one for input voltage V_{be} and one for the output I_c .

$$V_{be} = h_{ie} i_b + h_{re} v_{ce}$$

$$I_c = h_{fe} i_b + h_{oc} v_{ce}$$

if i_b is held constant ($i_b = 0$) then h_{re} and h_{oe} can be solved:

$$h_{re} = V_{be} / V_{ce} | i_b = 0$$

$$h_{oe} = I_c / V_{ce} | i_b = 0$$

Also if v_{ce} is held constant ($v_{ce} = 0$) that h_{ie} and h_{fe} can be solved.

$$h_{ie} = V_{be} / i_b | v_{ce} = 0$$

$$h_{fe} = I_c / i_b | v_{ce} = 0$$

Q2:- A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. Evaluate the CMRR & express it in decibels.

S&T:- Given.

$$\text{differential voltage gain} = 400,000$$

$$\text{common mode gain} = 0.6$$

Required:

$$\text{CMRR} = ?$$

Formula

$$\Rightarrow \text{CMRR} = \frac{\text{voltage gain}}{\text{common mode gain}}$$

$$\text{CMRR} = \frac{400000}{0.6}$$

$$\text{CMRR} = 666666.66$$

Now in decibels

by formula

$$CMRR = 20 \log (666666.6)$$

$$CMRR = 116.47 \text{ decibels}$$

Q No 3

a):- Explain the concept behind negative feedback in operational amplifiers.

Answer:-

Negative feedback :-

Negative feedback


is the process of feeding back a fraction of the output signal back to the input but to make the feedback negative, we must feed it back to the negative or inverting input terminal of the op-amp using an external feedback resistor called R_f . This connection between the

P.No 8


output and the inverting input terminal forces the differential input voltage towards zero

Inverting input effectively moves the feedback signal 180 deg of phase with the input signal

Diagram:-

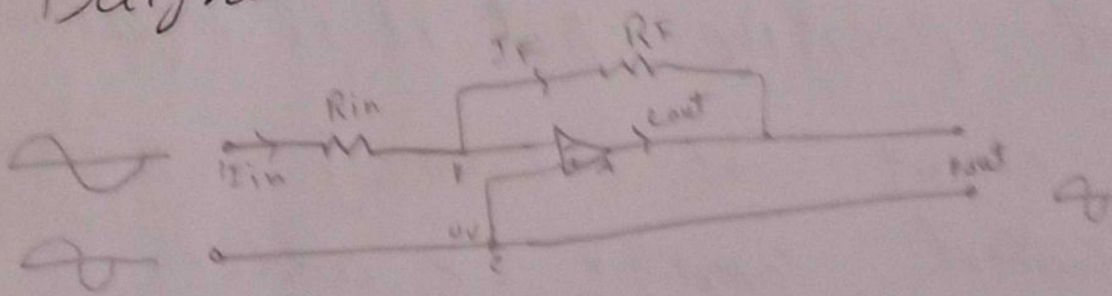

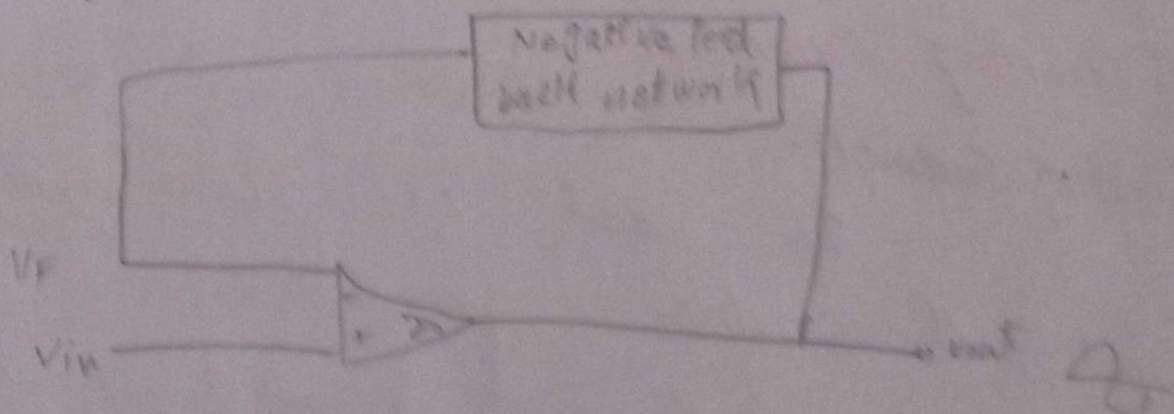The inverting operational amplifier configuration is one of the simplest and most commonly used operational amplifiers.



Q No 3

b):- state the following statement as true or False and also give the reason for your answer: "The output of a summing amplifier is positive:-"


Ans:- The statement is False because the output of summing amplifier is not positive but it is negative. The circuit of summing amplifier is called summer or adder.

Summing amplifier:-

there are two types of summing amplifier one is inverting summer and the other one is Non-inverting summer.

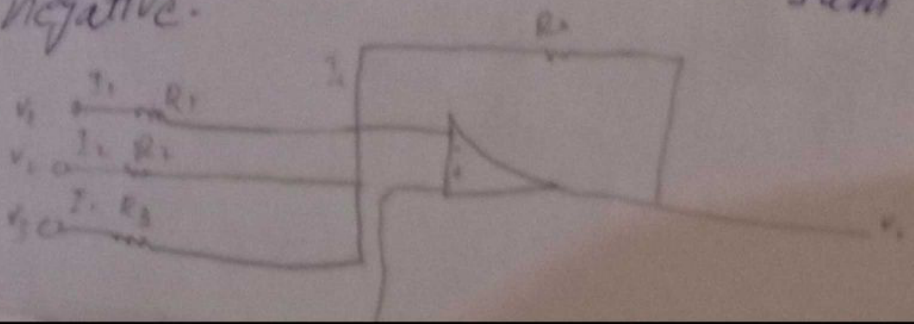1) Inverting summer:-

The output is linear sum of input with negative.



apply KCL

$$I_1 + I_2 + I_3 = I_f$$

$$\frac{v_1 - v_1}{R} + \frac{v_2 - v_2}{R_2} + \frac{v_3 - v_2}{R_3} = \frac{v_2 - v_0}{R_f}$$

by virtual ground concept

$$v_2 = v_3 = 0$$

we get

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = \frac{v_0}{R_f}$$

So output voltage

$$v_0 = -R_f \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right]$$

i) if $R_1 = R_2 = R_3 = R_f = R$

$$v_0 = -R_f \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right]$$

$$v_0 = -(v_1 + v_2 + v_3)$$

ii) If $R_2 = R_1 = R_3 = R$ & $R_f = R/n$

$$v_0 = -R_f \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right]$$

$$v_0 = -\frac{R}{n} \left[\frac{v_1 + v_2 + v_3}{R} \right]$$

P.No 11.

$$v_o = - \left(\frac{v_1 + v_2 + v_3}{n} \right)$$

Since $n = 3$ for 3 inputs

ii) If $R_1 \neq R_2 \neq R_3$

~~$$R_f / R_1 = A$$~~

$$R_f / R_1 = A$$

$$R_f / R_2 = B$$

$$R_f / R_3 = C$$

$$v_o = -R_f \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right]$$

$$v_o = [A v_1 + B v_2 + C v_3]$$