

Department of Electrical Engineering
Assignment

Date: 27/06/2020

Course Details

Course Title:	<u>Power Electronics</u>	Module:	<u>8th</u>
Instructor:	<u>Engr Shayaan</u>	Total Marks:	<u>50</u>

Student Details

Name:	<u>Raham Zeb</u>	Student ID:	<u>13074</u>
--------------	------------------	--------------------	--------------

Note: Plagiarism of more than 20% will result in negative marking.

Similar answers of students will result in cancellation of the answer for all parties.

Q1.	<p>Rectifiers are common circuits used in most electronic devices. There are multiple types of rectifiers used now a days. Explain in detail what are the similarities and differences between:</p> <ol style="list-style-type: none">1 – ϕ Uncontrolled Half Wave Rectifier and Full Wave Bridge Rectifier1 – ϕ Uncontrolled Rectifier and Controlled Rectifiers (Bridge Rectifier).	CLO 2 Marks 10
Q2.	<p>A AC voltage of $V_m =$ (Last 2 digits of ID) V has to be delivered to a Resistive DC load of $R =$ (First 2 digits of ID) ohms.</p> <p>The load and source are connected through 2 types of 1 – ϕ Uncontrolled rectifiers (Half Wave and Full Wave Bridge) and data is collected. Find the following for both rectifiers:</p> <ol style="list-style-type: none">1. V_{dc}2. I_{dc}3. V_{rms}4. I_{rms}5. Which rectifier do you think is better and why.	CLO 2 Marks 10
Q3.	<p>The Buck chopper is a type of DC-DC converter. Explain in detail the principals and working of Buck converter when the switch is open and closed.</p> <p>The buck converter is connected to a DC source voltage of $V_{in} = 50V$. The duty cycle is $D =$ (Last 2 digits of ID) %, load of $R =$ (First 2 digits of ID) ohms and switching frequency of 20kHz. What will be the</p> <ol style="list-style-type: none">1. V_{out}2. I_{out}3. I_{in}4. Inductor (L)	CLO 3 Marks 10

Q4	<p>The Boost chopper is a type of DC-DC converter. Explain in detail the principals and working of Boost converter when the switch is open and closed.</p> <p>The boost converter is connected to a DC source voltage of $V_{in} = 50V$. The duty cycle is $D = (\text{Last 2 digits of ID}) \%$, load of $R = (\text{First 2 digits of ID})$ ohms and switching frequency of 20kHz. What will be the</p> <ol style="list-style-type: none"> 1. V_{out} 2. I_{out} 3. I_{in} 4. Inductor (L) 	<p>CLO 3</p> <p>Marks 10</p>
Q5	<p>The Buck-Boost chopper is a type of DC-DC converter. Explain in detail the principals and working of Buck converter when the switch is open and closed.</p> <p>The Buck-Boost converter is connected to a DC source voltage of $V_{in} = 50V$. The Output voltage $V_{out} = (\text{Last 2 digits of ID}) \%$, load of $R = (\text{First 2 digits of ID})$ ohms and switching frequency of 20kHz. What will be the</p> <ol style="list-style-type: none"> 1. Duty Cycle (D) 2. I_{out} 3. V_{in} 4. Inductor (L) 	<p>CLO 3</p> <p>Marks 10</p>

name Raham Zeb

(11)

ID = 13074


Question no. 1:

Ans: Half wave Rectifier:-

The crucial differences b/w half wave and full wave Rectifier is that a half wave rectifier converts only one half cycle of the ac input supplied into pulsating dc signal.

Another major difference between the two is that the rectification efficiency of half wave rectifier is somewhat less as compared to the full wave rectifier.

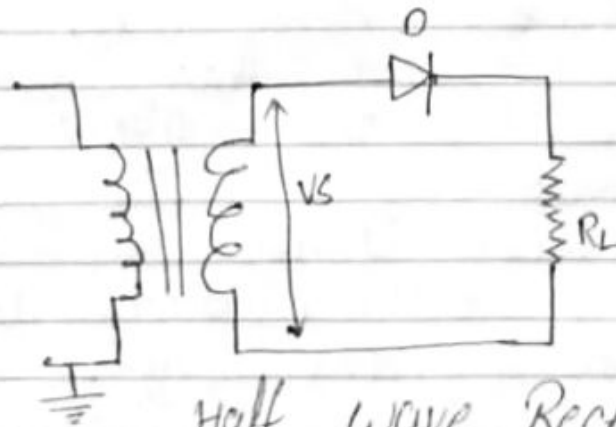The half wave rectifier is a circuit that passes only one half of the applied input signal and blocks the other. When positive half of the input is passed then negative half is blocked and vice-versa.



Half wave Rectifier

As we can in the figure that it is composed of an ac source, a diode, a step down transformer and a resistor that serves as a load.

Full wave Rectifier:-


A full wave rectifier is a circuit that has the ability to pass both

NAME = Rabam Zeb

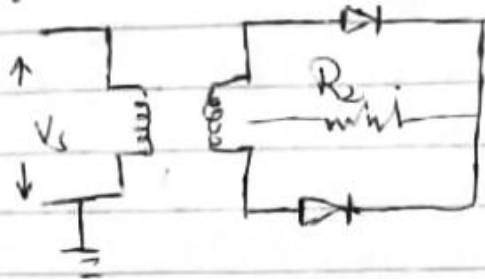(2)

ID = 13074

The halves of the applied input signal. AC input signal is converted into pulsating DC by the full wave rectifier.





It consists of a step down transformer along with 2 diodes connected with resistors (load).

When positive half on the input is applied to the circuit then it causes diode D_1 to get forward bias there by allowing the flow of the current through it hence the signal appears at the load.

At the same time the positive half reverse bias the diode D_2 there by condition does not take place through it hence no any out put is achieved at the load.

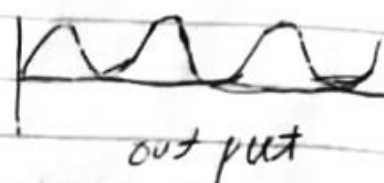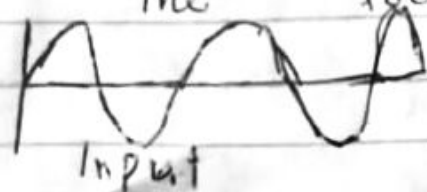Due to the negative half cycle diode D_2 will now be forward biased and now start condition due to which current flows through it and hence appear at the load.



NAME = Raham zeb (3)

ID = 13074

Parameters

Half wave

full wave

* Numbers of diode used in circuit

1

2 or 4

* Maximum efficiency for rectification.

40.6%

81.2%

* Basic ripple frequency

f

2f

Ripple factor

More

less

voltage regulation

Good

Better as compared to half wave

Transformer utilization factor

0.287

0.693

Peak inverse voltage

Maximum value of supplied input

Twice the maximum of ^{supply} input

Peak factor

2

1.414

form factor

$1 \text{ mV} / \pi$

$2 \text{ mV} / \pi$

Transformer core saturation

Possible

Not possible

NAME - Raham Zeb

(4)

ID = 13074

QUESTION no 2:- $V_m = 74$

$R = 13$

Find

1) $V_{DC} = ?$

2) $V_{DC} = ?$

3) $V_{rms} = ?$

4) $I_{rms} = ?$

$$V_{DC} = \frac{V}{\pi}$$

$$V_{rms} = \frac{V_m}{2} = 4.5V$$

$$I_{rms} = \frac{V_m}{2(R)} = \frac{74}{2(13)} = \frac{74}{26}$$

$$I_{rms} = 2.84A$$

$$I_{DC} = \frac{V_m}{\pi R} = \frac{74}{(3.14)(13)} = \frac{74}{40.82}$$

$$I_{DC} = 1.812$$

1-c Full bridge rectifier

$$V_s = V_o = V_{DC} = \frac{2V_m}{\pi} = \frac{2(74)}{3.14} = \frac{148}{3.14}$$

$$V_{DC} = 47.133$$

$$I_{DC} = \frac{V_m}{R} = \frac{74}{13} = 5.69A$$

$$V_{rms} = \sqrt{2} (47.133)$$

$$V_{rms} = 66.45V$$

Raham Zeb

(5)

ID = 13074

$$I_{rms} = \frac{I_m}{2}$$

$$= \frac{5.69}{2}$$

$$I_{rms} = 2.845$$

NAME = Raham Zeb

(6)

ID = 13074


Q: 3:- Principle of Buck Converter:

→ The main working principle of Buck converter is that the inductor in the input circuit resist sudden variation in input current. When switch is on the inductor stores energy from the input in the form of magnetic energy and discharge it when switch is closed the capacitor in the input is assumed large enough that the time constant of RC circuit in the output stage is high. The large time constant compared to switch's period ensures that in steady state a constant output voltage $V_o(t) = V_o(t) = V_o(\text{constant})$ exists across load terminals.

Working of Buck Converter:


The working of a Buck converter in to into a few steps

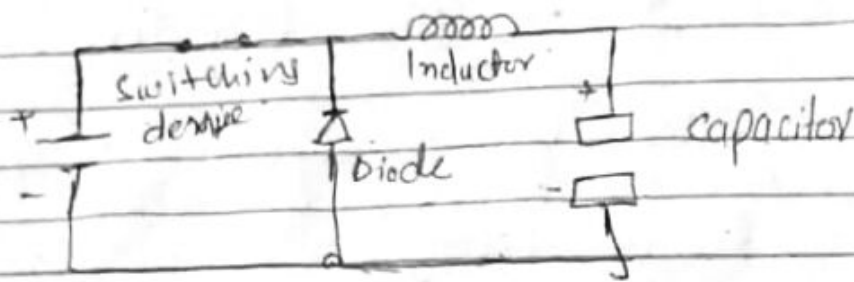Step 1: The switch on and lets current flow to the output capacitor, charging it up. Since the voltage across the capacitor cannot raise instantly and since the inductor limits the charging current, the voltage across the cap during the switching cycle is not the full voltage of the power source.



Step 2:-

The switch turns off since the current in an inductor cannot change suddenly, the inductor creates a voltage across it. This voltage is allowed to charge the capacitor and power the load through the diode when the switch is turned off, maintaining current output throughout the switching cycle.

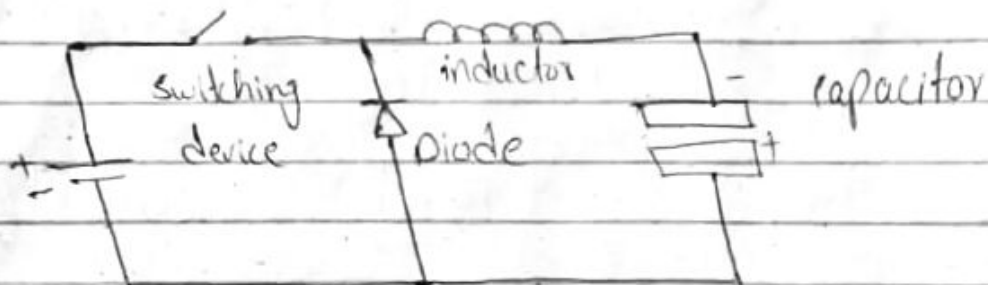

Qno 3:-

Numerical Solution :-

Given Data :-

$$V_{in} = 50V$$

$$\text{duty cycle} = d = 74\% = 0.74$$

↳ last digit of ID (13074)

$$R = 13\Omega$$

↳ first digit of ID (13074)

NAME = Raham Zeb

(8)

ID = 13074

$$f = 20 \text{ Khz} = 20000 \text{ Hz}$$

(i) $V_{out} = ?$

$$V_o = d(V_i)$$

$$= (0.74)(50)$$

$$\boxed{V_o = 37 \text{ V}}$$

(ii) $I_{out} = ?$

$$I_{out} = ?$$

$$I_{out} = \frac{V_o}{R}$$

$$I_o = \frac{37 \text{ V}}{13}$$

$$\boxed{I_o = 2.84 \text{ A}}$$

(iii) $I_{in} = ?$

$$I_{in} = \frac{V_i}{R}$$

$$I_{in} = \frac{50}{13}$$

$$\boxed{I_{in} = 3.84 \text{ A}}$$

(iv) Inductor () = ?

$$L = \frac{T \cdot F}{2} \times R \rightarrow \text{eqn (1)}$$

As we know that

$$V_o = dV_i$$

NAME = Raham zeb

(9)

ID = 13074

$$d = \frac{V_o}{V_i} = \frac{37}{50} = 0.74$$

$$\textcircled{*} \frac{T_{ON}}{T} = 0.74$$

$$T_{ON} = 0.74 \times T$$

$$\therefore d = \frac{T_{ON}}{T}$$

$$T_{ON} = \frac{0.74}{20 (10^3) \text{ Hz}} = 3.7$$

from eq (1) we have

$$\frac{T_{ON}}{T} = 0.74$$

$$\text{Now } T = T_{ON} + T_{OFF}$$

$$T = T - T_{ON}$$

$$T_{OFF} = 50 \mu\text{s} - 37 \mu\text{s} = 13 \mu\text{s}$$

$$T_{OFF} = 13 \mu\text{s}$$


Now put this value in eq (1) we get.

$$L = \frac{13 \mu\text{s}}{2} \times 13 = \boxed{84.5 \text{ mH}}$$

Ans.

Question no 400Boost Chopper:

A boost converter is one of the simplest types of switch mode converter. It takes an input voltage & boost it. All consist of an inductor, a semiconductor switch, a diode & a capacitor. It is also called as step-up converter.

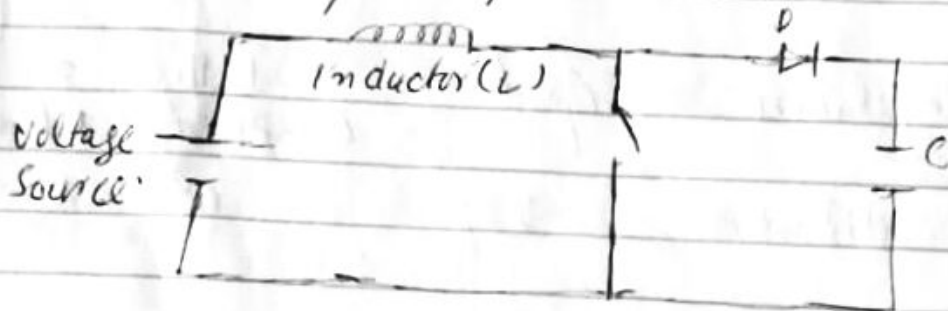
Working Principle:

The main working principle of boost converter is that the inductor in the input circuit resists sudden variations in input current. When switch is off, the inductor stores energy in the form of magnetic energy & discharges it when switch is closed. The capacitor in the output circuit is assumed large enough that the time constant of RC circuit in the output stays high.


NAME: Raham Zeb

(11)

ID = 13074

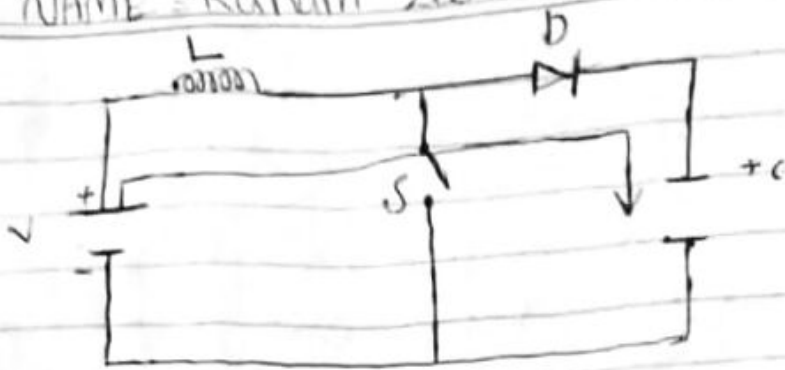

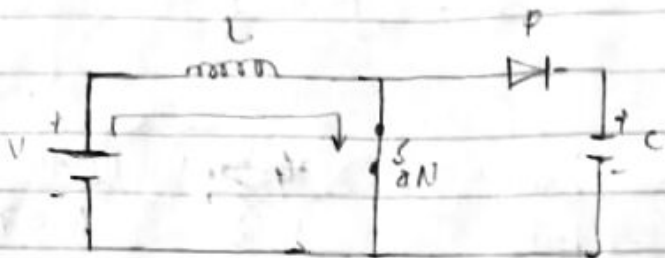The output capacitor is charged to the input voltage minus one diode drops.



when the switch is ON. our signal source goes high turning on the MOSFET. All the current is directed through the MOSFET through the inductor. The output capacitor stays charged since it can't discharge through now back-biased diode.

is ON for a time t_{ON} & is off for a time t_{OFF} . We define the time period, T as $T = t_{ON} + t_{OFF}$ & the switching frequency

$$f_{\text{switch}} = \frac{1}{T}$$

Now define another term duty cycle

$$D = \frac{t_{ON}}{T}$$

NAME = Raham Zeb

(12)

ID = 13074

Boost Converter is steady state operation for this mode using KVL.


$$V_{in} = V_L$$

$$V_L = L \frac{di_L}{dt} = V_{in}$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_{in}}{L}$$

Since the switch is closed for a time $T_{ON} = DT$ we can say that $\Delta t = DT$
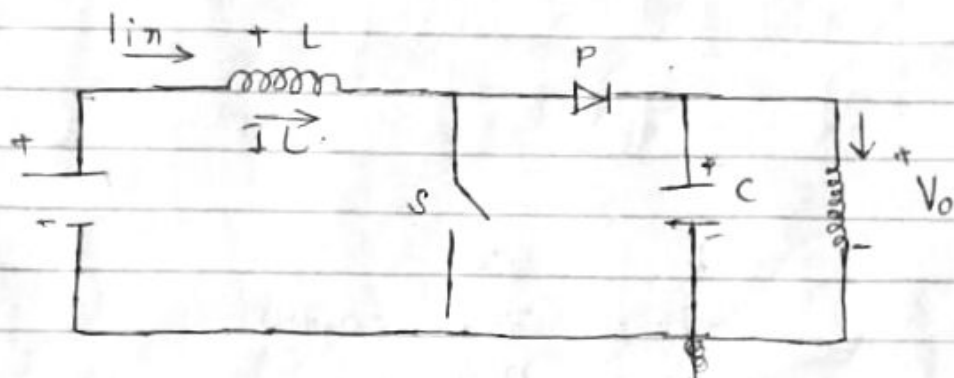
$$(\Delta i_L)_{closed} = \left(\frac{V_{in}}{L} \right) DT$$



In this mode, the polarity of the inductor is reversed. The energy stored in the inductor is released & is ultimately dissipated in the load resistance, & this helps to maintain the flow of current in the same direction through the load & also step-up the voltage as the inductor is now also acting as a source in conjunction with the input source.

Analyze the circuit using KVL.

NAME: Raham Zeb

(13)

ID = 13071

Boost Converter is in Steady state operation for mode 2 using KVL.

$$V_{in} = V_L + V_o$$

$$V_L = L \frac{di_L}{dt} = V_{in} - V_o$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-d)T} = \frac{V_{in} - V_o}{L}$$

Since the switch is open for a time $T_{off} = T - T_{on} = T - DT = \text{off } (1-D)T$.
We can say that $\Delta t = (1-D)T$

Qno 450

Numerical Solution:

Given Data:

$$V_{in} = 50V$$

$$D = 74\% = 0.74$$

$$R = 13\Omega$$

Switching frequency $f = 20\text{Hz}$.

- Find
- (1) V_{out}
 - (2) I_{out}
 - (3) I_{in}
 - (4) Inductance (L)

$$(1) V_{out} = \frac{V_s}{1-D} = \frac{50}{1-0.74}$$
$$= \frac{50}{0.26} = 192.30V$$

NAME Raham Zeb

(14)

$$(2) \quad I_{out} = \frac{V_{out}}{R} = \frac{112.80}{13} = 14.79 \text{ A}$$

$$(3) \quad I_{in} = \frac{I_{out}}{1-D} = \frac{14.79}{0.26} = 56.88 \text{ A}$$

Q: 5

Buck Boost Converter:

The buck boost Converter is a type of DC-DC that has output voltage magnitude that is either greater than or less than the input voltage magnitude it is equalated to the flyback converter using a single inductor instead of a transformer.

Principles and Working of buck Converters

The main working principle of buck converter is that the inductor in the input circuit result sudden variations in input current when switch is on. The inductor store energy in the form of magnetic energy and discharge it when switch is on. The inductor store energy in the form of magnetic energy and discharge it when switch is closed. The capacitor in the output circuit is assumed large is enough that the time constant of RC circuit in the output stage is high the large time constant compare to switching period ensure a constant output voltage

$$V_o(t) = V_i (\text{constant})$$

NAME = Raham Zeb

16

ID = 13074

Q5

$$V_{in} = 50$$

$$V_{out} = 74$$

$$R = 13$$

$$f = 20 \text{ KHz}$$

(1)

$$D = ?$$

$$1-D = \frac{-V_m}{V_o - V_{in}} \Rightarrow -D = \frac{-V_{in} - 1}{V_{out} - V_{in}}$$

$$= \frac{-V_{in} - 1}{V_{out} - V_{in}}$$

$$= \frac{50 + 1}{0.74 + 50}$$

$$D = 1.0051$$

(2)

$$I_{out} = \frac{V_o}{R} = \frac{0.74}{13} \Rightarrow I_{out} = 0.56A$$

(3)

$$I_n = \frac{I_o D}{1-D} = \frac{0.56 \times 1.0051}{1 - 1.0051}$$
$$= \frac{0.562}{-0.0051}$$

$$I_n = -110.19$$

(4)

$$L = \frac{V_{in} \times D}{f \times \Delta I}$$

$$= \frac{50 \times 1.0051}{20 \times 10^3 \times (I_{out} - I_{in})}$$

$$= \frac{50.25}{20000 \times (0.56 - (-110.19))}$$

$$= \frac{50.25}{20000 \times 110.75}$$

$$= \frac{50.25}{2215000}$$

$$L = 2.268$$

$$L = 2.268$$