

Name

Noor-ul-Iman

ID

12395

Semester

10th

Subject

Electronic
Circuit
Design.

Instructor
Name

1 Sir Mujtaba
Insan

Assignment
No

01

Date


03/06/2020

Q:-1

P-1

Explain the trans conductance curve for n-channel JFET given below. figure.

Ans
The transconductance curve of JFET transistor is the graph of the drain current, I_D versus the gate source voltage, V_{GS} . The ratio of change in ΔI_D , to the change in ΔV_{GS} , is the transconductance, g_m . and unit of transconductance is Siemens (S) while reciprocal of resistance (Ω). The transconductance curve as for all semiconductor devices, is non linear, for most of the curve, meaning changes to V_{GS} do not directly increase or decrease I_D . Below are the transconductance curves of N-channel JFET & P-channel JFET transistors.

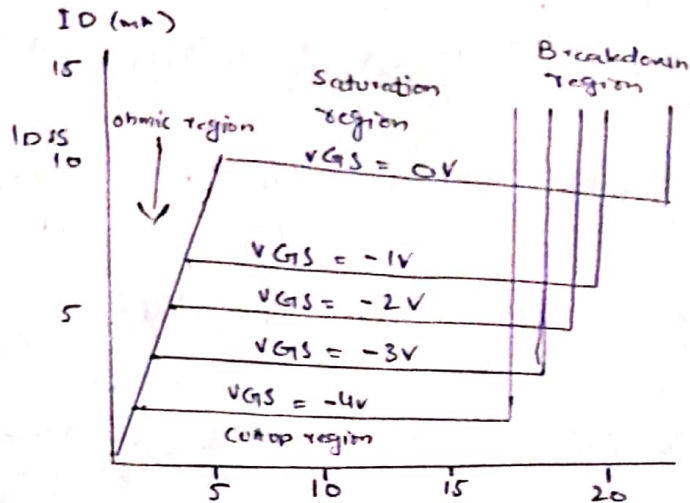

N-channel JFET Characteristic Curve

- (a) Cutoff Region:- This is the region where JFET transistor is off, meaning drain current, I_D flows from drain to source.
- (b) Ohmic Region:- At this region the JFET resistors show some resistance to I_D from drain to source. The response is linear at this curve.
- (c) Saturation Region:- During this region, JFET is on and off. At this region the JFET transistor has maximum current and fully operation and V_{GS} is supplied is flowing.

① Breakdown Region: At this region the voltage V_{DD} is supplied to drain of transistor exceeds the necessary maximum. The transistor is breakdown and the current flows from drain to source because at this stage the JFET loses its capacity to resist current because high voltage is applied across its drain-source terminals.


Q.2 State characteristics of Practical Operation amplifier?

Ans Practical OpAmp :-

Characteristics:-

- ① High input impedance
- ② Very low output impedance
- ③ High voltage gain.
- ④ It has both voltage and current limitations

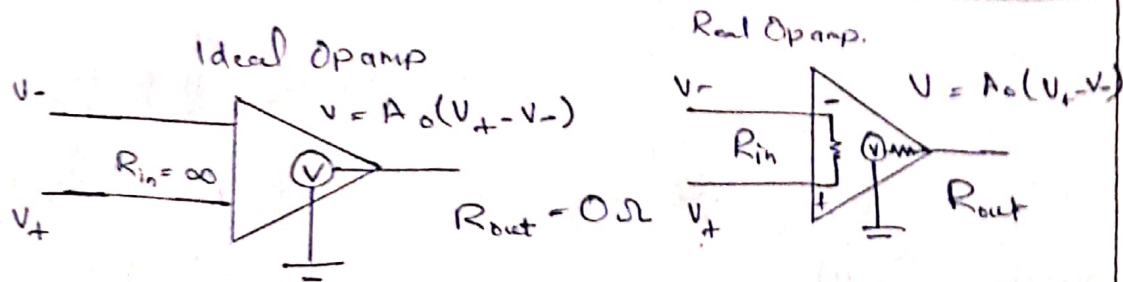The practical Op Amplifier characteristics can be approximated closely enough, for many practical op-amp. But basically they are different than ideal op-amp characteristics.



Bandwidth: The bandwidth of practical op-amp is very small in open loop. By application of negative feedback it can be increased to a desired value.

Output impedance: - With the help of negative feedback it can be reduced to a very small value like 1 or 2 ohms. It is typically few hundreds ohms.

Input Impedance: It is typically greater than I M O. and finite for the input stage using FET it can be increased upto several hundred M.

Open loop Gain: It is the voltage gain of OP. Amplifier when no feedback is practically it is several thousands.

Input offset voltage: The output voltage should be zero if both input terminals are ~~at earth or grounded~~. ideally, at this stage non-zero small voltage shown by practical OP-amp

Small voltage in millivolts is required to be applied to one of input such a voltage makes output voltage zero. The grounded terminal is called input offset voltage denoted as V_{ios} . The input offset voltage depends on the temperature.

Input Bias Current: For ideal op-amp, no current flow into input. The practical OP-amp do have some input currents which are very small, of the order of $10^{-6}A$ to $10^{-14}A$.

Most of op-amp use differential amplifier as input stage. The two transistors.

of different amplifier must be biased correctly

But practically, it is not possible to get

exact matching of two transistors. Thus the two

transistors, do conduct the small d.c current.

So input bias current can be defined as

current flowing into each of the two input

terminals when they are biased to same

voltage level i.e when the op-amp is

balanced. The two input current, I_{b1} when

op-amplifier is balanced are shown.

The two input currents, are never same.

Hence the manufacture specify the average

input bias current I_b , which is found

by adding the magnitudes of I_{b1} and I_{b2}


and dividing the sum by 2.

Mathematically:-
$$I_b = \frac{|I_{b1}| + |I_{b2}|}{2}$$

Input offset current: The difference in magnitudes of I_{b1} and I_{b2} is called as input offset current and is denoted as I_{ios} . Thus,

$$I_{ios} = |I_{b1} - I_{b2}|$$

The magnitude of this current is very small of order of 20 to 60 nA. It is measured under the condition that input voltage to op-amp is zero. If we supply equal d.c. current to two inputs, output voltage of op-amp must be zero. But practically, there exist some voltage at the output. To make it zero, the two input currents are made to differ by small amount. This difference is nothing but input offset current.

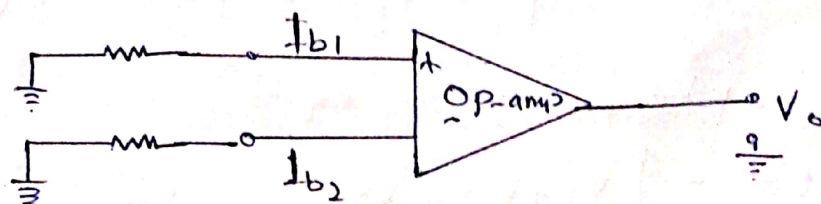

Input Bias Current.

Q.3

Calculate output voltage for summing amplifier.

if $V_1 = 0.2V$, $V_2 = 0.5V$, $V_3 = 2V$ & $R_1 = R_2 = R_3 =$

$$R_f = 6k\Omega.$$

Ans

To Find voltage for summing amplifier:

Solution:- according to ohm law

$$V = IR$$

$$V_1 = I R_1$$

$$\text{So, } I_1 = V_1 / R_1$$

$$I_2 = V_2 / R_2$$

$$I_3 = V_3 / R_3$$

Putting values in eq (3)

$$V_{out} = - \left[V_1 / R_1 + V_2 / R_2 + V_3 / R_3 \right]$$

~~$$R_f$$~~
$$R_f \dots \text{eq (4)}$$

When three resistors are equal then
i.e. $R_1 = R_2 = R_3 = R_f = R$

$$V_{out} = - \left[V_1 / R + V_2 / R + V_3 / R \right] R$$

$$V_{out} = - \left[V_1 + V_2 + V_3 \right] \dots \text{eq (5)}$$

~~$$\left[\frac{V_1 + V_2 + V_3}{R} \right] \dots \text{eq (5)}$$~~

$$V_{out} = - \left[V_1 + V_2 + V_3 \dots V_n \right]$$

So putting value in eqy.

$$V_{out} = - [V_1/R + V_2/R + V_3/R] R$$

$$V_{out} = - [0.2/6 + 0.5/6 + 2/6] 6$$

$$V_{out} = .$$

Q: No

1(a) You are working on an audio circuit in lab which class of amplifier will you not consider for your work?

Ans

- ① They are commonly used in RF circuits.
- ② Class C amplifiers are quite efficient.
- ③ However, the RF circuits where class C amplifiers are used, employ filtering so that final signal is completely acceptable.
- ④ Class C amplifiers are never used for audio circuits.
- ⑤ Class C amplifiers operate the output transistor in a state that results in tremendous distortion.

Reason:- Output devices conduct for less than 180 degrees (100 to 150) degrees typically) - Radio.

Frequency only. cannot be used for audio! This is sound heard when one of the output device goes open circuit in an audio amplifier. below figure shows time output device conduct.

Q.No
4(b)

Outline differences between an amplifier & a Rectifier.

~~Ans~~

Ans (b)

Amplifier: - An electronic device that increase or boosts voltage, current or power of a signal.

Application: - Audio amplifiers, hearing aids, music system, Operational amplifier.

Rectifier: - The function of rectifier is to convert incoming AC signal from transformer or other AC power source to some form of Pulsating DC.

Application: - The primary application of rectifier is to derive DC power from

an AC supply (AC to DC converter)

Rectifiers are used inside. The power supplies of virtually all electronic equipment

Uses:- It convert AC to DC,

at this method is known as rectification.

It is used as components of power supplies and as a detector of radio signal.

Rectifiers may be made of solid state diodes, vacuum tube diodes, mercury arc valves and other technologies