

Department of Electrical Engineering

Assignment

Date: 07/05/2020

Course Details

Course Title: Electrical Network Analysis _____

Module: 4th _____

Instructor: _____

Total: 20 _____

Submission Deadline: 05/06/2020



Marks: _____

Student Details


Name: _____

Student ID: _____

Student Signature: _____

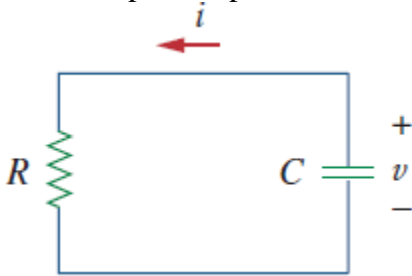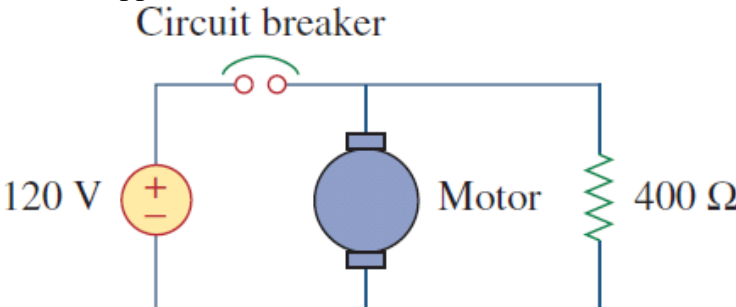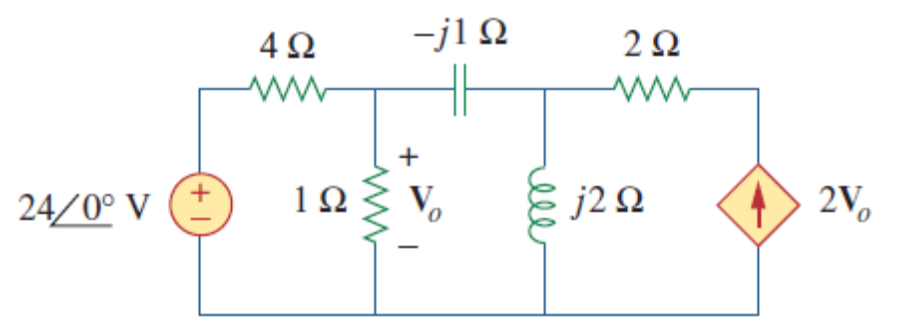Q1.	<p>For the circuit in Fig. 1, if $v = 10e^{-4t}$ V and $I = 0.2e^{-4t}$, $t > 0$</p> <p>(a) Find R and C. (b) Determine the time constant. (c) Calculate the initial energy in the capacitor. (d) Obtain the time it takes to dissipate 50 percent of the initial energy.</p> <div style="text-align: center;">  <p>Figure 1</p> </div>	<p>Marks 02</p> <p>CLO 01</p>
Q2.	<p>A 120-V dc generator energizes a motor whose coil has an inductance of 50 H and a resistance of 100 Ω. A field discharge resistor 400 Ω of is connected in parallel with the motor to avoid damage to the motor, as shown in Fig. 2. The system is at steady state. Find the current through the discharge resistor 100 ms after the breaker is tripped.</p> <div style="text-align: center;">  <p>Figure 2</p> </div>	<p>Marks 03</p> <p>CLO 03</p>

Q3.	<p>The responses of a series RLC circuit are $v_c(t) = 30 - 10e^{-20t} + 30e^{-10t}$ V $i_L(t) = 40e^{-20t} - 60e^{-10t}$ mA where v_c and i_L are the capacitor voltage and inductor current respectively. Determine the values of R, L, C</p>	<p>Marks 02 CLO 01</p>
Q4.	<p>The circuit in Fig. 3 is the electrical analog of body functions used in medical schools to study convulsions. The analog is as follows: C_1 = Volume of fluid in a drug C_2 = Volume of blood stream in a specified region R_1 = Resistance in the passage of the drug from the input to the blood stream R_2 = Resistance of the excretion mechanism, such as kidney, etc. v_0 = Initial concentration of the drug dosage $v(t)$ = Percentage of the drug in the blood stream</p> <p>Find $v(t)$ for $t > 0$ given that $C_1 = 0.5\mu\text{F}$, $C_2 = 5\mu\text{F}$, $R_1 = 5\text{M}\Omega$, $R_2 = 2.5\text{M}\Omega$ and $v_0 = 60u(t)$ V</p> <div data-bbox="535 745 1193 1008" data-label="Diagram"> </div> <p style="text-align: center;">Figure 3</p>	<p>Marks 03 CLO 03</p>
Q5.	<p>A power transmission system is modeled as shown in Fig. 4. Given the source voltage and circuit elements Source voltage $V_s = 115 \angle 0$ V, Source impedance $Z_s = 1 + j0.5 \Omega$, Line impedance $Z_l = 0.4 + j0.3 \Omega$, Load impedance $Z_L = 23.2 + j18.9 \Omega$, find the load current I_L</p> <div data-bbox="511 1312 1201 1690" data-label="Diagram"> </div> <p style="text-align: center;">Figure 4</p>	<p>Marks 02 CLO 03</p>

Q 6	<p>For the circuit in Fig. 5, find the average, reactive, and complex power delivered by the dependent current source.</p>  <p style="text-align: center;">Figure 5</p>	Marks 03 CLO 03
Q 7	<p>A balanced Y-load is connected to a 60-Hz three-phase source with $V_{ab} = 240 \angle 0^\circ$ V. The load has $\text{pf} = 0.5$ lagging and each phase draws 5 kW. (a) Determine the load impedance Z_Y. (b) Find I_a, I_b, and I_c.</p>	Marks 5 CLO02

Department of Electrical Engineering

Course Title: Signal And System


Module: 4th semester

Student Detail

Name :- Muhammad Ahmad.

Student ID # 14563.


Student Signature :-

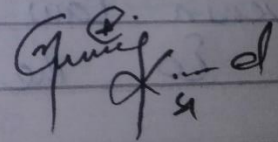

————— " —————"

QNo1:- For the RC in Fig 1 if $N = 10e^{-4t} V$ and $i = 0.2e^{-4t} A$, $t > 0$.

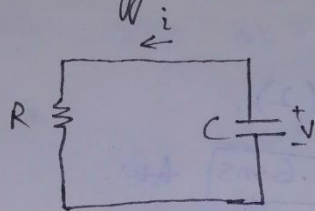- Find R & C .
- Determine the Time Constant.
- Calculate the initial energy in the capacitor.
- Obtain the time t takes to dissipate 50 percent of the initial energy.



Solution

$$\text{(a)} \quad Y = RC = \frac{1}{4}$$

$$-i = C \frac{dv}{dt}$$

$$-0.2e^{-4t} A = C(10)(-4)e^{-4t}$$

$$\boxed{C = 5 \text{ mF}}$$

$$R = \frac{1}{4C}$$

$$= \frac{1}{4(5 \text{ mF})}$$

$$\boxed{R = 50 \Omega}$$

$$\text{(b)} \quad Y = RC = \frac{1}{4} = \boxed{0.25 \text{ s}}$$

$$\text{(c)} \quad W_C(0) = \frac{1}{2} C V_0^2$$

$$= \frac{1}{2} (5 \times 10^{-3}) (100)$$

①

$$= \boxed{250 \text{ mJ}}$$

$$\textcircled{d} \quad W_c(0) = \frac{1}{2} C V_0^2 (1 - e^{-2t_0/\tau})$$

$$= \frac{1}{2} (5 \times 10^{-3}) (100)^2 (1 - e^{-2t_0/\tau})$$

$$0.5 = 1 - e^{-8t_0}$$

$$e^{-8t_0} = \frac{1}{2}$$

$$\text{or } e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2)$$

$$= \boxed{86.6 \text{ ms}} \quad \text{Ans.}$$

Q No # 2

Solution:-

Let the inductor current

for $t < 0$

$$i(0) = \frac{120}{100} = 1.2 \text{ A}$$

For $t > 0$

We have an RL circuit.

$$\tau = \frac{L}{R}$$

$$= \frac{50}{100 + 400} = \frac{50}{500}$$

$$= 0.1$$

②

$$i(\infty) = 0.$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}}$$

$$i(t) = 1.2 e^{-10t}$$

$$A\tau = \tau = \omega_{ms} = 0.1 \text{ s.}$$

$$i(0.1) = 1.2 e^{-1}$$
$$= 0.441 \text{ A}$$

Which is the same as the current (I) through the resistor.

$$\tau = RC_{ms} = 60 \mu\text{s.}$$

As An Integrator.

$$T < 0.1 \quad \tau = 6 \mu\text{s.}$$

$$T_{max} = 6 \mu\text{s.}$$

Q No # 3

Solution:-

We have RLC ckt.

$$V_c(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$V(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega]$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA.}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0].$$

Comparing these Equation.

$$V_s = 30$$

$$A_1 = -10 \quad ; \quad A_2 = 30;$$

$$s_1 = -20 \quad ; \quad s_2 = -10 \rightarrow \textcircled{1}.$$

ⓑ

$$V_s = \omega$$

$$A_1' = 40 ; A_2' = -60$$

$$S_1' = -20 ; S_2' = -10 \rightarrow \textcircled{2}$$

Now Equation ① and ②.

$$S_1 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \& \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_1 + S_2 = -2\alpha$$

$$S_1 \cdot S_2 = \omega_0^2$$

$$\text{Where } \alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$-30 = 2\alpha$$

$$\alpha = 15$$

$$\frac{R}{2L} = 15 \rightarrow \textcircled{3}$$

$$200 = \omega_0^2$$

$$\frac{1}{LC} = 200 \rightarrow \textcircled{4}$$

$$\text{Also } i(t) = C \frac{dV(t)}{dt}$$

$$= C [200e^{-20t} - 300e^{-10t}]$$

$$[S_1 = S_2' \quad \& \quad S_2 = S_2']$$

$$200C = A_1' = 40 \times 10^{-3}$$

$$C = 200 \times 10^{-6}$$

$$\boxed{C = 200 \mu\text{F}}$$

And hence by using Equation ③ and ④ we get ④.

$$L = \frac{1}{200} F$$

$$= \frac{1}{200 \times 200 \times 10^6}$$

$$= \boxed{25 H}$$

And $R = 30L$


$$= 30 \times 25$$

$$= \boxed{750 \Omega}$$

''-----''

Q No #5

Solution:-

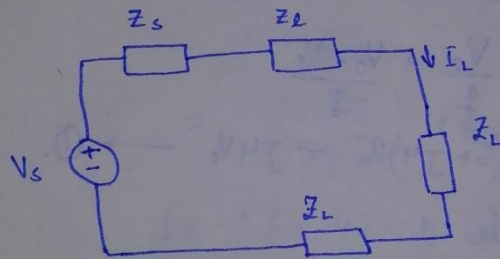

Transmission line load.

$$Z = Z_s + Z_L + Z_L$$

$$= (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$Z = 25 + j20$$

$$I_L = \frac{V_s}{Z}$$


$$= \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = \boxed{3.592 \angle -38.66^\circ \text{ A Ans}}$$

(5)

Q No # 6

Solution

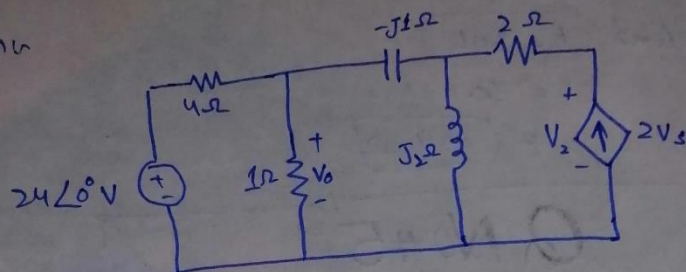

consider the ckt as shown.

At node 0

$$\frac{24 - V_0}{4} = \frac{V_0}{1} + \frac{V_0 - V_1}{-j}$$

$$24 = (5 + j4)V_0 - j4V_1 \rightarrow \textcircled{1}$$

At node 1.

$$\frac{V_0 - V_1}{-j} + 2V_0 = \frac{V_1}{j_2}$$

$$V_1 = (2 - j4)V_0 \rightarrow \textcircled{2}$$

substituting $\textcircled{2}$ into $\textcircled{1}$.

$$24 = (5 + j4 - j8 - 16)V_0.$$

$$V_0 = \frac{-24}{11 + j4}$$

$$V_1 = \frac{(-24)(2 - j4)}{11 + j4}$$

$\textcircled{6}$

The voltage across the dependent source

$$V_2 = V_1 + (2)(2V_0) = V_1 + 4V_0$$

$$V_2 = \frac{-24}{11 + j4} - (2 - j4 + 4)$$
$$= \frac{(-24)(6 - j4)}{11 + j4}$$

$$S = V_2 I = V_2 (2V_0)$$

~~W₂ =~~

$$S = \frac{(-24)(6 - j4)}{11 + j4} \cdot \frac{-48}{11 - j4}$$

$$= \left(\frac{1152}{137} \right) (6 - j4)$$

$$S = (50.45 - j33.64) \text{ VA.}$$

Q No #7

Solution:-

$$|V_{ab}| = \sqrt{3} V_p = 240$$

$$V_p = \frac{240}{\sqrt{3}} = 138.56$$

$$V_{in} = V_p \angle -30^\circ$$

$$P_f = 0.5 = \cos \theta$$

$$\theta = 60^\circ$$

(7)

$$P = S \cos \theta$$

$$S = \frac{P}{\cos \theta}$$

$$= \frac{5}{0.5} = 10 \text{ KVA.}$$

$$Q = S \sin \theta = 10 \sin 60$$

$$= 8.66$$

$$S_p = 5 + j 8.66 \text{ KVA.}$$

But

$$S_p = \frac{V_p^2}{Z_p^*}$$

$$Z_p^* = \frac{V_p^2}{S_p}$$

$$= \frac{(138.56)^2}{(5 + j 8.66) \times 10^3} = 0.96 - j 1.663$$

$$\boxed{Z_p = 0.96 + j 1.663 \Omega}$$

$$I_a = \frac{V_{an}}{Z_p} = \frac{138.56 \angle -30}{0.96 + j 1.6627} = \boxed{72.17 \angle -90^\circ \text{ A}}$$

$$I_b = I_a \angle -120^\circ = \boxed{72.17 \angle -210^\circ \text{ A}}$$

$$I_c = I_a \angle +120^\circ = \boxed{72.17 \angle 30^\circ \text{ A}}$$

ⓑ


Q No # 4

Solution

for $t = 0^-$

$$V(0) = 0.$$

for $t > 0,$

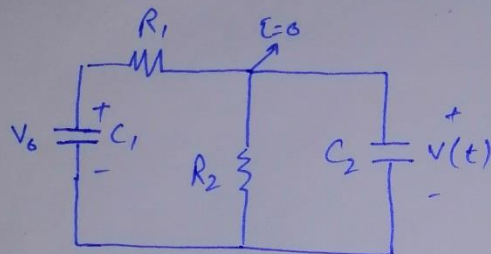

At Node (a)

$$V_0 - \frac{V}{R_1} = \frac{V}{R_2} + C_2 \frac{dV}{dt}$$

$$V_0 = V \left(1 + \frac{R_1}{R_2} \right) + R_2 C_2 \frac{dV}{dt}$$

$$60 = \cancel{3V} \left(1 + \frac{5}{2.5} \right) + (5 \times 10^{-6} \times 5 \times 10^{-6}) \frac{dV}{dt}$$

$$60 = 3V + 25 \frac{dV}{dt}$$

$$V(t) = V_s + \left(A e^{-\frac{3t}{25}} \right)$$

$$3V_s = 60 \text{ yields}$$

$$V_s = 20$$

$$V(0) = 0 = 20 + A$$

$$A = -20 \rightarrow$$

$$V(t) = 20 \left(1 - e^{-\frac{3t}{25}} \right) V$$

(9)