

NAME MUHAMMAD SALMAN
NASIR

ID 16664

COURSE TITLE :-
LINEAR CIRCUITAN
-ALYSIS

INSRTRCTOR :-
"SIR SOHAIL
IMIRAN"

MODULE :- 3

DATED :-
24-6-2020

FINAL PAPER

* ————— *

DEPARTMENT

OF

ELECTRICAL ENGINEERING

* * *

(1)

Q No 1:-


Find value of I_x
using:

* Nodal Analysis

* Mesh Analysis

* Super position theorem

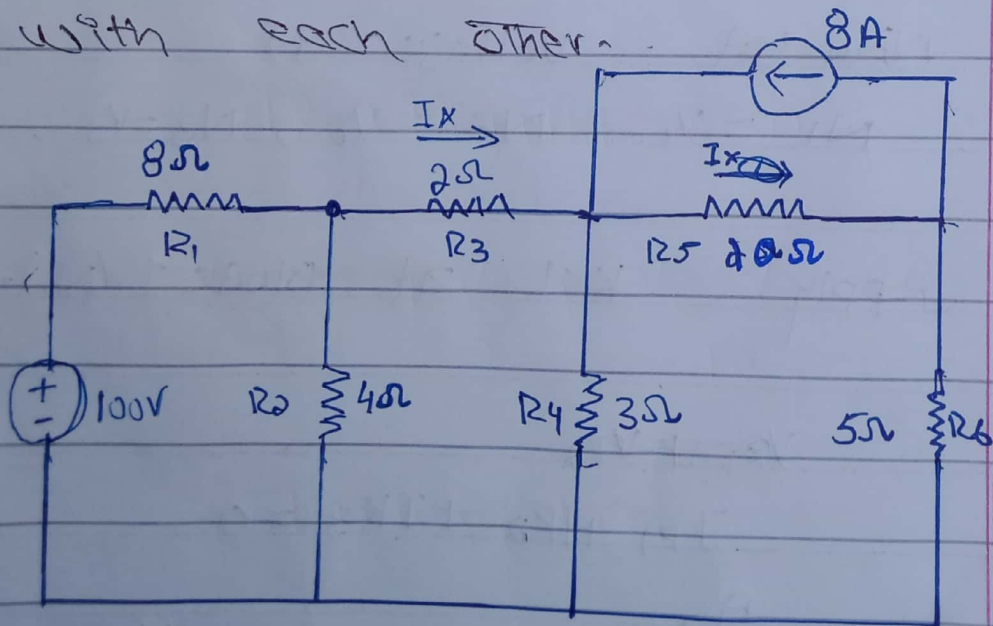* Compare number of steps and degree of difficulty of all the three method with each other.




(2)

Solution:

(1) By Nodal Analysis:-

Re draw the circuit and identify nodes.

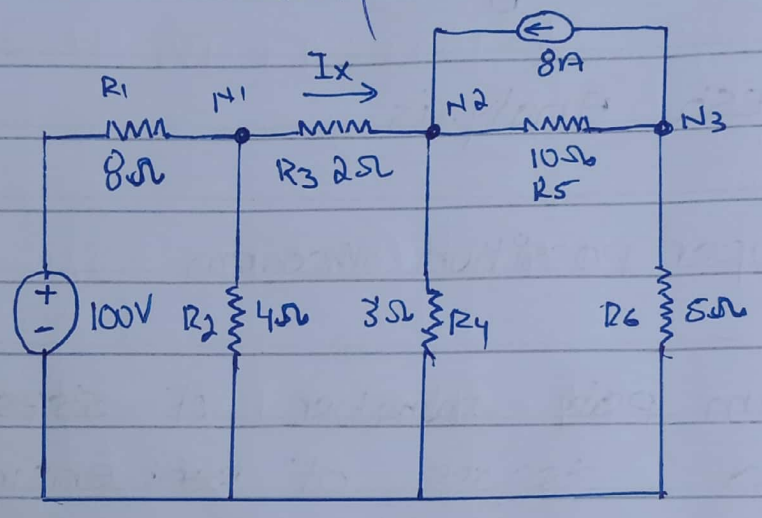

Let voltage at

$$N_1 = V_1 \quad N_2 = V_2, \quad N_3 = V_3$$

Apply KCL at Node 1 (N1).

~~V1 = 100~~

$$I_{R1} + I_{R2} + I_{R3} = 0$$

As

$$V = IR \Rightarrow I = \frac{V}{R}$$

$$\frac{V_1 - 100}{8} + \frac{V_1}{4}$$

(3)

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

Taking L.C.M.

$$\frac{V_1 - 100 + 2V_1 + 4(V_1 - V_2)}{8} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 = 8 \times 0$$

$$7V_1 - 4V_2 = 100 \rightarrow \textcircled{1}$$

Apply KCL at Node

$$IR_2 + IR_4 + IR_5 - 8 = 0$$

$$\Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 8$$

Taking Lcm.

$$\frac{30V_2 - 30V_1 + 20V_2 + 6V_2 - 6V_3}{60} = 8$$

(4)

$$\frac{30V_2 - 30V_1 + 20V_2 + 6V_2 - 6V_3}{60} = 8$$

$$-30V_1 + 56V_2 - 6V_3 = 8 \times 60$$

$$-30V_1 + 56V_2 - 6V_3 = 480 \rightarrow (2)$$

At Node 3:-

$$IR_5 + IR_6 + 8 = 0$$

$$\Rightarrow \frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

Take LCM

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$\frac{-V_2 + 3V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \rightarrow (3)$$

(5)

From eq (1)

$$7V_1 - 4V_2 = 100$$

$$7V_1 = 100 + 4V_2$$

$$V_1 = \frac{100 + 4V_2}{7}$$

$$V_1 = \frac{100 + 4V_2}{7} \rightarrow (H)$$

From equation (3)

$$-V_2 + 3V_3 = -80$$

$$3V_3 = -80 + V_2$$

$$= \frac{-80 + V_2}{3}$$

$$V_3 = \frac{-80 + V_2}{3}$$

$$V_3 = \frac{V_2 - 80}{3} \rightarrow (S)$$

(6)

NOW put equation
(5) & (4) in eq (2)

2 \Rightarrow

$$-30v_1 + 56v_2 - 6v_3 = 480$$

$$-30 \left(\frac{100 + 4v_2}{7} \right) + 56v_2 =$$

$$-6 \left(\frac{v_2 - 80}{3} \right) = 480$$

$$-30 \left(\frac{100}{7} + \frac{4v_2}{7} \right) + 56v_2$$

$$-6 \left(\frac{v_2}{3} - \frac{80}{3} \right) = 480$$

$$\Rightarrow -30(14.28 + 0.57v_2) + 56v_2 =$$

$$-6(0.33v_2 - 26.6) = 480$$

$$-428.4 - 17.1v_2 + 56v_2 - 1.98v_2 + 159.6 = 480$$

$$36.98v_2 - 268 = 480$$

$$36.98v_2 = 480 + 268$$

(7)

$$36.98 V_2 = 748$$

$$V_2 = 748 / 36.98$$

$$V_2 = 20.22 \text{ volt}$$

Put value of V_2 in eq (1)

$$H \Rightarrow V_1 = \frac{100 + 4V_2}{7}$$

$$V_1 = \frac{100 + (4 \times 20.22)}{7}$$

$$= \frac{100 + 80.90}{7}$$

$$V_1 = 25.8 \text{ volt}$$

(8)

Now For I_x
from ohm law

ϕ

$$V = IR$$

$$I = V/R$$

but here

$$V = V_1 - V_2$$

$$R_3 = 2 \Omega$$

$$I_x = \frac{V_1 - V_2}{R_3}$$
$$= \frac{25.8 - 20.22}{2}$$

$$I_x = \frac{5.624}{2}$$

$$I_x = 2.79$$

$$I_x = 2.8 A$$


$I_x = 2.79$
OR $I_x = 2.8 A \rightarrow \text{ANS}$

x — x — x — x — x

(9)

(a) MESH analysis:-

see draw circuit & identify loops:-

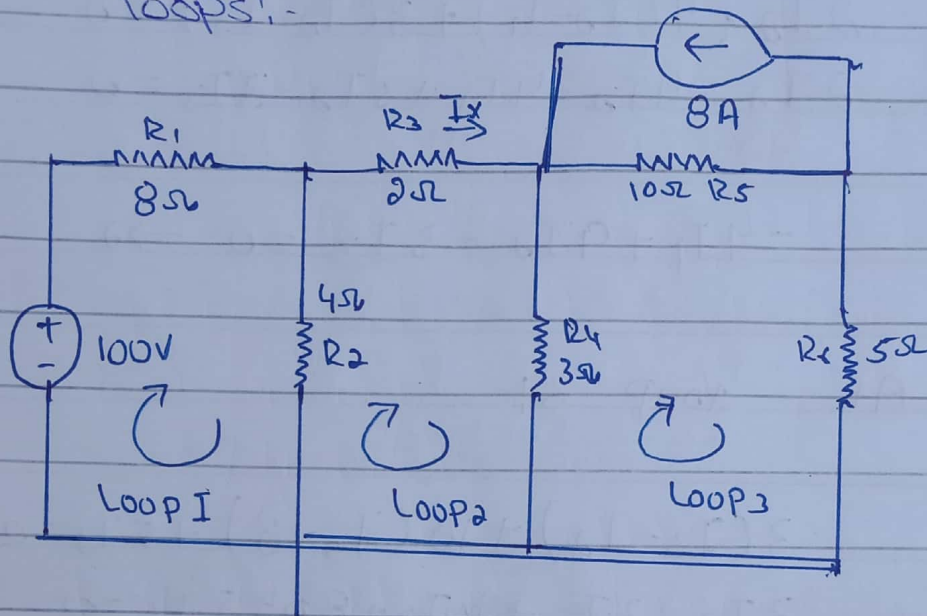

Current in loop 1 = I_1

Loop 2 = I_2 & loop 3 = I_3

Apply KVL at loop 1

$$V_{R1} + V_{R2} = 100 \quad \because V = IR$$

$$8I_1 + 4(I_1 - I_2) = 100$$

$$8I_1 + 4I_1 - 4I_2 = 100$$

$$12I_1 - 4I_2 = 100 \rightarrow \textcircled{1}$$

(10) (P)

At 100P 2I - 12I₁ + 10I₂ + 5I₃

$$VR_2 + VR_3 + VR_4 = 0$$

$$2I_2 + 4(I_2 - I_1) + 3(I_2 - I_3) = 0$$

$$2I_2 - 4I_2 - 4I_1 + 3I_2 - 3I_3 = 0$$

$$-4I_1 + 9I_2 - 3I_3 = 0 \rightarrow 2$$

At 100P 3I -

$$3(I_3 - I_2) + 10(I_3 + 8) + 5I_3 = 0$$

$$3I_3 - 3I_2 + 10I_3 + 80 + 5I_3 = 0$$

$$-3I_2 + 18I_3 = -80 \rightarrow 3$$

From eq (1)

$$12I_1 - 4I_2 = 100$$

$$I_1 = \frac{100 + 4I_2}{12}$$

$$I_1 = \frac{4I_2 + 100}{12} \rightarrow (N)$$

(11)

From eq (3)

$$-3I_2 + 18I_3 = -80$$

$$I_3 = \frac{3I_2 - 80}{18} \rightarrow K$$

put N & K in (2)

① \Rightarrow

$$-4I_1 + 9I_2 - 3I_3 = 0$$

$$-4 \left[\frac{4I_2 + 100}{12} \right] - 3 \left[\frac{3I_2 - 80}{18} \right] + 9I_2 = 0$$

$$-4(0.33I_2 + 8.3) - 3(0.16I_2 - 4.44) + 9I_2 = 0$$

$$-1.32I_2 - 33.33 - 0.5I_2 + 13.32 + 9I_2 = 0$$

$$7.18I_2 - 20.13 = 0$$

$$7.18I_2$$

$$I_2 = \frac{20.13}{7.18}$$

$$I_2 = 2.79$$

$$I_2 = 2.8$$

Here

$$I_2 = I_x \Rightarrow$$

$$I_x = 2.79$$
$$I_x = 2.8A$$

\rightarrow ANS

(12)

Super position Theorem.

We can find I_x by super position


1st Remove the current source
by open circuit
and calculate I_1

2nd Remove the voltage
source by short circuit
& calculate I_2 then

For I_x Add I_1 & I_2

$$I_x = I_1 + I_2.$$

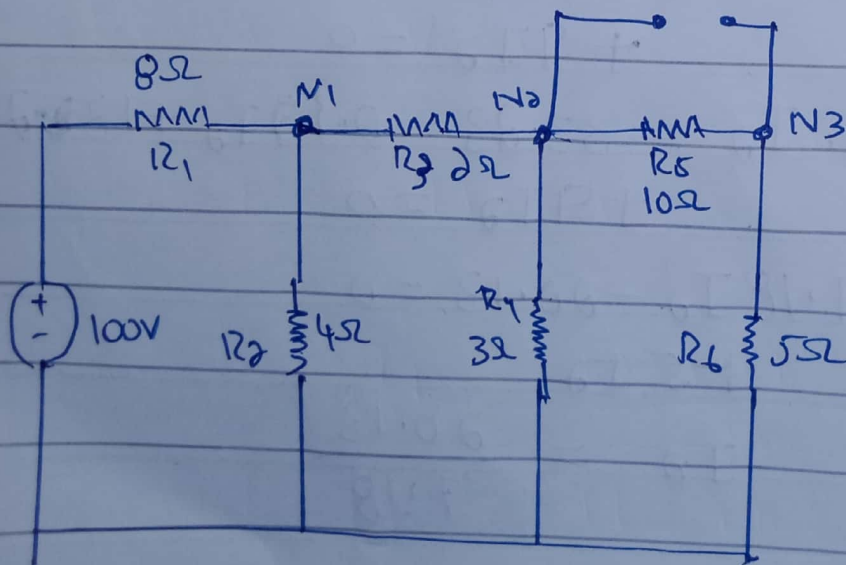Draw circuit by removing
current source by open
circuit also identify
nodes.



(13)

at Node 2

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 2V_2 + 2V_1 - 2V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 \rightarrow \textcircled{i}$$

at Node 2:-

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$\frac{30V_2 - 30V_1 + 20V_2 + 6V_2 - 6V_3}{60} = 0$$

$$-30V_1 + 56V_2 - 6V_3 = 0$$

$$-30V_1 + 56V_2 - 6V_3 = 0 \rightarrow \textcircled{ii}$$

at Node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + 2V_3}{10} = 0$$

$$-V_2 + 3V_3 = 0 \rightarrow \textcircled{iii}$$

(14)

From equation 1

$$7V_1 - 4V_2 = 100$$

$$\boxed{V_1 = \frac{100 + 4V_2}{7}} \rightarrow (5)$$

From equation (3):

$$-V_2 + 3V_3 = 0$$

$$\boxed{V_3 = \frac{1}{3}V_2}$$

Put value of V_1 &
 V_3 in equation (ii)

(ii) \Rightarrow

$$-30V_1 + 56V_2 - 6V_3 = 0$$

$$-30 \left(\frac{100 + 4V_2}{7} \right) + 56V_2 - 6 \left(\frac{1}{3}V_2 \right) = 0$$

$$-6 \left(\frac{1}{3}V_2 \right) = 0$$

$$-30(14.28 + 0.57V_2) + 56V_2 - 2V_2 = 0$$

$$-428.4 - 17.1V_2 + 56V_2 - 2V_2 = 0$$

$$-428.4 + 36.9V_2 = 0$$

(15)

$$V_0 = 428.4136.9$$

$$V_0 = 11.6 \text{ Volt}$$

put $V_0 = 11.6$ in eqv(s)

(5) \Rightarrow

$$V_1 = \frac{100 + \cancel{56}4V_0}{7}$$

$$V_1 = \frac{100 + (4 \times 11.6)}{7}$$

$$V_1 = 20.91 \text{ V}$$

From ohm law

$$I = V/R$$

Here $V = \cancel{V_0} V_1 - V_2$


$$R = 2 \Omega$$

$$I_1 = \frac{20.91 - 11.6}{2}$$

$$I_1 = 4.65 \text{ A}$$

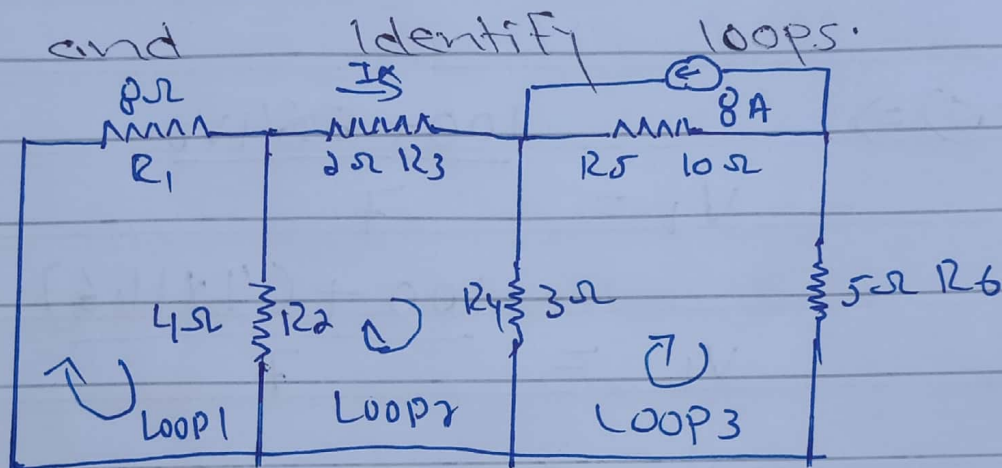(16)

Now remove volt source
and as short circuit-
Re-draw circuit by
removing voltage source
and



Current in loop 1 = I_1 , loop 2 = I_2
& loop 3 = I_3 .

Apply KVL to loop 1:-

$$8I_1 + 4(I_1 - I_2) = 0$$

$$8I_1 + 4I_1 - 4I_2 = 0$$

$$12I_1 - 4I_2 = 0 \quad \rightarrow (1)$$

$$4(3I_1 - I_2) = 0$$

$$3I_1 - I_2 = 0 \quad \rightarrow (1)$$

(17)

at loop 2:-

$$2I_2 + 4(I_2 - I_1) + 3(I_2 - I_3) = 0$$

$$2I_2 + 4I_2 - 4I_1 + 3I_2 - 3I_3 = 0$$

$$-4I_1 + 9I_2 - 3I_3 = 0 \rightarrow (1)$$

at loop 3:-

$$3(I_3 - I_2) + 10(I_3 + 8) + 5I_3 = 0$$

$$3I_3 - 3I_2 + 10I_3 + 80 + 5I_3 = 0$$

$$-3I_2 + 18I_3 = -80 \rightarrow (3)$$

From eq (1):-

$$3I_1 - I_2 = 0$$

$$I_1 = \frac{1}{3} I_2 \rightarrow (2)$$

From eq (3)

$$-3I_2 + 18I_3 = -80$$

$$\cancel{3I_2} = \cancel{-80} - 18I_3$$

$$I_3 = \frac{-80 + 3I_2}{18} \rightarrow (4)$$

$$8.6 = 18$$

(18)

Put eq (18) in eq (2)

② ⇒

$$-4I_1 + 9I_2 - 3I_3 = 0$$

$$-4\left(\frac{1}{3}I_2\right) + 9I_2 - \left(3 \frac{3I_2 - 80}{18}\right) = 0$$
$$-1.3I_2 + 9I_2 - 0.5I_2 + 13.3 = 0$$

$$-1.3I_2 + 9I_2 - 0.5I_2 + 13.3 = 0$$

$$7.2I_2 + 13.3 = 0$$

$$7.2I_2 = -13.3$$

$$I_2 = -1.83 \text{ A} \rightarrow *$$

Now from super position theorem

$$I_x = I_1 + I_2$$

put value of I_1 & I_2

$$I_x = 4.65 - 1.83$$

$$I_x = 2.79$$

$$I_x = 2.8$$

OR

$$I_x = 2.79$$

$$I_x = 2.8$$

(19)

(iv) Comparison:

* From Nodal Analysis
we get $I_x = 2.8A$

* From mesh Analysis
we get $I_x = 2.8A$

* From super position theorem
we get $I_x = 2.8A$

by ~~and~~ solving the
circuit different methods
we get same result
which $I_x = 2.8A$.

but super position theorem
is quite easier than nodal
& mesh analysis. because
it is very difficult to identify
nodes & loops in complex
circuit having current & voltage
source at a time. In super po
sition we ~~can~~ take one
source at a time which
makes circuit easy. I think
~~super position~~ is quite

(20)

Due to removal of one source i.e current or voltage it became to easy and the equation became also easy.

that why I think that super position method is quit easy than nodal & mesh analysis.


X — X — X — X — X — X

(21)

Q No 2:-

Consider the $200\ \Omega$ resistor as a load resistor and develop

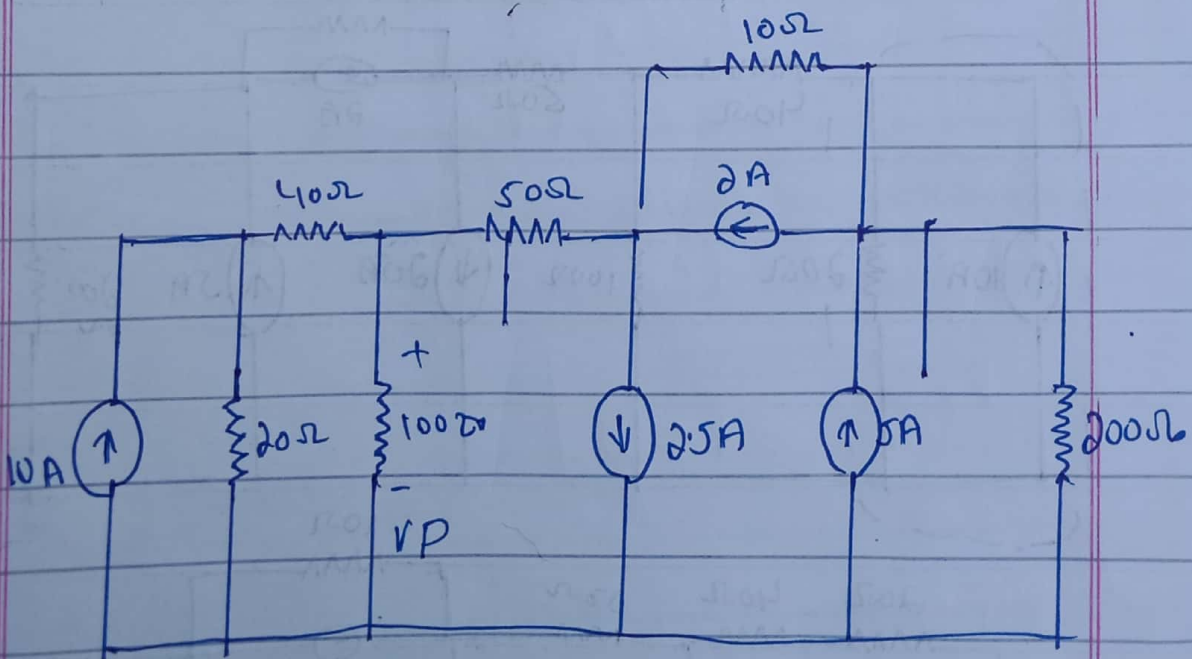- * Thevenin equivalent circuit
- * Norton equivalent circuit
- * Find out value of Thevenin resistance should be used to deliver max-power to the load.





(22) (6)

Solution:

THEVENIN'S THEOREM:-

In order to solve the question/circuit in THEVENIN'S Theorem we need a voltage source which

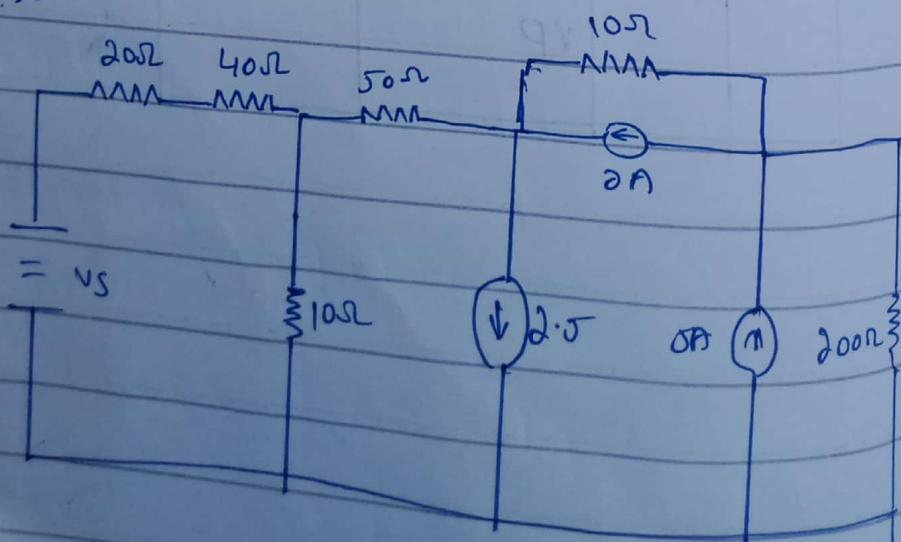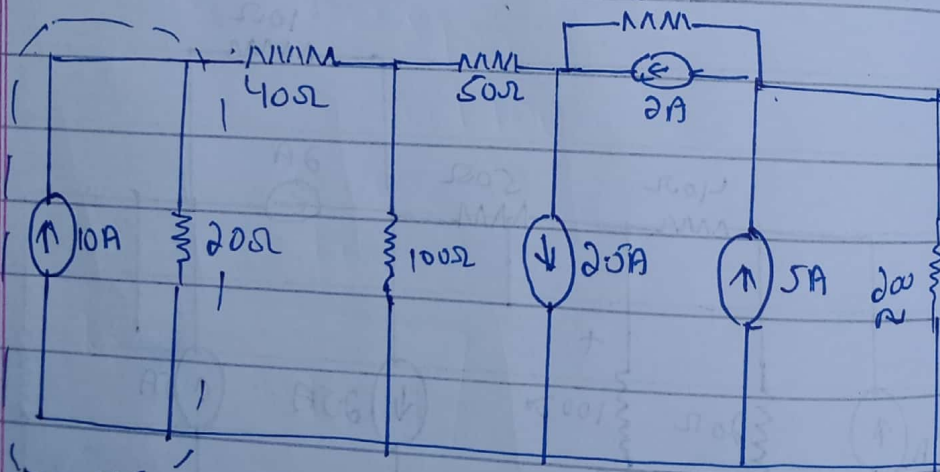So first convert 10A current source to voltage source and redraw circuit.



(23)


NOW

$$V_s = I R$$

$$V_s = 10 \times 20$$

$$V_s = 200 \text{ Volt.}$$

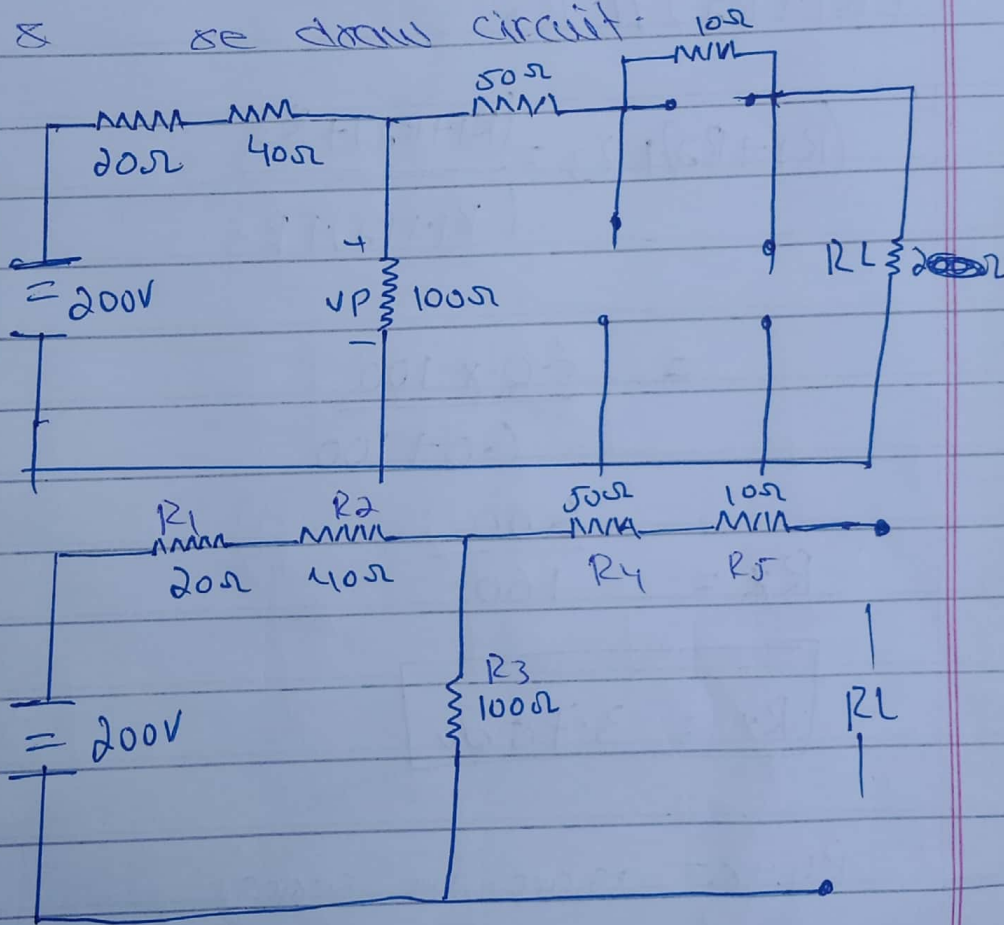For Thevenin equivalent resistance
"RTH" remove all current source
& re draw circuit.



In above Fig:-

~~20~~ R1 & R2 are in series
but parallel to R3

(24)

$$\Rightarrow R_1 + R_2 \parallel R_3$$

⊗ ALSO R_4 & R_5 in series but $\parallel R_3$

$$R_1 + R_2 = 20 + 40$$

$$R_1 + R_2 = 60 \Omega \parallel R_3$$

$$(R_1 + R_2) \parallel R_3$$

$$(R_1 + R_2) \parallel R_3 = \frac{(R_1 + R_2) \cdot R_3}{(R_1 + R_2) + R_3}$$

$$= \frac{60 \times 100}{60 + 100}$$

$$R_x = \frac{600}{160}$$

$$R_x = 3.75 \Omega$$

$R_4 + R_5$ are in series.

$$R_4 + R_5 = 5 + 10$$

$$R_4 + R_5 = 60 = R_y$$

$$R_y = 60$$


(22) (25)

R_1 & R_2 are in

$$R_{TH} = \frac{3.75 \times 60}{3.75 + 60}$$

$$R_{TH} = \frac{225}{63.7}$$

$$R_{TH} = 3.53 \Omega$$

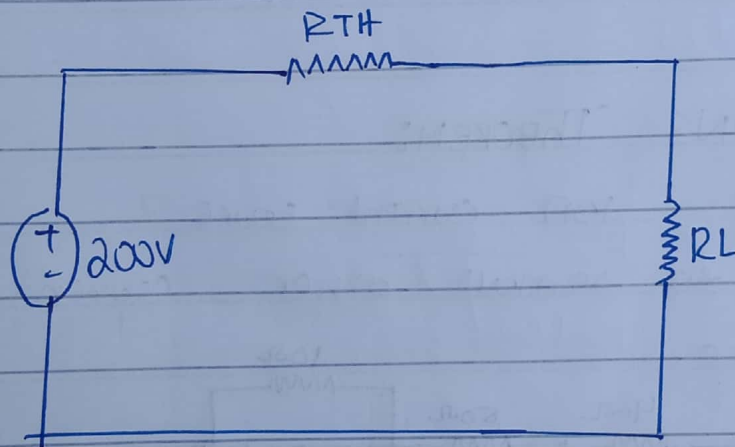


Now by voltage divider rule.

$$V_{TH} = \left(\frac{10}{20 + 40 + 10} \right) \times 200$$

$$V_{TH} = \left(\frac{10}{70} \right) \times 200$$

$$V_{TH} = 28.5 \text{ volt}$$


(28)

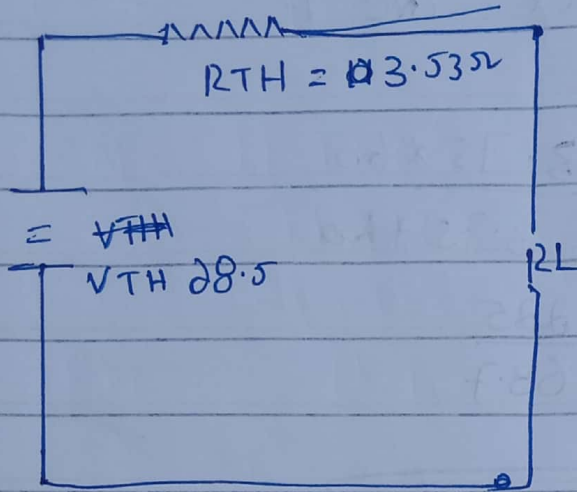

NORTON'S THEOREM:


Take 10A current source

& remove other current source.

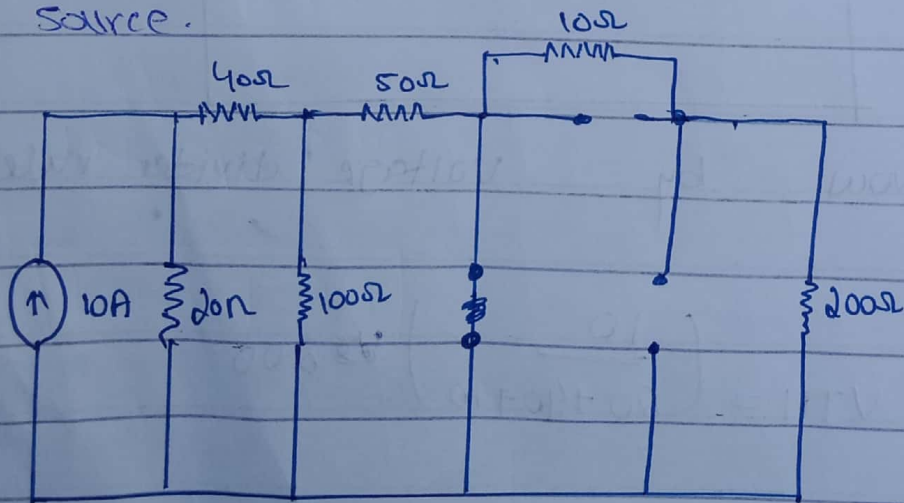

Consider $200\ \Omega$ as R_L And Find R_{N} & I_N .

(24) (27)

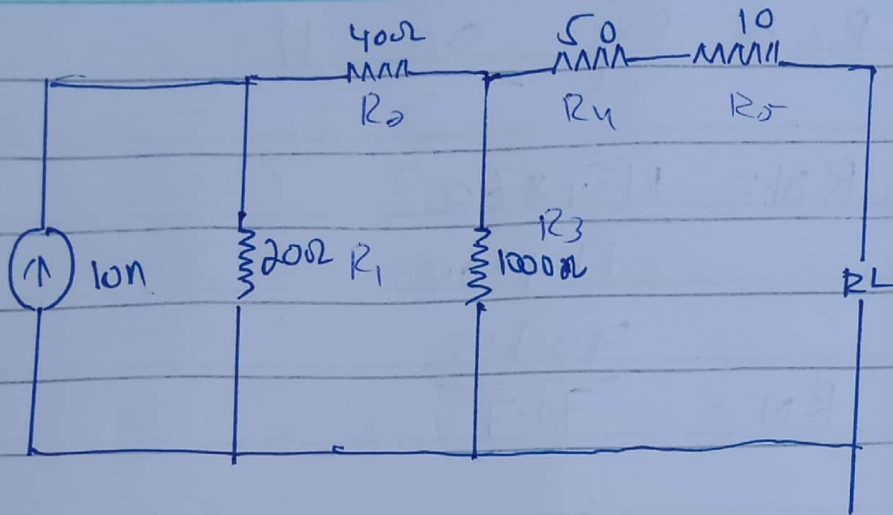

R_4 & R_5 series || R_3
⑥ R_1 & R_2 are parallel.

$$R_1 + R_2 = \frac{20 \times 40}{20 + 40} = \frac{800}{60}$$

$$R_x = 13.3 \Omega$$

R_x || R_3

$$R_x + R_3 = \frac{13.3 \times 100}{13.3 + 100}$$

$$= \frac{1330}{113.3}$$

$$R_y = 11.7 \Omega$$

Now $R_4 + R_5$ in series.

$$R_4 + R_5 = 50 + 10$$

$$R_z = 60 \Omega$$

R_z & R_y are ||
(20) (28)

$$R_N = \frac{11.7 \times 60}{11.7 + 60}$$

$$R_N = \frac{704.3}{71.7}$$


$$R_N = 9.8 \Omega$$

For I_N : we use current divider.

$$I_N = \left(\frac{10}{10 + 60} \right) \times 10$$

$$I_N = \frac{10}{70} \times 10$$

$$I_N = 1.4 \text{ A}$$

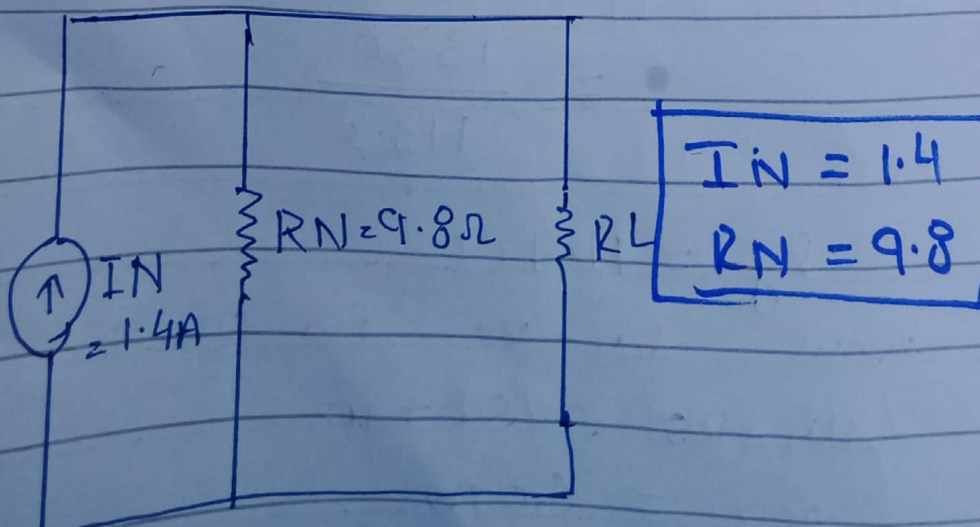


(C)

Value of Thevenin resistance
For deliver maximum power-

We know that

$$P_L = I^2 R_L =$$
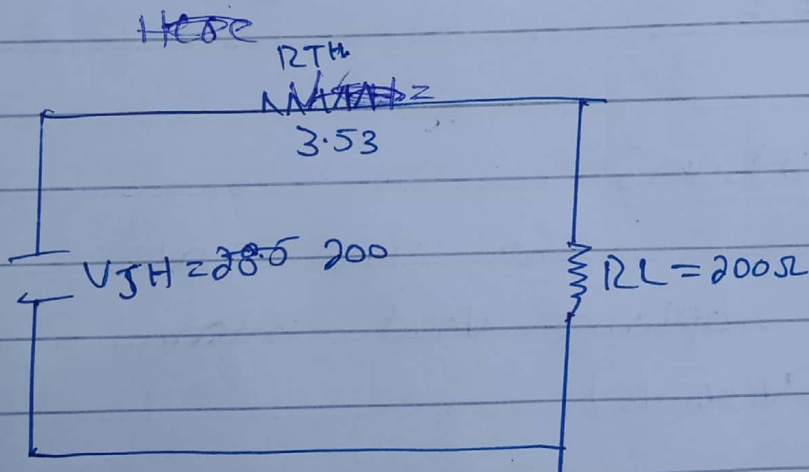
$$P_L = I^2 R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$




$$P_L = \frac{(28.5)^2 \cdot 200}{(200 + 3.53)^2}$$


$$P_L = \frac{11400}{203.5}$$

$$P_L = 56.1 \text{ Watt}$$

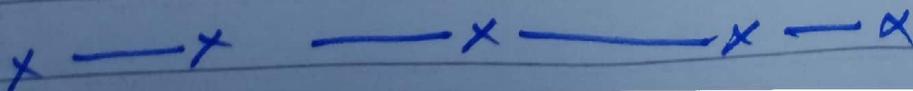maximum power is transfer
when $R_L = R_{TH}$ -



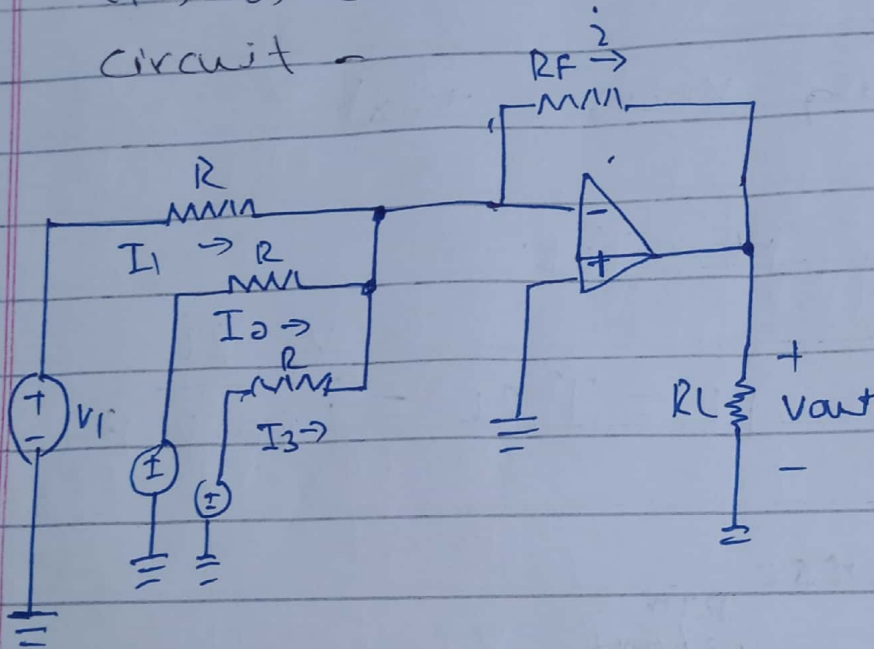Obtain an expression
 For V_{out} in term of
 V_1, V_2, V_3 for op amp
 circuit -



Solution:

As we have
 to obtain V_{out} in term
 (V_1, V_2, V_3)

No current can flow into
 the inverting input terminal

$$i = I_1 + I_2 + I_3$$

We use both value
 when analysis an op amp

Thus

$$V_a = V_b = 0$$

So we can write

$$0 = \frac{V_{out}}{R_F} + \frac{V_1}{R} + \frac{V_2}{R_3} + \frac{V_3}{R}$$

by re-arranging.

$$V_{out} = -\frac{R_F}{R} (V_1 + V_2 + V_3)$$

Here $V_2 = V_3 = 0$

we see that our result agrees, which was derived for essentially the same current.

So we write follow equation at V_a

$$0 = \frac{V_a - V_{out}}{R_F} + \frac{V_a - V_1}{R} + \frac{V_a - V_2}{R} + \frac{V_a - V_3}{R}$$

This equation contain both v_{out} & input voltage, to remove the unknown we need an equation. ~~so~~ remember that we haven't used op amp ~~is~~ rule 2. that ^{we} will certainly used when analyzing op amp circuit.

Thus

$$V_a = V_b = 0$$

$$0 = \frac{v_{out}}{R_F} + \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R}$$

by \times

$$\Rightarrow v_{out} = -\frac{R_F}{R} (V_1 + V_2 + V_3)$$

x — x — x — x —

THE END

x