


ELECTRIC NETWORK ANALYSIS

DARVISH KAYANI

15243

Dr. SHARYAR

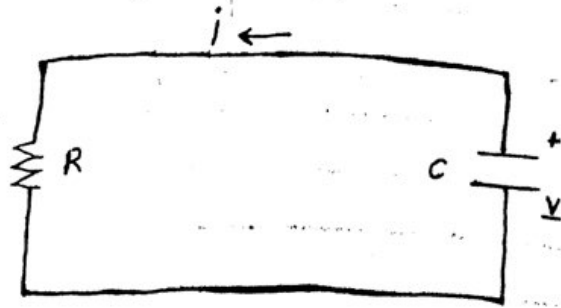Q.1 For the circuit in Fig 1. $i?$
 Find $v = 10e^{-4t}$ and $0.2e^{-4t}$ $t > 0$
 50% of the initial energy.



Step 1
 (A)

$$\tau = RC = \frac{1}{4}$$

$$\Rightarrow -1 = C \frac{dv}{dt}$$

$$\Rightarrow -0.2e^{-4t} = C(10)(-4)e^{-4t}$$

$$\Rightarrow C = 5\text{mF}$$

$$R = \frac{1}{4C} = 50\ \Omega$$

Step 2

(B) $T = RC = \frac{1}{4} = 0.250$

Step 3

(C) $W_e(t) = \frac{1}{2} CV^2$

$$\Rightarrow \frac{1}{2} (5 \times 10^{-3})^2 (100)$$

$$\Rightarrow 250\ \text{mJ}$$

Step 4

$$(D) \quad W_R = \frac{1}{2} \times \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{1}{2} C V_0^2 (1 - e^{-2t_0})$$

$$0.5 = 1 - e^{-8t} \Rightarrow e^{-8t_0} = \frac{1}{2}$$

OR


$$e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2)$$

$$= 86.6 \text{ ms}$$

Q-2

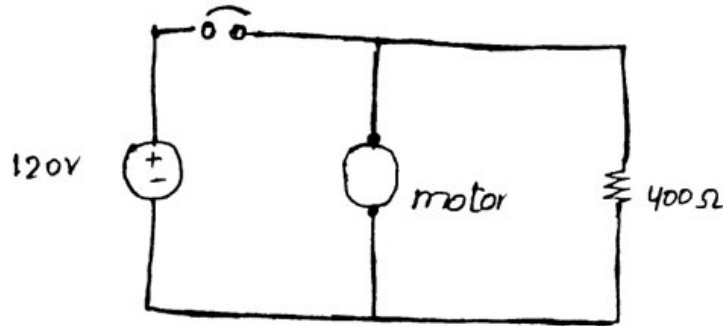120 -V dc generator energize a motor whose coil The breaker is tripped.



Let the inductor current.

For $t < 0$

$$i(0) = \frac{120}{100} = \frac{12}{10}$$

$$\Rightarrow \frac{6}{5} = 1.2 \text{ A}$$

For $t > 0$ we have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100 + 400}$$

$$= \frac{50}{500} \Rightarrow \frac{5}{50} \Rightarrow \frac{1}{10} \Rightarrow \boxed{0.1}$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$i(t) = 1.2e^{-10t}$$

4

$$\text{At } t = 100 \text{ ms} = 0.1 \text{ s}$$

$$i(0.1) = 1.2 e^{-1} = 0.441 \text{ A}$$

Q=3 The Response of Series RLC
the Value of R, L, C

Series RLC Circuit

$$V_1(t) = 30 - 10 e^{-20t} + 30 e^{-10t} \text{ V}$$

$$V(t) = V_1 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega]$$

$$40 e^{-20t} - 60 e^{-30t} \text{ mA}$$

$$\Leftrightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega]$$

Comparing these equation we get

$$V_s = 30$$

$$A_1 = -10 j \quad A_2 = 30 j$$

$$s_1 = -20 j \quad s_2 = -10 \quad (a)$$

$$A'_1 = 40 j \quad A'_2 = -60 j$$

$$s'_1 = -20 j \quad s'_2 = -10 \rightarrow (b)$$

Step 2:-

Now Equ (a) & (b)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega^2} \quad \text{And} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega^2}$$

$$s_1 + s_2 = -2\alpha \quad \text{and} \quad s_1 s_2 = \omega_0^2$$

$$\left[\text{where } \alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$\Rightarrow \alpha = 15$$

$$\Rightarrow \frac{R}{2L} = 15 \rightarrow (c)$$

$$200 = \omega_0^2 \Rightarrow \frac{1}{LC} = 200 \rightarrow (d)$$

Step 3:

$$i(t) = C \frac{di}{dt}(t) = C [200e^{-20t} - 300e^{-30t}]$$

$$(A_1 e^{s_1 t} + A_2 e^{s_2 t}) \times 10^{-3} \quad A = C \{ [200e^{-20t} - 300e^{-30t}] \}$$

OR

$$[s_1 = -20 \quad s_2 = -30]$$

$$\Rightarrow 200C = A_1 = 40 \times 10^{-3}$$

$$\Rightarrow 200C = A_2 = 40 \times 10^{-3}$$

$$\Rightarrow C = 200 \times 10^{-6} \text{ F} \Rightarrow C = 200 \mu\text{F}$$


using eqn (c) and (d)

$$L = \frac{1}{200C} = \frac{1}{200 \times 200 \times 10^{-6}} \Rightarrow L = 25 \text{ mH}$$

$$\& R = 30L = 30 \times 25 = 750 \Omega$$

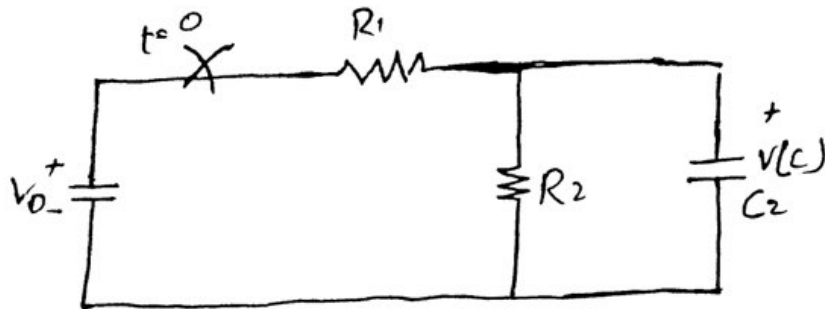
Q4 :-

The circuit in Fig. 3 is the electrical analog of body function



For $t=0$ $v(0) = 0$

For $t > 0$ the circuit is shown below

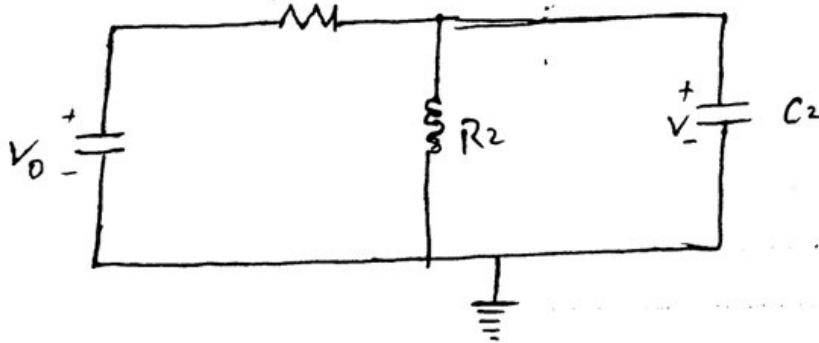

$$V_0 - v/R_1 = (v/R_2) + C_2 dv/dt$$

$$V_0 = v(1 + R_1/R_2) + R_1 C_2 dv/dt$$

$$60 = (1 + 5/2.5) + (5 \times 10^6 \times 5 \times 10^{-6}) dv/dt$$

$$60 = 3v + 25 dv/dt$$

$$v(t) = v_s + [Ae^{-3t/25}]$$


Where

$$3V_s = 60 \text{ yields } V_s = 20$$

$$V(0) = 0 = 20 + A \text{ or } A = -20$$

$$V(t) = 20 (1 - e^{-3t/25}) \text{ V.}$$

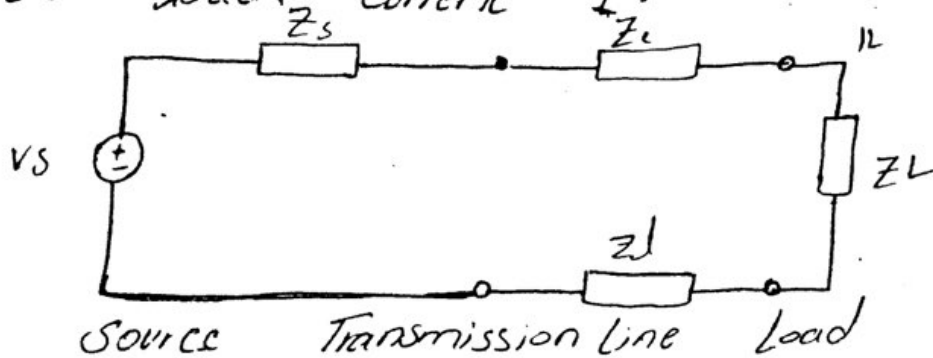Q=5 A Power Transmission System is modeled as shown --- Find the load current I_2 .



$$Z = Z_a + 2Z + Z_c$$

$$= (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$


$$Z = 25 + j20$$

$$I_2 = \frac{V_s}{Z} = \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_2 = 3.5926 \angle -38.66^\circ \text{ A}$$

Q=6 :-

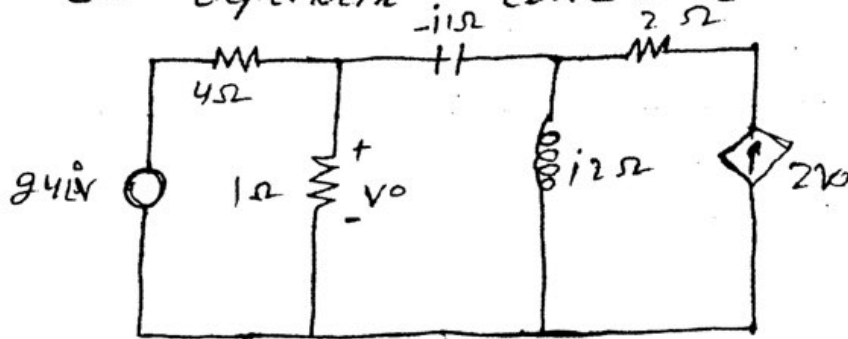For the circuit in Fig. 5. Find the dependent current source.



Consider the circuit as shown

At node 0

$$\frac{24 - V_0}{4} = \frac{V_0}{1} + \frac{V_0 - V_1}{-j}$$

$$24 = (5 + j4)V_0 - j4V_1 \quad \text{--- (1)}$$

At node 1

$$\frac{V_0 - V_1}{-j} + 2V_0 = \frac{V_1}{j2}$$

$$V_1 = (2 - j4)V_0 \quad \text{--- (2)}$$

Substituting (2) into (1)

$$24 = (5 + j4 - j8 - 16)V_0$$

$$V_0 = \frac{24}{11 + j4}, \quad V = \frac{(-24)(2 - j4)}{11 + j4}$$

Voltage is across the dependent source

$$V_2 = V_1 + (2)(2V_0) = V_1 + 4V_0$$

$$V_2 = \frac{-24}{11+j4} - (2-j4+4) = \frac{(-24)(6-j4)}{11+j4}$$

$$S = V_2 I = V_2 (2V_0)$$

$$S = \frac{(-24)(6-j4)}{11+j4} - \frac{-48}{11-j4} = \left(\frac{1152}{137} \right) (6-j4)$$

$$S = (50.48 - j33.64) \text{ VA}$$