

Department of Electrical Engineering

Assignment

Date: 24/06/2020

Course Details

Course Title: Electric Power Transmission Module: 4rth
Instructor: ENGR. AMIR AAMAN Total Marks: 50

Student Details

Name: AZHAD NIAZ Student ID: 15493

Q1	A single phase line has two parallel conductors 2 meters apart. The diameter of each conductor is 1.2 cm. Calculate the loop inductance per km of the line.	Marks 10
		CLO 1
Q2	A single phase transmission line has two parallel conductors 3 m apart, the radius of each conductor being 1 cm. Calculate the loop inductance per km length of the line if the material of the conductor is (i) Copper (ii) Steel with relative permeability of 100.	Marks 10
		CLO 1
Q3	A long transmission lines more than 240kms are consisting of high amount of capacitance and inductance distributed across the entire length of the line. Ferranti effect occurs when current drawn by the distributed capacitance of the line itself is greater than the current associated with the load at the receiving end of the line (during light or no load). Why Ferranti effect occurs in long transmission line? Back your answer with valid data, facts and figures.	Marks 10
		CLO 1
Q4	A 3-phase load of 2000 kVA, 0.8 p.f. is supplied at 6.6 kV, 50 Hz by means of a 33 kV transmission line 20 km long and 33/6.6 kV step-down transformer. The resistance and reactance of each conductor are 0.4 Ω and 0.5 Ω per km respectively. The resistance and reactance of transformer primary are 7.5 Ω and 13.2 Ω , while those of secondary are 0.35 Ω and 0.65 Ω respectively. Find the voltage necessary at the sending end of transmission line when 6.6 kV is maintained at the receiving end. Determine also the sending end power factor and transmission efficiency.	Marks 10
		CLO 2
Q5	A 132 kV line with 1.956 cm dia. conductors is built so that corona	Marks 10

	takes place if the line voltage exceeds 210 kV (r.m.s.). If the value of potential gradient at which ionization occurs can be taken as 30 kV per cm, find the spacing between the conductors.	CLO 2
--	---	-------

Student Details

Name: AZHAD NIAZ

Student ID: 15493

Q1: A single phase line has two parallel conductors 2 meters apart. The diameter of each conductor is 1.2 cm.

Calculate the loop inductance per km of the line.

Solution

Given data:

Spacing of conductors, $d = 2 \text{ m} = 200 \text{ cm}$

Radius of conductor, $r = \frac{1.2}{2} = 0.6 \text{ cm}$

Loop inductance per meter length of the line = $10^{-7} \left(\frac{1+4 \logged}{r} \right) \text{ H}$

$$= 10^{-7} \left(\frac{1+4 \log_e 200}{0.6} \right) \text{ H} = 24.23 \times 10^{-7} \text{ H}$$

Loop inductance per km of the line = $24.23 \times 10^{-7} \times 1000 \text{ H}$

$$= 24.23 \times 10^{-4} \text{ H} = 2.423 \text{ mH}$$

Ans.

Q2: A single phase transmission line has two parallel conductors 3 m apart, the radius of each conductor being 1 cm. Calculate the loop inductance per km length of the line if the material of the conductor is

(i) Copper

Steel with relative permeability of 100

Student Details

Name: AZHAD NIAZ

Student ID: 15493

ANS2:

Solution:

given data

Spacing of conductors, $d = 300$ cm

Radius of conductor, $r = 1$ cm

$$\text{Loop inductance} = 10^{-7} \left(\frac{\mu r + 4 \log_e d}{r} \right) \text{ H/m}$$

$$\therefore \text{Loop inductance/m} = 10^{-7}$$

$$\left(\frac{1 + 4 \log_e d}{r} \right) \text{ H} = 10^{-7}$$

$$\left(\frac{1 + 4 \log_e 300}{1} \right) \text{ H} = 23.8 \times 10^{-7}$$

$$\text{Loop inductance/km} = 23.8 \times 10^{-7}$$

$$\times 1000 = 2.38 \times 10^{-3} \text{ H} = 2.38 \text{ mH}$$

Student Details

Name: AZHAD NIAZ

Student ID: 15493

With steel conductors, $\mu_r = 100$

\therefore Loop inductance/m = 10^{-7}

$$\left(\frac{100 + 4 \log_e 300}{1}\right) H = 122.8 \times 10^{-7} H$$

Loop inductance/km = $122.8 \times 10^{-7} \times 1000$

$$= 12.28 \times 10^{-3} H$$

$$= 12.28 \text{ mH}$$

Q3:

A long transmission lines more than 240kms are consisting of high amount of capacitance and inductance distributed across the entire length of the line. Ferranti effect occurs when current drawn by the distributed capacitance of the line itself is greater than the current associated with the load at the receiving end of the line (during light

or no load). Why Ferranti effect occurs in long transmission line? Back your answer with valid data, facts and figures

Student Details

Name: AZHAD NIAZ

Student ID: 15493


ANS:

A long transmission lines more than 240kms are consisting of high amount of capacitance and inductance distributed across the entire length of the line. Ferranti effect occurs when current drawn by the distributed capacitance of the line itself is greater than the current associated with the load at the receiving end of the line (during light or no load) This capacitor charging current leads to a voltage drops across the line inductor of transmission system which is in phase with sending end voltages this voltage drop keeps on increasing additionally as we move toward the load end of the line and subsequently the receiving end voltage tend to get larger than applied voltage leading to the phenomena called Ferranti effect.

During no load or light load condition, the reactive power generated at a point on the Transmission Line will be more than the reactive power absorbed and therefore the voltage at that point will rise. Mind that during no load or light load condition the line capacitance will dominate to inductance.

The Ferranti Effect occurs when current drawn by the distributed capacitance of the transmission line itself is greater than the current associated with the load at the receiving end of the line. Therefore, the Ferranti effect tends to be a bigger problem on lightly loaded lines and especially on underground cable circuits where the shunt capacitance is greater than with a corresponding overhead line. This effect is due to the voltage drop across the line inductance (due to charging current) being in phase with the sending end voltages. As this voltage drop affects the sending end voltage, the receiving end voltage becomes greater. The Ferranti Effect will be more pronounced the longer the line and the higher the voltage applied.

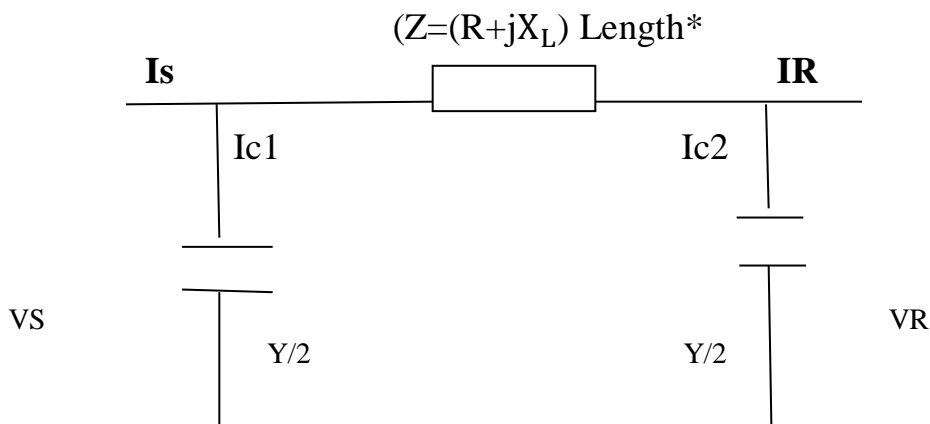The Ferranti Effect is not a problem with lines that are loaded because line capacitive effect is constant independent of load, while inductance will vary with load. As inductive load is added, the VAR generated by the line capacitance is consumed by the load.



Student Details

Name: AZHAD NIAZ

Student ID: 15493

V_R = receiving end voltage

V_S = sending end voltage

I_L = Line current

I_s = current at sending end

I_r = receiving end current

I_{c1} = line capacitive current at sending end

I_{c2} = line capacitive current at receiving end

Z = line impedance

R = line resistance

L = inductance of transmission line

C = capacitance of line

Y = conductance of line

L = length of conductor

X_L = inductive reactants of conductor

Student Details

Name: AZHAD NIAZ

Student ID: 15493

Q:A 3-phase load of 2000 kVA, 0.8 p.f. is supplied at 6.6 kV, 50 Hz by means of a 33 kV transmission line 20 km long and 33/6.6 kV step-down transformer. The resistance and reactance of each conductor are 0.4 Ω and 0.5 Ω per km respectively. The resistance and reactance of transformer primary are 7.5 Ω and 13.2 Ω , while those of secondary are 0.35 Ω and 0.65 Ω respectively. Find the voltage necessary at the sending end of transmission line when 6.6 kV is maintained at the receiving end. Determine also the sending end power factor and transmission efficiency

Solution:

The single diagram of the transmission system. Here, the voltage drop will be due to the impedance of transmission line and also due to the impedance of transformer.

$$\text{Resistance of each conductor} = 20 \times 0.4 = 8\Omega$$

$$\text{Reactance of each conductor} = 20 \times 0.5 = 10\Omega$$

Let us transfer the impedance of transformer secondary to high tension side i.e., 33 kV side.

Equivalent resistance of transformer referred to 33 kV side

$$= \text{Primary resistance} + 0.35 \left(\frac{33}{6.6}\right)^2$$

$$= 7.5 + 815 = 16.25\Omega$$

Equivalent reactance of transformer referred to 33 kV side

$$= \text{Primary reactance} + 0.65 \left(\frac{33}{6.6}\right)^2$$

$$= 13.2 + 16.25 = 29.45\Omega$$

Student Details

Name: AZHAD NIAZ

Student ID: 15493

Total resistance of line and transformer is

$$R = 8 + 16.25 = 24.25 \Omega$$

Total reactance of line and transformer is

$$x_L = 10 + 29.45 = 39.45 \Omega$$

Receiving end voltage per phase is

$$v_R = 33,000 / \sqrt{3} = 19052 \text{ V}$$

Line current

$$I = \frac{2000 \times 10^3}{\sqrt{3} \times 33000} = 35 \text{ A}$$



Student Details

Name: AZHAD NAIZ

Student ID: 15493

Using the approximate expression for sending end voltage v_s per phase.

$$v_s = v_R + IR \cos \phi_R + I x_L \sin \phi_R$$

$$= 19052 + 35 \times 24.25 \times 0.8 + 35 \times 39.45 \times 0.6$$

$$= 19052 + 679 + 828 = 20559 \text{ V} = 20.559 \text{ kV} = 45$$

$$\text{Sending end line voltage} = \sqrt{3} \times 20.559 \text{ kV} = 35.6 \text{ Kv}$$

$$\text{Sending end p.f.} \quad \cos \phi_s = \frac{v_R \cos \phi_R + IR}{V_s} = \frac{19052 \times 0.8 + 35 \times 24.25}{1000} = 89.12 \text{ Kw}$$

$$= \frac{3I^2R}{1000} \text{ kW} = \frac{3 \times (35^2) \times 24.25}{1000} = 89.12 \text{ Kw}$$

$$= 2000 \text{ Kva} \times 0.8 = 1600 \text{ Kw}$$

❖ Transmission efficiency

$$= \frac{1600}{1600 + 89.12} \times 100 = 94.75 \%$$

Student Details

Name: AZHAD NIAZ

Student ID: 15493

Q5:

A 132 kV line with 1.956 cm dia. conductors is built so that corona takes place if the line voltage exceeds 210 kV (r.m.s.). If the value of potential gradient at which ionization occurs can be taken as 30 kV per cm, find the spacing between the conductors.

SOLUTION:

$$r \frac{1.956}{2} = 0.978 \text{ cm}$$

$$E_0 = \frac{30}{\sqrt{3}} = 21.2 \text{ (r.m.s)}$$

$$m_0 = 1 \text{ (smooth conductor)}$$

$$\delta = 1 \text{ (standard pressure and temperature)}$$

$$V_0 = 21.1 m_0 \delta r \ln \frac{d}{r}$$

$$\text{Disruptive voltage/phase} = \frac{210}{\sqrt{3}} = 121.25 \text{ Kv}$$

$$\therefore 121.25 = 21.1 \times 1 \times 1 \times 0.978 \times \ln \frac{d}{r}$$

$$\ln \frac{d}{r} = 5.84$$

Ans.