

Name Muhammad Bilal Khan

ID 16434

Date 20-06-2020

Submitted to Sr. Sohail Imran

Subject Linear Circuit Analysis

Assignment Sectional

(ii) Applying KCL on node 2

$$\frac{V_0 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{50} = 0$$

$$\frac{5V_2 - 5V_1 + 2V_2 + 4V_2 - 4V_3}{100} = 0$$

$$-5V_1 + 11V_2 - 4V_3 = 0 \quad \text{--- (2)}$$

(iii) Applying KCL on node 3

$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_4}{10} = 2 - 2.5$$

$$\frac{5V_3 - 5V_2 + V_3 - V_4}{50} = -0.5$$

$$-5V_2$$

$$\frac{V_3 - V_2 + 5V_3 - 5V_4}{50} = -0.5$$

$$-V_2 + 6V_3 - 5V_4 = -25 \quad \text{--- (3)}$$

(4) Applying KCL on node (4)

$$\frac{V_2 - V_1}{10} + \frac{V_2}{200} = 5 - 1$$

$$\frac{20V_2 - 20V_1 + V_2}{200} = 3$$

$$-20V_1 + 21V_2 = 600 \quad (4)$$

Solving further by using calculator.

we get

$$V_1 = 180.46 \text{ V}$$

$$V_2 = 141.37 \text{ V}$$

$$V_3 = 163.22 \text{ V}$$

$$V_4 = 172.59 \text{ V}$$

As from the figure we know


$$V_2 = V_P$$

Result:

$$V_P = 141.37 \text{ V}$$



Q No 3  
ANIS 22 figure 8

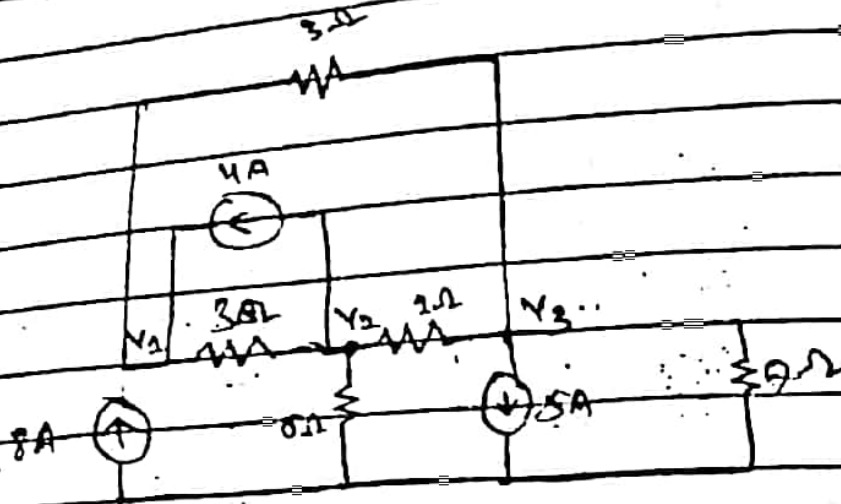

Solution:

Solving by node analysis

① Applying KCL on node 1

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{3} = 8 + 4$$

$$\frac{V_1 - V_2 + V_1 - V_3}{3} = 12$$

$$2V_1 - V_2 - V_3 = 36 \quad \text{--- (1)}$$

② Applying KCL on node 2

$$\frac{V_2 - V_1}{3} + \frac{V_2}{3} + \frac{V_2 - V_3}{1} = 4$$

$$5V_2 - 5V_1 + V_2 + 15V_2 - 15V_3 = 4$$



$$-5V_1 + 23V_2 - 15V_3 = -60 \quad \text{--- (2)}$$

(13) Applying KCL on node (3) n

$$\frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{3} + \frac{V_3}{7} = 5$$

$$21V_3 - 21V_2 + 7V_3 - 7V_1 + V_3 = 5 \times 21$$

$$-7V_1 - 21V_2 + 31V_3 = -105 \quad \text{--- (3)}$$

Solving by Cramer's rule

2	-1	-1	$V_1$	36
-5	2	-15	$V_2$	4
-7	-21	31	$V_3$	-105
A			X	B

$ A  =$	2	-1	-1
	-5	2	-15
	-7	-21	31

2	2	-15	1	-5	-15	1	5	2
	-21	31		-7	31		-7	-21

$$= -506 - 260 - 119$$

$$= -786$$

$$V_1 = \frac{|AB|}{|A|} = \frac{\begin{vmatrix} 36 & -1 & -1 \\ 4 & 2 & -15 \\ -105 & -21 & 31 \end{vmatrix}}{\begin{vmatrix} 2 & -5 & -7 \\ 4 & 2 & -15 \\ -105 & -21 & 31 \end{vmatrix}}$$

$$= \frac{36 \begin{vmatrix} 2 & -15 \\ -21 & 31 \end{vmatrix} + \begin{vmatrix} 4 & -15 \\ -105 & 31 \end{vmatrix} - 1 \begin{vmatrix} 4 & 2 \\ -105 & -21 \end{vmatrix}}{\begin{vmatrix} 2 & -5 & -7 \\ 4 & 2 & -15 \\ -105 & -21 & 31 \end{vmatrix}}$$

$$= \frac{-9108 - 1451 - 126}{-10625} = \frac{786}{10625}$$

$$V_1 = 13.59$$

$$V_2 = \frac{\begin{vmatrix} 2 & 36 & -1 \\ -5 & 4 & -15 \\ -7 & -105 & 31 \end{vmatrix}}{\begin{vmatrix} 2 & -5 & -7 \\ 4 & 2 & -15 \\ -105 & -21 & 31 \end{vmatrix}}$$

$$= \frac{2 \begin{vmatrix} 4 & -15 \\ -105 & 31 \end{vmatrix} - 36 \begin{vmatrix} -5 & -15 \\ -7 & 31 \end{vmatrix} - 1 \begin{vmatrix} -5 & 4 \\ -7 & -105 \end{vmatrix}}{\begin{vmatrix} 2 & -5 & -7 \\ 4 & 2 & -15 \\ -105 & -21 & 31 \end{vmatrix}}$$

$$= \frac{-2902 - 9360 - 553}{-12815} = \frac{786}{12815}$$

$$V_2 = 16.30$$

Date:   /  /  

$$V_3 = \begin{vmatrix} 2 & -1 & 36 \\ -5 & 2 & 4 \\ -7 & -21 & -105 \end{vmatrix}$$

$$= \begin{vmatrix} 2 & 4 & +1 & -5 & 4 & +36 & -5 & 2 \\ -21 & -105 & & -7 & -105 & & -7 & -21 \end{vmatrix}$$

$$= -35280 + 553 + 4284$$

$$= -30443$$

$$= 786$$

$$V_3 = 38.73$$

Now we know that

$$V_{s-2} = V_2$$

$$V_{s-2} = 16.30V$$


$$P = \frac{V^2}{R} = \frac{V_3^2}{7}$$

$$P = \frac{(38.73)^2}{7}$$

$$P = 2149.8 \text{ W}$$



QNO 4  
ANS:

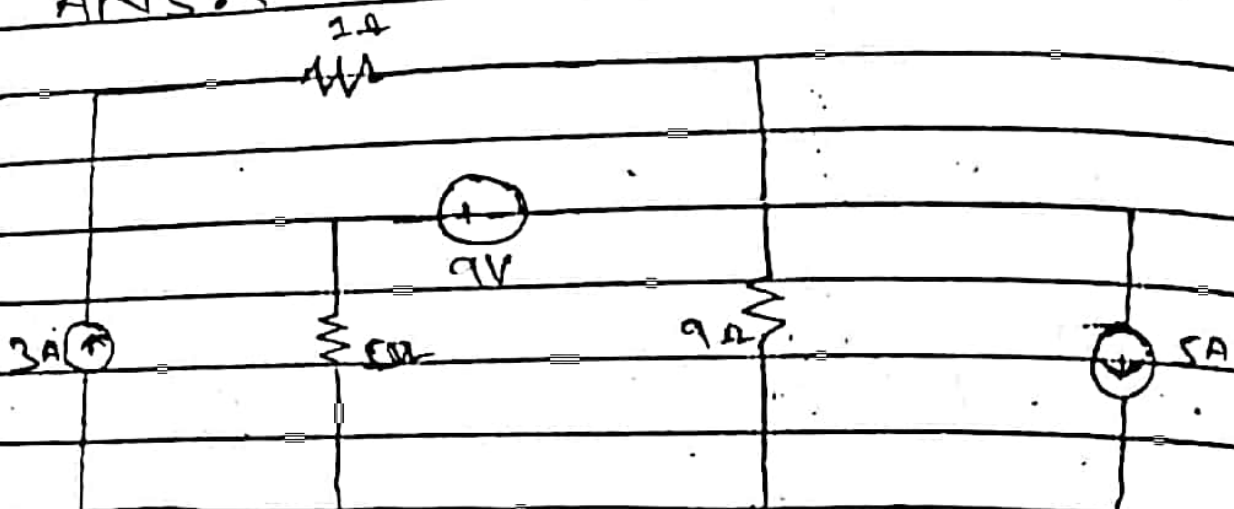

Solution:

Considering  $V_1$  &  $V_2$   
as a supernode

Applying KCL on supernodes

$$\frac{V_1 - V_2}{1} + \frac{V_1}{5} + \frac{V_2 - V_1}{1} + \frac{V_2}{9} = 3 - 5$$

$$45V_1 - 45V_2 + 9V_1 + 45V_2 - 45V_1 + 9V_2 = 27 - 45$$

$$9V_1 + 9V_2 = 135 \quad \text{--- (1)}$$

$$V_1 - V_2 = 9 \quad \text{--- (2)}$$

Combining eq (1) & (2)

$$\begin{aligned} 9V_1 + 9V_2 &= 135 \\ 9V_1 - 9V_2 &= 81 \\ \hline 18V_1 &= 216 \end{aligned}$$

$$V_1 = \frac{216}{18}$$

$$V_1 = 12V$$


Putting in eq (2)

$$\begin{aligned} V_2 &= V_1 - 9 \\ V_2 &= 12 - 9 \end{aligned}$$

$$V_2 = 3$$

Q105

ANS: figure 8

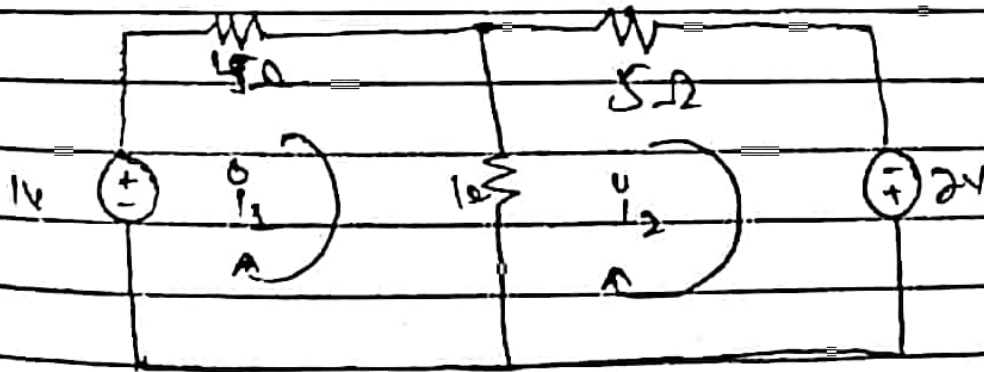

Solution

Solving by MESH analysis.

Applying KVL on  $i_1$

$$4i_1 + 2(i_1 - i_2) = 1$$



$$5i_1 - i_2 = 1 \quad \text{--- (1)}$$

(ii) Applying KVL on  $i_2$ :

$$1(i_2 - i_1) + 5i_2 = 2$$

$$-i_1 + 6i_2 = 2 \quad \text{--- (ii)}$$

Multiplying 5 with eq (2)

By adding with eq (1)

$$\cancel{5i_1} - i_2 = 1$$

$$-5i_1 + 30i_2 = 10$$

$$\hline 29i_2 = 11$$

$$i_2 = 11/29$$

$$i_2 = 0.3794$$

Putting in eq (1)

$$5i_1 = 1 + 0.379$$

$$i_1 = 0.275A$$

Result


$$i_1 = 0.275A$$

$$i_2 = 0.379A$$



QNO 6

ANS figure on

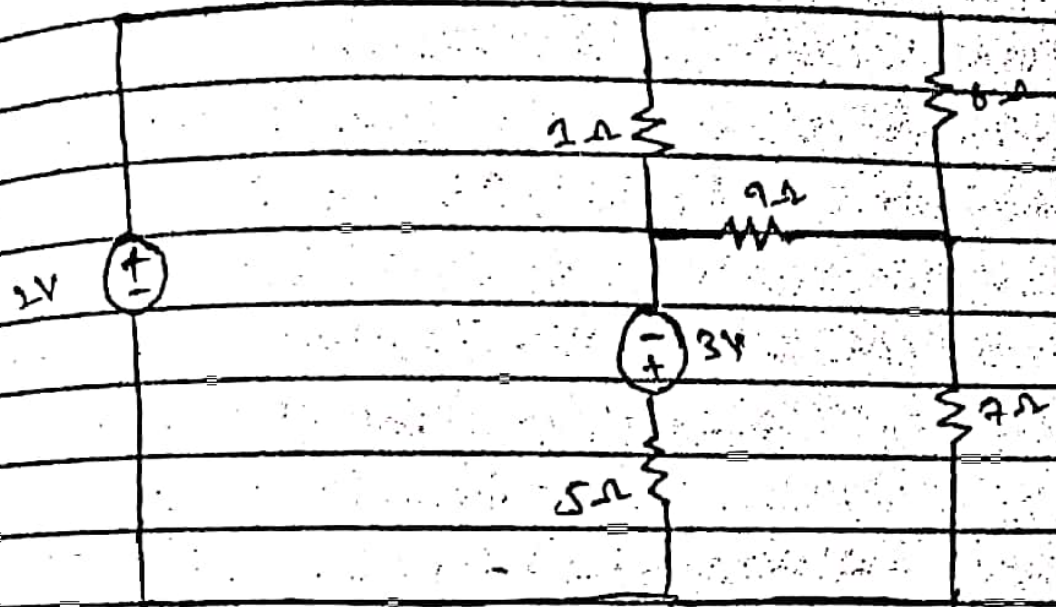

Soln

APPLYING KCL ON  $i_2$  MESH 2

$$1(i_2 - i_1) + 5(i_2 - i_3) = 3 + 2$$

$$i_2 - i_1 + 5i_2 - 5i_3 = 5$$

$$6i_2 - i_1 - 5i_3 = 5 \quad \text{--- (1)}$$

APPLYING KCL ON  $i_3$  MESH 3

$$1(i_2 - i_1) + 6i_3 + 9(i_2 - i_3) = 0$$

$$-i_1 + 16i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

Applying KCL on loop 1

$$5(i_3 - i_2) + 9(i_3 - i_2) + 7i_3 = -3$$

$$-5i_2 - 9i_2 + 21i_3 = -3 \quad \text{--- (2)}$$

Solving by Cramer's rule

$$\begin{bmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 0 \\ -3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{vmatrix}$$

$$= 6 \begin{vmatrix} 16 & -9 \\ -9 & 21 \end{vmatrix} - (-1) \begin{vmatrix} -1 & -9 \\ -5 & 21 \end{vmatrix} - 5 \begin{vmatrix} -1 & 16 \\ -5 & -9 \end{vmatrix}$$

$$= 6(295) - (-1)(-66) - 5(89)$$

$$= 1015$$

$$i_1 = \frac{\begin{vmatrix} 3 & -1 & -5 \\ 0 & 16 & -9 \\ -3 & -9 & 21 \end{vmatrix}}{1015}$$

$$= \frac{3 \begin{vmatrix} 16 & -9 \\ -9 & 21 \end{vmatrix} - (-1) \begin{vmatrix} -1 & -9 \\ -3 & 21 \end{vmatrix} - 5 \begin{vmatrix} -1 & 16 \\ -3 & -9 \end{vmatrix}}{1015}$$



$$i_2 = \frac{1008}{1015}$$

$$i_2 = 0.993$$

$$i_2 = \begin{array}{|ccc|} \hline 6 & 5 & -5 \\ \hline -1 & 0 & -9 \\ \hline -5 & -3 & 21 \\ \hline \end{array}$$

$$= \begin{array}{|ccc|cc|cc|cc|} \hline 6 & 5 & -5 & -1 & 0 & -9 & -5 & -3 & 21 \\ \hline -1 & 0 & -9 & -5 & -3 & 21 & -5 & -3 \\ \hline \end{array}$$

$$i_2 = \frac{153}{1015} = 0.150$$

$$i_3 = \begin{array}{|ccc|} \hline 0 & -1 & 5 \\ \hline -1 & +16 & 0 \\ \hline -5 & -9 & 3 \\ \hline \end{array}$$

$$= \begin{array}{|ccc|cc|cc|cc|} \hline 6 & 16 & 0 & +1 & -1 & 0 & +5 & -1 & 16 \\ \hline -9 & 3 & -5 & -5 & 3 & -5 & -9 \\ \hline \end{array}$$

$$= \frac{730}{1015}$$


$$i_3 = 0.719$$



Q. NO 7 b

ANS in

figure on

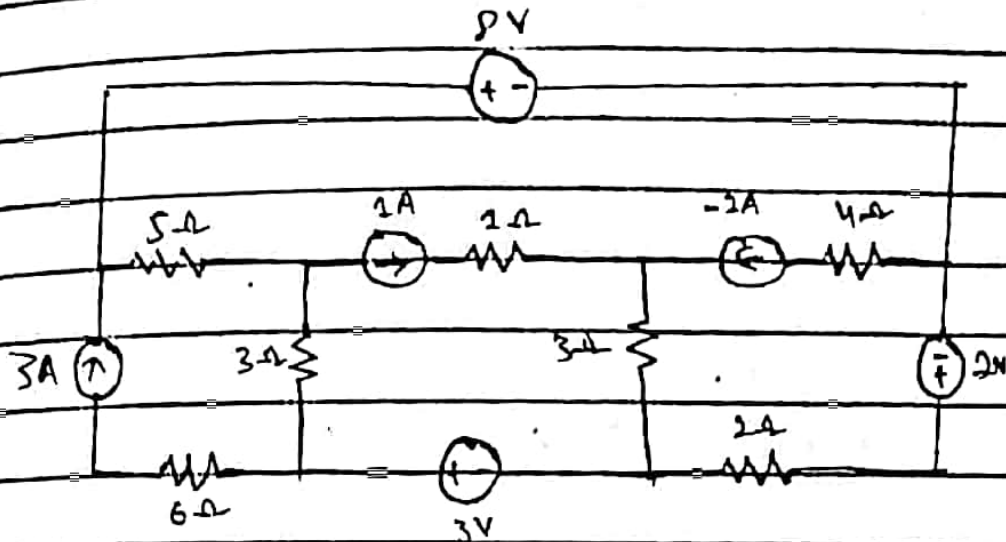

Considering  $i_1, i_2, i_3$  as a  
Supernode,  
Applying KCL Supernode,

$$5(i_1 - 3) + 3(i_2 - 3) + 2i_3 = 3 + 2 - 8$$

$$5i_1 - 15 + 3i_2 - 9 + 2i_3 = -3$$

$$5i_1 + 3i_2 + 2i_3 = 12 \quad \text{--- (1)}$$

we also know that

$$i_2 - i_1 = 1$$

where  $i_2 = 1 + i_1 \quad \text{--- (2)}$

$$i_1 - i_3 = -2$$

$$i_3 = 1.2 + i_1 \quad \text{--- (3)}$$

Putting in eq (1)

$$5i_1 + 3(1 + i_1) + 2(-2 + i_1) = 12$$

$$5i_1 + 3 + 3i_1 - 4 + 2i_1 = 12$$

$$10i_1 - 1 = 12$$

$$i_1 = \frac{13}{10}$$

$$i_1 = 1.3 \text{ A}$$

Putting in eq A & B

$$i_2 = 1 + 1.3$$

$$i_2 = 2.3 \text{ A}$$

$$i_3 = 1 + 2 + 1.3$$

$$i_3 = 4.3 \text{ A}$$

Result


$$i_1 = 1.3 \text{ A}$$

$$i_2 = 2.3 \text{ A}$$

$$i_3 = 4.3 \text{ A}$$



Q.2  
ANS in figure in

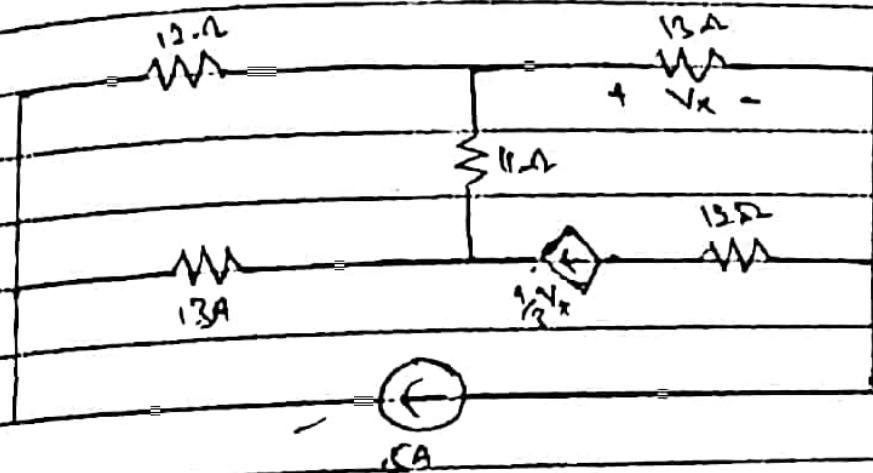

from the figure we know that 5A current is flowing through  $i_2$

$$i_1 = 5A$$

now

there is an independent source  $i_2$  by  $i_3$

So  $V_1 - V_3 = \frac{1}{3} V_x$

or  $V_x = 13i_3$

$$i_3 = \frac{13i_3}{13} + 5$$

$$i_3 = -1.5A$$

Applying mesh analysis on  $i_2$ .



$$13(i_2 - i_1) + 11(i_2 - i_3) + 12i_2 = 0$$

$$13i_2 - 13i_1 + 11i_2 - 11i_3 + 12i_2 = 0$$

$$36i_2 - 13(8) - 11(-1.5) = 0$$

$$36i_2 = 65 - 16.5$$

$$i_2 = \frac{48.5}{36}$$

$$i_2 = 1.347 \text{ A}$$

QNO2 CHAPTER 5

ANSW (2)

Figure 2



Solutions


Setting the right-hand side voltage as a short circuit & the current source as an open circuit

Re-drawing the circuit.



As  $5\Omega$  &  $2\Omega$  are in parallel combining both.
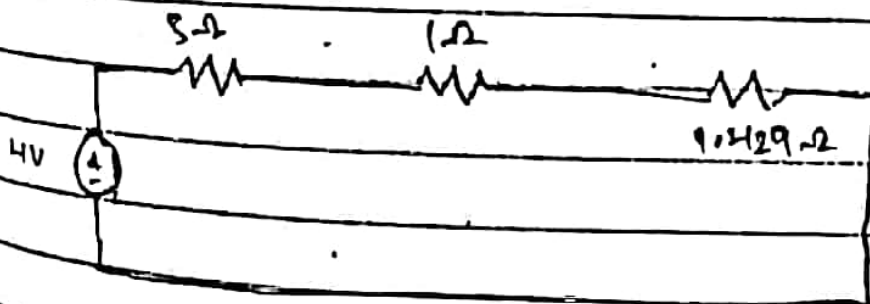
$$= \frac{5 \times 2}{5 + 2} = 1.429 \Omega$$




Apply mesh analysis

$$3i_1 + 1i_2 + 1.429i_2 = 4$$

$$i_2 = \frac{4}{5.429}$$

$$i_1 = V_x = 0.736$$

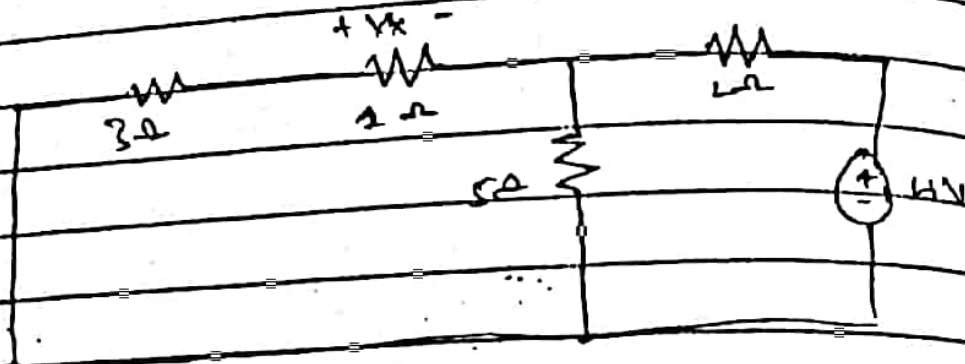
now let the left hand side voltage source as a short circuit of current source as an open circuit.



As  $5\Omega$  is in parallel with  $3\Omega$  &  $2\Omega$

$$R_{eq} = \frac{5 \times (3+1)}{5+3+1} = \frac{20}{9}$$

$$= 2.222 \Omega$$

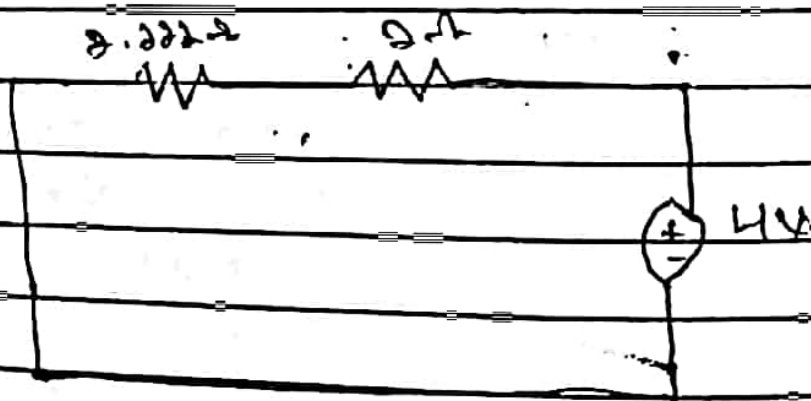


now by mesh analysis

$$i_2 = \frac{4}{4.222} = -0.947$$



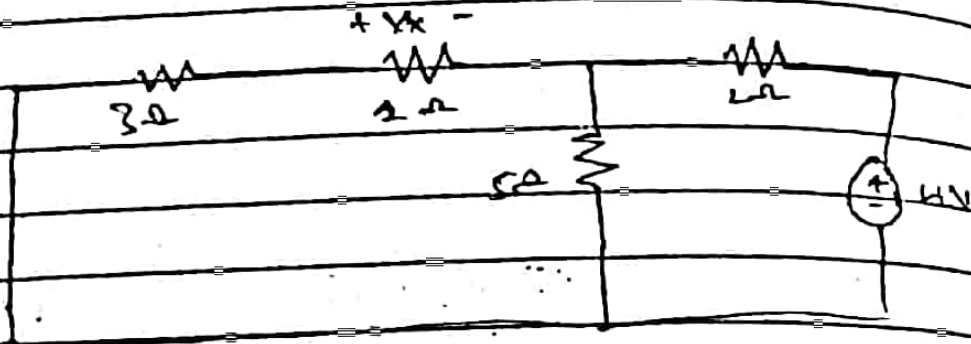
Now set the left hand side voltage source as a short circuit by current source as an open circuit.



As  $5\Omega$  is in parallel with a  $3\Omega$  &  $2\Omega$

$$R_{eq} = \frac{5 \times (3+2)}{5+3+2} = \frac{20}{9}$$

$$= 2.222 \Omega$$

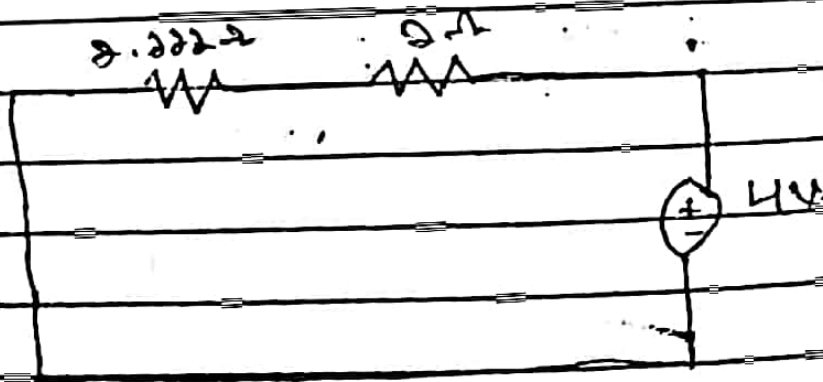

Now by mesh analysis

$$i_2 = \frac{4}{4.222} = -0.947$$

$$V_{2.222\Omega} = \frac{4 (2.222)}{2.222 + 2}$$


$$V_{2.222\Omega} = -2.10531$$

Now for  $2 \rightarrow$

$$V_{22} = \frac{-2.1053 (1)}{1 + 3}$$


$$V_{22} = -0.5623 \text{ V}$$

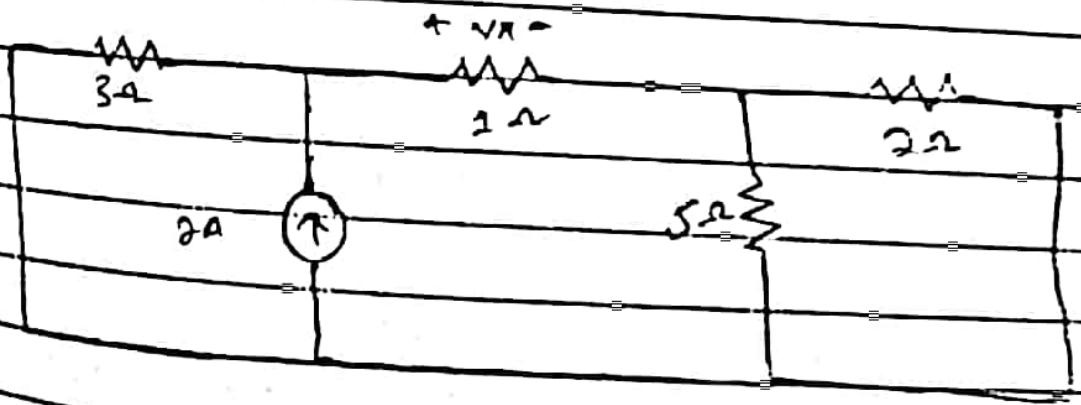Now putting the two voltages at a short circuit and re-drawing the circuit.



$$R_{eq} = 5 \parallel 2 = \frac{2 \times 5}{5 + 2} = \frac{10}{7} = 1.429\Omega$$

Redrawing the circuit.

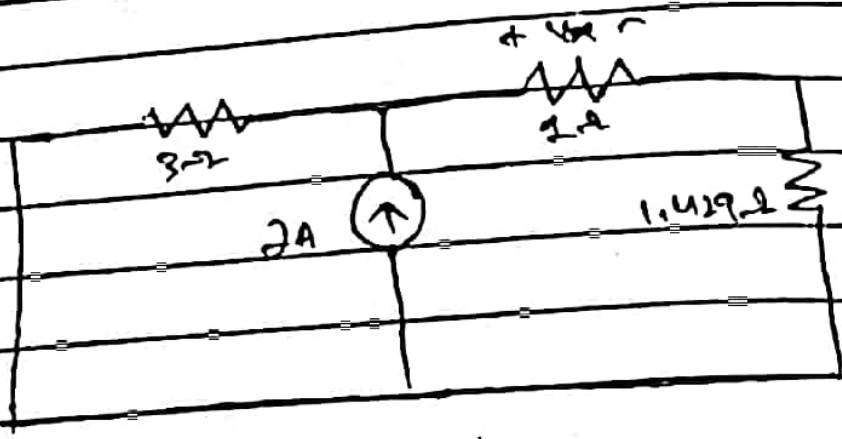

Applying Current dividing rule

$$I_{2\Omega} = \frac{2(3)}{3+1.429}$$

$$I_{2\Omega} = 1.105$$

Now

$$V_x = IR$$

$$V_x = (1.105)(2)$$

$$V_x = 1.105$$

Now

adding all the voltages

$$V_x = V_{x1} + V_{x2} + V_{x3}$$

$$= 0.73684 + (-0.52632) + 1.105$$


$$V_x = 1.3155 \text{ V}$$




Q1002

ANS is

Figure 3

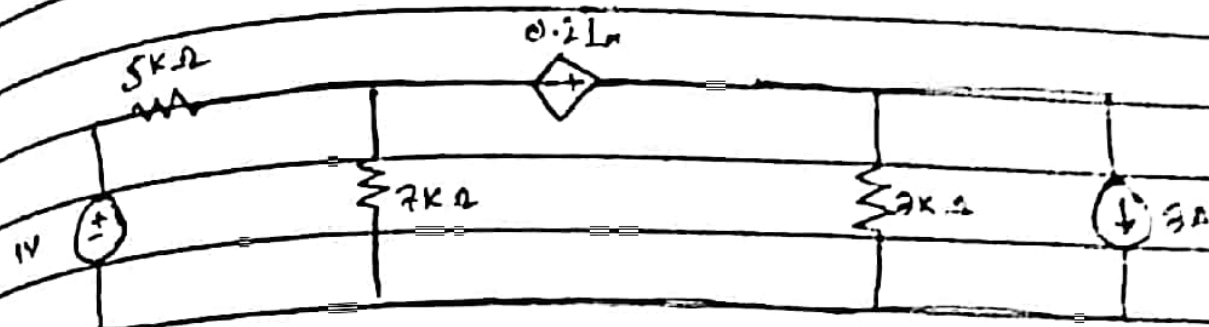

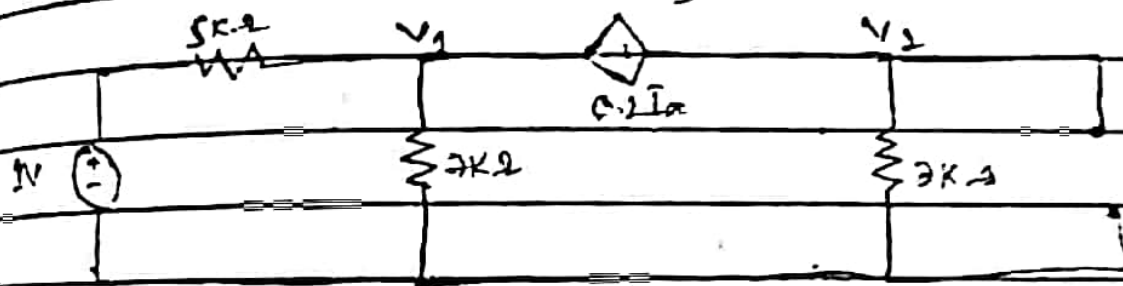Removing the current source so it will be as act on open circuit - Redrawing the circuit.



$V_2$  &  $V_2$  will be a super node applying KCL on a super node

$$\frac{V_2 - 1}{5000} + \frac{V_1}{7000} + \frac{V_2}{2000} = 0$$

Now  $V_1 - V_2 = 0.2 I_x$

$$V_2 = 0.2 I_x + V_2$$

$$\frac{V_2 - 1}{5000} + \frac{V_1}{7000} + \frac{0.2 I_x + V_2}{2000} = 0$$

But  $V_2 = 7000 I_{x2}$


$$\frac{7000 I_{x2} - 1}{5000} + \frac{7000 I_{x2}}{7000} + \frac{7000 I_{x2} + 0.2 I_{x2}}{2000}$$

$$1.4 I_{x2} - 0.2 + I_{x2} + 3.5 I_{x2} + 0.2 I_{x2} = 0$$

$$6 I_{x2} = 0.2$$

$$I_{x2} = 0.03333 \text{ A}$$

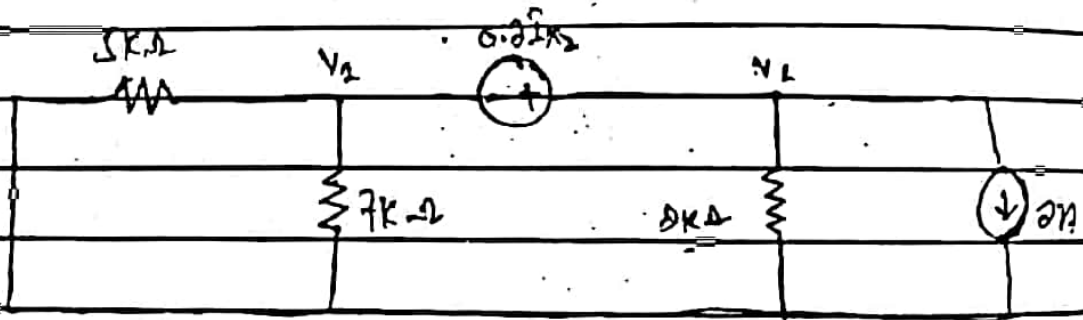Now the voltage source will be get short circuit



Applying KCL on supernode

$$\frac{V_2}{5000} + \frac{V_1}{7000} + \frac{V_2}{2000} = -2$$

$$\therefore V_2 = V_1 + 0.2 I_{x2}$$

$$\frac{V_1}{5000} + \frac{V_1}{7000} + \frac{V_1 + 0.2 I_{x2}}{2000} = -2$$

$$\therefore V_2 = 7000 I_{x2}$$

Date: / /

$$\frac{2000 I_{x1}}{5000} + \frac{2000 I_{x2}}{2000} + \frac{2000 I_{x2} + 0.2 I_{x2}}{2000} = -2$$

$$1.4 I_{x2} + I_{x2} + 3.1 I_{x2} + 0.2 I_{x2} = -2$$

$$6 I_{x2} = -2$$

$$I_{x2} = -2/6$$

$$I_{x2} = -0.3333 \text{ A}$$


$$I = I_{x1} + I_{x2}$$

$$I = 0.0333 - 0.3333$$

$$I = -0.3 \text{ A}$$

Q. NO 3

ANS (a) Figure

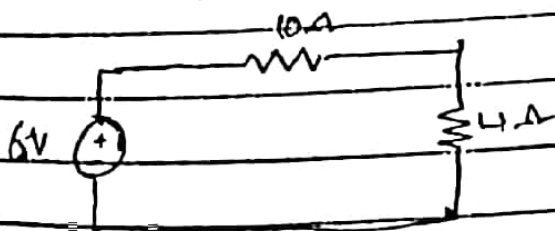

According to Ohm's Law

$$V = IR$$


$$I = \frac{V}{R} = \frac{6}{10}$$

$$I = 0.6 \text{ A}$$



Date: 1/1

# Re drawing Circuit

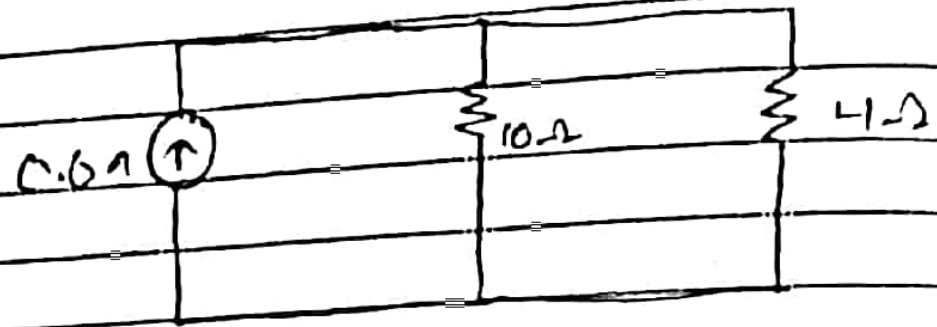

(ii) Figure (2) h



$$V = IR$$

$$V = (6)(10)$$

$$V = 60\text{V}$$


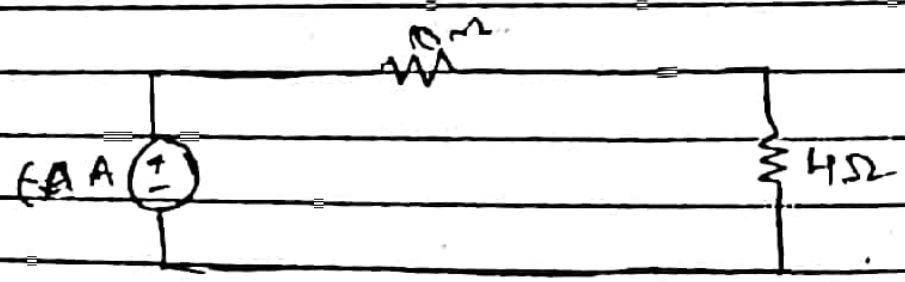


Figure (2) i

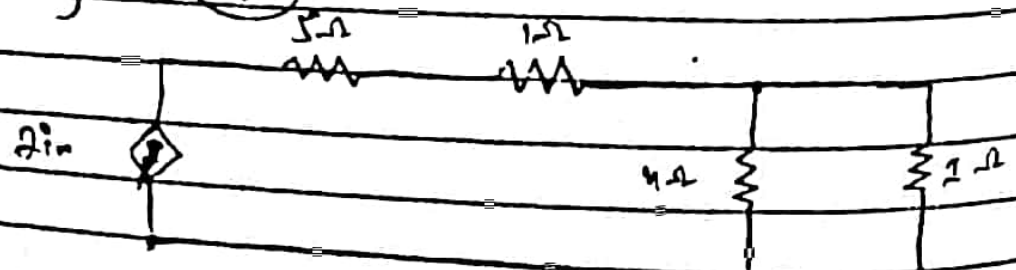


Date:   /  /  

$$V = IR$$

$$I = \frac{V}{R}$$


$$= \frac{2}{5}$$

$$I = 0.4 \text{ A}$$

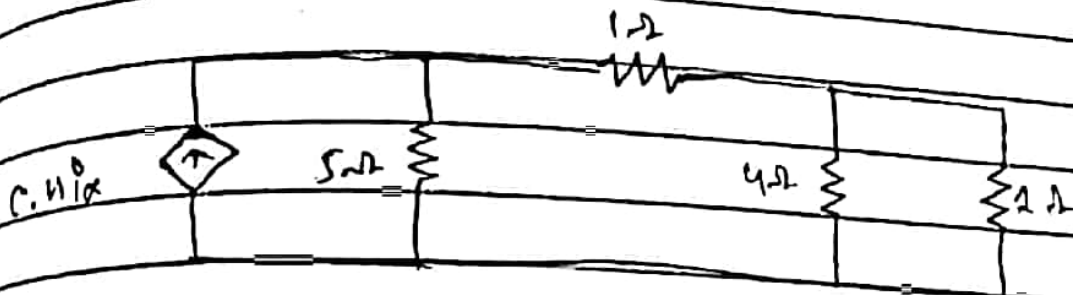

QNO 4

Ans :-

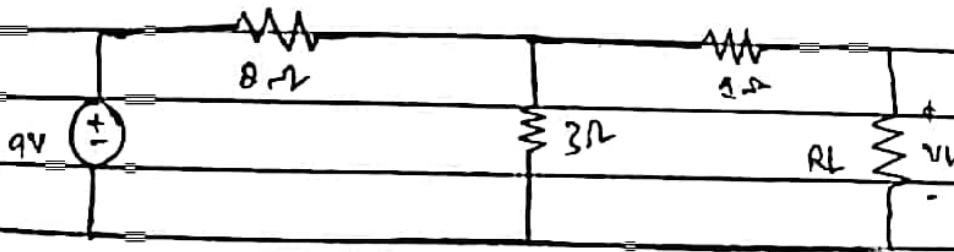

Soln

To get  $R_{th}$  we will add all the resistors except  $R_L$

$$R_{th} = 8 + 3 + 2$$

$$= \frac{6 + 1}{5}$$


$$R_{th} = 2.2 \Omega$$

Need Solving by source transformation



$$I = \frac{V}{R} = \frac{4}{2} = 2 \text{ A}$$


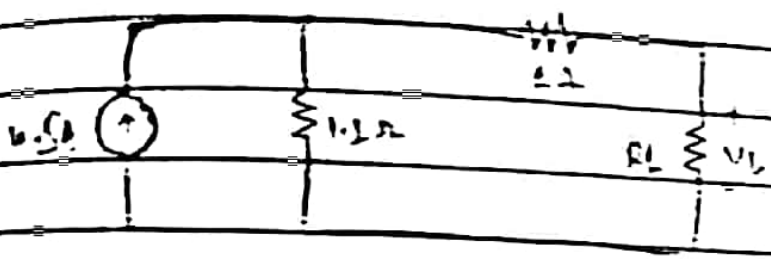
$$R_{eq} = \frac{2 \times 2}{2+2} = \frac{4}{4} = 1 \Omega$$



$$V = IR = (4.5)(1.5) = 5.4 \text{ V}$$

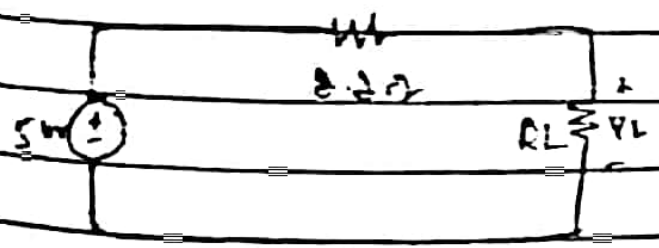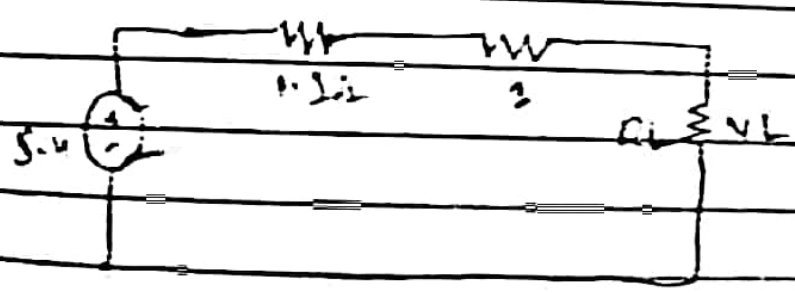

$$V_{Th} = 5.4 \text{ V}$$

$$R_{Th} = 2.5 \Omega$$



Now calculating each value of  $R_L$

$$(i) R_L = 1 \Omega = \frac{5.4 (1)}{1 + 2.2}$$

$$V_L = 1.688V$$

$$(ii) R_L = 3.5 \Omega$$

$$= \frac{(5.4)(3.5)}{3.5 + 2.2}$$

$$V_L = 3.316V$$

$$(iii) R_L = 6.257 \Omega$$

$$= \frac{(5.4)(6.257)}{(6.257)(2.2)}$$


$$V_L = 3.995V$$

$$(iv) R_L = 9.8 \Omega$$

$$= \frac{(5.4)(9.8)}{2.2 + 9.8}$$

$$V_L = 4.41V$$

Q.105  
 Find Power


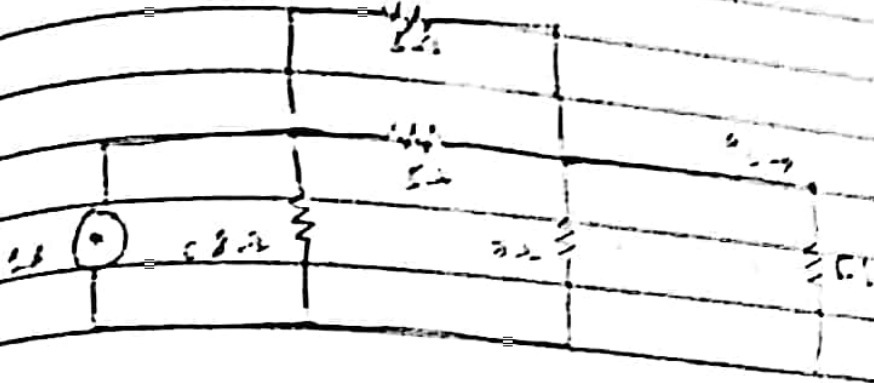


Gain


$$G_{AV} = \frac{3 \times 2}{3 + 2} \cdot \frac{2}{2 + 2} = 0.5$$

$$V = IR$$

$$= (1) (0.8) = 0.8$$

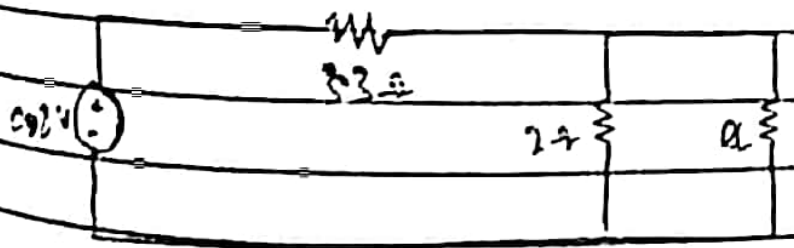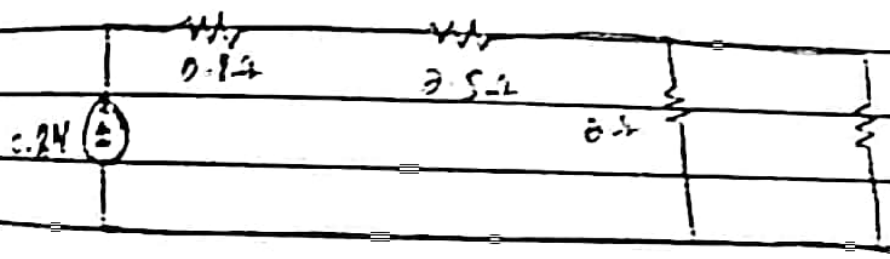


$$I = 0.8 / 3.3 = 0.24$$

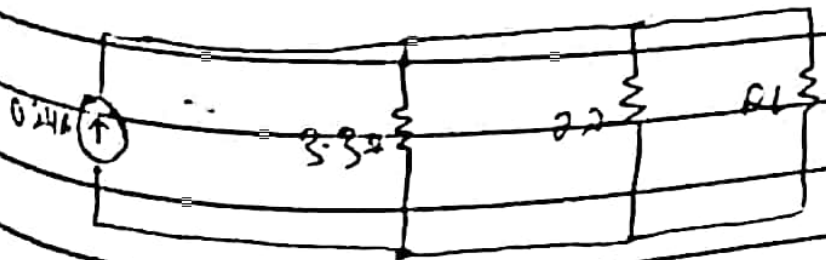

$$R_{eq} = \frac{3.3 \times 2}{2 + 3.3} = \frac{6.6}{5.3}$$

$$R_{eq} = 1.245 \Omega$$

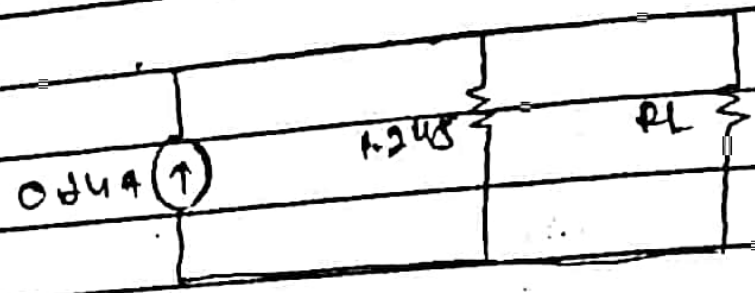

$$I_n = 0.24A$$

$$R_n = 1.245 \Omega$$

Now

$$V = IR$$

$$V_{th} = I_n \cdot R_n = (0.24)(1.245)$$

$$V_{th} = 0.302V$$

∴

$$R_n = R_{th}$$

$$R_{th} = 1.245 \Omega$$

Find each value for RL

$$(1) R_L = 0.2$$

$$= \frac{0.302}{1.245 + 0}$$

$$I_L = 0.243A$$



Date:   /  /  

$$\textcircled{2} \quad R_L = 1 \Omega$$

$$I = \frac{0.302}{1.245 + 1} = 0.135 \text{ A}$$

$$I_L = 0.135 \text{ A}$$

$$\textcircled{3} \quad R_L = 4.923 \Omega$$

$$I = \frac{0.302}{1.245 + 4.923}$$

$$I_L = 0.0499 \text{ A}$$

$$\textcircled{4} \quad R_L = 8.107 \Omega$$


$$I = \frac{0.302}{1.245 + 8.107}$$

$$I_L = 0.030 \text{ A}$$

# Q102 Part (11)


Ex: 5.3

Figure 8

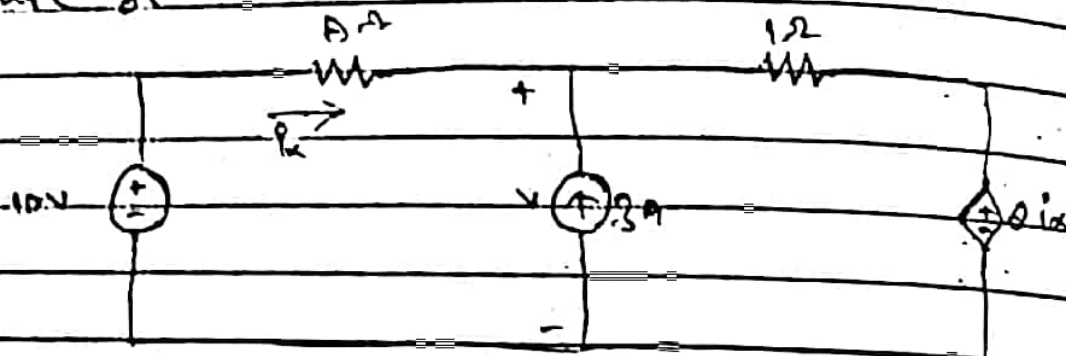

Solution

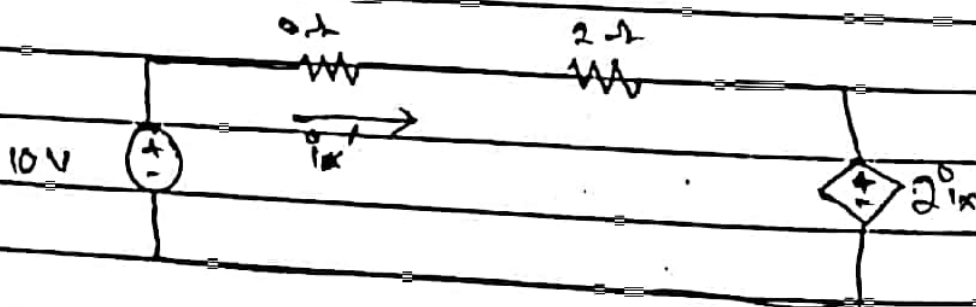First we will remove current source and will make it an open circuit. Redrawing the circuit.




Applying KVL on mesh.

$$2i_x + 2i_x + 2i_x = 10$$

$$6i_x = 10$$

$$i_x = 2A$$

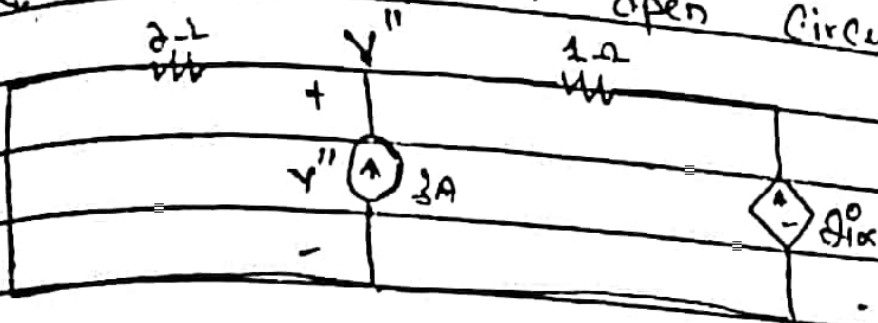Remove voltage source  
make it an open circuit.



Applying KCL on  $V''$

$$\frac{V''}{2} + \frac{V'' - 0.5i_x''}{1} = 3$$

$$V'' + 0.5V'' - 0.5i_x'' = 3$$

$$3V'' - 0.5i_x'' = 6$$

We know from the figure

$$V'' = -0.5i_x''$$

$$3(-0.5i_x'') - 0.5i_x'' = 6$$

$$-1.5i_x'' = 6$$

$$i_x'' = -0.6A$$

$$i_x = i_x' + i_x''$$


$$= 2 + (-0.6)$$

$$i_x = 1.4A$$



# Build Example 5.4

Figure 5.4

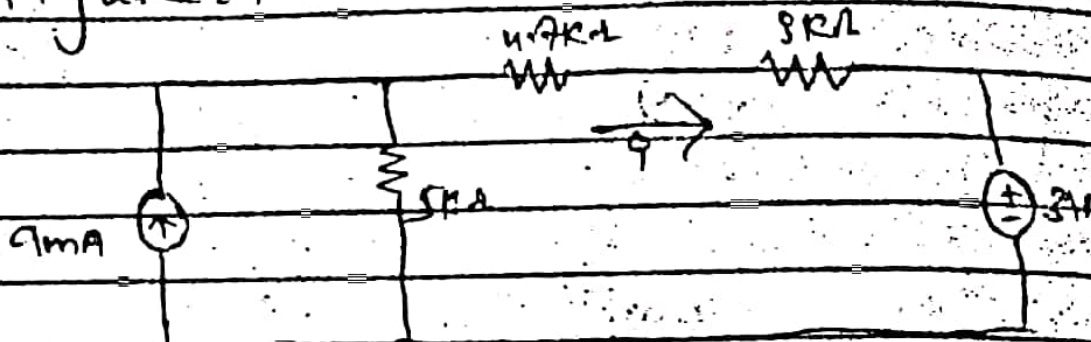

Soln

we know that


$$V = IR$$

$$V = (9 \times 10^{-3})(5000)$$

$$= (0.009)(5000)$$

$$V = 45$$

Re drawing the circuit

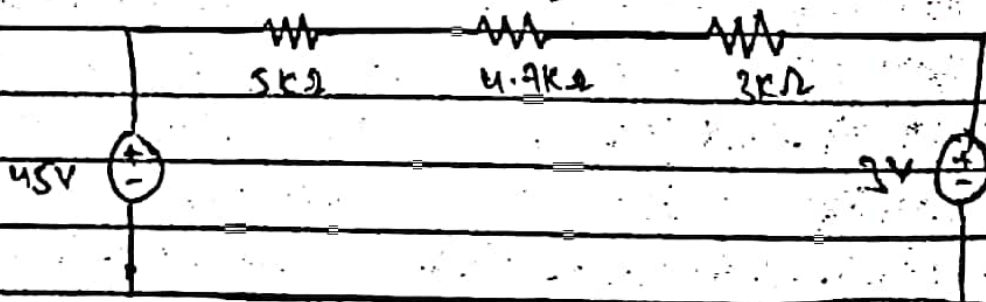

Applying KVL on mesh


$$5000i + 4700i + 3000i = 45 - 3$$

$$12700i = 42$$

$$i = 0.0033 \text{ A}$$

## Example 5.5

Figure 8

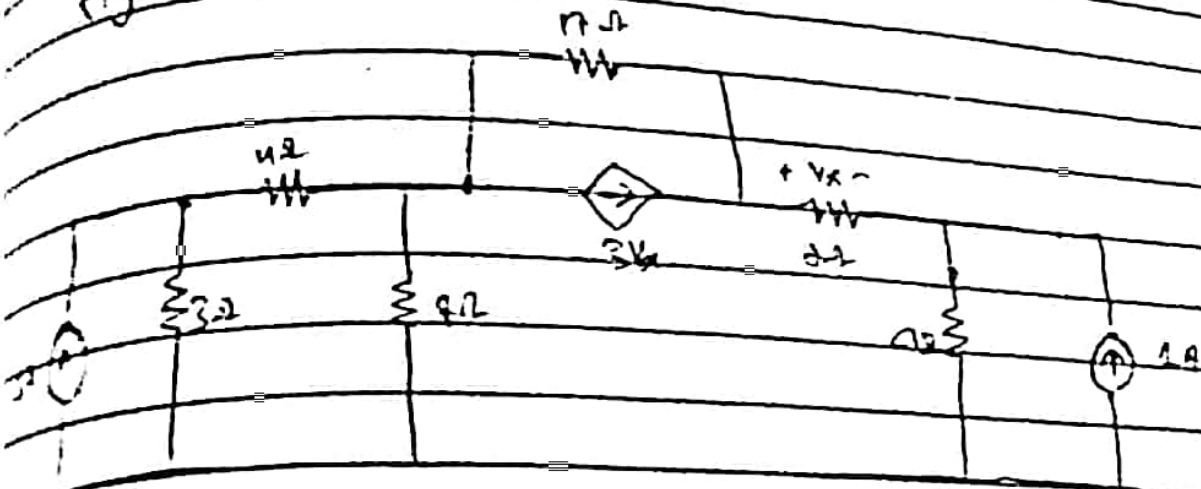


$$V = IR$$

$$V = 5(3) = 15V$$

$$V_x = 3(4.7)$$

$$V_x = 51$$

Re drawing a circuit

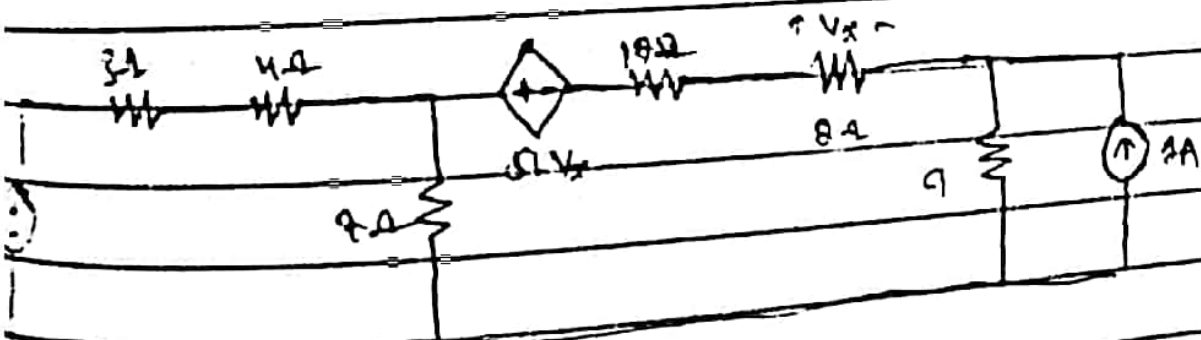


$$R = 3 + 4$$

$$= 7\Omega$$

$$I = \frac{V}{R} = \frac{15}{7} = 2.14$$

$$V_x = IR = 9(2.14)$$

# Redrawing a Circuit

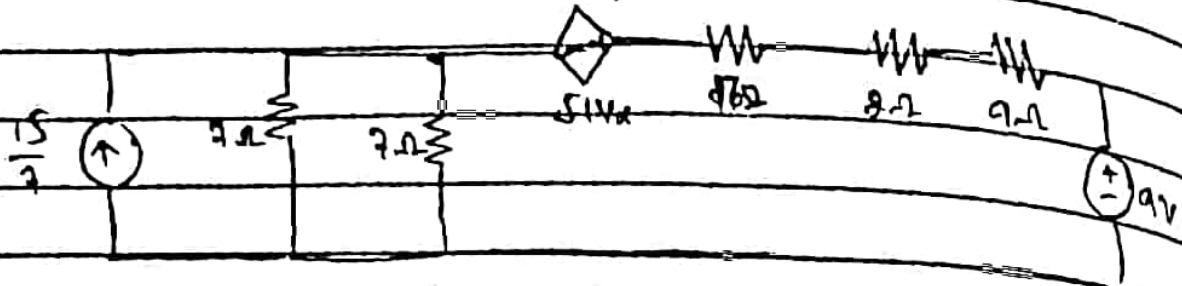


$$V = IR = \left(\frac{15}{7}\right)(7)$$

$$V = 7.5$$

$$R = 1\Omega + 9$$

$$R = 26\Omega$$

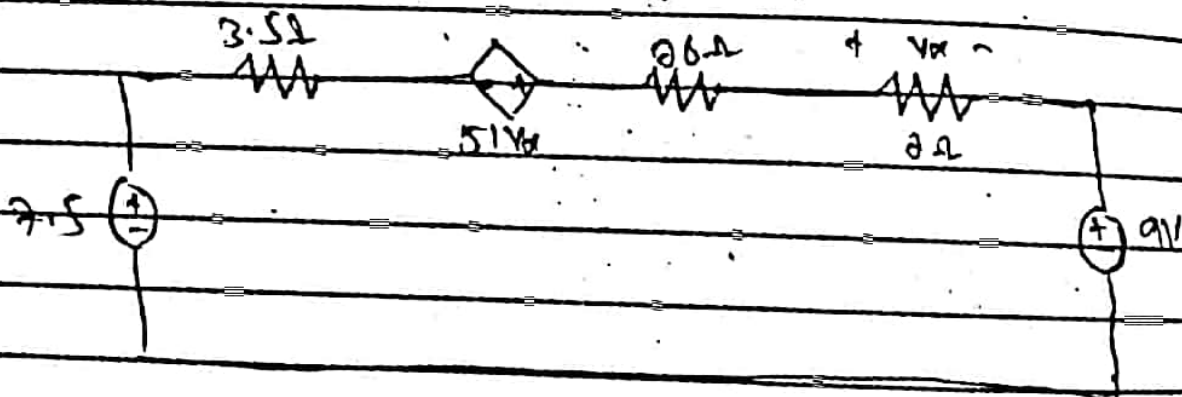

Applying KVL on mesh 1

$$3.5i - 5V_x + 2i = 7.5 - 9$$

$$V_x = 2i$$

$$3.5i - 5(2i) + 2i = -1.5$$


$$-1039.5i = -1.5$$

$$i = \frac{-1.5}{-1039.5}$$




### Example 5.6

Figure 5.6

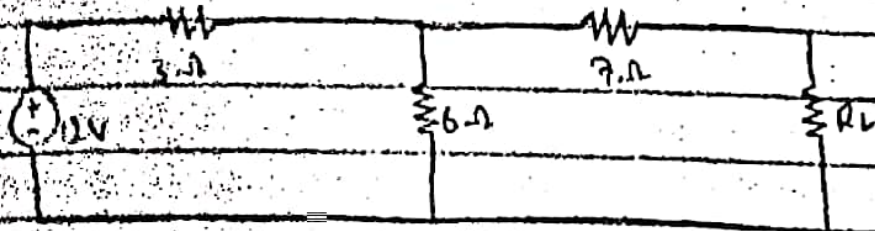


Solution

$$I = V/R = 12/3 = 4A$$

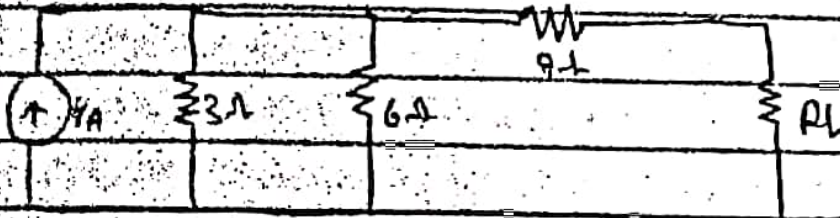

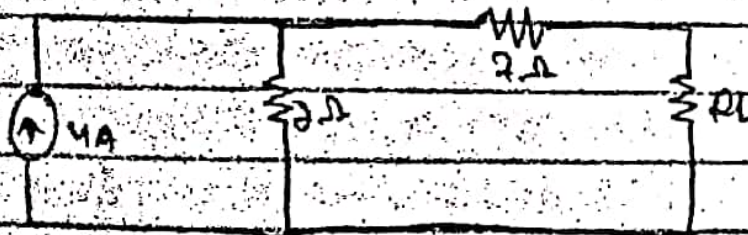
$$R_{eq} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$




$$V = IR = (4)(2)$$

$$V = 8V$$

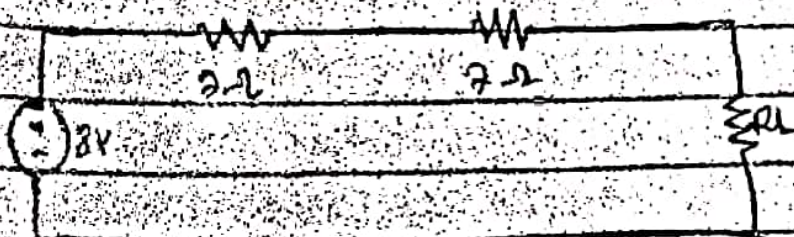

$$R = 2 + 7 = 9$$

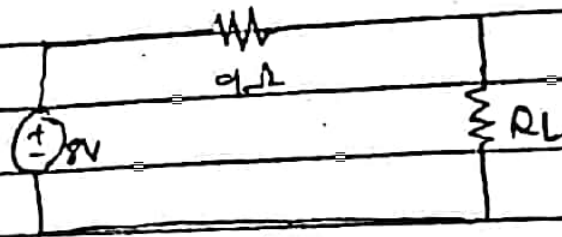

$$V_{th} = 8V$$


$$R_{th} = 9\Omega$$

$$P = \left( \frac{8}{9 + R_L} \right)^2 R_L$$

For any value of  $R_L$  will have different solutions.

Example 5.7


Figure 5

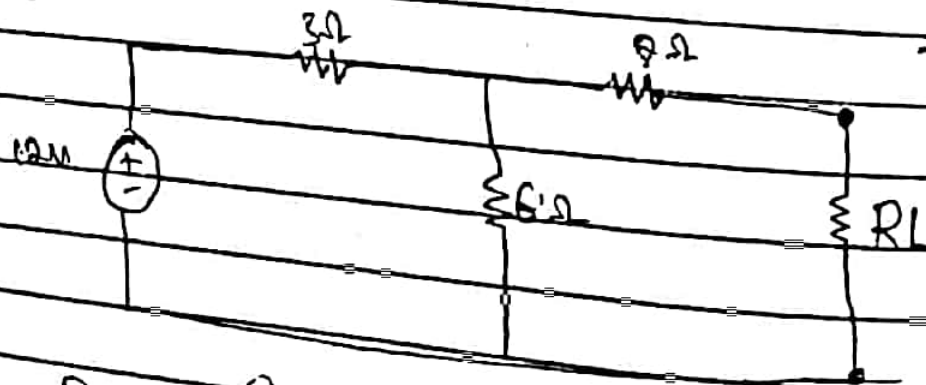

For finding  $R_{th}$  we will remove voltage source & make short circuit.

Bilal Register




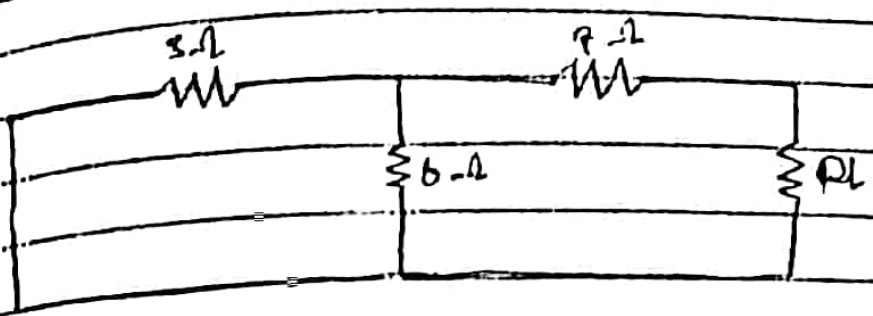

For  $R_{TH}$  we will add all the resistors except  $R_L$ .

$$\begin{aligned} R_{TH} &= 3 + 6 + 7 \\ &= \frac{18}{1} + 7 \\ R_{TH} &= 9 \end{aligned}$$

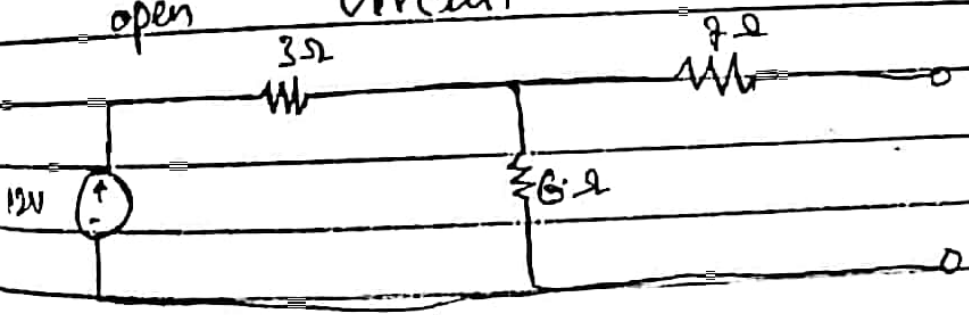For  $V_{OC}$  we will remove  $R_L$  and make it as an open circuit.




$$V_{OC} = 12 \left( \frac{6}{3+6} \right)$$

$$V_{OC} = 8V$$



Q No 3  
ANCh Figure 4

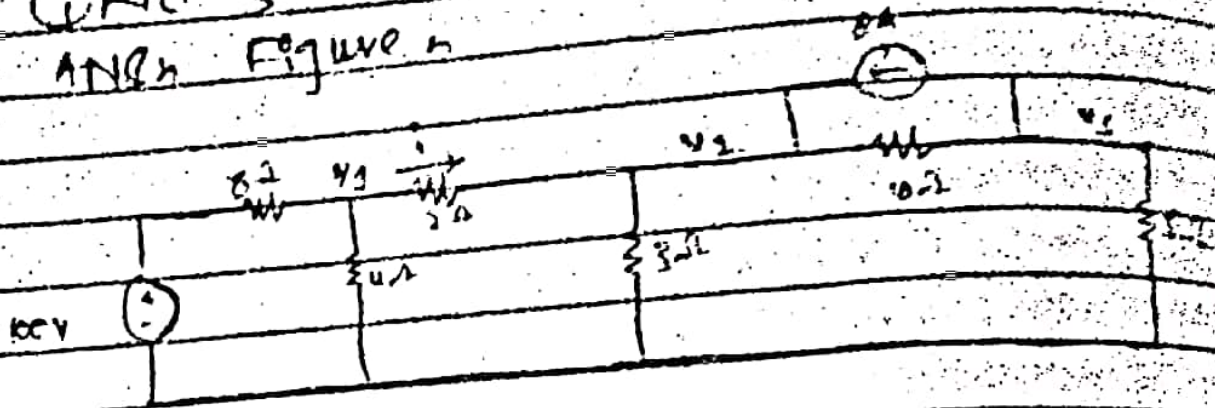

Applying KCL on node 1

$$\frac{v_1 - 100}{2} + \frac{v_1}{4} + \frac{v_1 - v_2}{3} = 0$$

$$\frac{v_1 - 100}{2} + \frac{v_1}{4} + \frac{v_1 - v_2}{3} = 0$$

$$3v_1 - 4v_2 = 100 \quad \text{--- (1)}$$

Applying KCL on node 2

$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{10} = 8$$

$$30v_2 - 20v_1 + 20v_2 + 3v_2 - 3v_3 = 240$$

$$-20v_1 + 53v_2 - 3v_3 = 240 \quad \text{--- (2)}$$

Applying KCL on Node 3

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = 8$$

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = 8$$

$$-v_2 + 3v_3 = 80 \quad \text{--- (3)}$$

Taking eq (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Taking eq (2)

$$-16 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting eq (a) & (b) in eq (2)

$$-30(0.571V_2 + 14.28) + 53V_3 - 3(0.331V_2 - 26.67) = 480$$

$$-17.1V_2 - 428.4 + 53V_3 - 0.99V_2 + 80.01 = 480$$

$$34.91V_3 = 828.39$$

$$V_3 = \frac{828.39}{34.91}$$

$$V_3 = 23.73$$

Putting in eq (a)


$$V_1 = \frac{4(23.73) + 100}{7} = 25.89$$

$$I_x = \frac{V_1 - V_3}{2} = \frac{25.89 - 23.73}{2}$$

$$I_x = 1.08 \text{ A}$$



④ Solving by mesh analysis.

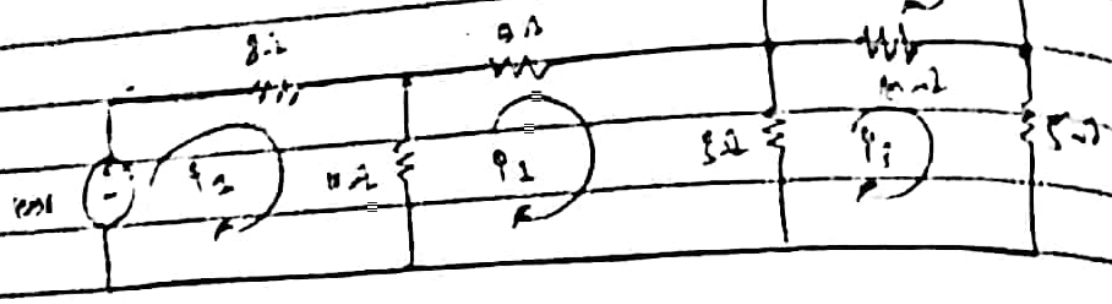

Applying KVL on loop 1

$$8i_1 + 4(i_1 - i_2) = 100$$

$$8i_1 + 4i_1 - 4i_2 = 100$$

$$12i_1 - 4i_2 = 100 \quad \text{--- (1)}$$

Applying KVL on loop 2.

$$5(5 + 4(i_2 - i_1)) + 3(i_3 - i_2) = 0$$

$$25i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_1 + 9i_2 + 3i_3 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

As  $i_4 = 8$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$



Taking eq (1)

$$I_1 = \frac{17I_2 - 100}{19} \quad (4)$$

Taking eq (3)

$$3I_2 + 18I_3 = -80$$

$$I_3 = \frac{-3I_2 - 80}{18}$$

$$I_2 = \frac{-3I_2 + 80}{18} \quad (5)$$

Putting eq (4) &amp; (5) in eq (2)

$$-4(0.33I_2 - 8.33) + 9I_2 - 3(0.16I_2 + 4.44) = 0$$

$$\Rightarrow -1.32I_2 + 33.32 + 9I_2 - 0.48I_2 - 13.32 = 0$$

$$7.2I_2 = -20 = 80/7.2$$

$$I_2 = 2.777$$

$$I_2 = I_A$$

$$I_A = 2.777$$

Applying KCL on node (1)

$$\frac{V_2 - V_1}{10} + \frac{V_3}{5} = 0$$

$$V_3 - V_2 + V_3 = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) & (3)

$$7V_2 - 4V_3 = +100$$

$$V_2 = \frac{4V_3 + 100}{7} \quad \text{--- (4)}$$

Now

$$-V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3}V_2 \quad \text{--- (5)}$$

Putting in eq (2)

$$-30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 428.4 - 4V_2 + 0.66V_2 = 0$$

$$20.44V_2 = 428.4$$

$$V_2 = -20.95$$

Putting in eq (4)

$$V_2 = 2.31$$

$$I_1 = \frac{2.31 + 20.95}{2} \Rightarrow I_1 = 11.63$$

Applying KCL on node (3).

$$\frac{V_2 - V_1}{10} + \frac{V_3}{5} = 0$$

$$V_3 - 2V_2 + V_3 = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) & (3).

$$7V_1 - 4V_2 = +100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (4)}$$

Now

$$-V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3}V_2 \quad \text{--- (5)}$$

Putting in eq (2)

$$-30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 428.4 - 4V_2 + 0.66V_2 = 0$$

$$-20.44V_2 = 428.4$$

$$V_2 = -20.95$$

Putting in eq (4)


$$V_1 = 2.31$$

$$I_1 = \frac{2.31 + 20.95}{2} \Rightarrow I_1 = 11.63$$



Date: 1/1

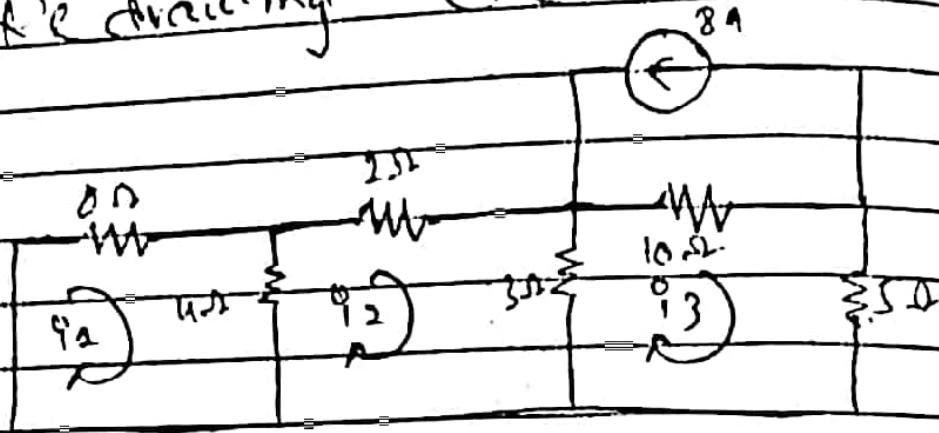Now Remaining voltage  
 source and making it short circuit.  
 Drawing circuit.



$$I_1 = 8A$$

Applying KVL on loop 2

$$8i_1 + 4i_1(i_2 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \quad \text{--- (1)}$$

Applying KVL on loop 1

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$4i_2 + 2i_2 - 3i_3 - 4i_1 = 0 \quad \text{--- (2)}$$

Applying KVL on loop 3

$$10i_3 + 5i_3 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80$$

taking eq (1)  
 $3i_1 - i_2 = 0$

$i_1 = 0.33 i_2$  — (5)

taking eq (2)

$-3i_2 + 18i_3 = -80$

$i_3 = \frac{3i_2 - 80}{18}$  (6)

$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$

$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$

$i_2 = 1.254$

Now  $i = i_1 + i_2$

$i = 1.44 + 1.35$

$i = 2.79 A$

Result:-

$i = 2.79 A$

Date: 1/1

Q No 1: Evaluate determinant:  
Answer (1) Given

$$\begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}$$

Solution

$$\begin{aligned} & \begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix} \\ &= 6 - (-4) \\ &= 6 + 4 \\ &= 10 \end{aligned}$$

Q No 11 Given:

$$\begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

Solution


$$\begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

$$\begin{aligned} &= 0 - 2(30 - 3) + 11(-6 - 12) \\ &= -2(27) + 11(-18) \\ &= -54 - 198 \\ &= -252 \end{aligned}$$



QNO 2  
ANLS 2

Figure 2

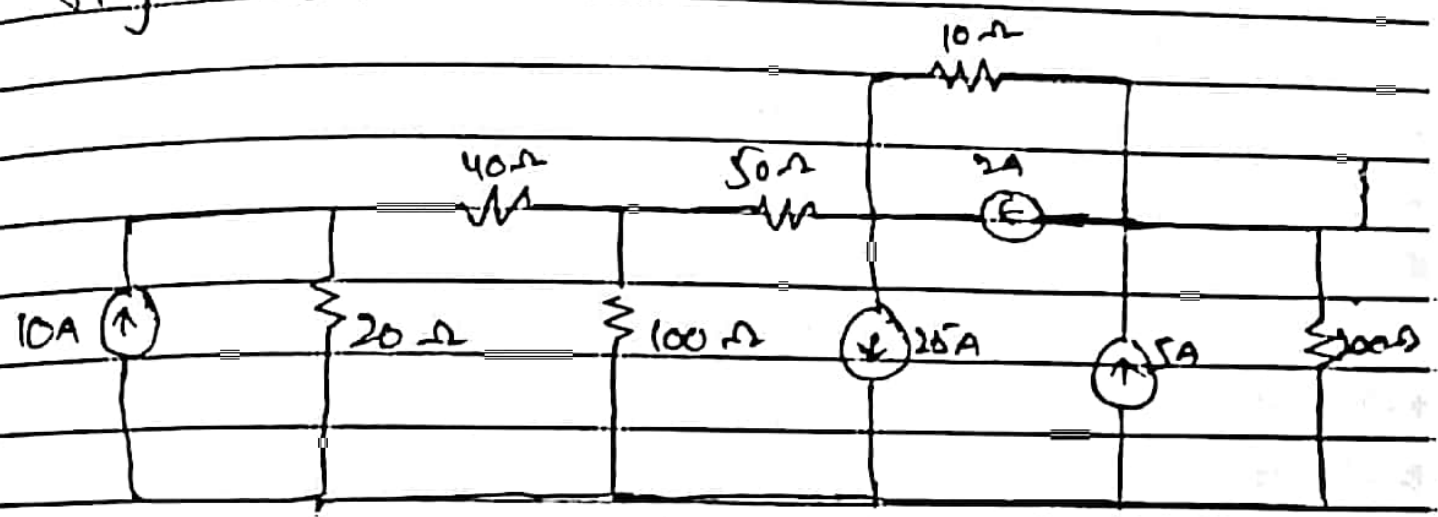

Solution 2

All nodes in the above circuit is verified now applying or solving through node analysis.

① Applying KCL on node 2 is

$$\frac{V_1}{20} + \frac{V_1 - V_2}{40} = 10$$

$$\frac{2V_1 + V_1 - V_2}{40} = 10$$

$$3V_1 - V_2 = 400 \quad \text{--- (1)}$$