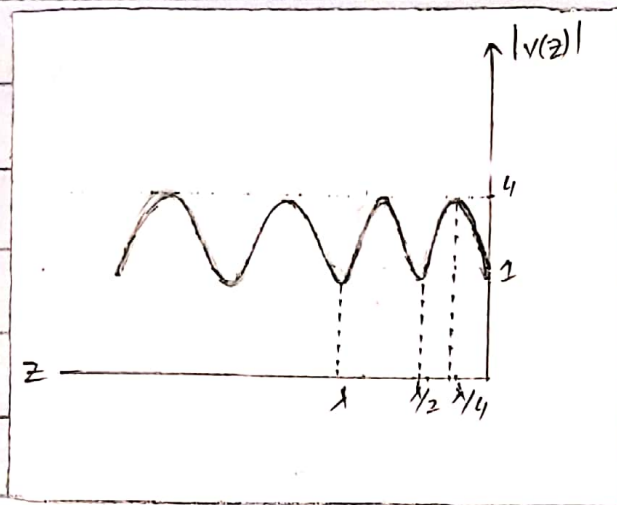






Question No 2:- Voltage Standing Wave pattern in a lossless transmission line with characteristics impedance  $50\Omega$  and resistive load as show in figure.



Solution:-

Given Data

$$Z_0 = 50\Omega$$

$$V_{\max} = 4$$

$$V_{\min} = 1$$

Required data

$$Z_i = ?$$

$$S. \text{ Wave ratio} = ?$$

As we know that

S. Wave ratio =  $V_{max} / V_{min}$ .

Putting values.

S. Wave ratio =  $4/1$

S. Wave ratio = 4.

Now find  $Z_L$

S. Wave ratio =  $Z_0 / Z_L$


$Z_L = Z_0 / \text{S. Wave ratio}$

Putting value

$Z_L = 50/4.$

$Z_L = 12.5 \Omega$

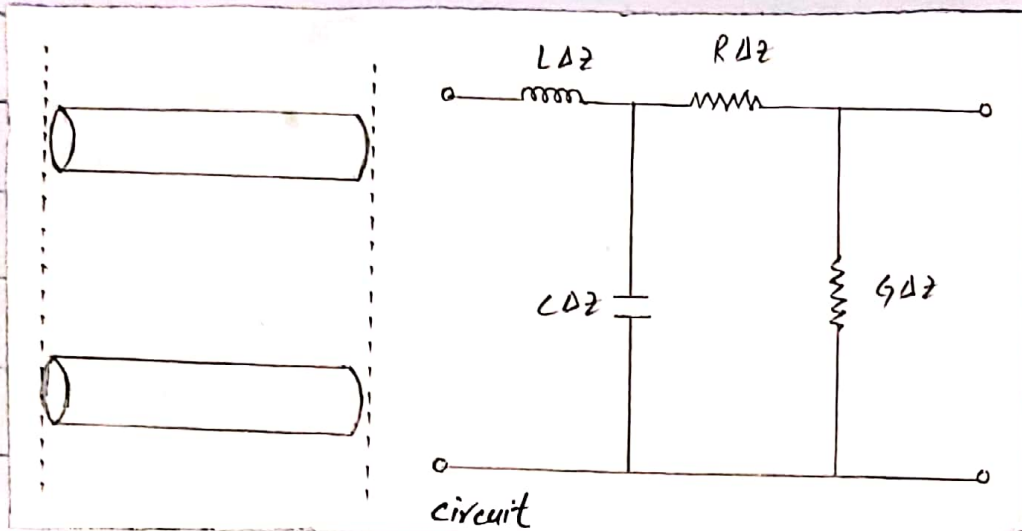Question No 1 (b) :- Draw and explain Equivalent circuit model of transmission line.




We know that a constant parameter of the transmission line is our RLGC the only variable parameter changing are voltage and current that varies on the position ( $z$ -axis) with respect to time " $t$ ". We have designed the characteris "distributed" circuit Model.

Suppose an infinite line of length  $\Delta z$  by ampere's law whenever in a closed conductor current changing it produces an effect of that causing magnetic flux

Now when current are changing with respect to time "t" it directly effect on magnetic flux and voltage variation in the conductor along with electromotive force induced and attempts to drive the current oppositely (lenz law) ( $v = L di/dt$ ) at the same time the two adjacent oppositely infinitesimal line conductor (upper and lower line) adoped the behaviour infinitesimal line conductor and capacitor which is model as a shunt capacitor as show in figure.

In the present of imperfect conductor and faulty insulating materials voltage drop and current leakage occurs in the line. The model daigram clearly designed by series resistor and ~~shu~~ shunt capacitor.

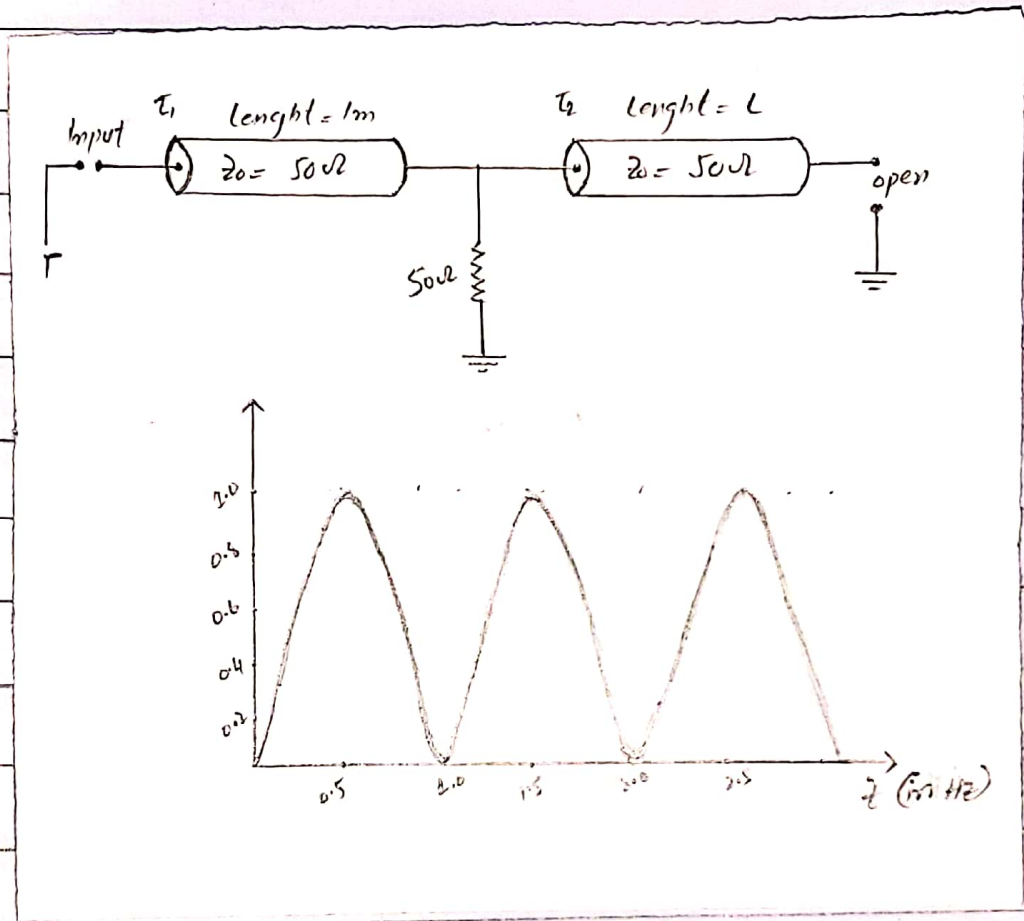Question No 28-(a): A microwave circuit analysis consisting of lossless transmission line  $T_1$  and  $T_2$  is shown in figure



Solution:-

As we know that

$$T = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

We know the frequency is 1 GHz.

$$Z_1 = 50 \Omega, Z_0 =$$

$$z_b = jz_0 \cot \beta L$$

$$z_{eq} = z_a \parallel z_b = 50 \Omega$$

$$z_b = \alpha$$

So

$$z_b = -jz_0 \cot \frac{2\pi}{\lambda} \cdot L$$

putting value of  $z_0$

$$z_b = -j50 \cot \frac{2\pi}{\lambda} \cdot L$$

$$\cot \frac{2\pi}{\lambda} \cdot L = \alpha$$

$$L = \lambda/2$$

$$\text{So } \cot \frac{2\pi}{\lambda} \cdot \lambda/2 = \alpha$$

Now

$$L = \lambda/2$$

$$v_p = 2 \times 10^8$$

$$v_p = \omega/\beta$$

$$\omega/\beta = 2 \times 10^8$$

At  $f = 1 \text{ GHz}$ .

$$\lambda = 2 \times 10^8 / 1 \times 10^9$$

$$\lambda = 0.2 \text{ m.}$$



Now

$$L = 1/2$$

$$= 0.2/2$$

$$L = 0.1 \text{ m Ans}$$

Question No 2 (b) :-


Derive transmission line equation and describe what it says?

Transmission line equation :-

The design of transmission line is depending on many factors. The most distinctive quality of Electrical Engineering problem involve the transmission of electrical power from the generation station to the consumer end.

The most common way of transmitting Electrical power are parallel wire and coaxial cable.

### Generator

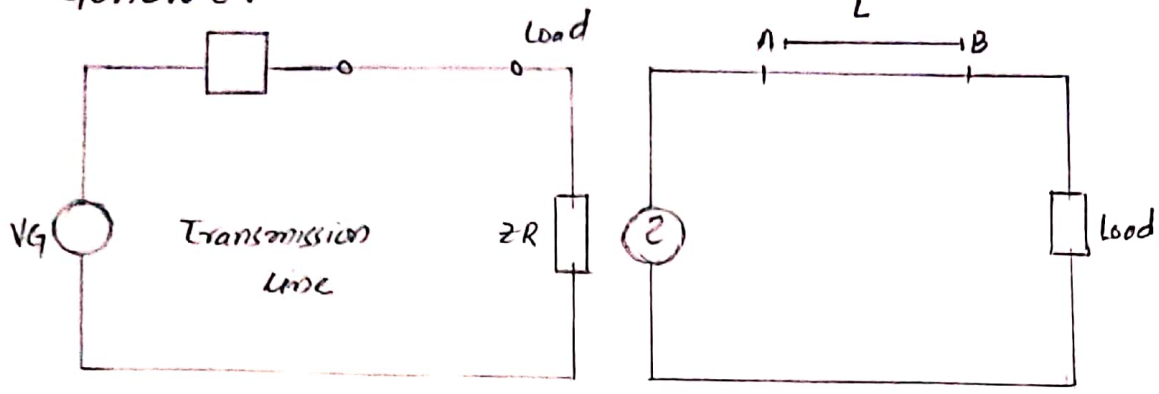

Transit time effect :-


$$\tau \gg \tau_r$$

$$\tau \gg \frac{l}{v}$$


$$\frac{1}{\tau} \gg R/v$$

$$v/\tau \gg R$$


$$\lambda \gg l$$

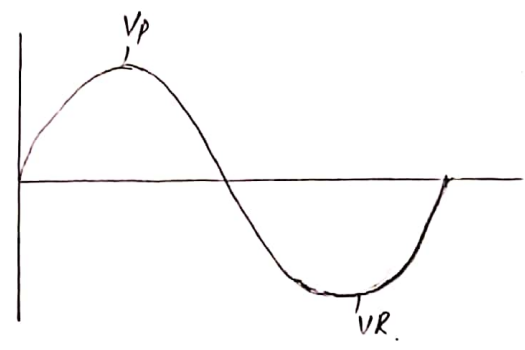

Primary constant of transmission line :-

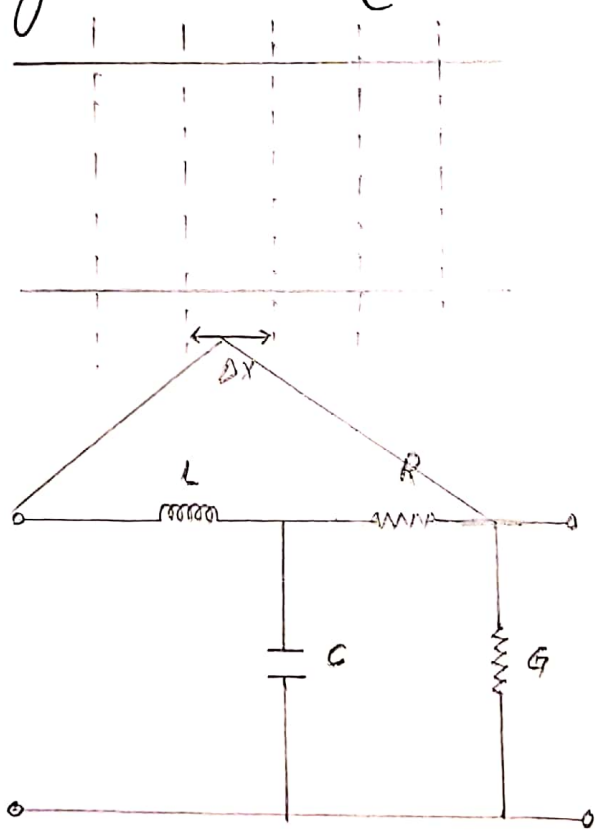

Transmission line equation :-

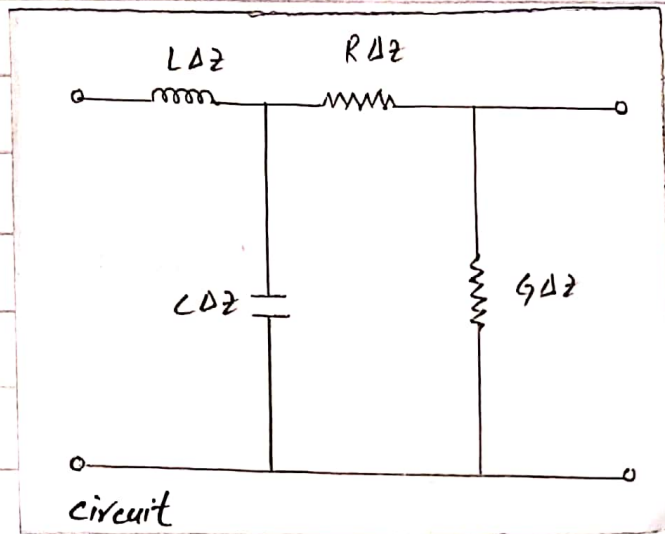

Solution :-

$$\Delta I = -(G\Delta x + j\omega C\Delta x) V$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C) V$$

$$\frac{dI}{dx} = -(G + j\omega C) V \quad \text{--- (i)}$$

$$\Delta V = -(R\Delta x + j\omega L\Delta x) I$$

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = -(R + j\omega L) I$$

$$\frac{dV}{dx} = -(R + j\omega L) I \quad \text{--- (ii)}$$

Take derivative

$$\frac{d^2V}{dx^2} = -(R + j\omega L) \frac{dI}{dx}$$

$$\frac{d^2V}{dx^2} = (R + j\omega L) (G + j\omega C) V$$

We know that

$$(R + j\omega L)(G + j\omega C) = \gamma^2$$

$$d^2V/dx^2 = \gamma^2 V$$

$$V(x,t) = (V^+ e^{-\gamma x} + V^- e^{+\gamma x}) e^{j\omega t}$$

$$= V^+ e^{-j\beta x} e^{j\omega t} + V^- e^{j\beta x} e^{j\omega t}$$

$$= V^+ e^{+j(\omega t - \beta x)} + V^- e^{j(\omega t + \beta x)}$$

We know that

$$\vec{E} = E_0 e^{-\alpha z} \cos(\omega t - \beta z) \hat{x}$$


$$\vec{E} = E_0 \cos(\omega t - \beta z) \hat{x}$$

$$V(x,t) = V^+ \cos(\omega t - \beta x) + V^- \cos(\omega t + \beta x)$$

Travelling +x  
direction

Travelling -x  
direction

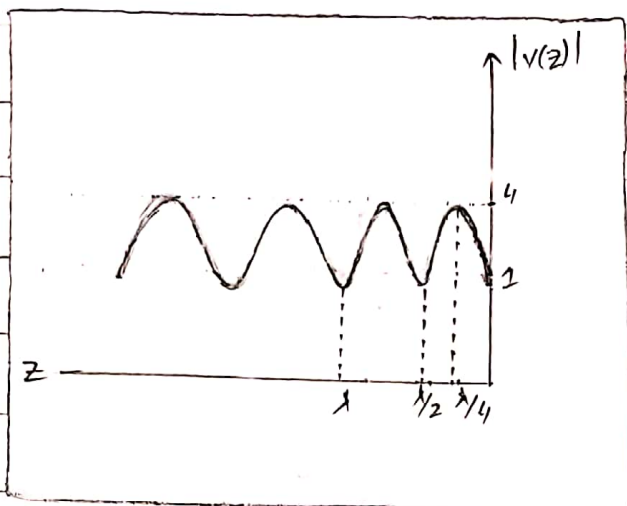Question No 3 (a) :- Voltage standing wave pattern is a lossless transmission line with characteristics impedance  $50 \Omega$  and resistive load is shown in figure.



Solution :-

Data

$$Z_0 = 50 \Omega$$

$$Z_L = 12.5 \Omega$$

Required

Reflective coefficient = ?

So

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{--- (i)}$$

$$\Gamma = \frac{12.5 - 50}{12.5 + 50}$$

$$\Gamma = \frac{-37.5}{62.5} \Rightarrow \underline{\underline{-0.6 \text{ Ans}}}$$

Question No 3 (b) :- Explain two impedance matching techniques in detail?

Impedance matching technique :-

Transmission Line

section can be used for the purpose of impedance matching. Impedance matching is the one of the important aspects of high frequency circuit analysis. To avoid reflections and for maximum power transfer the circuits have to be impedance matched.

There are various impedance matching techniques which are discussed in the following.

(A) Single-Stub Matching :-

A stub is a short circuited section of a transmission line connected in parallel to the main transmission line. A stub of appropriate length is placed at some distance from the load such that the the impedance seen beyond the stub is equal to the characteristic impedance. Conceptually this can.

be achieved by adding a stub to the main line such that the reflected wave from the short circuit end of the stub and the reflected wave from the load on the main line completely cancel each other at point "B" to give no net reflected wave beyond point "B" toward the generator.

Advantage :-

The single stub matching technique is superior to the quarter wavelength transformer as it make use of only one type of transmission line for the main line as well as the stub. This technique also in principle is capable of matching any complex load to the characteristic impedance/admittance the single stub matching fixed impedance at microwave frequencies.

(B) Quarter Wavelength Transformers.

This technique is generally used for matching a resistive load to a transmission line.

(i) Single section for matching two resistive load

(ii) Multiple section for matching two transmission lines with unequal characteristic impedances

(iii) Binomial design for all cases are identical in principle as all require matching b/w two purely resistive impedances.

Two resistive impedance can be matched by a section of a transmission line which is quarter-wavelength long and has characteristic impedance equal to the geometric mean of the two resistances.

The quarter wavelength transformer is commonly used at the junction of two transmission lines of unequal characteristic impedance

