

Department of Electrical Engineering

Assignment

Date: 20/04/2020

Course Details

Course Title: Power Electronics
Instructor: ENGR. AMIR AMAAN

Module: 4th
Total Marks: 30

Student Details

Name: SALMAN FAROOQ

Student ID: 15276




Q1. (a) In some applications, power semiconductor diodes are required to conduct several kilo amperes of current in the forward direction with very little power loss while blocking several kilo volts in the reverse direction. Explain the main differences of constructional features of a power diode and a signal diode. Illustrate your answer with the help of sketches to make a clear difference between the two.

Marks 10
CLO 1

Q2. (a) Explain operational features of the power MOSFET. Support your explanation using MOSFET operation as a switch. Also, illustrate the conditions to derive power MOSFET in the different regions of operation.

Marks 10
CLO 1

Q3. (a)

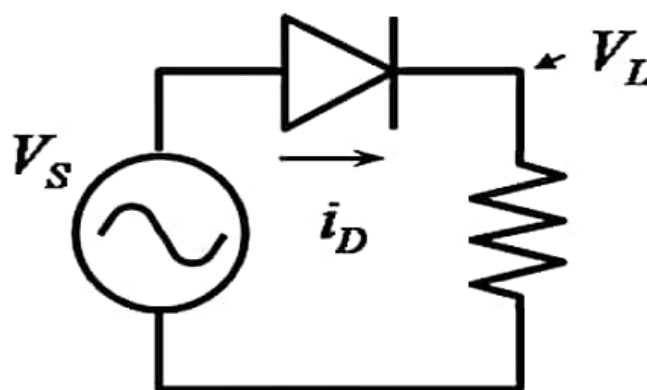

Marks 10
CLO 2

Consider $V_s = 220\sin 2\omega t$, $R = 1000\text{k}\Omega$ and 1N4004 uncontrolled rectifier diode for the circuit shown above. Find

- i) V_{avg}
- ii) I_{oavg}
- iii) V_{rms}
- iv) I_{orms}
- v) Output Power
- vi) Input Power Factor

	<ul style="list-style-type: none">vii) Conduction angle of a diodeviii) Extension angle of diodeix) Comparison of both conduction angle and extension angle of diodex) Peak Inverse Voltagexi) Circuit turnoff time, t_cxii) By putting inductor of your own choice repeat all the findings and compare both circuits result and comment.	
--	---	--

☺GOOD LUCK☺



Name: Salman Farooq

ID: 15276

Page # 1

Answer No 1 :-

SIGNAL DIODE

Diodes are often used as straightforward rectifiers as mixers in computing the signal and as switches to open or close a circuit. Diodes in the mixers are utilized for detecting the signal and these diodes are typically referred as signal diodes. The simple and conventional application of signal diodes is that it acts as a basic diode switch. Signal diode enable the current capability up to 100 milliamperes and they are known for processing the information found in electrical signal sent from electrical transmitter. Germanium diodes have a forward voltage drop about 0.3 volts are used as detecting circuits in radios. The PN junction signal diode is usually fabricated in glass case or plastic case and generally has a black or a red band at the cathode end of the terminal.

POWER DIODE :-

Definition :- A diode that has two terminals

Name :- Salman Farooq

ID : 15976

Page No # 2

like cathode and two layers like p & n used in the power electronics circuits is as power diode. This diode is more complex in construction as well as in operation because low power device has to change to make them appropriate in high power.

Application: The junction of normal diodes can be formed through semiconductor like p-type and n-type the terminal at the p-type is known as anode whereas the terminal at the n-type is known as the cathode. In power electronic circuits this diode plays an essential role it can be used as the rectifier in converter circuits voltage regulation circuits.

Answer No # 2 :-

Switching characteristic of MOSFET :-

In power conversion, a MOSFET is essentially used as a switch. As MOSFET switching characteristics the turn-on delay time $T_d(\text{on})$, rise time t_r , turn off delay time $T_d(\text{off})$, and fall time t_f are generally indicated. For example, the turn-on delay time may be called the on/off delay falling time and the rise/fall time may be the rising/falling time and so on,

Name:- Salman Farooq

ID :- 15276

page No # 3

turn-on delay time: Time from 10% of the rise of VGS.

> Rise time: Time from 10% to 90% of the rise of VDS.

> turn-off delay time: Time from 90% of the fall of VGS until 90% of the fall of VDS.

> fall time: Time from 90% to 10% of the fall of VDS.

the three operating regions of MOSFET is

1). ohmic region at low voltage VDS here the current is proportional to VDS for given VGS.

2). The knee region at slightly higher value VDS here the current is not on VDS value at all [practically very less in micro ampere level]

3). Breakdown region at very high value of VDS. The device breaks down.

Answer 3:-

$$V_S(t) = \frac{V_{pmk}}{2} \text{ or } V_m$$

for half wave Rectifier S.n (got
Input voltage. and sinusoidal

Name:- Salman Farooq

ID :- 15976

Page No 4

$$V_{avg} = \frac{V_{peak}}{\pi} \quad \therefore V_{peak} = V_m = V_i$$

$$V_{RMS} = \frac{V_{peak}}{2}$$

$$1) V_{avg} = \frac{V_{peak}}{\pi} = \frac{220}{\pi} = 70.02V$$

$$2) I_{avg} = \frac{V_{avg}}{R} = \frac{70.02}{1000} = 70 \mu A$$

$$3) V_{RMS} = \frac{V_{peak}}{2} = \frac{220}{2} = 110V$$

$$4) I_{RMS} = \frac{V_{RMS}}{R} = \frac{110}{1000} = 110 \mu A$$

$$5) \text{Input power factor } \cos \phi = \frac{V_{RMS}}{V_{peak}}$$
$$\cos \phi = \frac{110}{220} = \frac{1}{2} = 0.5$$

6) Diode is conducting only for 1st half
therefore conduction angle $\alpha = \pi$

(7) out put power.

$$P_o = I_{RMS}^2 R$$

$$= (110 \mu A)^2 \times 100 \text{ k}\Omega$$

$$P_o = 0.0121 \text{ W}$$

8) Extension angle of diodes-

Diode is conduction up to π

Name: Salman Farooq

ID: 15976

Page No # 5

(first cycle)

So, $B = \pi$

9) In all diode rectifier circuits:

conduction Extension

Angle . Angle

(α)

(β)

10) Peak Inverse Value (PIV)

During negative half cycle diode acts as open circuit and therefore all voltage appears across diode. Thus.

11) circuit turn-off time t_c
 $\omega t_c = \pi$

$t_c = \pi / \omega$; assuming $f = 50 \text{ Hz}$

$t_c = \frac{\pi}{2\pi f} = 0.01 \text{ sec}$