

Digital Logic Design

Assignment 5

Sir. Muhammad Amin

Muhammad Yasir

15459

Csc-201

Q1

$$A=1, B=0, C_{in}=1 \quad \left| \quad C_{out} = AB + (A \oplus B) C$$

Sol:

$$\Sigma = (A \oplus B) \oplus C$$

$$\Sigma = (1 \oplus 0) \oplus 1$$

$$\Sigma = (1) \oplus 1$$

$$C_{out} = (1)(0) + (1 \oplus 0)1$$

$$C_{out} = 0 + (1)(1)$$

$$\boxed{C_{out} = 1}$$

$$\boxed{\Sigma = 0}$$

Ans.

Q2:

$$\Sigma = 0, C_{out} = 0$$

$$A=? , B=?$$

for Σ and C_{out} both to be zero. the A and B must be zero

$$\boxed{\begin{matrix} A=0 \\ B=0 \end{matrix}}$$

$$\Sigma = A \oplus B$$

$$C_{out} = AB$$

Ans.

$$0 = 0 \oplus 0$$

$$C_{out} = 0 \cdot 0$$

Q3)

$$A=1, B=1, C_{in}=1$$

$$\Sigma = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B) C_{in}$$

$$\Sigma = (1 \oplus 1) \oplus 1$$

$$\text{Cout} = 1 \cdot 1 + (1 \oplus 1) \cdot 1$$

$$\Sigma_1 = (0) \oplus 1$$


$$\text{Cout} = 1 + (0) \cdot 1$$

$$\Sigma_1 = 1$$

$$\text{Cout} = 1$$

Ans.

Q4):-

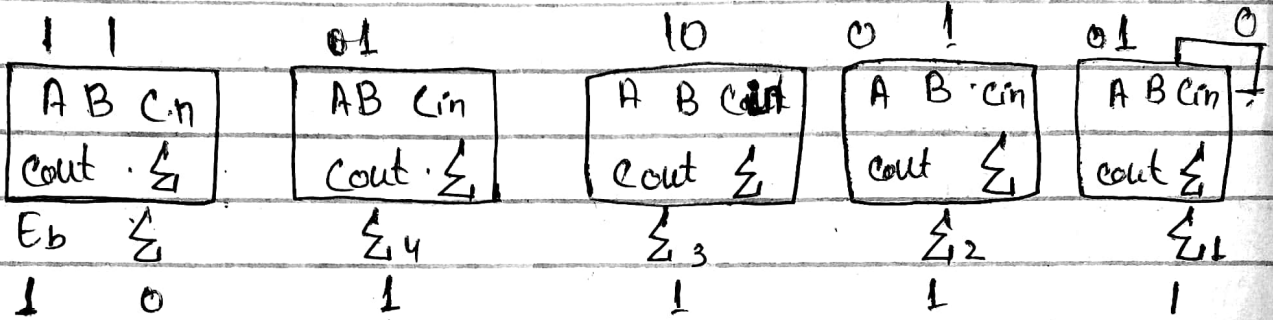

$$\begin{array}{r}
 + \quad A = 10110 \\
 + \quad B = 11001 \\
 \hline
 10111
 \end{array}$$

Ans.

Q3)

(a) When the Add/subt is High, the input bits of B will be complemented, and the resulting Σ will be the subtraction of the input bits.

(b) When the Add/subt is Low, the input bits of B will not be elonged, and the circuit will work as a paralleled adder for the input bits.

Q6:

Add/subt = 1, A = 1010, B = 1101

for Σ_0 : $A_0 = 0$, $B_0 = 1 \oplus 1$, $C_{in} = 1$

$$\Sigma_0 = 0 + 0 + 1 = \boxed{1}, \text{Cout} = 0$$

for Σ_1 : $A_1 = 1$, $B_1 = 1 \oplus 0$, $C_{in} = 0$

$$\Sigma_1 = 1 + 1 + 0 = \boxed{0}, \text{Cout} = 1$$

for Σ_2 : $A_2 = 0$, $B_2 = 1 \oplus 1$, $C_{in} = 1$


$$\Sigma_2 = 0 + 0 + 1 = \boxed{1}, \text{Cout} = 0$$

for Σ_3 : $A_3 = 1$, $B_3 = 1 \oplus 1$, $C_{in} = 0$

$$\Sigma_3 = 1 + 0 + 0 = \boxed{1}, \text{Cout} = 0$$

$$\Sigma = \Sigma_3 \Sigma_2 \Sigma_1 \Sigma_0 = 1101, \text{Cout} = 0 \text{ Ans.}$$

Q7:-

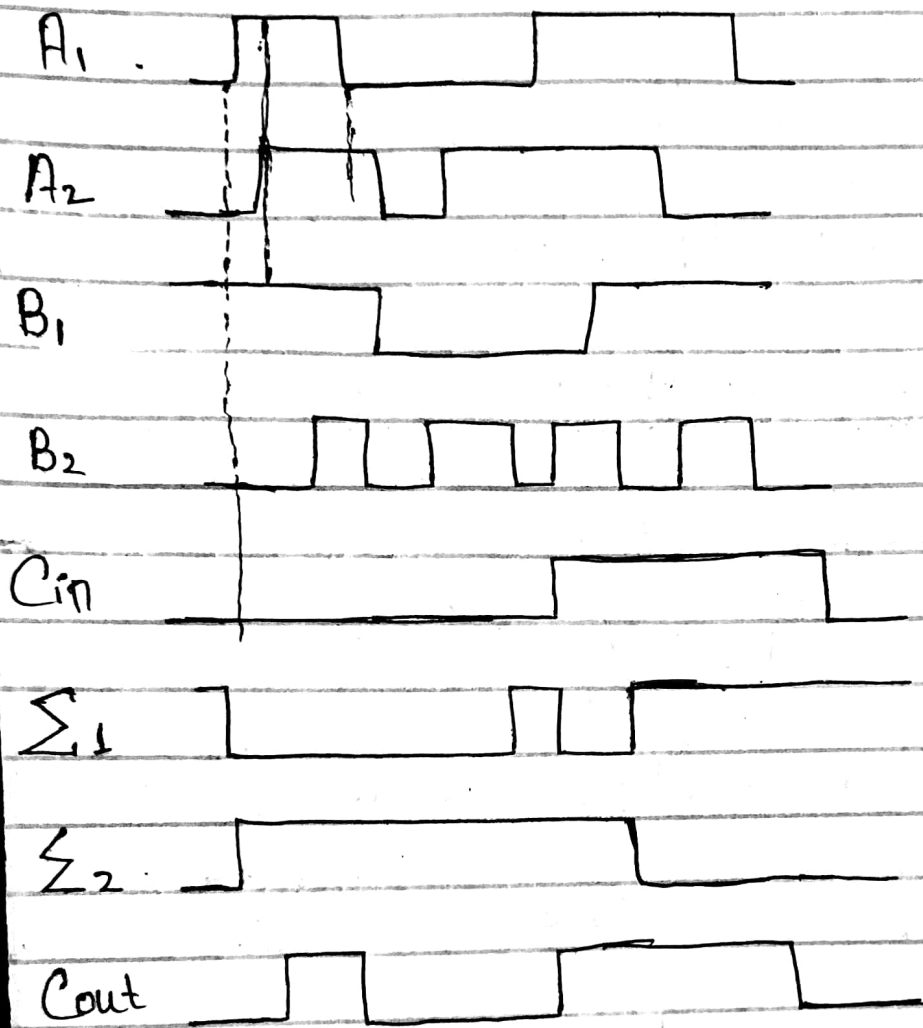

Q8)

$$A_1 = 1010, A_2 = 1100, A_3 = 0101, A_4 = 1101$$

$$B_1 = 1001, B_2 = 1011, B_3 = 0000, B_4 = 0001$$

Soln

A_4	A_3	A_2	A_1	+	B_4	B_3	B_2	B_1	=	Σ_5	Σ_4	Σ_3	Σ_2	Σ_1
1	0	1	1		0	0	1	1		0	1	1	1	0
1	1	1	0		0	0	0	0		0	1	1	1	0
0	0	0	1		0	0	1	0		0	0	0	1	1
1	1	0	0		1	0	1	1		1	0	1	1	1

$$\Sigma_5 = 0'001$$


$$\Sigma_4 = 1100$$

$$\Sigma_3 = 1101$$

$$\Sigma_2 = 1111$$


$$\Sigma_1 = 0011 \text{ ans.}$$

Q10)

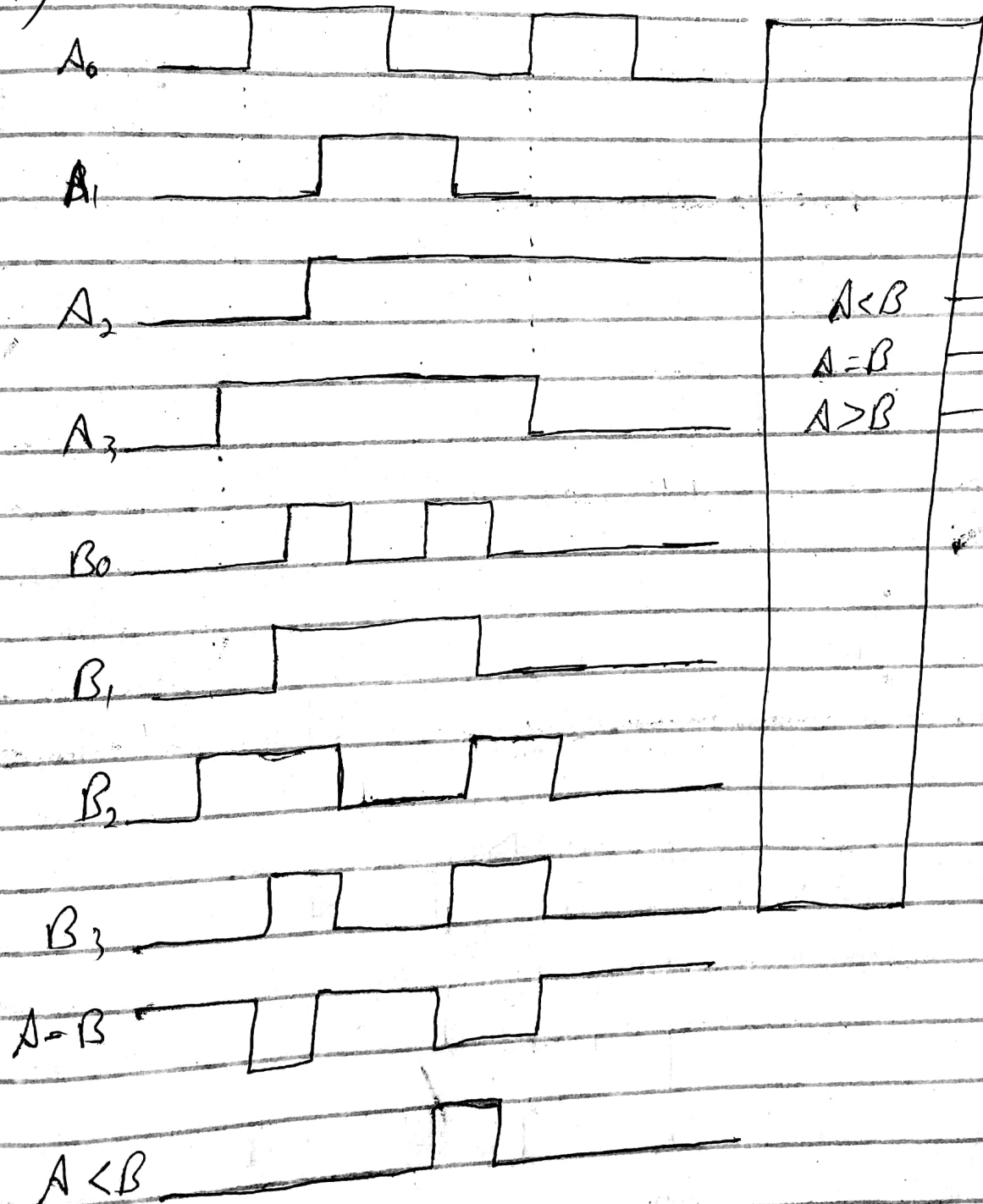

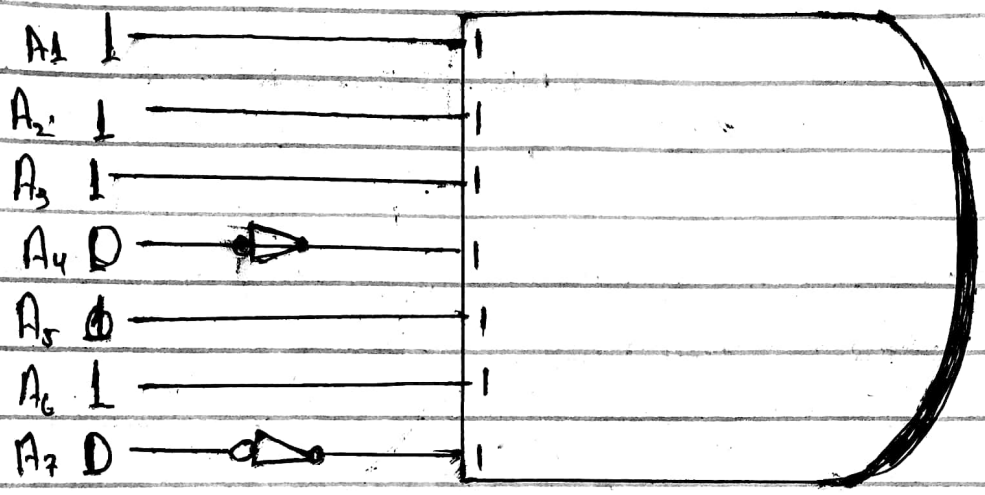Q11)


For the output to be high for the given code 1110110, following is the decoding logics that can be used to decode the given code.




$$X = A_7 A_6 A_5 A_4 A_3 A_2 A_1$$

Ans.


Q12)

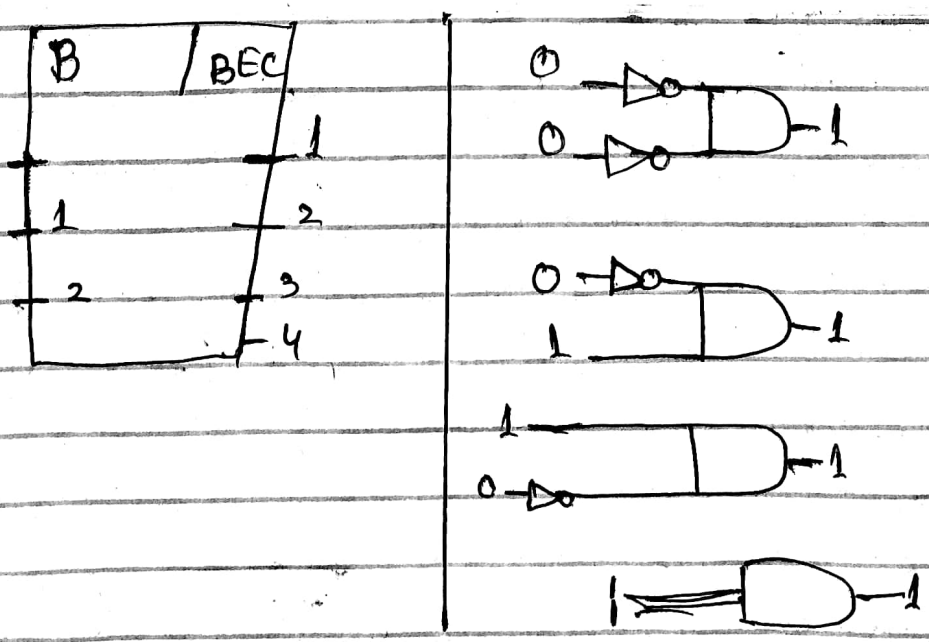


Q13)

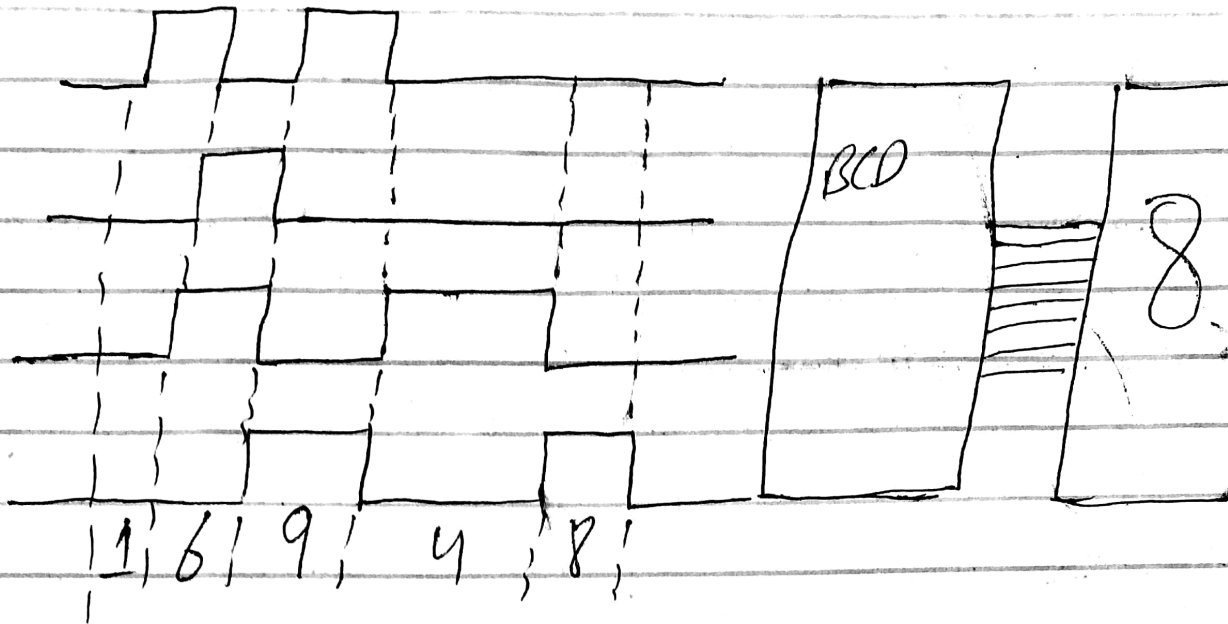

Q14:

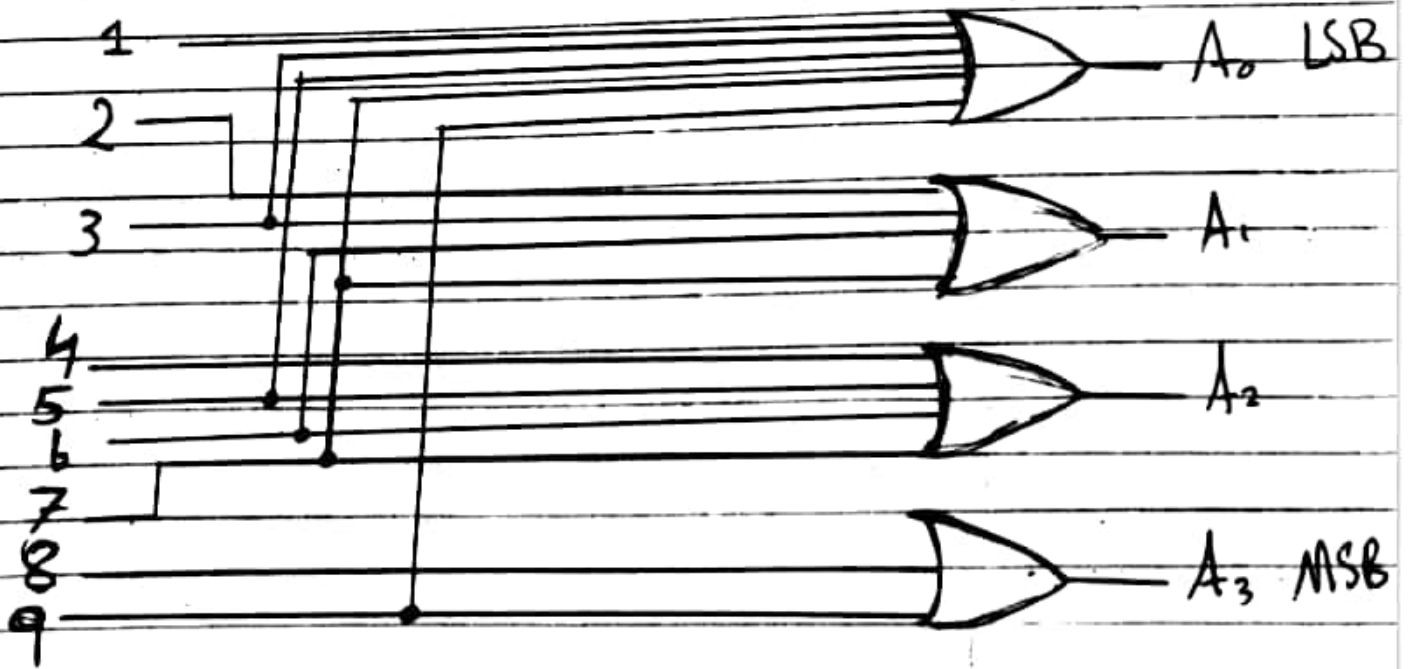


Q15

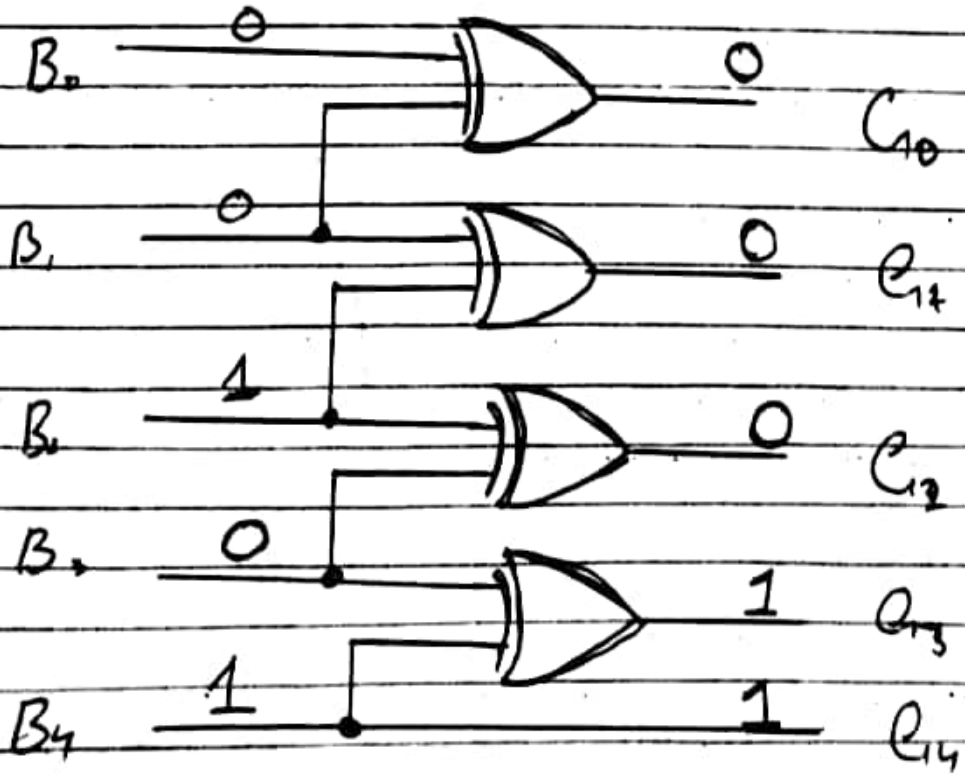

$$10100_2 = 11000_6$$

Q16:

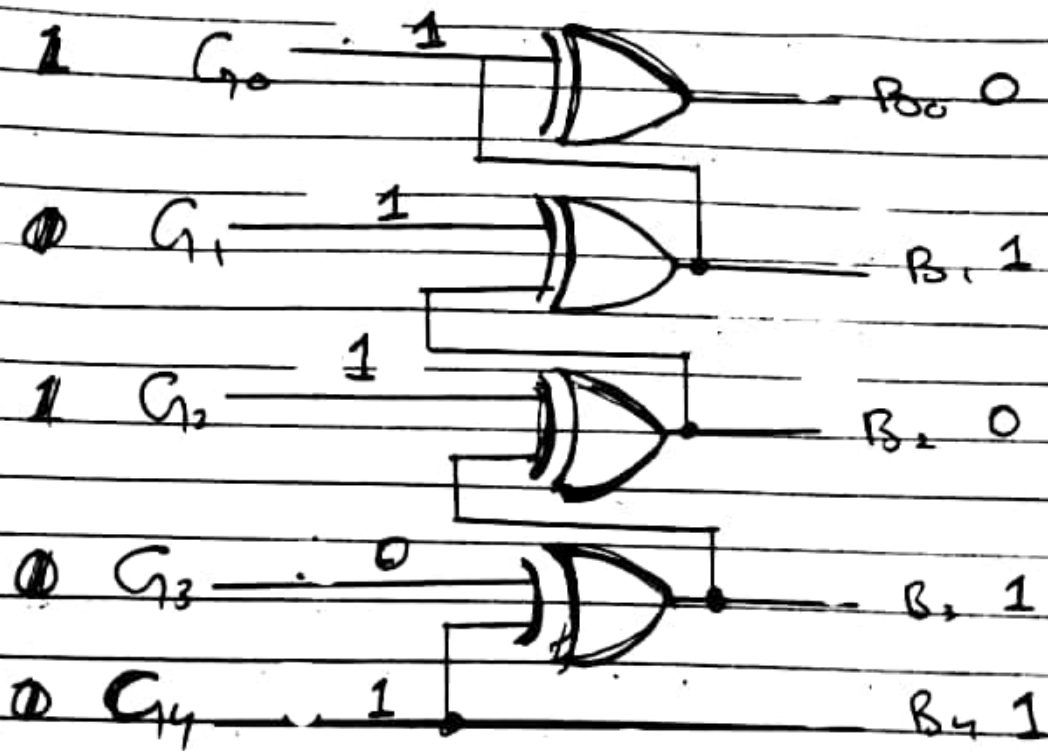


$$10111_e =$$

$$11010_e$$

Ans


Q17)

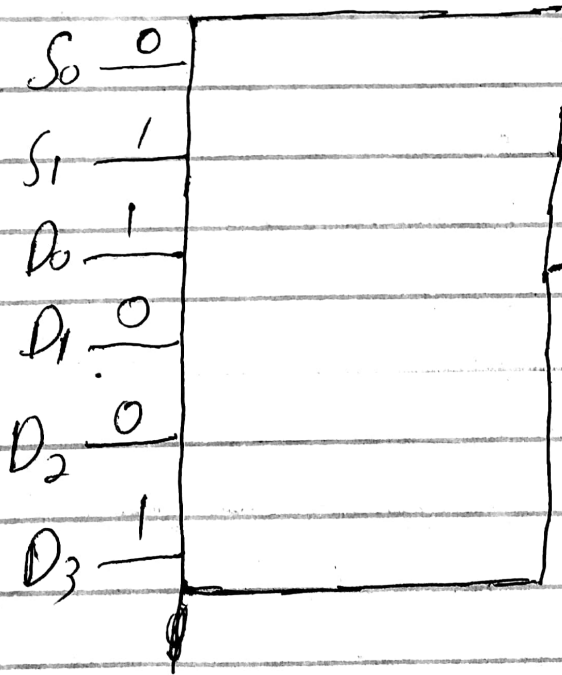


$$D_1 = \frac{0}{1}$$

$$S_0 S_1 = 0/1 \Rightarrow 0$$


18)

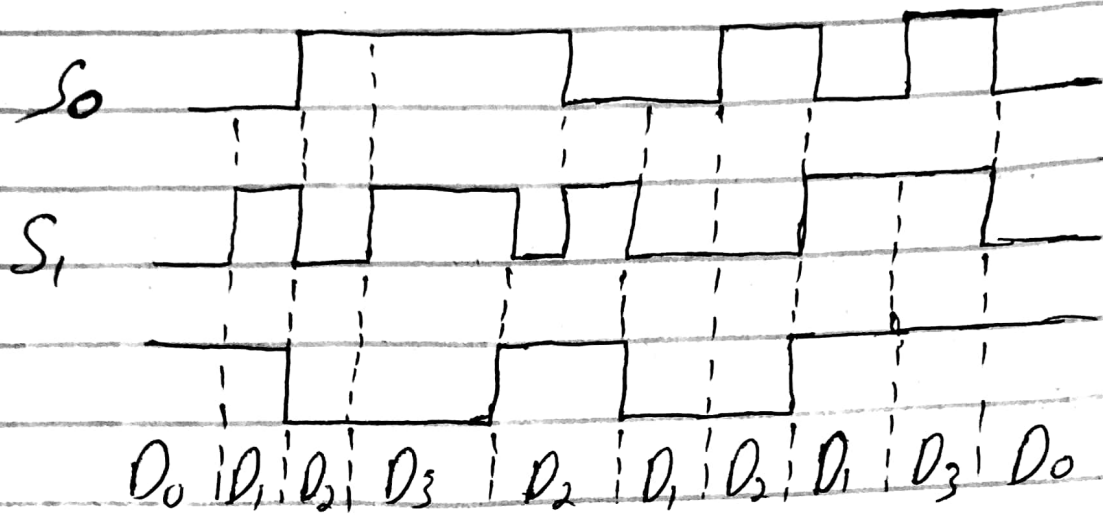


Q19)

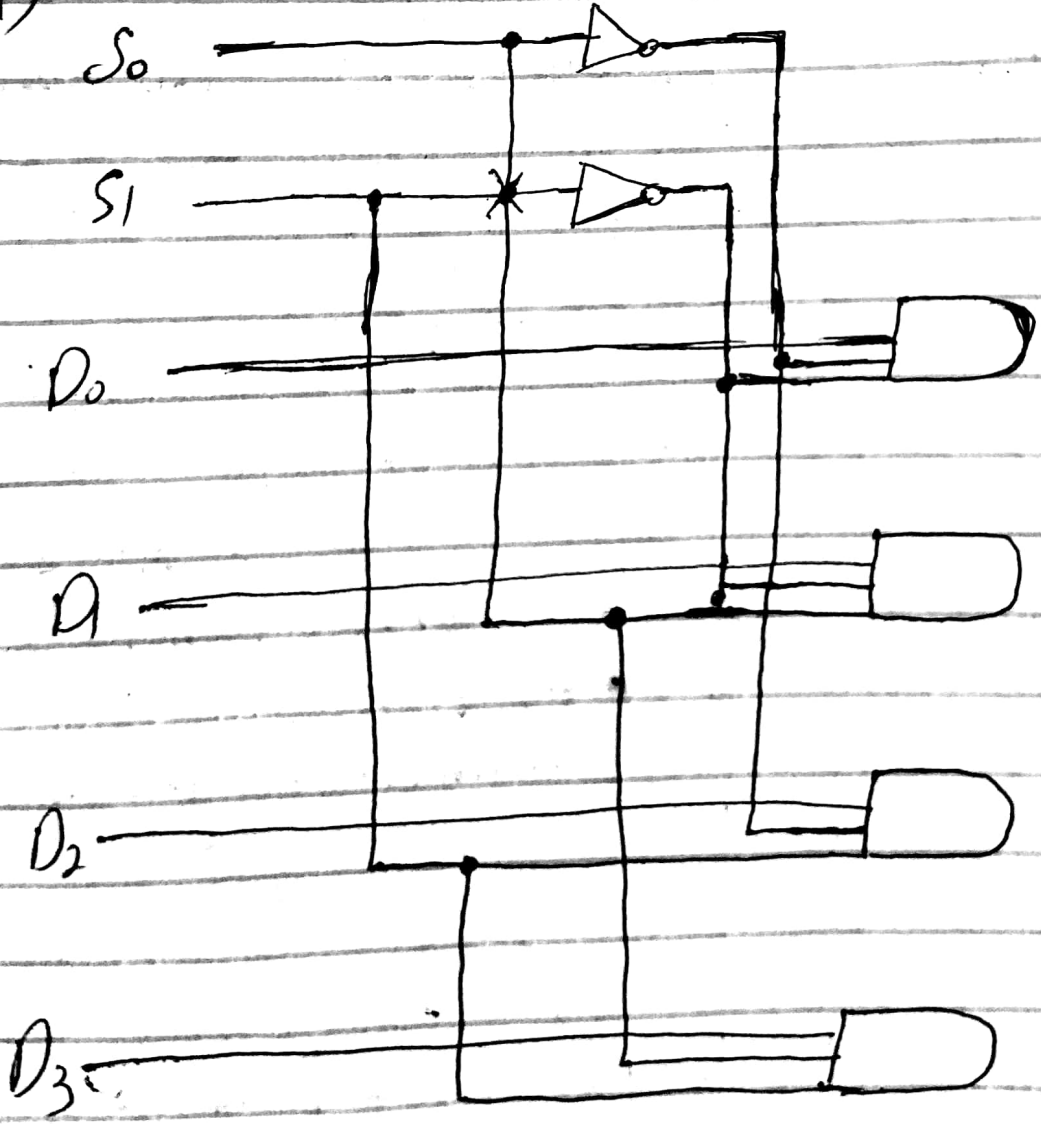

Q26)

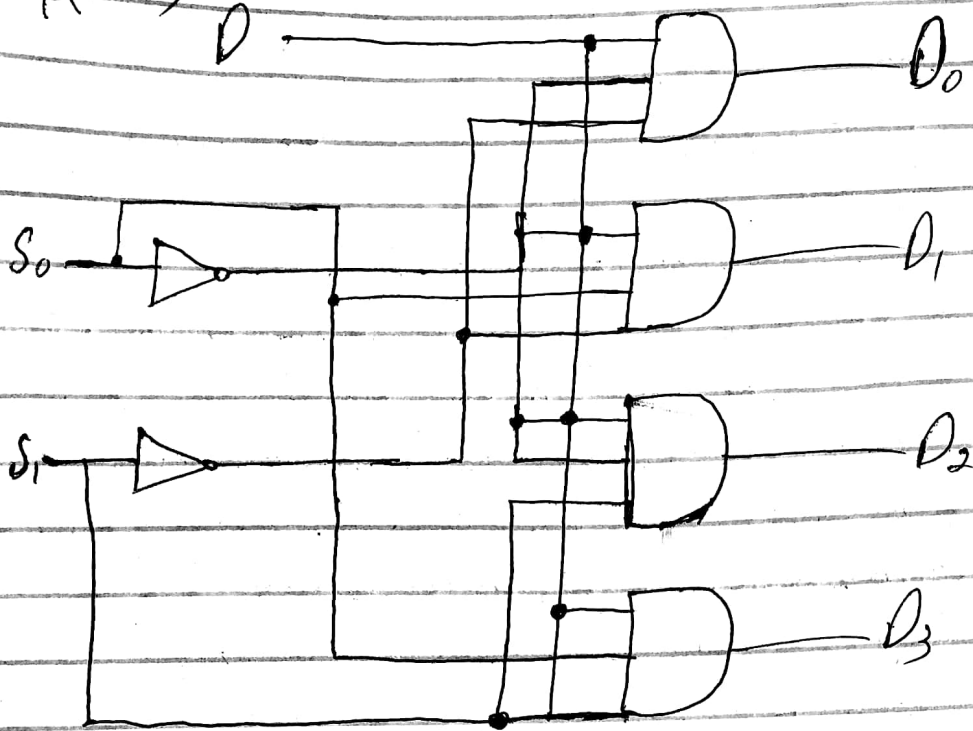


Q20)

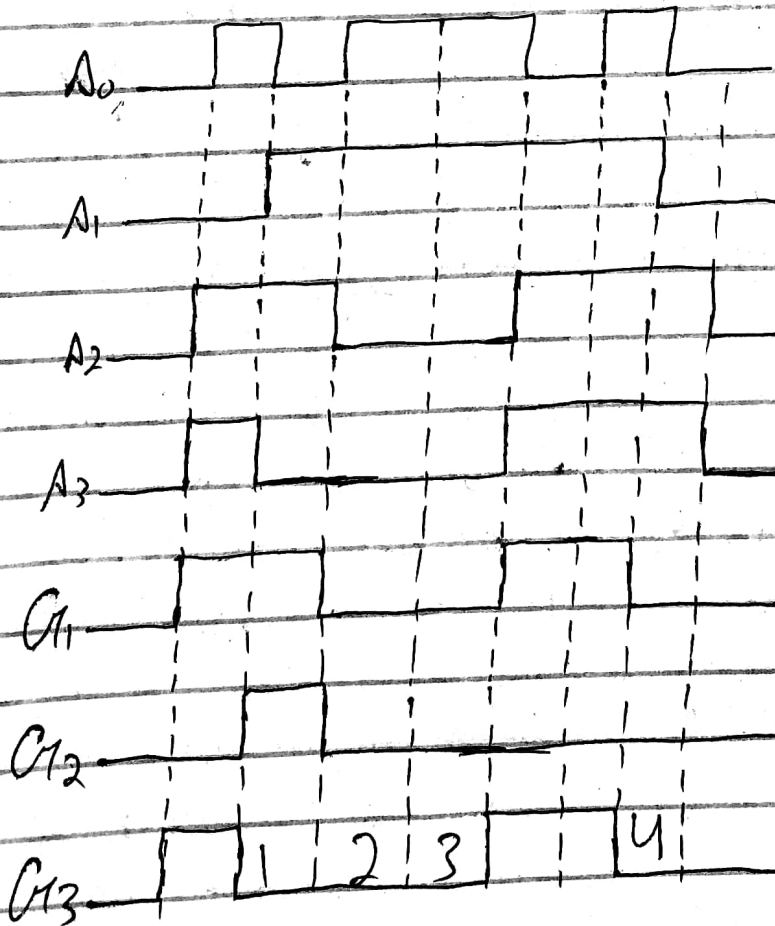

Even Parity occurs 7000s time and is shown by low.

Even

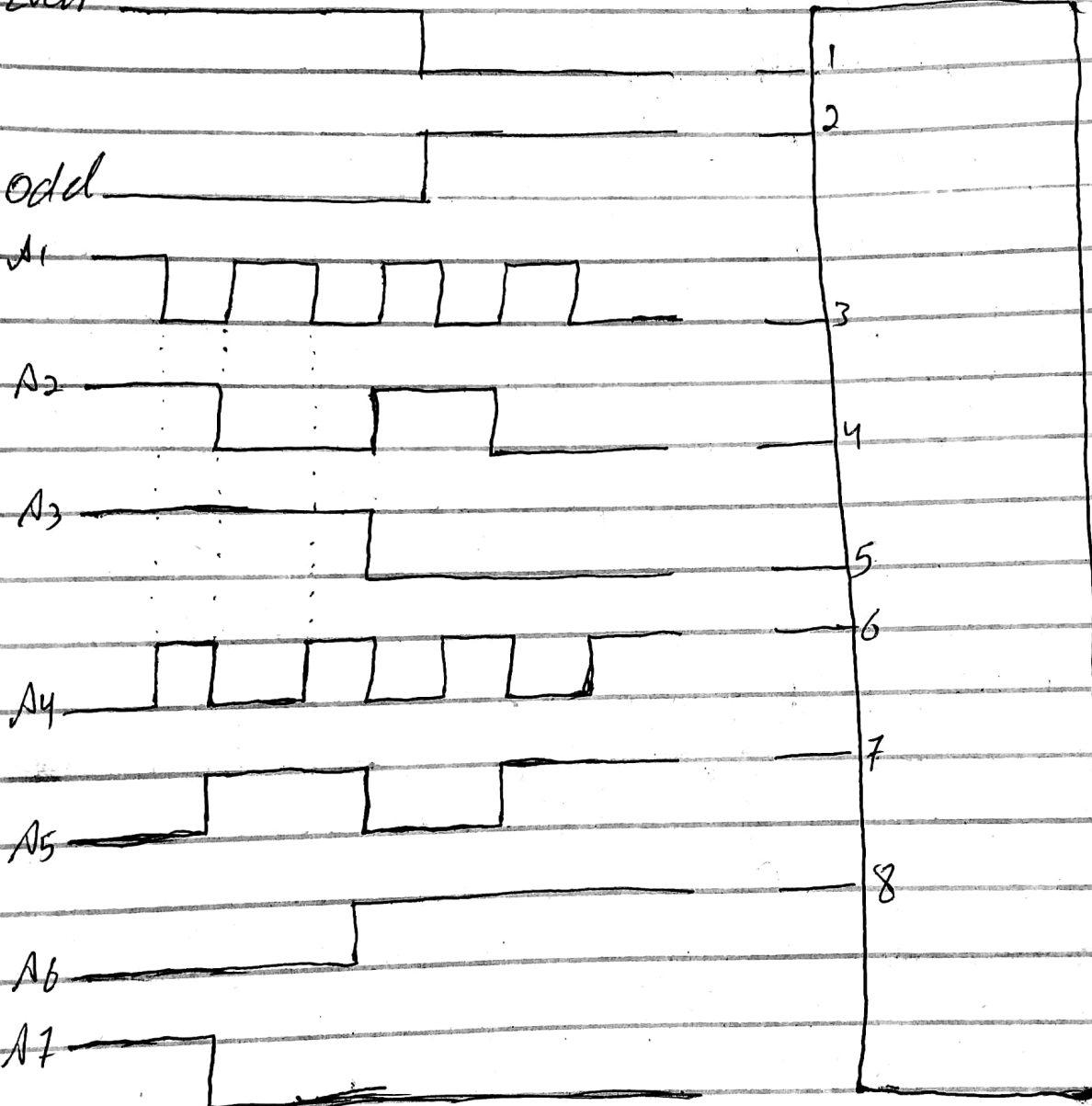

Even

Odd

Even

Odd

Q23

