

Course Title :- ECD

Instructor Name :- Engr. Mujtaba Ihsan.

Module :- 4th Semester.

→ Student Detail:-

Name :- Naveed Alam

Student ID No. :- 14965

Ans No. 1:-

The transconductance curve of a JFET transistor is the graph of the drain current,  $I_D$  versus the gate-source voltage,  $V_{GS}$ .

The ~~unit~~ ratio of change in drain current,  $\Delta I_D$ , to the change in gate-source voltage,  $\Delta V_{GS}$ , is the transconductance,  $g_m$ .

The units of transconductance is the siemen (S) - It is the reciprocal of resistance ( $\Omega$ ).


The transconductance curve, as for all semiconductor devices, is non-linear, for most of the curve, meaning changes to  $V_{GS}$  do not directly increase or decrease drain current,  $I_D$ .

Below are the transconductance curve of N-channel JFET transistors and P-channel JFET Transistors.

The Regions that make up a transconductance curve are the following-



## N-Channel JFET Characteristics Curve.

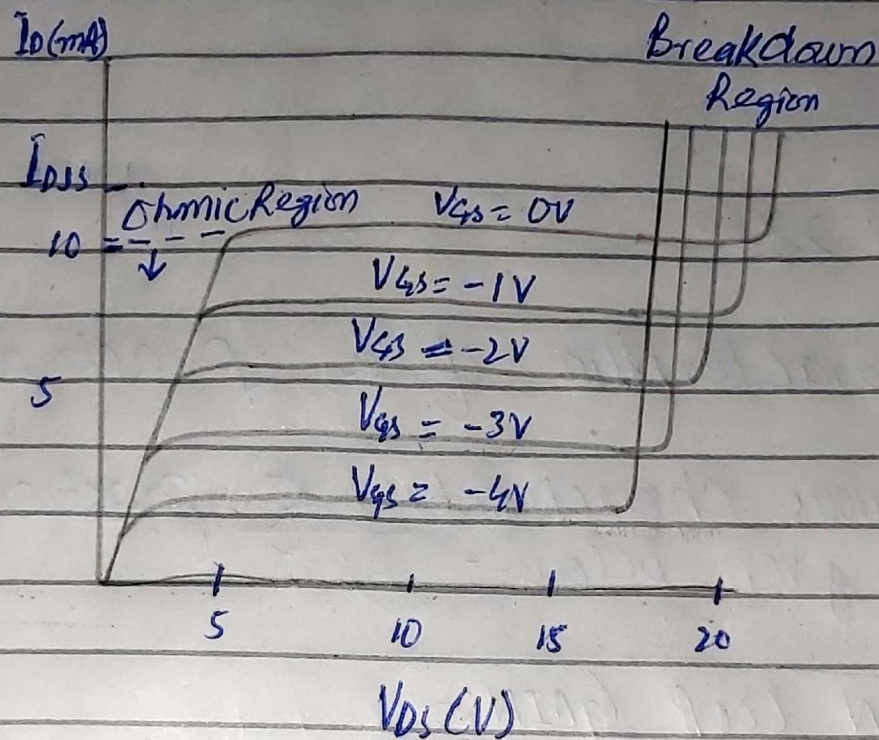

### → Cut-off Region:-

This is the region where the JFET transistor is off, meaning no drain current,  $I_D$  flows from drain to source.

### → Ohmic Region:-

This is the region where the JFET transistor begins to show some resistance to the drain current,  $I_D$  that is beginning to flow from drain to source. This is the only region in the curve where the response is linear.



Ans NO. 29-

→ Characteristic of a practical op-amplifier:-

Various characteristic of practical op-amplifier is given below:-

① OPEN LOOP GAIN:-

It is the voltage gain of the op-amplifier when no feedback is. Practically it is several thousand.

② Input Impedance:-

It is finite and typically greater than  $1\text{M}\Omega$ . But using PETS for the input stage ~~it~~ it can be increased upto several hundred  $\text{M}\Omega$ .

③ Output Impedance:-

Typically few hundred ohms with the help of negative feedback it can be reduced to a very small value like 1 or 2 ohms.

(9) :- Slow Rate (SR) :-

It is define as the maximum rate of change of output voltage w.r.t time

$$SR = \left[ \frac{dV_o}{dt} \right]_{max}$$



Ans No. 3 :-

$$V_{out} = -R_f/R (V_1 + V_2 + V_3)$$

$$V_{out} = -\frac{6k\Omega}{6k\Omega} (0.2 + 0.5 + 2)$$

$$V_{out} = -2.7$$

Ans

No. 4 Part B :-

outline the difference between an Amplifier and Rectifier.

→ Amplifier:-

An Amplifier is used to increase the strength of an electric signal.

→ Rectifier

Where as a rectifier allow current to pass only one direction and is used to produce Dc from Ac.