

Haroon Rashid



Reg# 16549

Semester 6th

Assignment: DLD Lab

Submitted to: Sir MUHAMMAD AMIN

Lab 4: HALF Subtractor

  

Logic Circuit of Half Subtractor

Table 4.1:

Inputs		Outputs	
A	B	D	Bo
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Lab = 4

4.7 Observation Table

Full Subtractor Input Variable - A, B, Bin
Output Variable - D, Bout

Table

Inputs			Outputs	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1