

**Department of Electrical Engineering
Assignment**

**Date:
13/04/2020**

Course Details



Course Title: Linear Circuit Analysis
Instructor: Dr. Sohail Imran


Module: 2
Total Marks: 30

Name: Ali Raza


Student ID: 16309

**Student
Details**

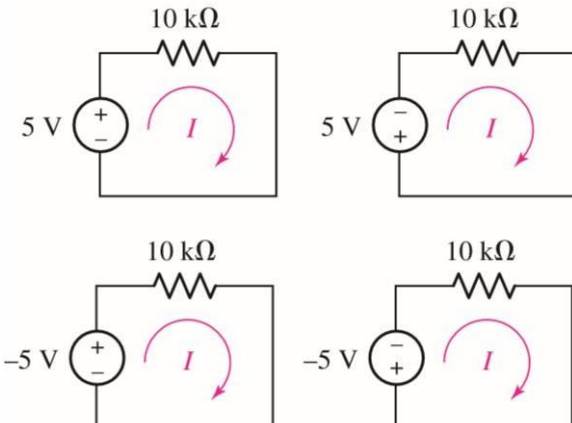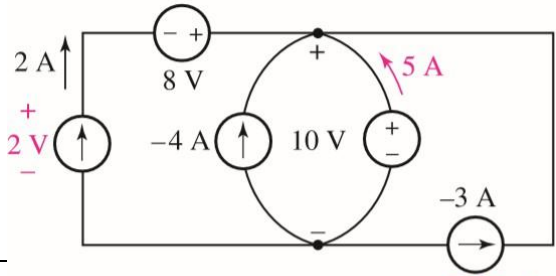
Q1	(a)	<p>For each of the circuits in figure, find the current I and compute the power absorbed by the resistor</p> <div style="display: flex; justify-content: space-around; align-items: center;">  </div>	<p>Marks 3</p> <p>PLO1</p>
	(b)	<p>Determine the power supplied by the leftmost element in the circuit of following figure</p> <div style="text-align: center;">  </div>	<p>Marks 4</p> <p>PLO1</p>
	(c)	<p>Following figure - 10 V + of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.</p>	<p>Marks 3</p> <p>PLO1</p>

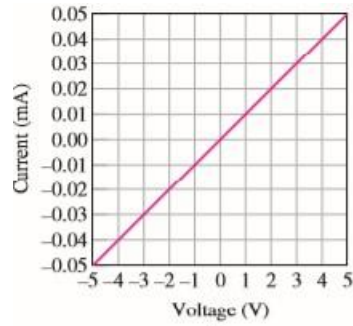

(a)

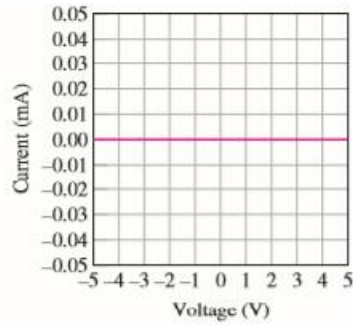

(b)


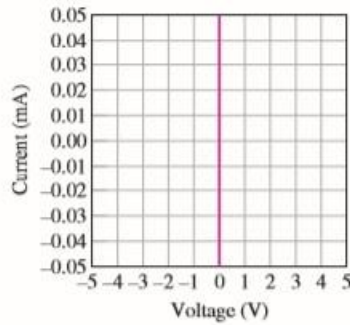


(c)

Q2 (a)

Refer to the circuits of following figures, and answer the following:

1. How many distinct nodes are contained in the circuit?
2. How many elements are contained in the circuit?
3. How many branches does the circuit have?
4. Determine if each of the following represents a path, a loop, both, or neither:
 - i. A to B
 - ii. B to D to C to E
 - iii. C to E to D to B to A to C
 - iv. C to D to B to A to C to E

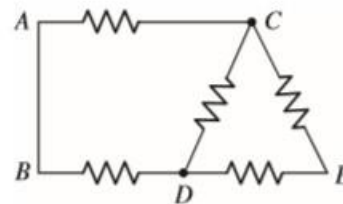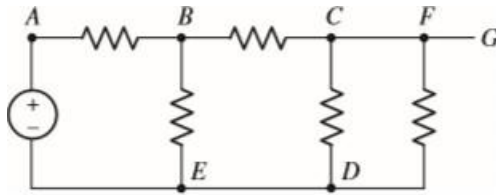Marks
4


PLO2

(b)

For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region), I_B is measured to be $100 \mu\text{A}$. Determine I_C and I_E

Marks
6

PLO2

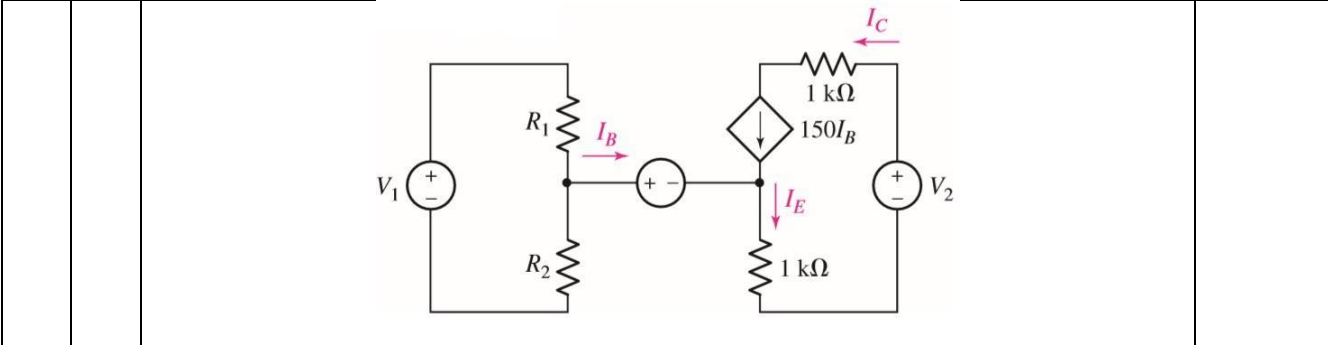


Q3

(a)

Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.

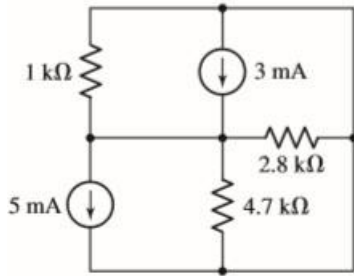- Determine the power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).




Marks
5

PLO1

(b)

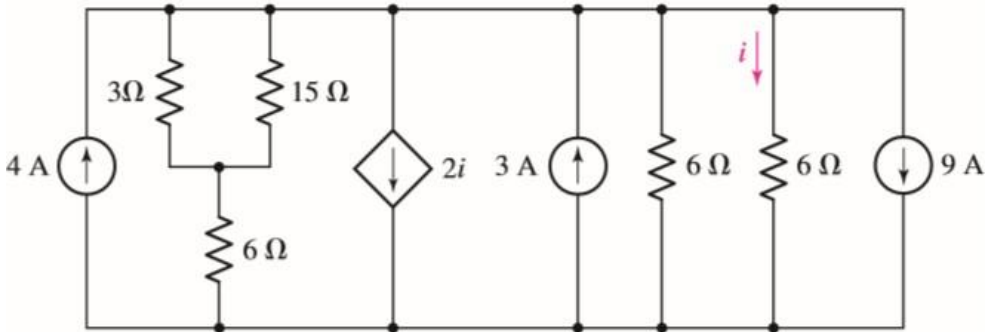Determine the power absorbed by the 15 Ω resistor in the circuit of following figure



Marks
5

PLO1

Question 1)

Part (A)

SOLUTION:

Finding current(I)

a)

Ohm's law state that

$$V=I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{5V}{10K\Omega}$$

$$I = 0.5mA$$

b)

Solution:-

$$V=I \times R$$

$$I = \frac{V}{R}$$

$$I = \frac{-5V}{10K\Omega}$$

$$I = -0.5mA$$

c)

solution :-

$$I = \frac{V}{R}$$

$$I = \frac{-5V}{10K\Omega}$$

$$I = -0.5mA$$

d)

solution:-

$$I = \frac{V}{R}$$

$$I = \frac{-(-5V)}{10K\Omega}$$

$$I = 0.5mA$$

Now finding Power,

Power absorbed by all the resistors is

$$P_R = I^2 \times R$$

Putting values

$$P_R = ((\pm 0.5)^2 \times 10^{-3}) \times (10 \times 10^3)$$

$$P_R = 2.5mW$$

PART (B)

Solution:-

Since we know both the value of I and V is the left most element we can calculate,

$$P = VI$$

$$P = (2V \times 2A)$$

$$P = 4W$$

Because of the direction of current through the element we know that the power is supplied.

PART (C)

Ohm's law states that

$$V=IR$$

$$R = \frac{V}{I}$$

So we can calculate R from the slope on the graph

We can take any point on line to get the value of I and V.

a)

$$R = \frac{V}{I}$$

$$R = \frac{2}{0.02 \times 10^{-3}}$$

$$R = 100k\Omega$$

b)

$$I=0A, V=1v$$

$$R=\frac{V}{I}$$

$$R=\frac{1}{0}$$

$$R=\infty\Omega$$

c)

$$I=0.03mA, V=0v$$

$$R=\frac{V}{I}$$

$$R=\frac{0}{0.03 \times 10^{-3}}$$

$$R=0\Omega$$

QUESTION 2

SOLUTION:-

1. If we look at the given figure we get,

a) Nodes =4

b)

now if we start at point A and move to point B we move to another node and that means we formed a path but we visited each node only once so there is no loop,

Path=yes

Loop=No

c)

And we do the same for part. After moving from C to F ,F to G. we are still in the same node. Therefore ,

Path =No

Loop = No

2. Number of elements in the circuit are 6

Part B(2nd diagram)

a) As seen in the given circuit point B to A and Care the the same node additionally we have other 2 nodes E and D. Thus the number of node is 3.

b) We have 4 resistors in the given circuit thus the number of elements is 4.

c) We define a branch as a single path in a network, composed of one simple element and the node at each end of that element. Thus we have 4 branches in the given circuit.

d)

i) This is neither a path nor a loop nor both. This is because point A and B are the same (considered as a single node).

ii) This is a path because no node was encounter more than once.

iii) This is both a path and a loop because the node at which we started (C) is the same as the node on which we ended (C),then this path is by definition a closed path or a loop.

iv) This is neither a path nor a loop nor both,because the node C was encountered twice but the path was ended at the node E not C.

QUESTION 2

PART (B)

SOLUTION:-

Applying KCL

$$I_B + I_C = I_E$$

So,

$$I_c = 150 \times I_B$$

$$I_c = 150 \times 100 \times 10^{-6}$$

$$I_c = 15mA$$

Now we can find I_E

$$I_E = I_c + I_B$$

$$I_E = 15 \times 10^{-3} + 100 \times 10^{-6}$$

$$I_E = 15.1mA$$

QUESTION 3)

PART (A)

We can find V by combining similar elements

$$V=IR$$

$$V=2 \times 10^{-3} \times 637$$

$$=1.274V$$

Now lets find I of each

$$I_X = \frac{1.274}{1000}$$

$$=1.274mA$$

$$I_Y = \frac{1.274}{2800}$$

$$=0.455mA$$

$$I_Z = \frac{1.274}{4700}$$

$$=0.271mA$$

Now finding Power

$$P=VI$$

$$P_{(2.8K)}=(1.274)(0.455)$$

$$=0.5792mW$$

$$P_{(4.7k)} = (1.274)(1.271)$$

$$=1.623mW$$

$$P_{(1k)} = (1.274)(1.274)$$

$$=1.523mW$$

$$P_{(5mA)} = (1.274)(-5)$$

$$=6.37mW$$

$$P_{(3mA)} = (1.274)(3)$$

$$=3.822mW$$

PART B

SOLUTION:-

$$R_{(X)} = [(3 \parallel 15) + 6] \parallel 6$$

$$=[2.5+6] \parallel 6$$

$$=8.5 \parallel 6$$

$$= \frac{8.5 \times 6}{8.5+6}$$

$$= \frac{102}{29} \Omega$$

The equivalent current source,

$$I_T = -4 + 2i - 3 + 9$$

$$=2+2i \text{ (downward)}$$

Applying KCL

$$2+2i + \frac{v_x}{\frac{102}{29}} + i = 0$$

$$2+3\left(\frac{v_x}{6}\right) + \frac{v_x}{\frac{102}{29}} = 0$$

Solving this equation, We obtain

$$v_x = -2.55V$$

(a) The equivalent resistance of the parallel two resistors

$$3 \parallel 15 = \frac{3 \times 15}{3+15} = 2.5 \Omega$$

(b) Using ohm's law, we obtain

$$i_6 = \frac{v_x}{2.6+6} = \frac{-2.55}{8.5}$$

$$= -0.3\text{A}$$

Thus,

$$v_{15} = 2.5 \times i_6$$

$$= (2.5)(-0.3)$$

$$= -0.75\text{v}$$

Therefore, the power absorbed by the 15 Ω is

$$P_{15\Omega} = \frac{v_{15}^2}{15}$$

$$\frac{(-0.75)^2}{15}$$

$$= 37.5\text{mW}$$

First, we will simplify the circuit by calculating source and resistor equivalences

$$I_{eq} = 4 - 2i + 3 - 9$$

$$= -2 - 2i$$

$$R_{eq} = (6 + 3 \parallel 15) \parallel 6 \parallel 6$$

$$R_{eq} = 8.5 \parallel 3$$

$$= 2.2174 \Omega$$

Now, we can calculate voltage v as,

$$V = I_{eq} \times R_{eq}$$

$$V = (-2 - 2i) \times 2.2174 \Omega$$

And from the diagram we can see that,

$$V = 6i$$

$$6i = (-2 - 2i) \times 2.2174$$

$$10.4348i = -4.4348$$

$$i = -0.425\text{A}$$

$$V = -2.55\text{v}$$

To get the power consumed by the 15 ohm resistor we need the voltage on that resistor two,

$$P = \frac{V^2}{R}$$

$$P_{15\Omega} = \frac{V_{15\Omega}^2}{15\Omega}$$

$$V_{15\Omega} = \frac{6}{6 + 2.5} \times v$$

$$V_{15\Omega} = 1.8\text{v}$$

And the power is,

$$P_{15\Omega} = \frac{1.8^2}{15\Omega}$$

$$P_{15\Omega} = 0.216\text{W}$$

For calculating equivalent resistance we use the following expressions,
Series ($R_1 + R_2$)

$$R_{eq} = R_1 + R_2$$

Parallel($R_1||R_2$)

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$$

Now we can calculate the equivalnces as,

$$R_{eq} = 1\Omega + 2\Omega || 2\Omega$$
$$R_{eq} = 1\Omega + \frac{2\Omega \times 2\Omega}{2\Omega + 2\Omega}$$
$$R_{eq} = 1\Omega + 1\Omega$$
$$R_{eq} = 2\Omega$$

b)

$$R_{eq} = 4\Omega + \frac{1\Omega \times 2\Omega}{1\Omega + 2\Omega} + 3\Omega$$

$$R_{eq} = 7.667\Omega$$