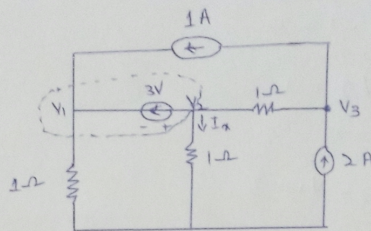


Muhammad Zeshan ID \Rightarrow 11596 Page No = 01

Part A (objective type)

- ① A network have ten nodes and 17 branches. The number of different node pair voltage would be 45
- ② Assuming ideal element in the circuit shown below, the voltage across A, B, V_{AB} is -3
- ③ Which of the following theorem is applicable for both linear and non linear circuits None of these
- ④ Maxwell's loop current method of solving electrical networks utilize kirchhoff's voltage law
- ⑤ For the network shown below, when $I=0$, $V_{p0} = 20V$ and when $r=0$, $I=10A$. If now $R=3$ ohms, ~~what~~ what is the value of current I 6.67 A
- ⑥ The rms value of wave in figure is about 50V
- ⑦ A capacitor store 0.15C at 5V. Its capacitance will be 0.03F
- ⑧ System function $H(s) = \frac{1}{s+3}$, For a signal $\sin 2t$, the steady state response is $\frac{1}{8}$
- ⑨ An ideal transformer has a turn ratio of 2:1. Taking hv side as a port and Iv as port 2 transmission parameters of transformer are $\begin{bmatrix} 2 & 0 \\ 0 & 0.5 \end{bmatrix}$
- ⑩ Wave $A = 100 \sin \omega t$ and wave $B = 100 \cos \omega t$, then rms values of A is more than that of B.

Q :

Ans : Solⁿ

The presence of a voltage source between the node 1 and node 2 make the combination of nodes 1 and node 2 a supernode. Hence.

$$\frac{V_1}{1} - 2 + \frac{V_2}{1} + \frac{V_2 - V_3}{1} = 0 \quad \text{--- (A)}$$

For node 3,

$$\frac{V_3 - V_2}{1} - 2 + 1 = 0 \quad \text{--- (B)}$$

and auxiliary equation

$$V_2 - V_1 = 3 \quad \text{--- (C)}$$

Now combine the above three equations

so

$$V_1 - 2 + V_2 + V_2 - V_3 = 0 \quad \rightarrow \text{From eq (A)}$$

$$V_1 + 2V_2 - V_3 = 2$$

$$V_3 - V_2 - 1 = 0 \quad \rightarrow \text{From eq (B)}$$

$$V_3 - V_2 = 1$$

$$V_2 - V_1 = 3 \quad \rightarrow \text{From eq (C)}$$

Now combining equation (A), (B) and (C)

$$V_1 + 2V_2 - V_3 + V_3 - V_2 + V_2 - V_1 = 2 + 1 + 3$$

So

$$2V_2 = 6$$

$$V_2 = \frac{6}{2} \Rightarrow \boxed{V_2 = 3}$$

Now

$$V_2 - V_1 = 3 \quad \text{From eq (C)}$$

$$2 - V_1 = 3$$

$$-V_1 = 3 - 2 \Rightarrow -V_1 = 1 \Rightarrow \boxed{V_1 = -1}$$

Now

$$V_3 - 2 = 1$$

$$V_3 = 1 + 2 \Rightarrow \boxed{V_3 = 3}$$

Finally


$$I_x = \frac{V_2}{1} = \frac{2}{1} = 2 \text{ A}$$

So

$$\boxed{I_x = 2 \text{ A}}$$

I-D \Rightarrow 1159

page No = 04

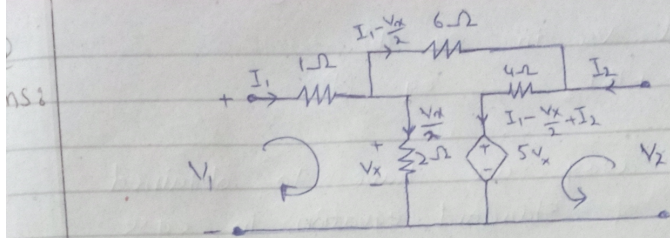

$$\Rightarrow +V_1 - I_1 \times 1 - V_x = 0$$

$$\Rightarrow V_1 = I_1 + V_x \quad \text{--- (A)}$$

$$\Rightarrow +V_2 - (I_1 - \frac{V_x}{2} + I_2) \times 4 - 5V_x = 0$$

$$\Rightarrow V_2 = 4I_1 + 4I_2 + 3V_x \quad \text{--- (B)}$$

Now when we compare equation (A) and (B) with their standard form you will find they are not in standard form and therefore we cannot proceed further and the problem is there because we ~~are~~ V_x is present both the equations so to have these standard equation we have required to write down V_x in term of I_1 and I_2 .

Now apply KVL

$$\Rightarrow V_x - (I_1 - \frac{V_x}{2}) \times 6 - (I_1 - \frac{V_x}{2} + I_2) \times 4 = 5V_x$$

$$\Rightarrow V_x = 10I_1 + 4I_2$$

put $V_x \rightarrow$ eq (A)

$$V_1 = 11I_1 + 4I_2 \quad \text{--- (C)}$$

I-D = 11596

Page No = 05

Now put V_1 in eq (b)

$$V_2 = 34I_1 + 16I_2 \quad \text{--- eq (c)}$$

By this way we have to obtained the set of standard equation in case of Z parameter.

$$\therefore Z_{11} = 11 \quad Z_{12} = 4$$

$$Z_{21} = 34 \quad Z_{22} = 16$$

we know that

$$A = Z_{11}/Z_{21}, \quad B = 1/Z_{21}$$

$$C = 1/Z_{21}, \quad D = Z_{22}/Z_{21}$$