

Name

Noor-ul-Wahab

ID

12395

Subject

Electronics Circuit Design

Instructor Name

Eng Sir Mujtaba Ihsan

Date

24/06/2020

Ans
01(a)

Multistage Amplifiers :-


Two or more amplifiers can be connected to increase the gain of an ac signal

The overall gain can be calculated by

Simply multiplying each gain together

$$A_v = A_{v1} A_{v2} A_{v3} \dots$$

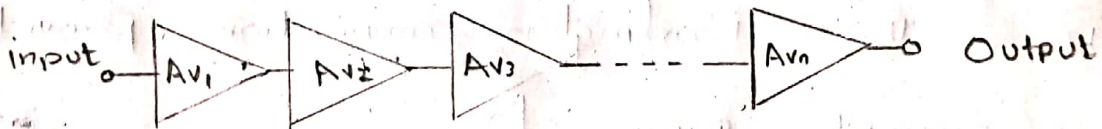Multistage amplifiers are amplifier circuits cascaded to increased gain. We can express gain in decibels (dB)



Darlington Connection :-

The main feature is that the composite transistor acts as a single unit with

a current gain that is the product of the current gains of the individual transistors.

Provides high current gain than a single BJT

The connection is made using two separate transistors having current gains

$$B_1 \text{ and } B_2$$


So the current gain

$$B_D = B_1 B_2$$

$$B_1 = B_2 = B$$

if, the Darlington connection provides a current gain, \Rightarrow

$$B_D = B^2$$

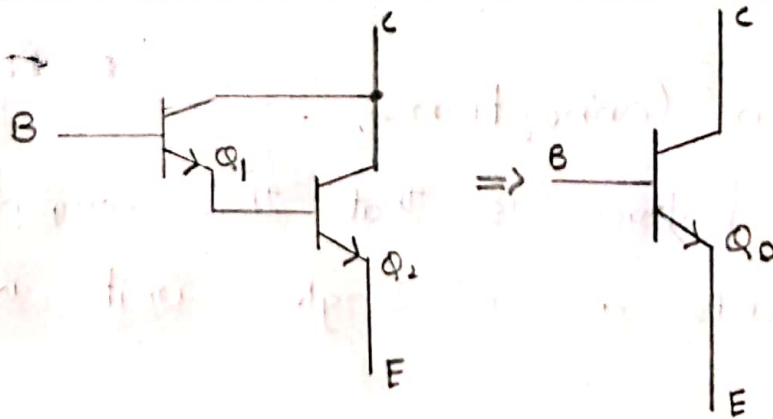

Darlington Transistor

Ans
16)Solution:

$$\text{Line Reg} = \frac{0.062}{4.5} \times 100\%$$

$$= 1.377\%$$

and

$$\text{Lin Reg} = \frac{0.062}{4.0} \times 100\%$$


$$4.5$$

$$= 0.034\% \text{ V}$$

Ans
2

Colpitts Oscillator :-

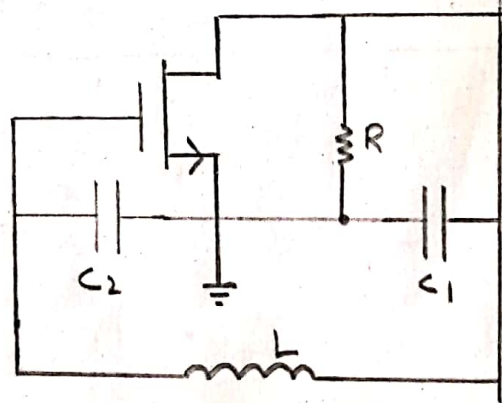
- The Colpitts Oscillator is a type of oscillator that uses an LC circuit in the feedback loop.
- The feedback network is made up of a pair of tapped capacitor (C_1 & C_2) and an inductor L to produce a feedback necessary for oscillations.
- The output voltage is developed across C_1 .
- The feedback voltage is developed across C_2 .



Hartley Oscillator:

- The Hartley Oscillator is almost identical to the Colpitts Oscillator.
- The primary difference is that the feedback network of the Hartley

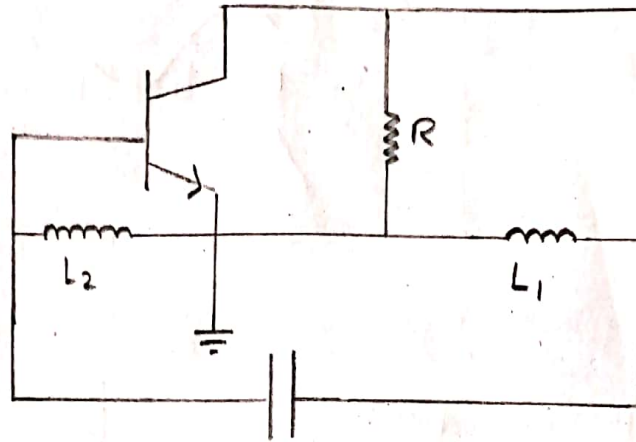Oscillator uses tapped inductor (L_1 and L_2) and a single capacitor (C).





Ans

3(a)

Power Amplifier (Class "B")

- Opposite of class A: A both output devices are never allowed to be on at the same time
- Each output device is on for exactly one half of a complete sinusoidal signal cycle.
- Class B design shows high efficiency but poor linearity around the crossover region due to the time it takes to turn one device off and other device on.
- Class B-design restricted to low power application, e.g. battery operated equipment such as communication Audio.

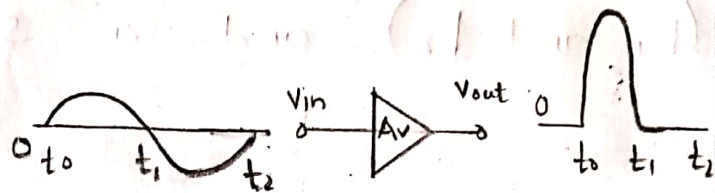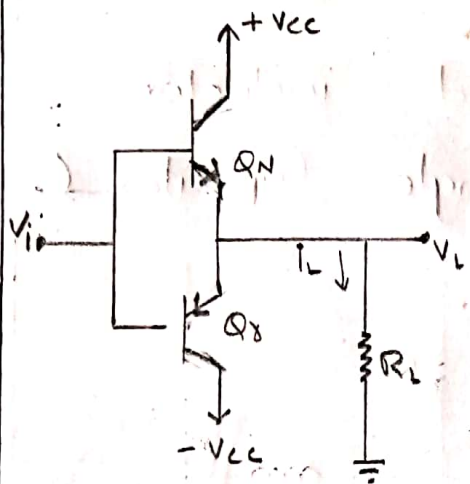


Class B output stage


Circuit Operation:

Class B Output Stage:

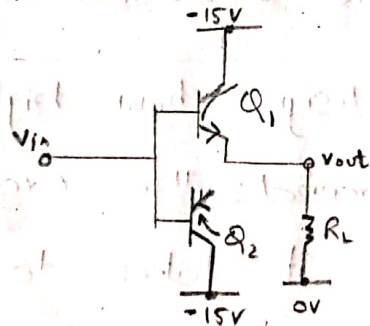- Q_1 and Q_2 form two unbiased emitter followers.
- Q_1 only conducts when input is positive.
- Q_2 only conducts when input is negative.
- When input is zero, neither conducts.
- i.e. the quiescent power dissipation is zero.



Class B Current wave form:

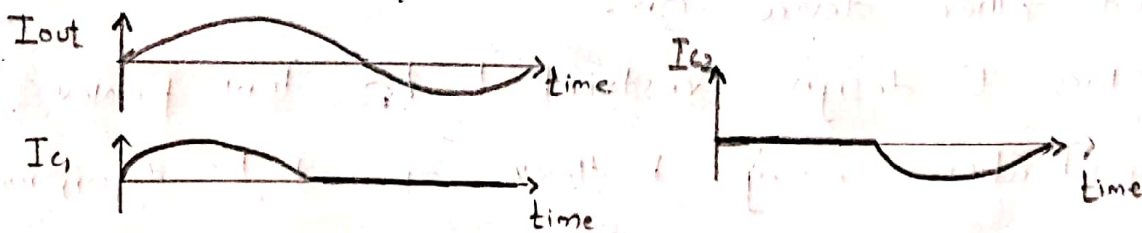

Efficiency/Power Dissipation:-

- Peak efficiency of class B output stage is 78.5% much higher than class A.
- Unlike class A, power dissipation varies with output amplitude.
- Remember, there are two output devices so the power dissipation is shared between them.

Class B:-

- A class B output stage can be far more efficient than a class A stage (78.5% maximum efficiency compared with 25%).
- It also requires twice as many output transistors.
- and, it is not very linear cross-over distortion can be significant.
- Class B amplifiers are used in low cost designs or designs where sound quality is not that important.
- Class B amplifiers can be significantly more efficient than class A amplifiers.
- Class B is used most often where economy of design is needed.
- Before the advent of IC amplifiers, class B amplifiers were common in clock radio circuits, Pocket transistor Radio, or other applications.

Ans
3 (b)

Types of Voltage Regulation:-

There are two basic categories of voltage regulation :-

① Line Regulation

② Load Regulation

- The purpose of line regulation is to maintain a nearly constant output voltage when the input voltage varies.
- The purpose of load regulation is to maintain a nearly constant output voltage when the load varies.

Types of Voltage Regulator


① Linear Regulators:

② Switching Regulator:

- Two basic types of linear ~~is~~ Regulator are series regulator and the shunt regulator.
- The series regulator is connected in series with the load and shunt regulator is connected in parallel with load.

Ans

3 (b)

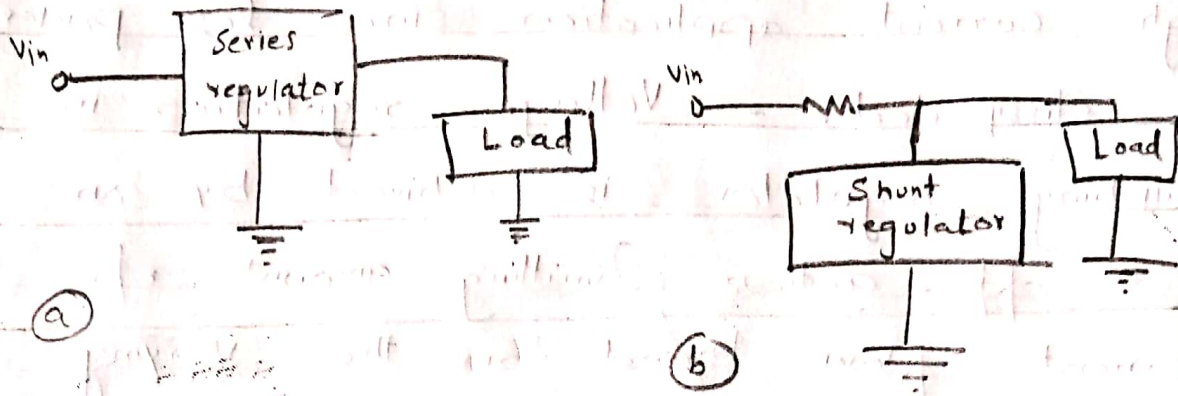

Series Regulator Circuit

- Control element in series with load between input and output. - Output sample circuit senses a change in output voltage. - Error detector compares sample voltage with reference voltage.

Transistor Shunt Regulator:-

- Resistor R_s drops the unregulated voltage depending on current supplied to load R_L .
- Voltage across the load is set by zener diode and transistor base-emitter voltage.
- load current, I_L is larger maintaining the regulated voltage across load.

Switching Regulator:-

- The switching regulator is more efficient than the linear series or shunt type.
- This type of regulator is ideal for

high current application since less power is dissipated. - Voltage regulation in switching regulator is achieved by on and off action limiting amount of current flow based on the varying line and load condition.

In with switching regulators, 90% efficiency can be achieved.

Ans
4




"Flash" ADC:-

Series of comparators, each one compare input to a unique reference voltage.


Comparators output connect to priority encoder circuit produce binary circuit

Working of Flash ADC:-

- As analog input voltage exceed the reference voltage at each comparator, the comparator outputs will sequentially saturate to a high state.
- The priority encoder generates a binary number based on the highest-order active input, ignoring other active inputs.

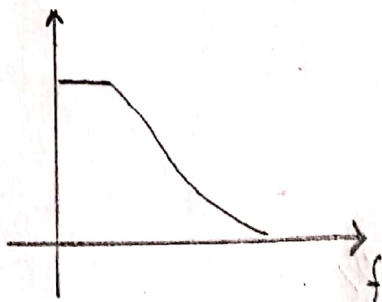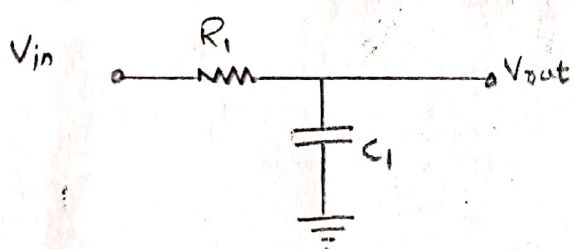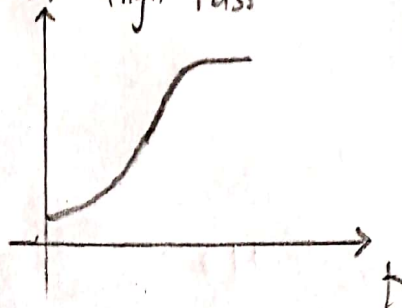$|H(\omega)|$ Low Pass $|H(\omega)|$ High Pass

Passive

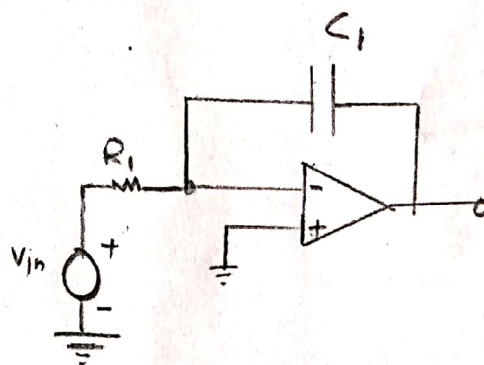

Active

The major difference between low pass and high pass filter is range of frequency which they pass. If we talk about high pass filter so it is a circuit which allows high frequency to pass filter in an electronic circuit which allows frequency to pass through it.

Comparison Chart:-

High Pass filter:-

It is a circuit which allows the frequency above cut off frequency to pass through it.

Circuit Architect :- It consists of capacitor
 u r e followed by resistor.

Significance:- It is significant when distortion due to low frequency signal such as noise is to be removed.

Operating frequency:- Higher than cut off frequency

Applications:- In audio amplifier, low noise amplifier etc.

a) Low Pass filter:-

It is circuit which allow frequency below cutoff frequency to pass through it

It consist of resistor followed by capacitor.

It is significant in removing aliasing effect.

Lower than cutoff frequency

In communication circuit as antialiasing filter.

b) Comparison chart :-

| Basis for comparison:- | Active Filter | Passive Filter: |
|------------------------|--|--|
| Composed of | Active components like opamp, transistor | Passive components like resistor, inductor |
| Cost | High | Comparatively Low |
| Circuit Complexity | More Complex | Less Complex |
| Weight | Low | Comparatively bulkier due to presence of inductors |
| Q. factor | High | Vary Low |
| Sensitivity: | More Sensitive | Less sensitive. |