

(1)

Name \approx Rafiqat Ullah Khan

ID \approx 14107

Question = 01 :-
Part :- (b) :-

Solution :-

i) :- Line Reg = $\frac{0.062}{4.5} \times 100\%$
 $= 1.37\%$

ii) :- Line regulation in $\% / v \Rightarrow$

$$\Rightarrow \frac{0.062}{40} \times 100\%$$
$$4.5$$

$$\Rightarrow 0.034\% / v$$


(2)

Question = 02 :-

Answer :-

Colpitts Oscillator :-

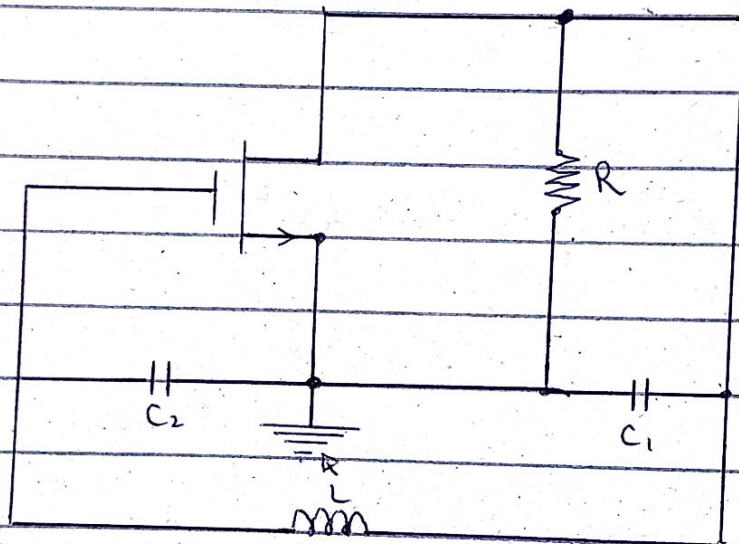• It is a type of Oscillator that uses an LC circuit in the feedback loop



• The feedback network is made up of a pair of tapped capacitor (C_1 and C_2) and an inductor L to produce a feedback necessary for oscillations.

The output voltage is developed across C_1 .


The feedback voltage is developed across C_2 .

$$f_t \approx \frac{1}{2\pi\sqrt{LC_T}} \Rightarrow C_T = \frac{C_1 C_2}{C_1 + C_2}$$

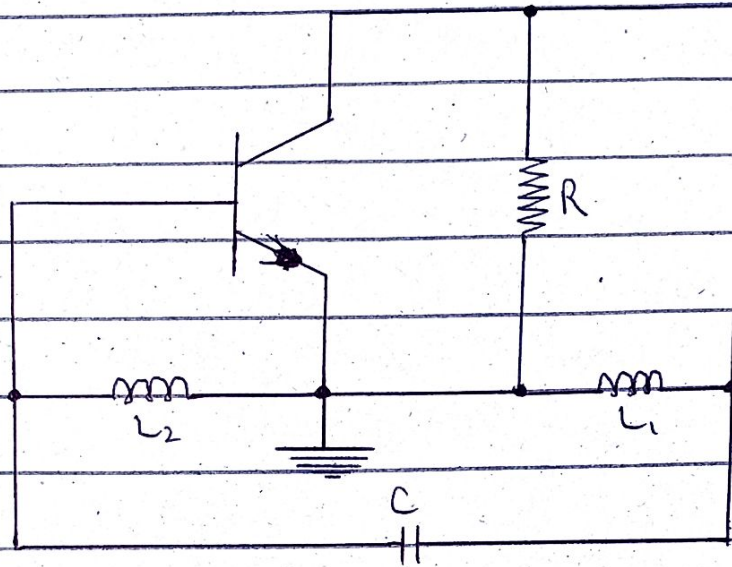(3)

Hartley Oscillator:-

It is almost identical to the Colpitts oscillator



The primary difference is that the feedback network of Hartley oscillator uses tapped inductors (L_1 and L_2) and a single capacitor C .

$$Q > 10$$

$$f_r = \frac{1}{2\pi\sqrt{L_1 C}}$$

$$L_T = L_1 + L_2$$



Question = 3 :-

Part :- (a) :-

Answer :-

Class B amplifier :-

- Opposite A class A both outputs devices are never allowed to be on the same time.
- Each output device is on for exactly one half of a complete sinusoidal signal cycle.
- Its design show high efficiency but poor linearity around the crossover region.
- Its design is restricted to low power application eg:- battery.
- Efficiency:- Peak efficiency of the class B output stage is 78.5% much higher than class A.
- It is used in low cost designs.
- It suffer from bad distortion when the signal level is low.
- Before the advent of IC amplifier class B amplifier were common in clock radio circuits, pocket transistor radios, and others where quality of sound is not critical.

Question :- 3 :-

Part :- (b) :-

Answer :-

Types of voltage regulator :-

There are two types of voltage regulator.

1:- Linear voltage regulator :-

2:- Switching voltage regulator :-

1):- Linear voltage regulators :-

It acts as a voltage divider in a ohmic region. It uses FET. The resistance of voltage regulator varies with load resulting in constant output voltage.

Advantages :-

→ It gives low output ripple voltage.

→ Fast response time to load or line change.

→ Low electromagnetic interference and less noise.

Disadvantages :-

→ It efficiency is low.

→ Requires large space - heatsink is needed.

→ Voltage above the input cannot be increased.

(6):-

ii):- Switching voltage regulator :-

This regulator rapidly switches a series device on and off. The switches duty cycle sets the amount of charge transferred to load. This is controlled by a feedback mechanism similarly to that of a linear regulator. It is efficient because the series element is either fully conducting or switched off because it dissipates almost no power.

Advantages:-

Its ^{switched power} supply are efficient, size and weight. Its also a more complex design which is capable of high power efficiency. It provide outputs, which is greater, less or inverts the input voltage.

Disadvantages:-

- High output ripple voltage.
- Slower transient recovery time.
- EMI produce very noisy output.
- Very expensive.

(7):-

Question = 06.-

Solution:-

Given data:-

$$A_{ol} = 400,000$$

$$A_{om} = 0.6$$

Required:

$$CMRR = ?$$

Solution:-

$$CMRR = \frac{A_{ol}}{A_{om}} \Rightarrow \frac{400,000}{0.6}$$

$$\Rightarrow 666,666.6$$

Expressed in decibels:-

$$CMRR = 20 \log(666,666.6)$$

$$\Rightarrow 116.47 \text{ dB}$$


Questions: 07::

Answer:

Negative feedback:-

→ It is a process where by a portion of output voltage of an amplifier is returned to the input with a phase angle that opposes the input signal.

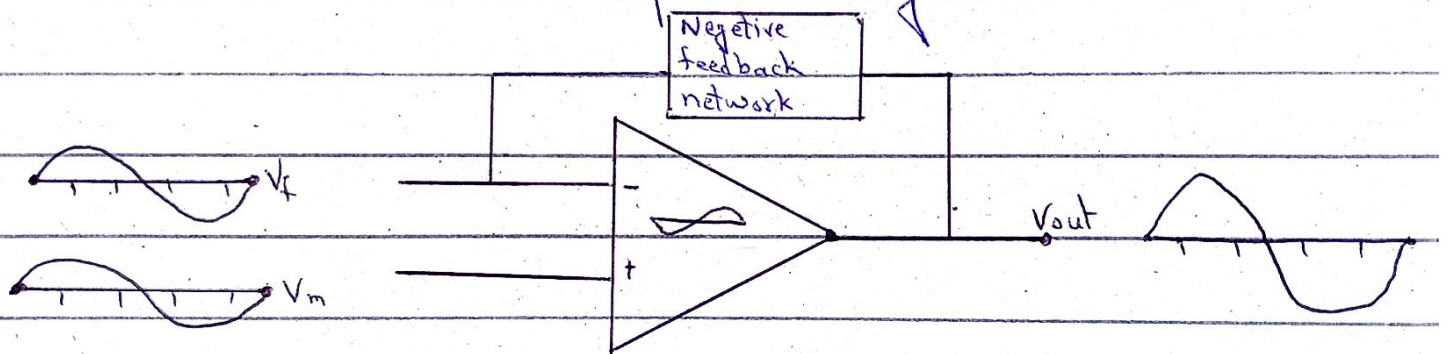→ Inverting (-) inputs effectively makes the feedback signal 180° out of phase with the input signal.



It occurs when some function of the output of a system or mechanism is feedback in a manner that tends to reduce the fluctuations in the output, whether caused by changes in the input or by other disturbance.

(9):-

Question = 05 :-

Part:- A:-

Low Pass Filter	High Pass Filter
→ Used for smoothening image	→ Use for sharpening the image.
→ It attenuates the high frequency	→ It attenuates the low frequency.
→ Low frequency is preserved in it.	→ High frequency is preserved in it.
→ Below cut off frequency is allowed to pass through it.	→ Above cut off frequency is allowed to pass through it.
→ Consist of resistor followed by capacitor.	→ Consist of capacitor followed by resistor.
→ It helps in removal of aliasing effect.	→ It helps in removal of noise
$G(u,v) = H(u,v)$ $F(u,v)$	$H(u,v) = 1 - H'(u,v)$

(10).-

Question = 05 :-

Part :- (B) :-

Active Filter

→ Composed of components like op-amp, transistor etc

→ Cost is high

→ Its circuit is more complex

→ Its weight is low.

→ Q factor is high.

→ External power supply is required

→ It is more sensitive

Passive Filter

→ Composed of component like resistor, inductor etc

→ Its cost is low

→ Less complex than active.

→ Comparatively high.

→ Q factor is very low

→ External power supply is not required

→ It is less sensitive

Question:- 04.-

Answer:-

ADC basic principle:-

→ The basic principle of operation is to use the comparator principle to determine whether or not to turn on a particular bit of the binary number output.

→ It is typical for an ADC to use a digital to analog converter (DAC) to determine one of the input to the comparator.

Flash ADC:-

- Consist of a series of a comparators each one comparing the input signal to a unique reference voltage.

- The comparator outputs connect to the input of a priority encoder circuit, which produce a binary output.

How Flash works:-

- As the analog input voltage exceeds the reference voltage at each comparator output, will sequentially

(12):

Saturate to a high state

- The priority encoder generates a binary number based on the highest-order active input, ignoring all other active inputs.

Flash Advantages:-

- Simplest in term of operational theory.
- Most efficient in term of speed, very fast limited only in term of comparator and gate propagation delays.

Flash disadvantages:-

- Lower resolution
- Expensive
- For each additional output bit, the number of comparators is doubled i.e. for 8 bits, 256 comparators needed

~~~~~



(13):-

Question: 01 :-

Part: (a):

Darlington connection:

→ The main feature is that the composite transistor acts as a single unit with a current gain that is the product of current gain of individual transistor provide high current gain than a single BJT.


→ The connection is made up of using two separate transistor having current gain of  $\beta_1$  and  $\beta_2$ .

So the current gain

$$\beta_D = \beta_1 \beta_2$$

→ If  $\beta_1 = \beta_2 = \beta$

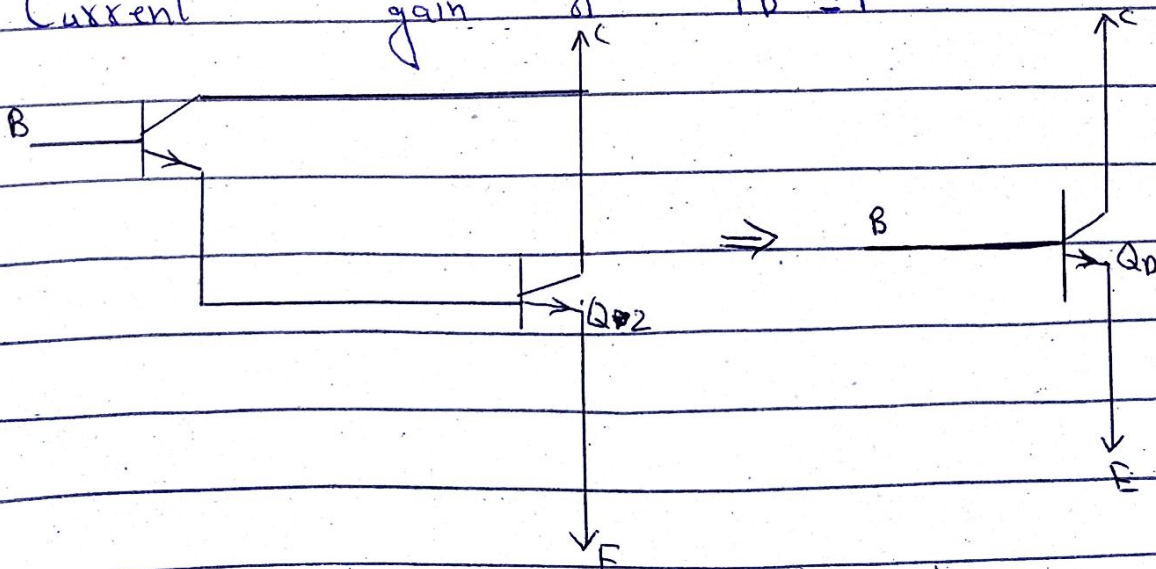The darlington connection provides a current gain of  $\beta_D = \beta^2$



Darlington transistor.

(13):-

→ The small current gain:-  
 $A_i = I_o / I_i$

Since

$$V_{\pi 1} = I_i r_{\pi 1}$$

Therefore

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

Then

$$V_{\pi 2} = (I_i + \beta_1 I_i) r_{\pi 2}$$

The output current is

$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

→ The overall gain is

$$A_i = I_o / I_i \Rightarrow \beta_1 + \beta_2 (1 + \beta_1) \cong \beta_1 \beta_2$$

The overall small signal current gain = The product of individual current gain.

→ The input resistance:-

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + I_i (1 + \beta_1) r_{\pi 2}$$

So, the input resistance is

$$R_i = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$



(15)

The base of  $Q_2$  is connected to the emitter of  $Q_1$  which means that the input resistance to  $Q_2$  is multiplied by factor  $(1 + \beta_1)$  as we saw in circuit with emitter resistor.

$$r_{\pi} = \beta_1 V_T / I_{CQ1} \quad \text{and} \quad I_{CQ1} \cong I_{CQ2} / \beta_2$$

$$r_{\pi 1} = \beta_1 (\beta_2 V_T / I_{CQ2}) = \beta_1 r_{\pi 2}$$

$$R_i = 2 \beta_1 r_{\pi 2}$$

The input resistance tends to be large because of  $\beta$  multiplication.

