

(1)

Date: _____

Mid-Term


MON TUES WED

Name: Mir-Muhammad ID: 15062

Depart: BE (E) Module: 4th Sem

Instructor: Mujtaba Ikhsan

Subject: Electronic Circuit Design

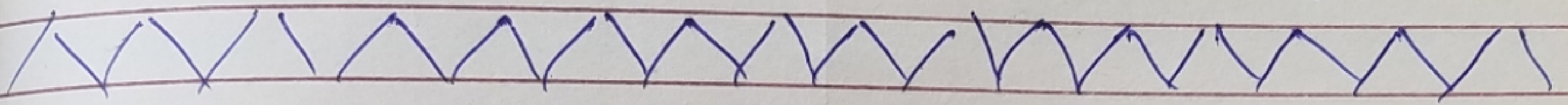


Q No. 1:- Explain drain characteristic curve of D-MOSFET?

Answer:-

D-Type Mosfet:-

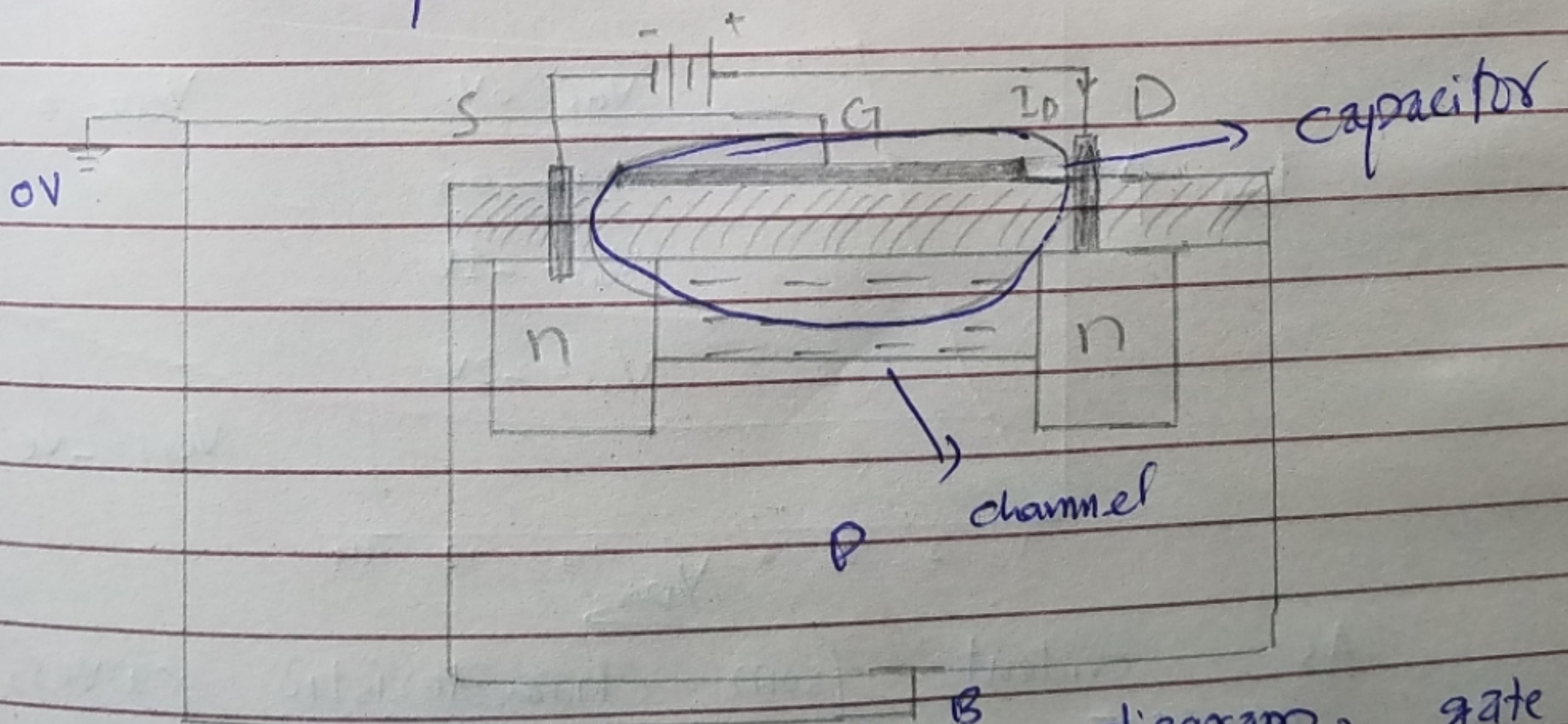
A depletion type mosfet has a channel permanently fabricated at the time of its construction itself.




As shown in above diagram, gate to - source voltage is set to zero by shorting gate and drain and source. V_{ps} is applied between

Since $V_{GS} = 0$, no change in capacitor and no change in channel.

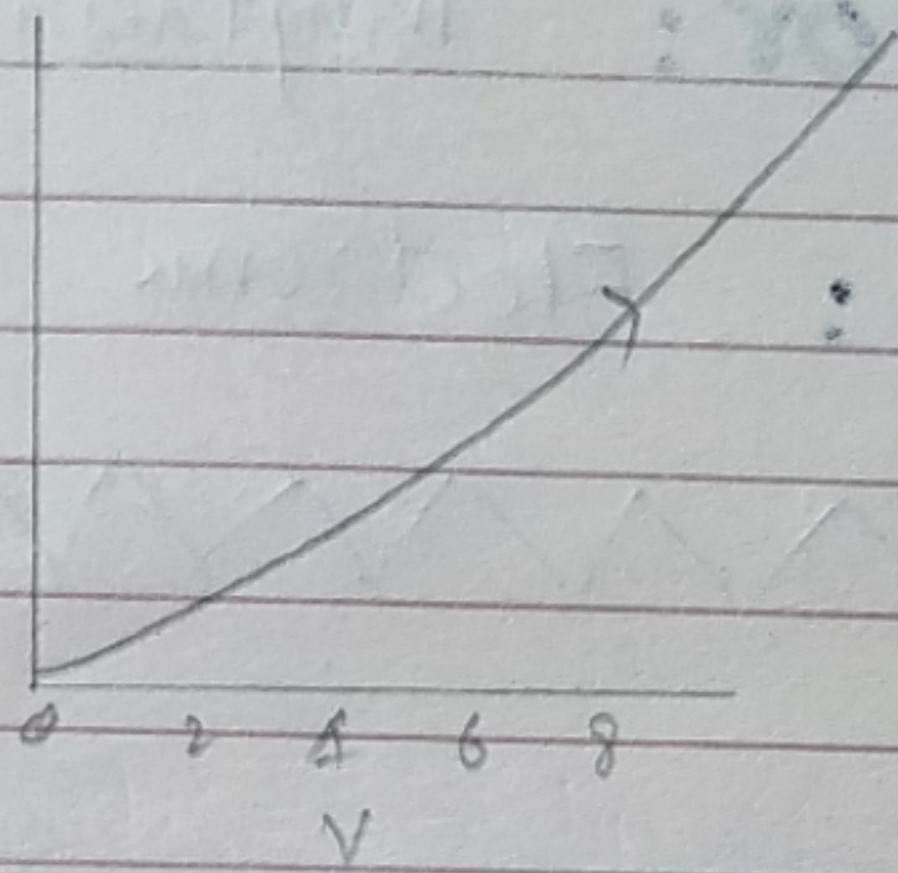Let's set $V_{GS} = -1$. Capacitor charges and channel should be positive.



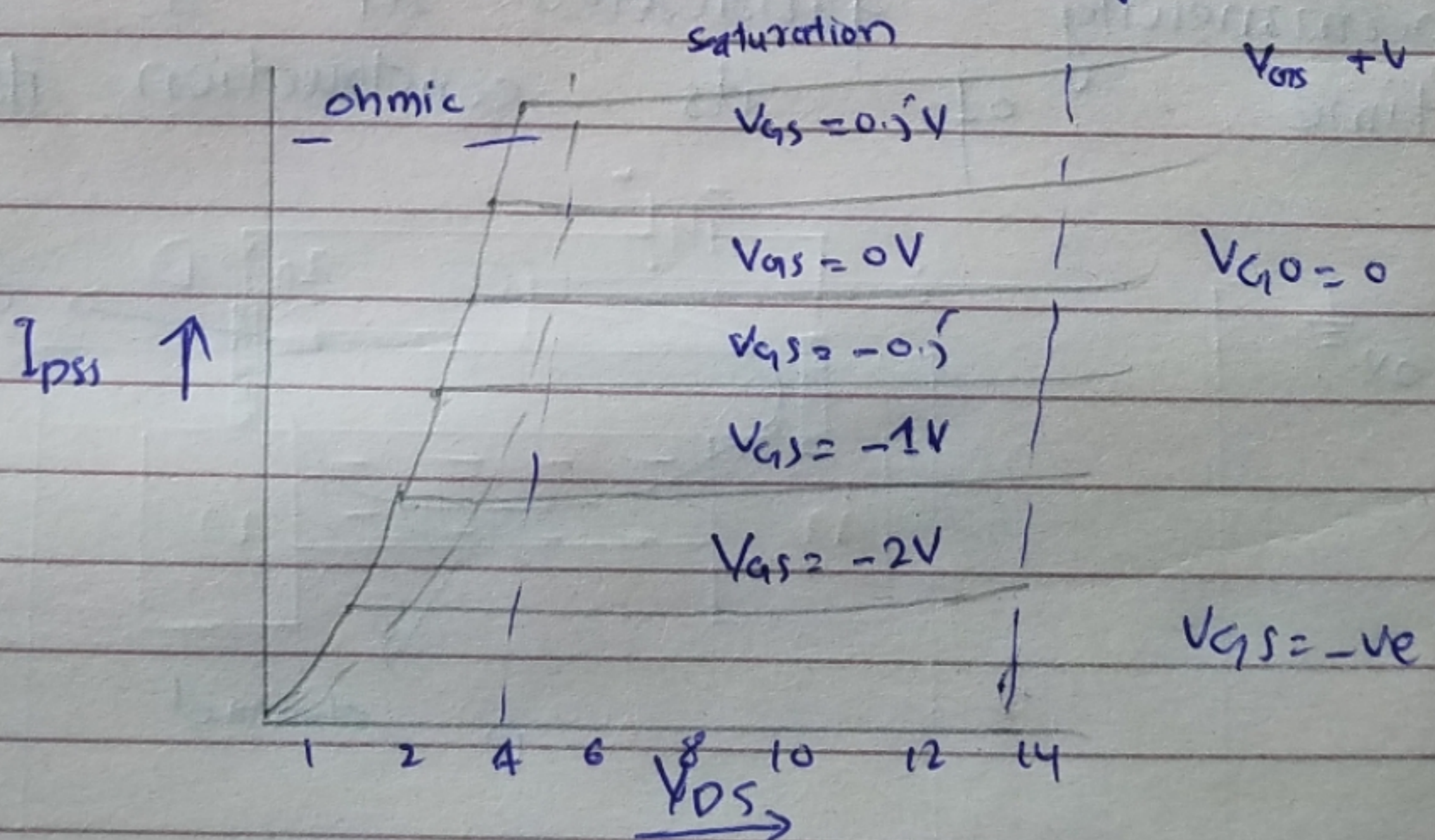Depending upon the magnitude of V_{GS} , electrons and holes recombine will reduce the number of free electrons available for conduction. As we keep increasing the negative V_{GS} , I_{DS} keep decreasing and finally become zero at particular V_{GS} , which is known as pinch-off voltage.



As evident from characteristic curves, a MOSFET has three operating regions,

1) Cut-off — In cut-off region, the circuit behaves like an open circuit.

2) Ohmic / Linear region \rightarrow

increases with increase in V_{DS} , I_{DS} in ohmic.


3) Saturation region \rightarrow

constant in spite of increase in V_{DS} . I_{DS} is constant in this.

Q No.1 Part (b)

Sketch hybrid model and write equation for transistor in common emitter configuration.

Ans:- Transistor Hybrid Model:

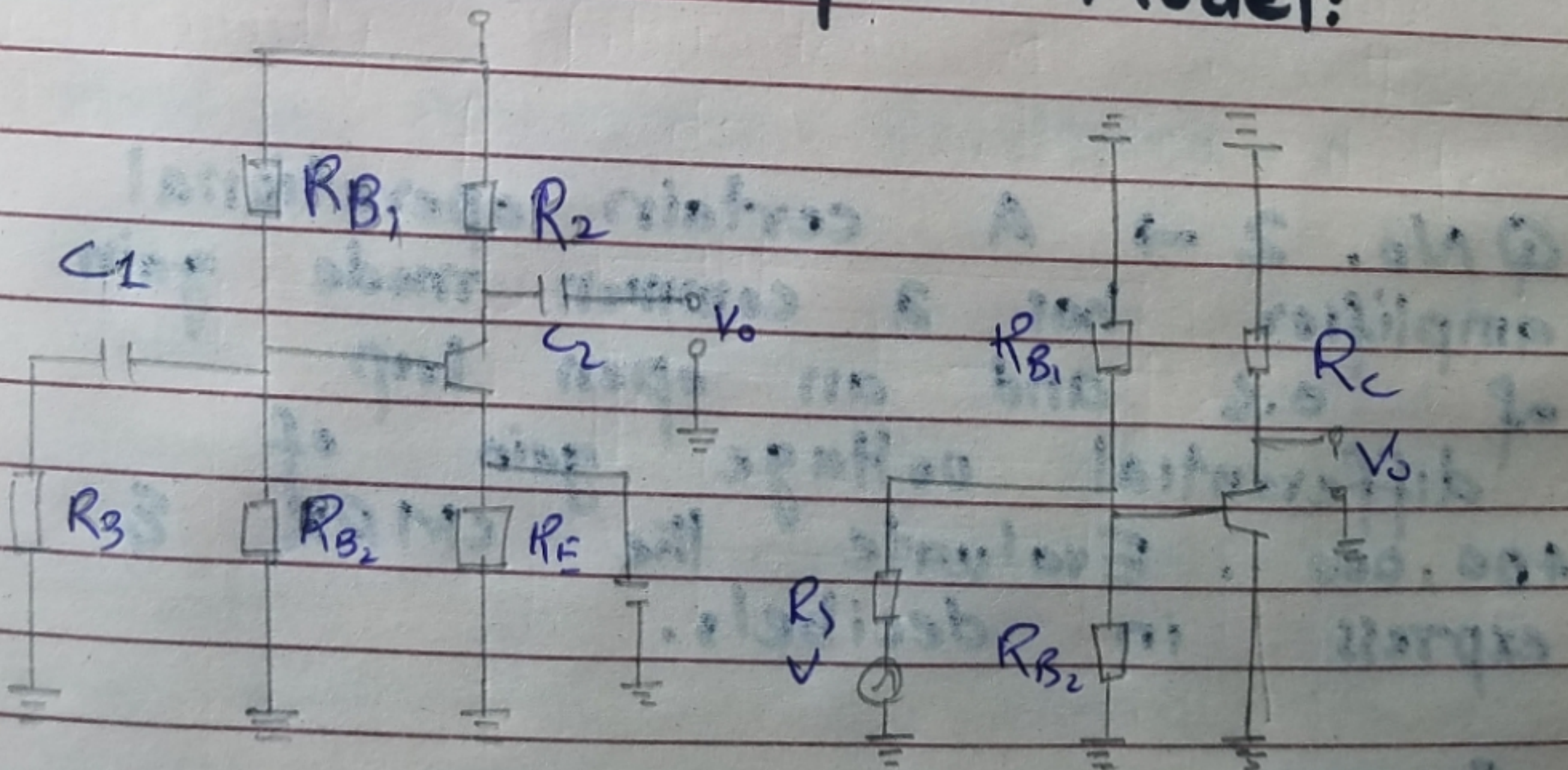

Equation for transistor C_E :-

In common emitter transistor configuration, the input signal is applied between the base and emitter terminals of transistor and output appears between

the collector and emitter terminals.
The input voltage and output current are given belows

$$V_{be} = h_{ie} \cdot i_b + h_{re} \cdot V_c$$

$$i_e = h_{fe} \cdot i_b + h_{oe} \cdot V_c$$

Current Gain →

$$A_i = - (h_{fe} / (1 + h_{oe} \cdot r_L))$$

Input Resistance →

$$R_i = h_{ie} + h_{re} \cdot A_i \cdot r_L = h_{ie} - (h_{re} \cdot h_{fe}) / (h_{oe} + 1/r_L)$$

Q No. 2 → A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. Evaluate the CMRR & express in decibels.

Answer:

Given:-

Open differential voltage = 400,000
common mode gain = 0.6

Req:

CMRR = ?

Solution :-

Using formula as

$$CMRR = \frac{V_{gain}}{\text{Common gain}}$$

$$= \frac{400,000}{0.6}$$

$$CMRR = 666666.66$$

In decibel

$$CMRR = 116.478 \text{ decibels}$$

Q No. 3 Explain the concept behind negative feedback in operational amp.

Ans :- Negative feedback :-

feedback is the process of "feeding back" a fraction of the output signal back to the input, but to make the feedback negative or "inverting input" terminals of the op-amp using an external feedback resistor called R_f . This feedback connection between the output and inverting input terminal forces the differential input voltage towards zero.

Concept :-

This effect produces

A closed loop circuit to the amplifier resulting in the gain of the amplifier now being called its closed loop gain. An inverting amplifier uses negative feedback to accurately control the overall gain of the amplifier, but at a cost in the reduction of the gain.

Q No. 3 : State the following statement as True or False

"

The output of a summing amplifier is positive."

Ans:- Note that when the summing point is connected to inverting input of the op-amp the circuit will produce the negative sum of any number of input voltages. Likewise, when the summing point is connected to the non-inverting input of the op-amp, it will produce the positive sum of the input voltages.

So this statement is
False.

Thank you.