

COURSE TITLE :- ENA

MODULE :- 4<sup>th</sup>


INSTRUCTOR :- SIR SHAHRAYAR

:- STUDENT DETAILS :-

NAME :- NAVEED ALAM

STUDENT ID NO. :- 14965

STUDENT SIGNATURE :-

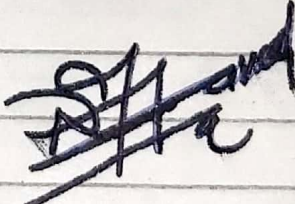

Q.No.1:- The switch in fig.1 has been in position A for a long time. At  $t = 0$  the switch moves to B. Determine  $V(t)$  for  $t > 0$  and calculate its value at  $t = 2s$  and  $8s$ .

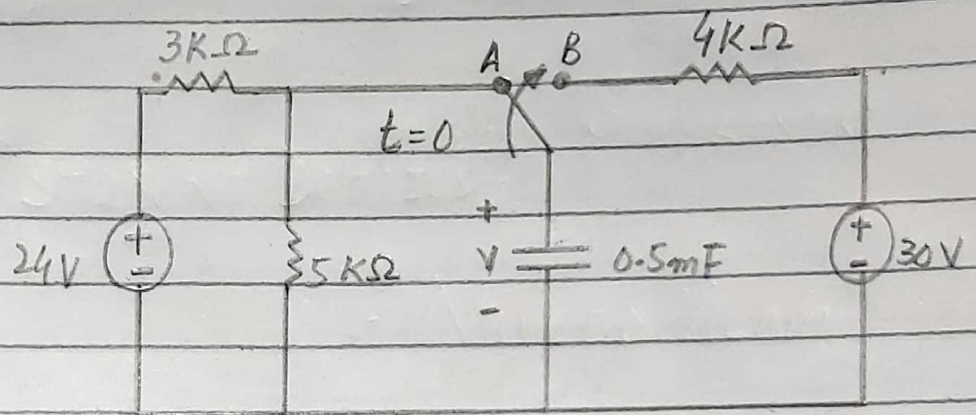


Figure 1

Solution:- For  $t < 0$  the switch is at position A. Capacitor act like an open circuit to DC. But  $V$  is same as the voltage across  $5k\Omega$  resistor. Hence the voltage across the capacitor just before  $t=0$  is obtained by voltage division as.

$$V(0) = \frac{5}{5+3} (24)$$

$$V(0) = \frac{5}{8} (24)$$

$$V(0) = 15 \text{ V}$$



Using the fact that capacitor voltage cannot change instantaneously -

$$V(0) = V(0^-) = V(0^+) = 15 \text{ V}$$

$t > 0$  the switch is position B. Thevenin resistance connect to the capacitor

$R_{Th} = 4 \text{ k}\Omega$  the time constant is

$$\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\tau = 2 \text{ s}$$

Since the capacitor act like an open circuit to DC at steady state

$$V(\infty) = 30 \text{ V}$$

Thus

$$V(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$$

$$V(t) = 30 + (15 - 30)e^{-t/2}$$

$$V(t) = 30 + (-15)e^{-t/2}$$

$$V(t) = (30 - 15e^{-0.5t}) \text{ V}$$

At

$$t = 2, \quad V(2) = 30 - 15e^{-2/2}$$

$$V(2) = 30 - 15e^{-1}$$

$$V(2) = 24.48 \text{ V}$$

At

$$t = 8, \quad V(8) = 30 - 15e^{-8/2}$$

$$V(8) = 30 - 15e^{-4}$$


$$V(8) = 29.72 \text{ V}$$



QNO.

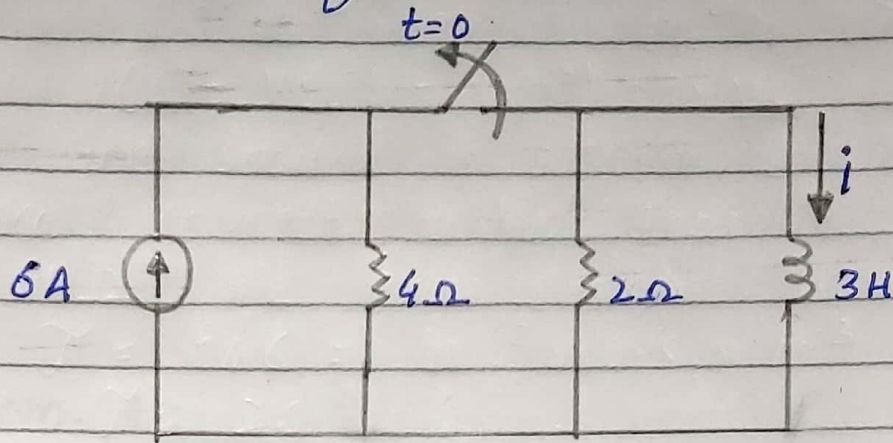2:-

Determine the inductor current for both  $t > 0$  and  $t < 0$  for the circuit in Fig. 2-



Sol.:-

For

2

$t < 0$ , the switch is closed and inductor act as short circuit. Therefore inductor current  $i = 6A$ .

For

$t > 0$ , the switch is opened and time constant

$$\tau = \frac{L}{R}$$

$$\tau = \frac{3}{2}$$

Now the inductor current  $i(t) = \frac{-t}{\tau}$

$$i(t) = 6e^{-t/3/2}$$

$$i(t) = 6e^{-\frac{2t}{3}} u(t) A.$$



Q No. 3:- A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Find the response when  $L = 0.5H$ ,  $R = 4\Omega$  and  $C = 0.2F$ . Let  $i(0) = 1$ ,  $di(0)/dt = 0$ .

Sol:- **STEP NO. 1:-**

The step response of branch voltage of the given RLC circuit is describe by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by  $L$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10}{L}$$

Right hand side of equation multiply by  $\frac{C}{C}$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10C}{LC}$$

And  $C = 0.2 F$  thus

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{2}{LC}$$

Substitute

$$\frac{d^2 i}{dt^2} + \frac{8di}{dt} + 10i = 20 \dots (1)$$

G- Equation for source-free series RLC circuit is given by-

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{I_s}{LC} \dots (2).$$

STEP NO. 2 :-

Compare 1 and 2

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \rightarrow (4)$$

$$\frac{I_s}{LC} = 20 \rightarrow (5)$$

STEP NO. 3 :-

From (3)  $\alpha$  is given by

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/s} \rightarrow (6)$$

Natural frequency  $\omega_0$  is given by

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

From (4)

$$\omega_0 = \sqrt{10} \text{ rad/s} \rightarrow (7)$$



From (6) and (7)

$$\therefore \alpha > \omega_0$$

$\therefore$  The circuit is overdamped

Root of characteristic eqn are given

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -4 + \sqrt{4^2 - 10^2}$$

$$s_1 = -4 + \sqrt{6} \text{ rad/s}$$

and,

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -4 - \sqrt{4^2 - 10^2}$$

$$s_2 = -4 - \sqrt{6} \text{ rad/s}$$

As from (5) steady state current is given by

$$I_s = 20 \times LC$$

$$20 \times 0.5 \times 0.2 = 2A \rightarrow (8)$$

STEP NO. 4:-

Current for overdamped case is given by  $i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$

Substitute  $t = 0,$

$$i(0) = I_s + A_1 + A_2$$

Substitute,

$$1 = 2 + A_1 + A_2$$

Thus

$$A_1 + A_2 = -1 \rightarrow (10)$$

STEP NO. 5:-

From (9) find  $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 S_1 + A_2 S_2$$

Substitute the value

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0 \rightarrow (11)$$

Solve (10) and (11) simultaneously

$$A_1 = -1.316$$

$$A_2 = 0.316$$

STEP NO. 6:-

$$i(t) = 2 - 1.316e^{(-4 + \sqrt{6})t} + 0.316e^{(-4 - \sqrt{6})t}$$




Q No.

4 :-

A Series RLC circuit has  $R = 100 \Omega$ ,  $L = 240 \text{ H}$  and  $C = 20 \text{ mF}$ . If the input voltage is  $V(t) = 10 \cos 2t$ , find the current flowing through the circuit.

Solution

4 :-

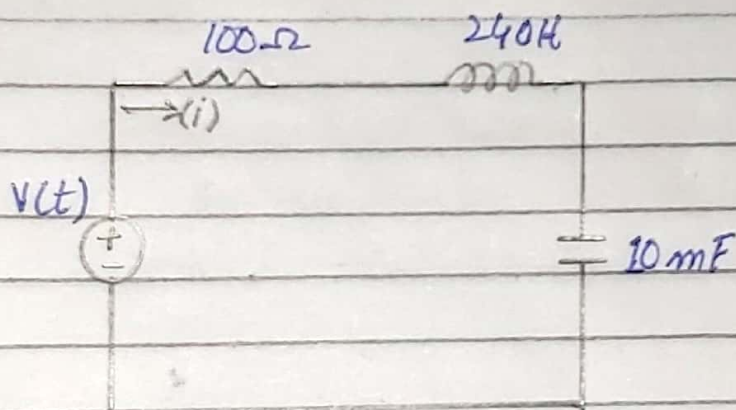

Consider the following voltage is applied the series RLC circuit -

$$V(t) = 10 \cos 2t \text{ V}$$

Here

$$\text{Amplitude } V_m = 10 \text{ V}$$

$$\text{Angular frequency } \omega = 2 \text{ rad/s}$$

$$\text{Phase Angle } \phi = 0^\circ$$

So phase for voltage,  $V(t)$ .

$$V(t) = 10 \angle 0^\circ \text{ V}$$

Inductive Reactance of the circuit.

$$X_L = \omega L$$

$$\omega = 2 \text{ rad/s}, L = 240 \text{ H}$$

$$X_L = (2 \text{ rad/s})(240 \text{ H})$$

$$X_L = (480 \Omega)$$

Now for Capacitive reactance

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2 \text{ rad/s}, \quad C = 10 \text{ mF}$$

$$X_C = \frac{1}{2(10 \times 10^{-3})}$$

$$X_C = \frac{1}{2(10^{-3})}$$

$$X_C = \frac{1}{2(10^{-2})}$$

$$X_C = \frac{1 \times 10^2}{2} = \frac{100}{2} = 50$$

$$X_C = 50 \Omega$$

Now for impedance of the circuit -

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, \quad X_L = 480 \Omega, \quad X_C = 50 \Omega$$

$$Z = (100 + 480 - 50)$$

$$Z = (100 + j430) \Omega$$

Represent the impedance,  $Z$  is phasor  
from



$$Z = (100 + j430) \Omega$$

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left( \frac{430}{100} \right)$$

$$Z = \sqrt{10000 + 184900} \angle \tan^{-1}(4.3)$$

$$Z = \sqrt{194900} \angle \tan^{-1}(4.3)$$

$$Z = 441.47 \angle 76.90^\circ \Omega$$

Now the current flowing "i".

$$i = \frac{V(t)}{Z}$$

$$V(t) = 10 \angle 0, Z = 441.47 \angle 76.9^\circ$$

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.9^\circ \Omega}$$

$$i = \frac{10}{441.47} \angle [0 - 76.9] \text{ A}$$


$$i = 22.6 \times 10^{-3} \angle -76.9^\circ \text{ A}$$

$$i = 22.6 \angle -76.9^\circ \text{ mA}$$

So the General expression for current "i".

$$i = 22.6 \cos(2t - 76.9^\circ) \text{ mA}$$

Q No. Find  $v(t)$  and  $i(t)$  in the circuit shown  
 5:- in figure 3.

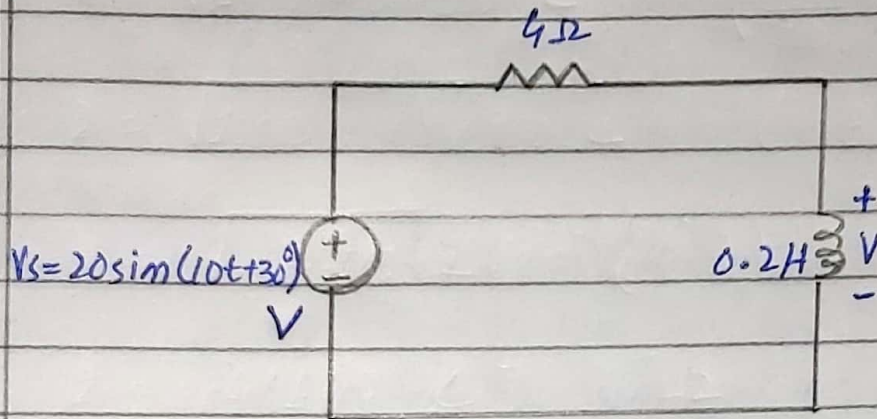

Solution 5:-  $v_s = 20 \sin(10t + 30^\circ)$  V,  $R = 4\Omega$ ,  $L = 0.2H$ .

$$v_s = 20 \sin(10t + 30^\circ)$$

$$v_s = 20 \cos(10t + 30^\circ - 90^\circ)$$

$$v_s = 20 \cos(10t - 60^\circ)$$

$$v_s = 20 \angle -60^\circ$$

$$\omega = 10 \text{ rad/sec}$$

$$X_L = i\omega L$$

$$0.2H = i \times 10 \times 0.2$$

Now

$$Z = 4 + i2\Omega$$

$$i = \frac{20 \angle -60^\circ}{4 + i2}$$

$$I = \frac{20 \angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$



$$I = \frac{20 \angle -60^\circ}{4.72 \angle 26.57^\circ}$$

$$I = 4.472 \angle -86.57^\circ$$

Now

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

As

$$V = j_2 \times (4.47 \angle -86.57^\circ)$$

$$V = j_2 \times (0.2675 - j4.464)$$

$$V = 8.92 + j0.53512$$

from Rectangular to polar form

$$V = \sqrt{(8.926)^2 + (0.53512)^2} \angle \tan^{-1}\left(\frac{0.5312}{8.928}\right)$$

$$V = 8.944 \angle 3.4^\circ$$

Now

$$v(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$

