

Electronic device and circuit

Ali darrish Kayani

~~15243~~ 15243

Dr. sharyar

Summer

$Q = 4 :-$

For a transistor to act a "switch" you need to join each of the following condition on the left "ON" or "OFF" state.

Transistor Fully ON.

Transistor Fully OFF.

Input and base are at 0V

Collector current $I_C = 0$.

$V_{CE} = V_{CC}$

BE junction is reverse bias.

BC junction is Forward bias.


Maximum of saturation current I_C flows.

BE junction is Forward bias.

BC junction is Forward bias.

$V_{CE} = 0V$


BE junction is less than 0.7V

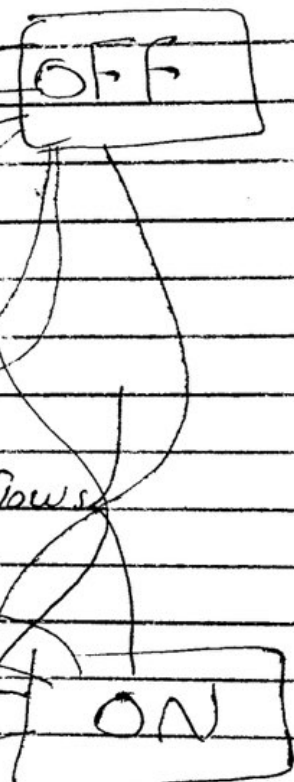

Q1:- Part (a)

Find the data Sheet

Sol:-

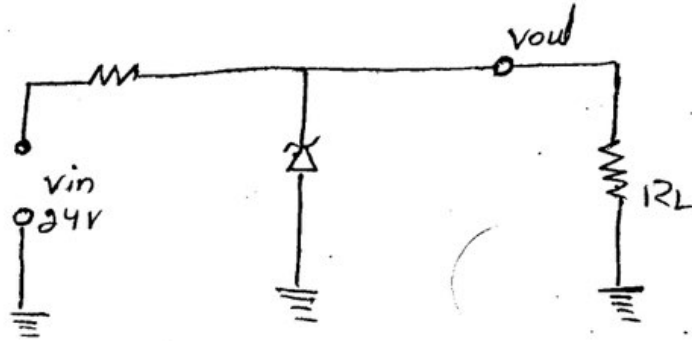

From the datasheet IN4747A

$$V_Z = 15 \quad a) \quad \bar{I}_Z = 12.5 \quad \text{and} \quad Z_Z = 22 \Omega$$

$$\bar{I}_{ZK} = 0.25$$

(a) For \bar{I}_{ZK} :-

$$v_{out} = V_Z - O\bar{I}_Z Z_Z$$

$$= 15 - (\bar{I}_Z - \bar{I}_{ZK}) Z_Z$$

$$= 15 - (12.25 \text{ mA}) (22 \Omega)$$

$$= 15 \text{ V} - (0.01225) (22)$$

$$= 15 \text{ V} - 0.2695$$

$$= 14.7305 \text{ V}$$

Page = 3

Calculating Zener Max Current the maximum Power dissipation is 1W

$$\bar{I}_{ZM} = \frac{P_{o(max)}}{V_Z} = \frac{1W}{15} = 0.066667A$$

$$\bar{I}_{ZM} = 66.7mA$$

For \bar{I}_{ZM} :

$$\begin{aligned}v_{out} &= V_Z + \Delta I_Z Z_Z \\&= 15 + \Delta I_Z Z_Z \\&= 15V + (\bar{I}_{ZM} - \bar{I}_Z) Z_Z \\&= 15V + (54.2mA) (22\Omega) \\&= 15V + (0.0542) (22) \\&= 16.1924V\end{aligned}$$

Part B: - calculate value of R For Max zener current that occurs when there is no load


$$R = \frac{V_{in} - v_{out}}{\bar{I}_{ZM}}$$

Page 4


$$I_{ZM} = \frac{24V - 16.1924V}{66.7mA}$$

$$= 116.5313$$

$$R_s = 120\Omega$$

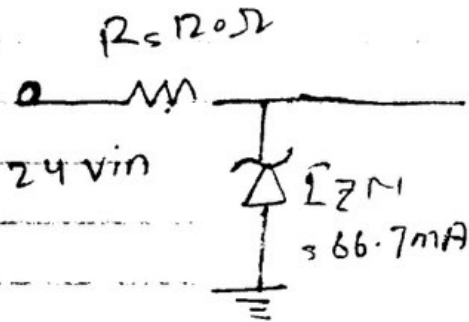

a)

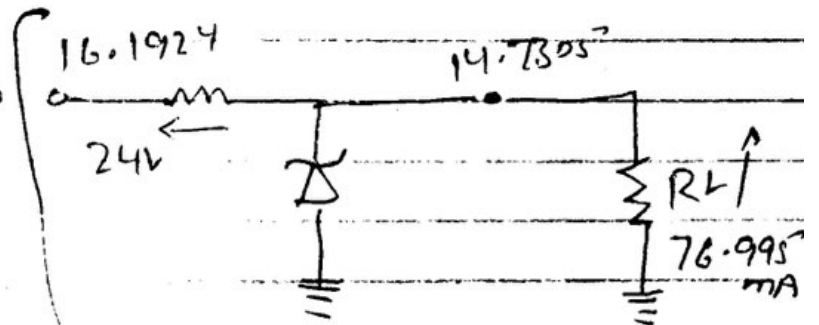

b)

Page 5

Part C

For the minimum level resistance

(maximum load current) the Zener current is ($I_{ZK} = 0.25 \text{ mA}$)

$$I_T = \frac{V_{in} - V_{out}}{R} = \frac{24 - 14.7305}{120 \Omega}$$

$$I_T = 0.077245$$

$$I_T = 77.245 \text{ mA}$$

$$I_L = I_T - I_{ZK}$$

$$= 77.245 - 0.25 \text{ mA}$$

$$I_L = 76.995 \text{ mA}$$


$$R_L(\text{min}) = \frac{V_{out}}{I_L} = \frac{14.7305}{76.995 \text{ mA}} = \frac{14.7305}{0.076995}$$

$$= 191.317618 \Omega$$

$$R_L(\text{min}) = 192 \Omega$$

Page 56

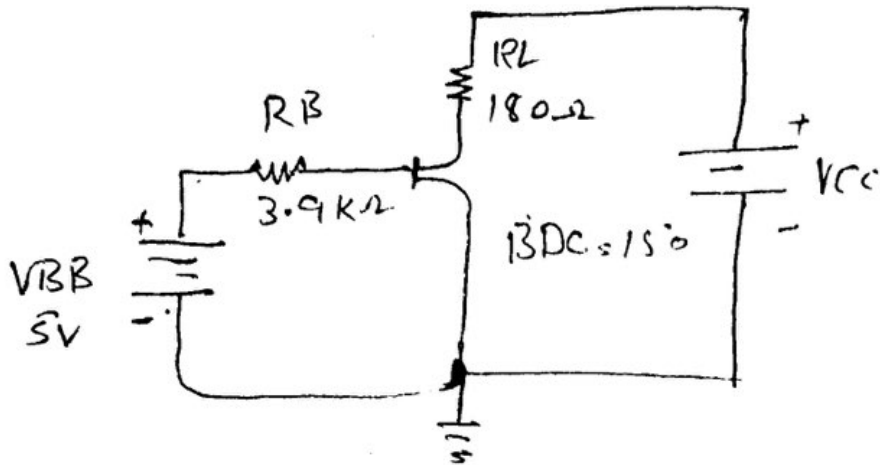Qs 2 :- Determine \bar{I}_B , \bar{I}_C , \bar{I}_E , V_{BC} , V_{CE} and V_{CB} in the circuit shown in fig 2



Sol :-

$$\Rightarrow V_{BE} = 0.7\text{ V}$$

$$\Rightarrow \bar{I}_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5\text{ V} - 0.7\text{ V}}{3.9\text{ k}\Omega} = \boxed{1102\ \mu\text{A}}$$

$$\Rightarrow \bar{I}_C = \beta_{DC} \cdot \bar{I}_B \Rightarrow (150) (1102\ \mu\text{A}) = \boxed{165.3\ \text{mA}}$$

$$\Rightarrow \bar{I}_E = \bar{I}_C + \bar{I}_B = 165.3\ \text{mA} + 1102\ \mu\text{A} = \boxed{166.4\ \text{mA}}$$

Solve for V_{CE} & V_{CB}

Page 57

$$V_{CE} = V_{CC} - I_C R_C = 15V - (165.3 \text{ mA})(180 \Omega)$$

$$= 15V - 29.7V = \boxed{-14.7V}$$

$$V_{CB} = V_{CE} - V_{BE} \Rightarrow -14.7V - 0.7V$$


$$= \boxed{-15.4V}$$

Page 8

Q.6 For the transistor circuit given in Fig 3 calculate the following.

a) What is V_{CE} when $V_{in} = 0V$?

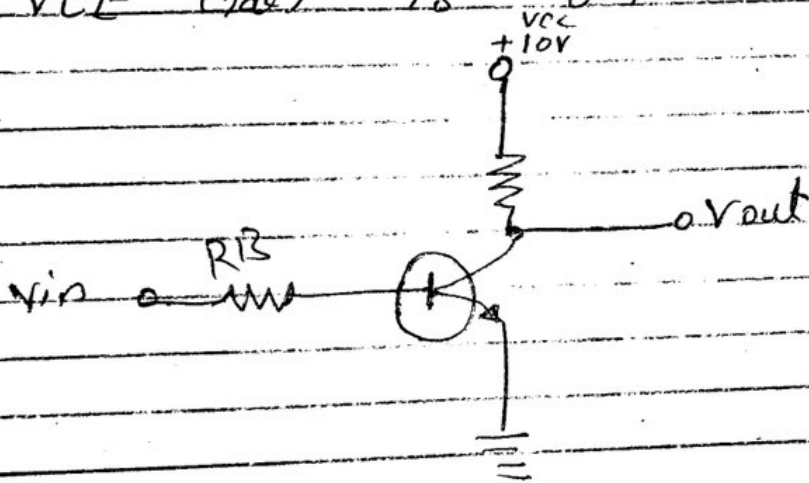b) Determine the maximum value of I_B is required to saturate this transistor if β_{DC} is 125 and $V_{CE(sat)}$ is $0.4V$.



Solution:-

Part (a) :-


$V_{CE} = ?$ $V_{in} = 0V$

When $V_{in} = 0V$, so transistor is in cut off $0A$ and $V_{CE} = V_{CC} = 10V$.


Page = 9

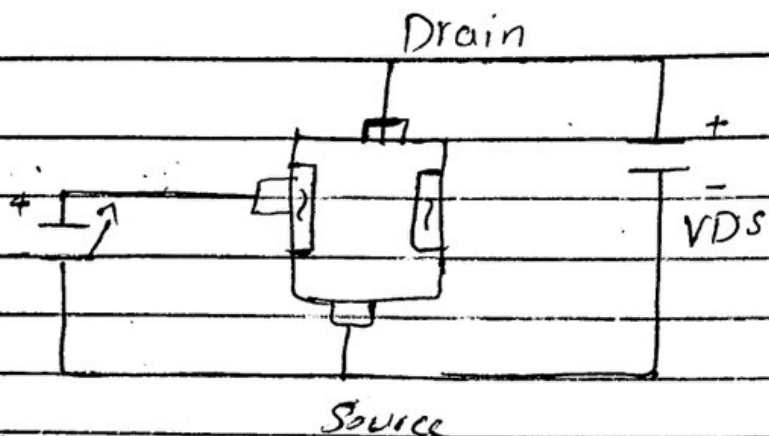Q.5-


JFET is a type of junction field effect transistor which is voltage controlled device as differ from BJT which is current controlled.



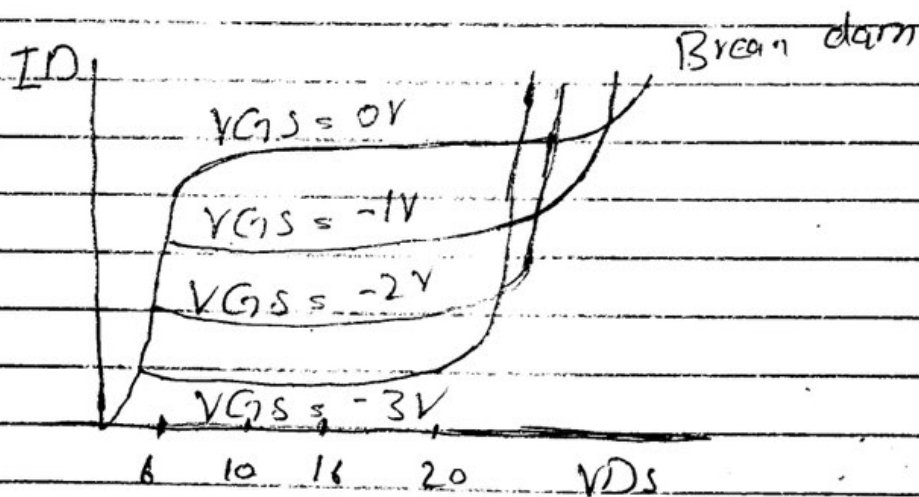Actually in FET the drain to source current is controlled by the width of the channel the electric field is produced by the gate to source voltage




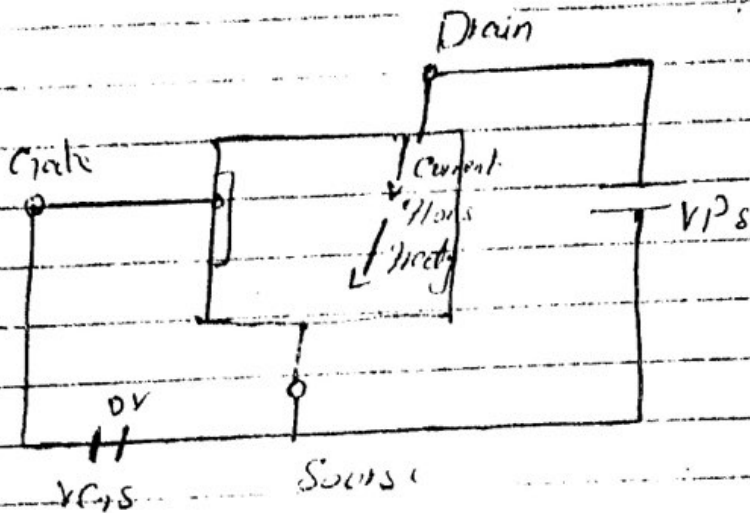So if we see to the graph with the zero voltage applied to the gate the current flows freely



The channels are wider and Drain current moves freely if we move V_{GS} to negative value the channel width start to decrease and current cannot move

Page 5 12

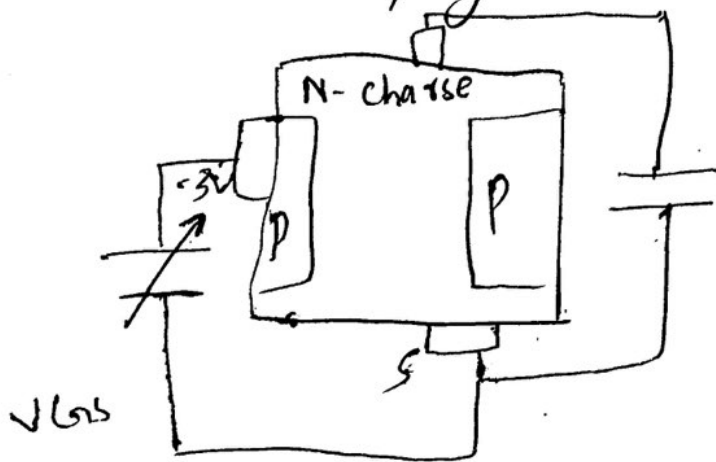


So V_{GS} is more negative
So no current flows and
this effect is called pinch
off region no current or
less current flows

Q38-

for Using BJT as an amplifier

We need to set them in Active region because BJT working as an amplifier when use is active.

- | | | |
|--------|------------|-------------|
| 1) F.B | Active | Amplifier |
| 2) FB | saturation | no switch |
| 3) R.B | Cut off | rarely used |
| 4) R.B | Inverted | BJT |

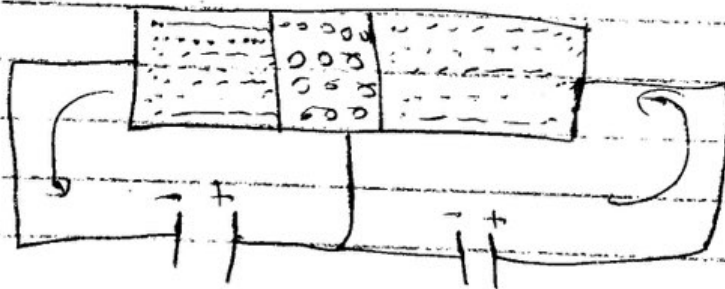

The diagram shows the basic configuration using BJT in active region.