
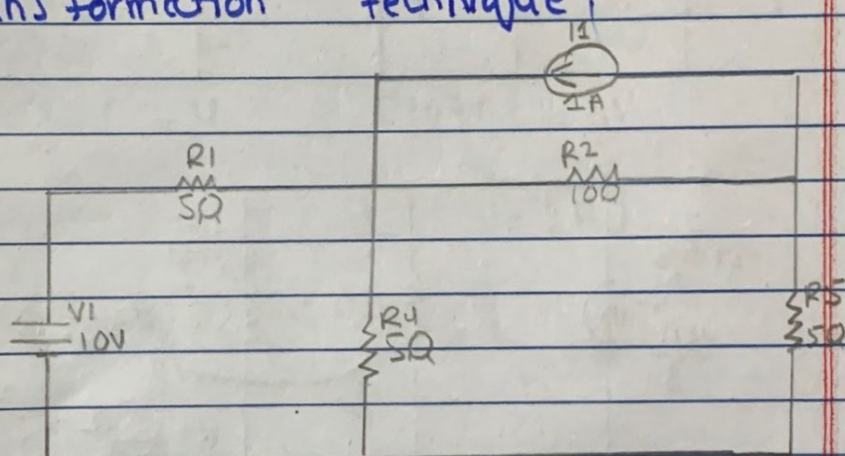


Name Waqas Bangash
 Assignment Linear Circuit Analysis
 ID 16323
 Summer Final Term




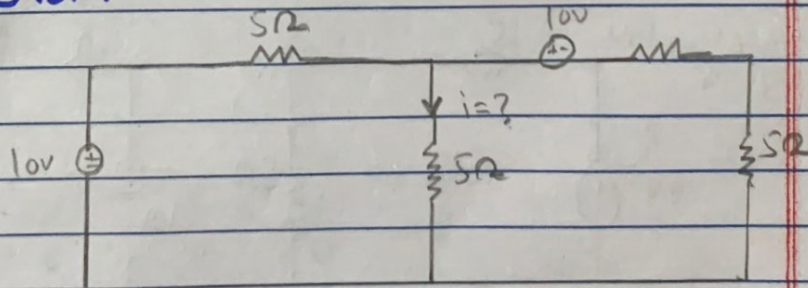
Q3 Find the current through the central $5\ \Omega$ resistor using source transformation technique.



Solution:




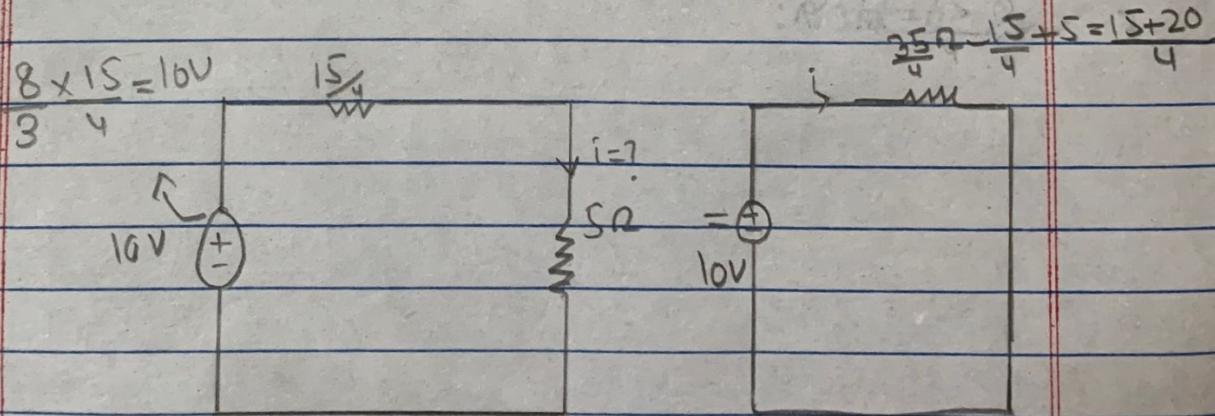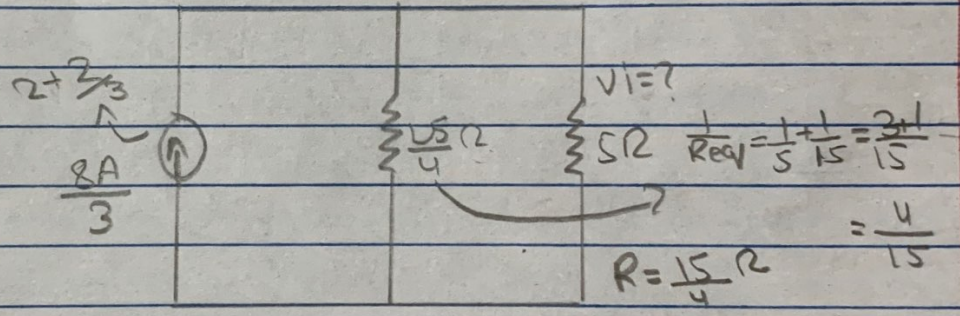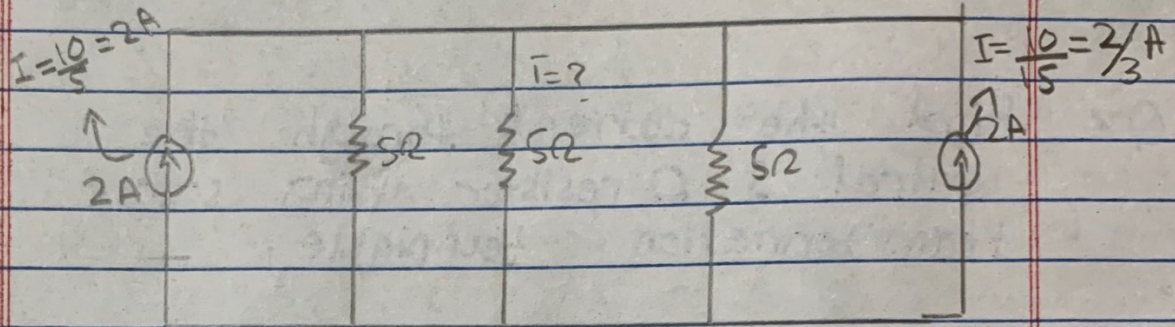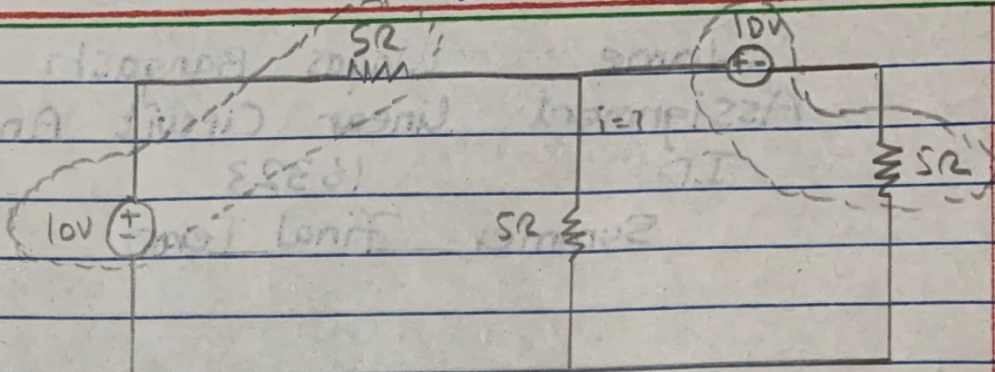Note that the +ve terminal of the 10V source is placed to the left because the current source ~~was~~ arrow was pointing to the left.



$$i = \frac{10}{\frac{35}{4}} = \frac{10 \times 4}{35} = \frac{8A}{7}$$

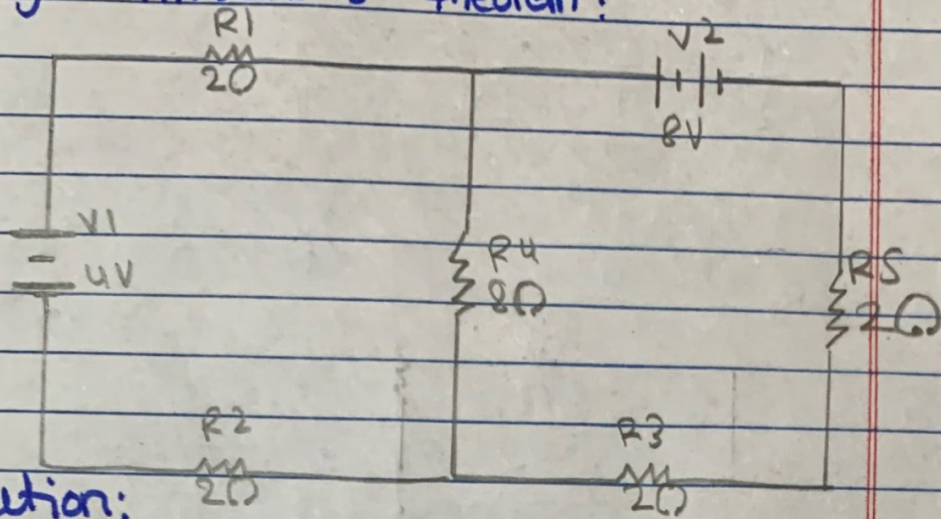Q2 Find the current in 8Ω resistor using Thevenin's theorem:



Solution:

$$V_{\text{TOTAL}} = 4$$

$$R_{\text{total}} = 8\Omega$$

$$I = \frac{V}{R} \quad (\because V = IR)$$

$$I = \frac{4}{8} = 0.5A$$

$$V_1 = 1V$$

$$V_2 = 1V$$

$$V_3 = 1V$$

$$V_4 = 1V$$

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{4}$$


$$\frac{4+1}{4} = \frac{5}{4} = \frac{4}{5}$$

$$V_{\text{th}} = 6V$$

$$R_{Th} = 2 \Omega$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$
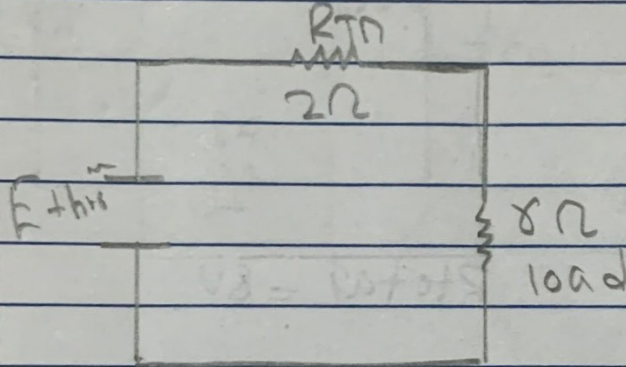
$$\frac{1}{R} = \frac{1+1}{4} = \frac{2}{4} = \frac{1}{2} \Rightarrow R = 2$$



$$V = IR$$


$$I_D = \frac{V}{R} = \frac{6}{10} = 0.6 A$$

$$I = 0.6 A$$

Question (4) Part (a)

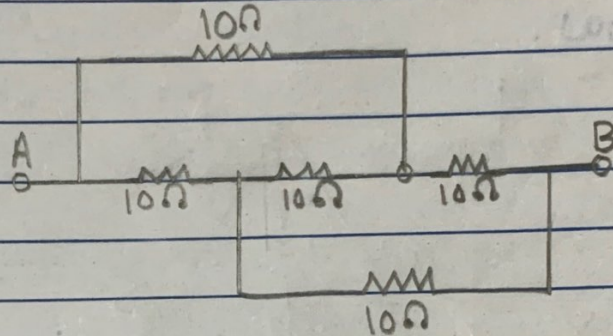
part (a)

calculate the resistance between terminal A and B for the circuit show below:




$A = VA$

$B = VB$

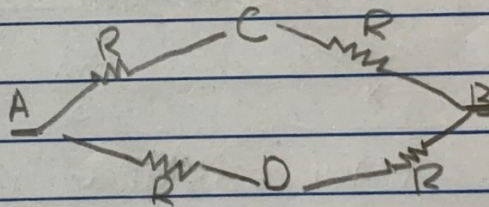

all have same value

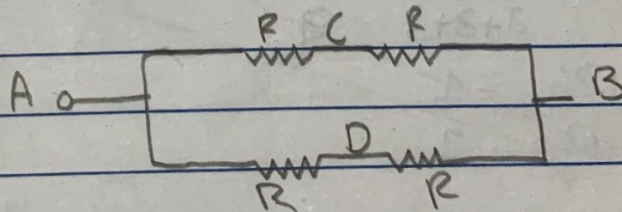


$$R_{eq} = \frac{2R \times 2R}{2R + 2R} \Rightarrow \frac{2(10) \times 2(10)}{2(10) + 2(10)}$$

$R_{eq} = R$

Question (4)

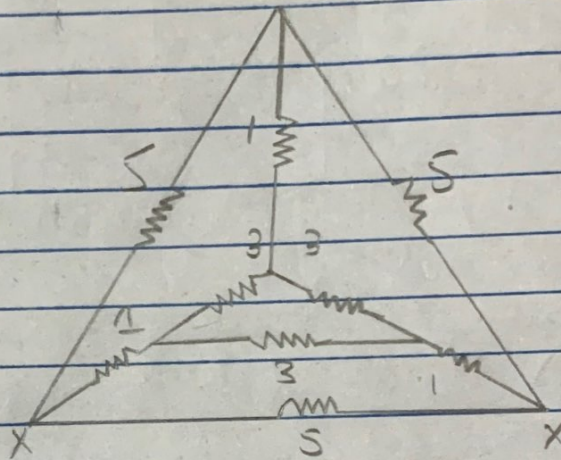part (B)

Determine the resistance b/w terminal X and X for the circuit shown in the figure below.






(All resistance in ohm)


$$R_1 = \frac{3 \times 3}{3 + 3 + 3} = \frac{9}{9} = 1$$

$$R_2 = 1$$

$$R_3 = 1$$

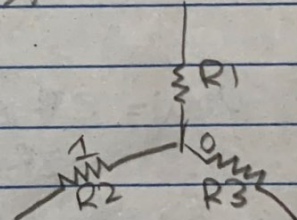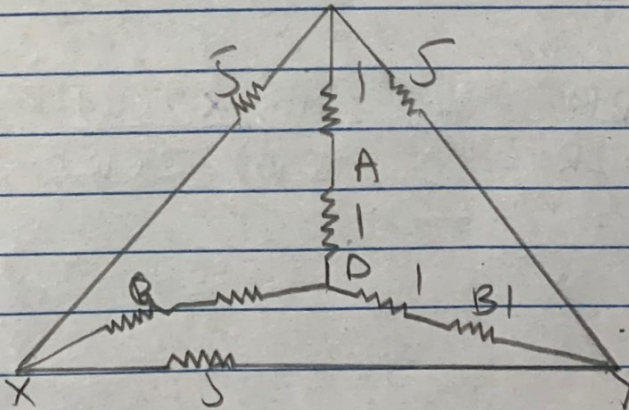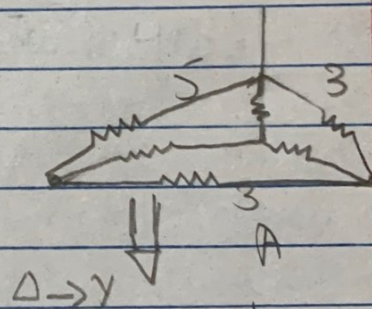

Put in CRT (A)



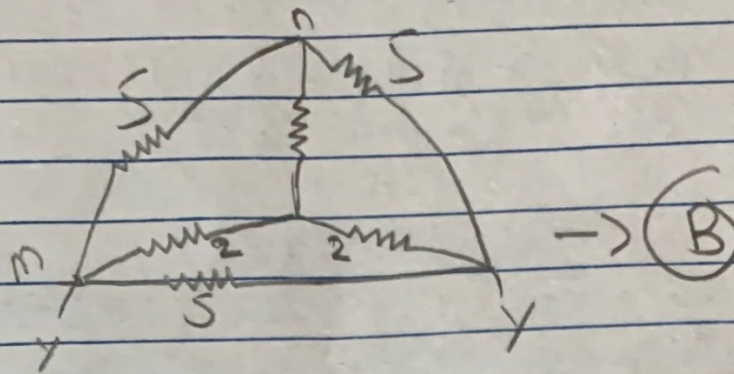


$$R_4 = \frac{2+2 + 2 \times 2}{2}$$

$$R_4 = 4 + 2 = 6\Omega$$

$$R_5 = 4 + 2 = 6\Omega$$

$$R_6 = 6\Omega$$

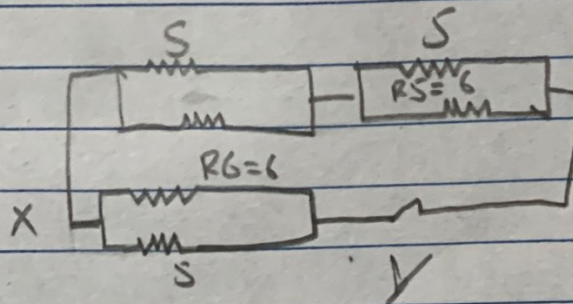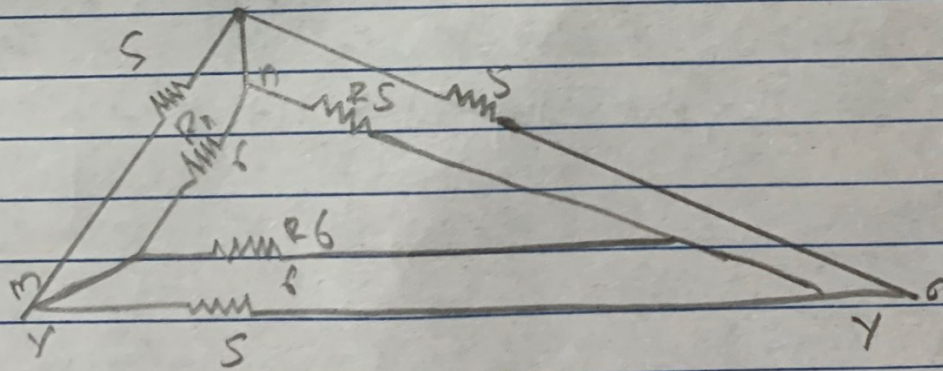
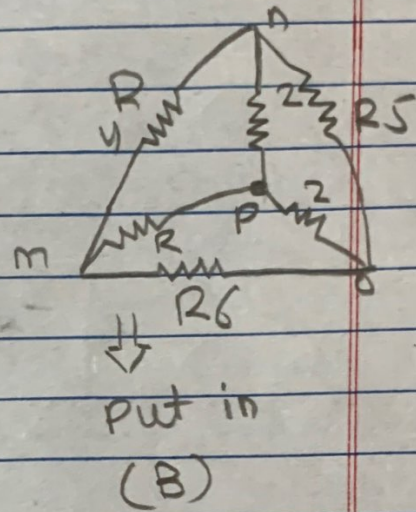


So

$$R_{eq} = 5 \parallel R_1 = 5 \parallel 6 = \frac{5 \times 6}{5 + 6} = \frac{30}{11}$$

$$R_{eq} = \frac{30}{11} = 2.727 \Omega$$


$$2.727 + 2.727$$

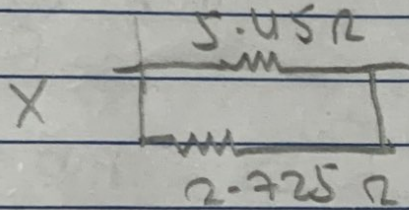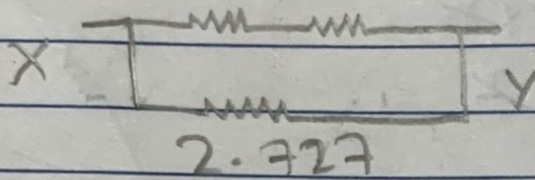

$$\frac{1.81717}{1} \Omega = \frac{5.45 \times 2.725}{5.45 + 2.725}$$

$$Z_{eq} = Z_{ny} = 1.81717 \Omega$$

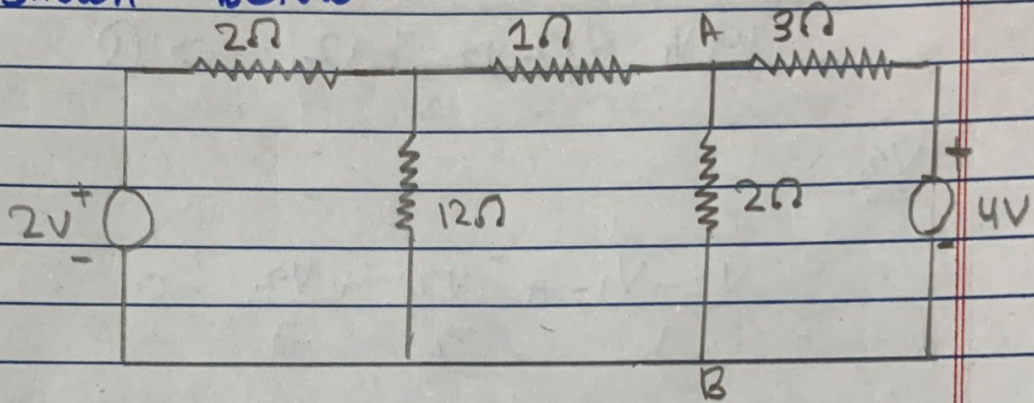Q1 Using superposition principle, determine the current through 2Ω resistor connected b/w terminal A and B in the circuit shown below.




Required $V_{AB} = ?$

Solution: -

using superposition theorem.

Suppose to use 2V source ϵ_1 short ckt.

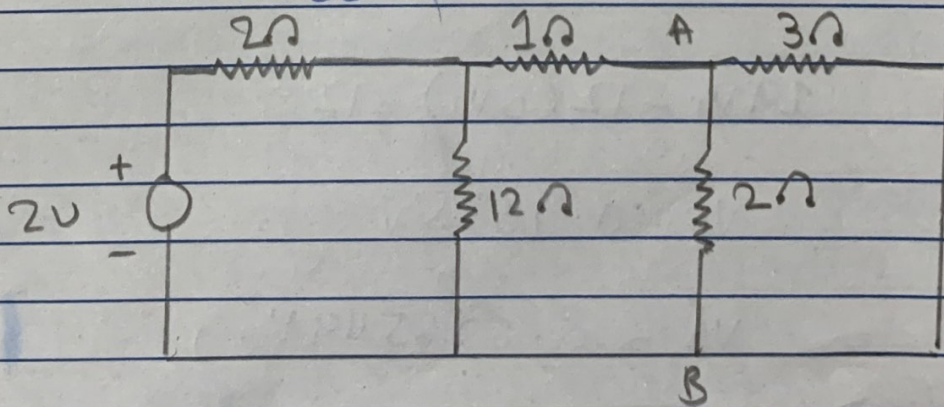

$V_{AB} = ?$

using Nodal Analysis.

↓

$$\frac{V_1 - 2}{2} + \frac{V_1}{12} + \frac{V_1 - V_2}{1} = 0$$

$$6V_1 - 12 + V_1 + 12V_1 - 12V_2 = 0$$

$$19V_1 - 12V_2 = 12 \rightarrow \textcircled{1}$$

V₂

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2}{3} = 0$$

$$6V_2 - 6V_1 + 3V_2 + 2V_2 = 0$$

$$-6V_1 + 11V_2 = 0$$

$$V_2 = \frac{6V_1}{11} \rightarrow \textcircled{2} \text{ put in } \textcircled{1}$$

$$19V_1 - 12(6V_1) = 12$$

$$V_1 = 0.9635 \text{ V}$$


$$V_2 = 0.525549 \text{ V}$$

$$V_{AB} = V_2 - 0 = 0.5255 \text{ V}$$

Now

2V is short ckt

and 4v act as source

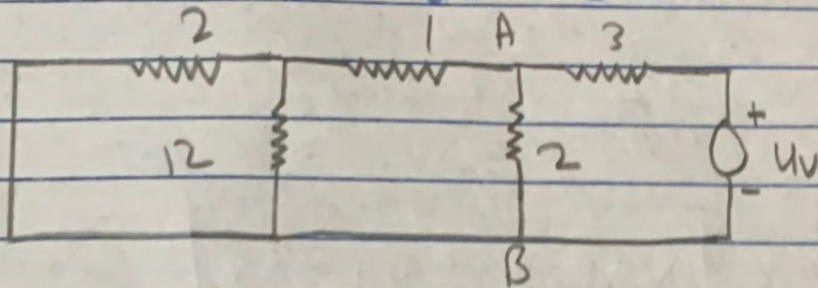


after parallel E_p sources simpli
creator =

$$= 2 \parallel 12$$

R_{12}

$$R_{123} = 2 \parallel 12 + 1$$

$$R_{123} = 1.5 + 1 = 2.5 \Omega$$

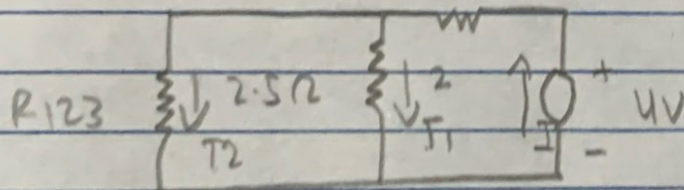

$$V_{AB}'' = I_1 (2) \rightarrow (A)$$

$$I = \frac{4}{2.5 \parallel 2 + 3} = \frac{4}{4.11} = 0.9729 \text{ A}$$

using ~~the~~ current division method

$$I_1 = \left(\frac{2.5}{2+2.5} \right) I = 0.5405 \text{ A}$$

$$V_{AB}'' = I_1 (2) = (0.5405) (2) = 1.081 \text{ V}$$

So

Not voltage

$$V_{AB} = V_{AB}^{\prime} + V_{AB}^{\prime\prime} = 0.5225 + 1.081V$$

$$V_{AB} = 1.6035V$$

$$V_{AB} = 1.6035V$$