

Name → Hamza

ID → 13042

D/p → Electrical

Date → 25-09-2020

Paper → Electrical Machine

(1)

QNO1 (A part)


Definition:

Speed control is intentional change in speed of motor.

Speed control of DC Series Motor.

ARCM (Armature Resistance Control Method):

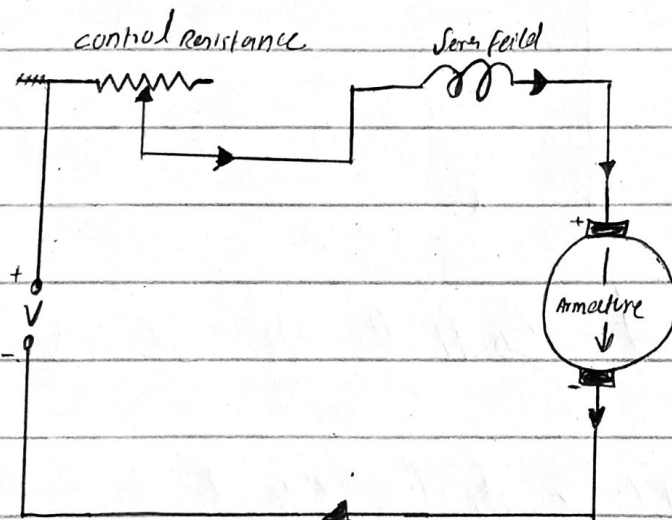The controlling resistance is connected directly in series with the supply of the motor as shown




This will reduce the voltage available across the armature and hence the speed falls. By changing the value of variable resistance. This method of speed control is most economical for constant torque.

(2)
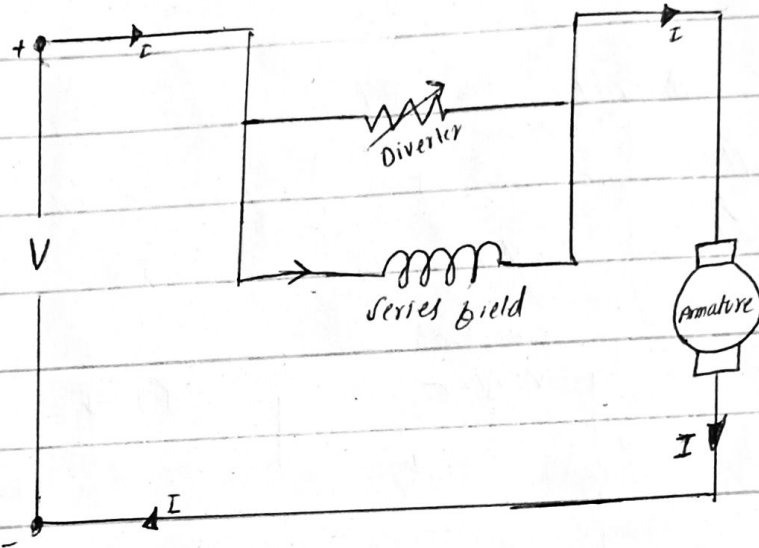
### Field Diverter Method.

This method uses a diverter. Field flux can be reduced by shunting a portion of motor current around the series field. Lesser the diverter resistance less is the field current less, flux therefore more speed.




### Speed Control OF DC Shunt Motor:-

#### ① Flux control Method.

In this method, a variable resistance (known as shunt field rheostat) is placed in series with shunt field winding.

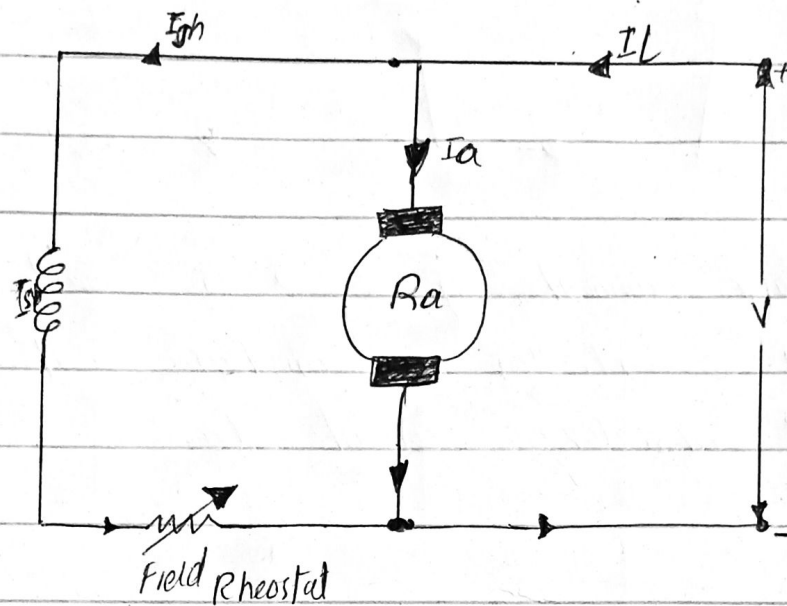(3)

An increase in controlling resistance reduces the field current with a reduction in flux and an increase in speed.




### Armature Control Method

This is done by inserting a variable resistance  $R_c$  (known as controller resistance) in series with the armature ~~and~~.

The flux remains constant while armature current is changed, produces change in speed.

(4)

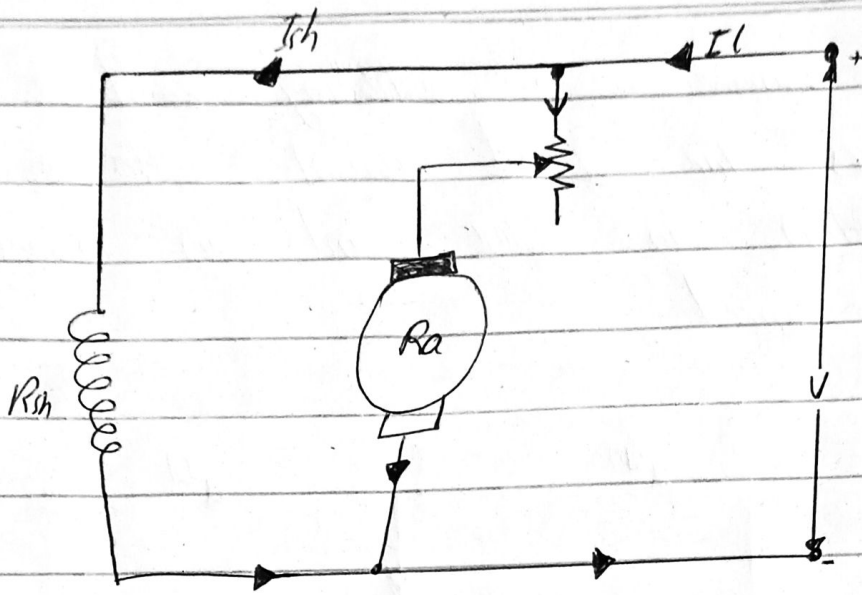

large amount of power is wasted in the controller resistance if carries full armature current  $I_a$ .

(5)

Q1 (B Part):-

Given data:-

DC generator = 8 poles

$Z = 480$

Emf per 10 conductor = 2.2V

current per conductor = 100 A

Required:- Terminal voltage  $E_t = ?$

output current  $I = ?$

power generated for both lap and wave windings = ?

Solution:-

No of conductors per path

$$480/8 = 60$$

we know that

Terminal voltage = emf per conductor  $\times$

number of conductors

$$= 2.2 \times 60 = 132 \text{ V}$$

Terminal voltage = 132V

(b)

output current

current per conductor  $\times$  no of parallel paths.

$$= 100 \times 8 = 800 \text{ A}$$

$$\boxed{\text{output current} = 800 \text{ A}}$$

Power generated for lap winding is

output current  $\times$  generated EMF

$$\Rightarrow 800 \times 132 = 105600 \text{ W}$$

$$\boxed{\text{Power generate lap} = 105.6 \text{ kW}}$$

For wave winding,

no of parallel paths = 2

no of conductors per path.

$$480 / 2 = 240$$

$$\text{Terminal voltage} = 2.2 \times 240 = 528 \text{ V}$$

(7)

$$\text{out put current} = 100 \times 2 = 200A$$

Power generated for wave winding is

$$200 \times 528 = 105600 W$$

$$\text{Power generated wave} = 105.6 \text{ kW}$$

Ans.



(8)

QNO 2 (A part):

Torque and Armature current  
Relationship:-

We have

$$P_e = P_m$$

$P_e$  = Electrical power

$P_m$  = Mechanical power

$$P_e = E_a I_a \quad \text{as } (E_a = E_b + I_a R_a) \text{ kVL}$$

$$P_e = (E_b + I_a R_a) I_a$$

$$P_e = E_b I_a + I_a^2 R_a$$

$$P_e = E_b I_a \quad \because I_a^2 R_a \rightarrow \text{dissipated}$$

now

in form of

$$P_m = T_g W$$

heat.

$\because T_g$  is (Torque in N.M)

$\because W$  is (angular speed in rad/sec)

$$1 \text{ rotation} = 2\pi$$

$$\therefore \text{In RPM} = N \cdot 2\pi / 60 = \text{rad/sec}$$

$$P_m = T_g N \cdot 2\pi / 60$$

$$P_m = P_e$$

$$T_g N \cdot 2\pi / 60 = E_b I_a$$

$$E_b = P \cdot \omega \cdot Z \cdot N / 60 \cdot A$$

$$T_g = \frac{P \cdot Z \cdot \omega \cdot I_a}{2 \cdot \pi \cdot A}$$

$T_g$  is directly pro to  $I_a$ .

(9)

QNO2 (B Part)

Differentiation b/w lap winding and wave winding:-

LAP Winding	Wave Winding
① The coil is lap back to the succeeding coil.	The coil of the winding form the wave shape.
② The end of the armature coil is connected to an adjacent segment on the commutator	The end of the armature coil is connected to commutator segments some distance apart
③ The numbers of parallel path are equal to the total of numbers poles.	The numbers of parallel paths is equal to two.
④ Parallel winding or multiple winding is other name.	Two circuit or series winding. is other name.
⑤ EMF less	EMF more.
⑥ Brushes equal to the number of parallel paths	Brushes are two

(10)

①	Types simplex and Duplex lap winding.	Progressive and Retrogressive wave winding.
⑧	Efficiency is less	Efficiency is high.
⑨	Additional coil is Equalizer Ring	Additional coil is Dummy coil.
⑩	Winding cost is high	Winding cost is low.
⑪	Use in low voltage and high current machines.	Use in high voltage and low current Machines.

END.