

Course Details

Instructor Name * Sir Mujtaba Ihsan
Course Name * Electronic circuit device.

Student Details.

Name Faiz ur Rehman


ID 14623

Semester/Module 4th

Student sign

Faiz ur
Rehman

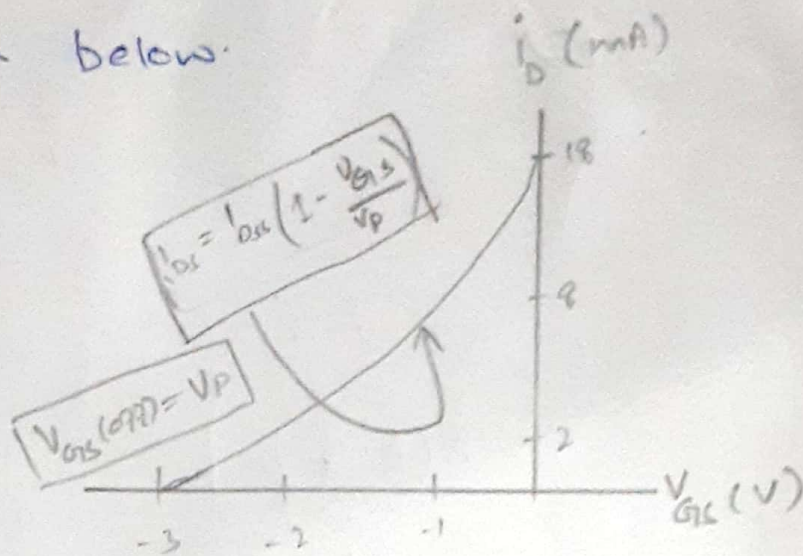Q1 Explain the trans conductor ----- n-channel JFET given below.



Transconductance curve of JFET transistor graph of drain current, I_D for a given change in gate to source voltage (ΔV_{GS}) with the drain-to source voltage const.

* unit of Siemens (S)

$$* g_m = \Delta I_D / \Delta V_{GS}$$

$$* g_m = \Delta I_D / \Delta V_{GS}$$


Other common designation for parameter are g_{fs}

& Y_{fs} (F. Transfer admittance). g_{fs} is

important factor in determining the voltage gain of FET amplifier

Because the transfer characteristic curve for JFET is nonlinear, g_m varies in value

depending the location on curve JFET.

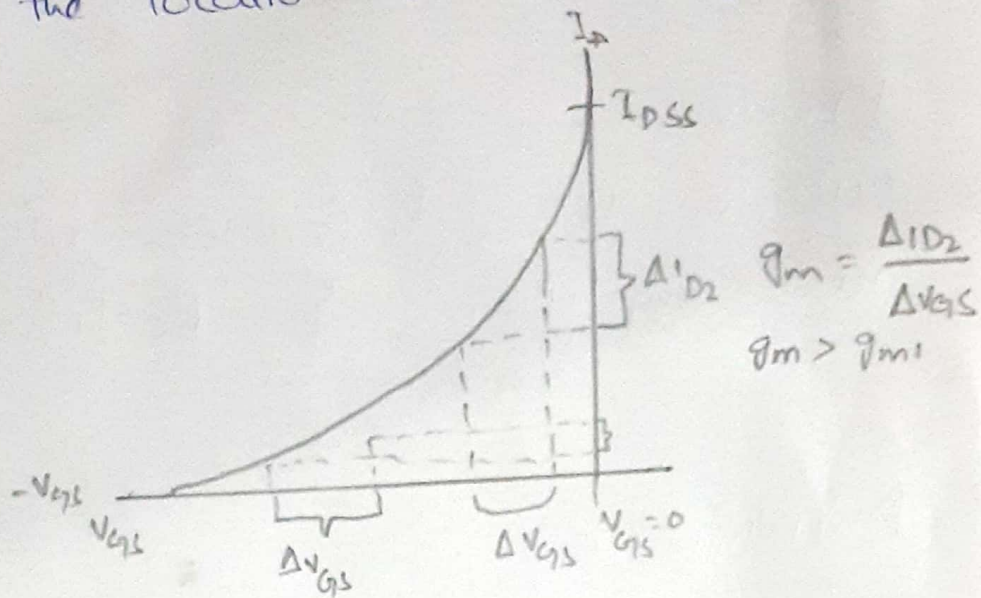

Datasheet normally give the value of g_m measured same unit siemens (s) $V_{GS} = 0V$ (g_{m0}) of the mho is $V_{DS} = 15V$

Equation

When a value g_{m0} is not available, you can calculate it using I_{DSS} & $V_{GS}(OFF)$

* Vertical line show an absolute value (no sign)

Equation

input Resistance & capacitance.

When the vertical line indicate absolute value (no sign)

$$R_{in} = V_{GS} / I_{DSS}$$

Q₂ State the characteristic of a Practical operational amplifier.

Characteristic of a practical op amplifier.

Various characteristic of practical Op-amplifier is given below.

(1) Open loop gain:

It is the voltage gain of the op-amp when no feedback is practically it is several thousand.

(2) input impedance:

It is finite and typically greater than ~~1MΩ~~. 1 MΩ. But using FETs for the input stage. it can be increased upto several hundred M.

(3) output impedance:

Typically few hundred ohms. With the help of negative feedback, it can be reduce to a very small value like 1 or 2 ohms.

(4) Slew Rate :- (SR)

It is defined as the maximum rate of change of output voltage w.r.t time

$$SR = \left[\frac{dv_o}{dt} \right]_{\max}$$

For practical op-amp

$$0.5 \text{ V}/\mu\text{s}$$

For ideal op-amp it is infinite.

(5) Bandwidth :-

The bandwidth of practical op-amp in open loop configuration is very small. By application of negative feedback, it can be increased to a desired value.

Q3 Calculate output voltage for
Summing amplifier if $V_1 = 0.2V$, $V_2 = 0.5V$
and $V_3 = 2V$ and $R_1 = R_2 = R_3 = R_f = 6K\Omega$

Given Data:

$$V_1 = 0.2V$$

$$V_2 = 0.5V$$

$$V_3 = 2V$$

~~$R_1 = R_2 = R_3 = R_f = 6K\Omega$~~

$$R_1 = R_2 = R_3 = R_f = 6K\Omega$$

Required:

$$V_{out} = ?$$

Solution: \rightarrow

Formula: $V_{out} = - \left(\frac{R_f}{R} \right) (V_1 + V_2 + V_3 \dots)$

$$\Rightarrow - \left(\frac{6K\Omega}{6K\Omega} \right) (0.2V + 0.5V + 2V)$$

$$\Rightarrow - (2.7)V$$

$$\Rightarrow - 2.7V$$

Q4 (a) Part.

You are working on an audio circuit in the lab. -----? justify your answer with reason.

Class A

Class A is always on. Used for "signal" level circuits (where power requirements are small) b/c they maintain low distortion. They are very inefficient & are rarely used for high power designs. 75% or more of the supplied power is dissipated by DC.

Class B

Peak efficiency of class B. output stage 78.5%. much higher than class A. class B amplifiers are used in low cost design or design sound quality not important.

- * Class B amplifiers significantly more efficient than class A.
- * class B amplifiers common in clock radios circuit. pocket transistor radio.

Class C :

- * Common used RF circuit
- * class C amplifier never used audio eq circuit.

Class C amplifier operate output transistor
in a ^{state that} result in tremendous distortion.

* Totally unsuitable for audio ~~circ~~ reproduction.

* class C is not able for audio circuit.