

Name: Haris Khan

ID : 13169.

Subject : Power Electronics.

Assign. : Paper mid.


Submitt. : Engr. Sir Shayyem Tariq Jan.

21-04-20.

Q1 (a)

Answer:

=> R-L Connected in series with Diode:

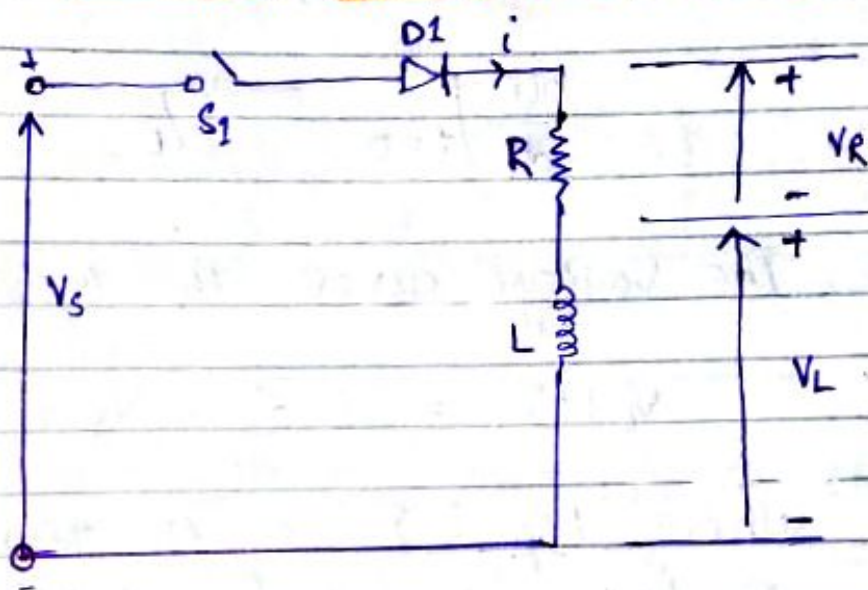

when S_1 is closed at $t=0$, the current through the inductor increases and is expressed as:

$$V_s = V_L + V_R = L \frac{di}{dt} + Ri$$

=> with the initial condition $i(t=0) = 0$, $i(t)$ is expressed as:

$$i(t) = \frac{V_s}{V_R} (1 - e^{-tR/L})$$

=> The rate of change of this current can be obtained from.

$$\frac{di}{dt} = \frac{V_s}{L} e^{-tR/L}$$



⇒ The initial rate of rise of the current (at $t=0$) is obtained:

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_s}{L}$$


The voltage across the inductor is

$$V_L(t) = L \frac{di}{dt} = V_s e^{-tR/L}$$

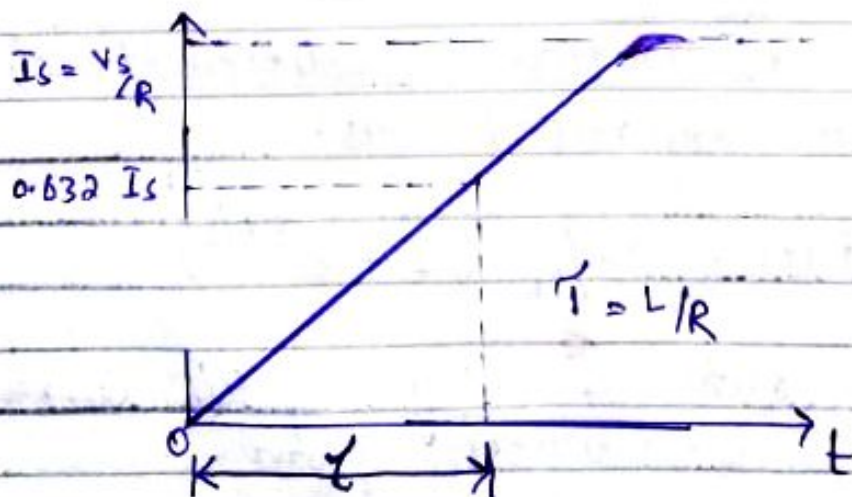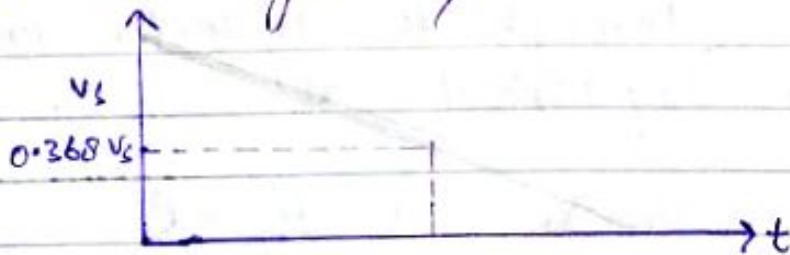
where $L/R = \tau$ is the time constant of R, L load. The waveforms for the voltage & current are shown.



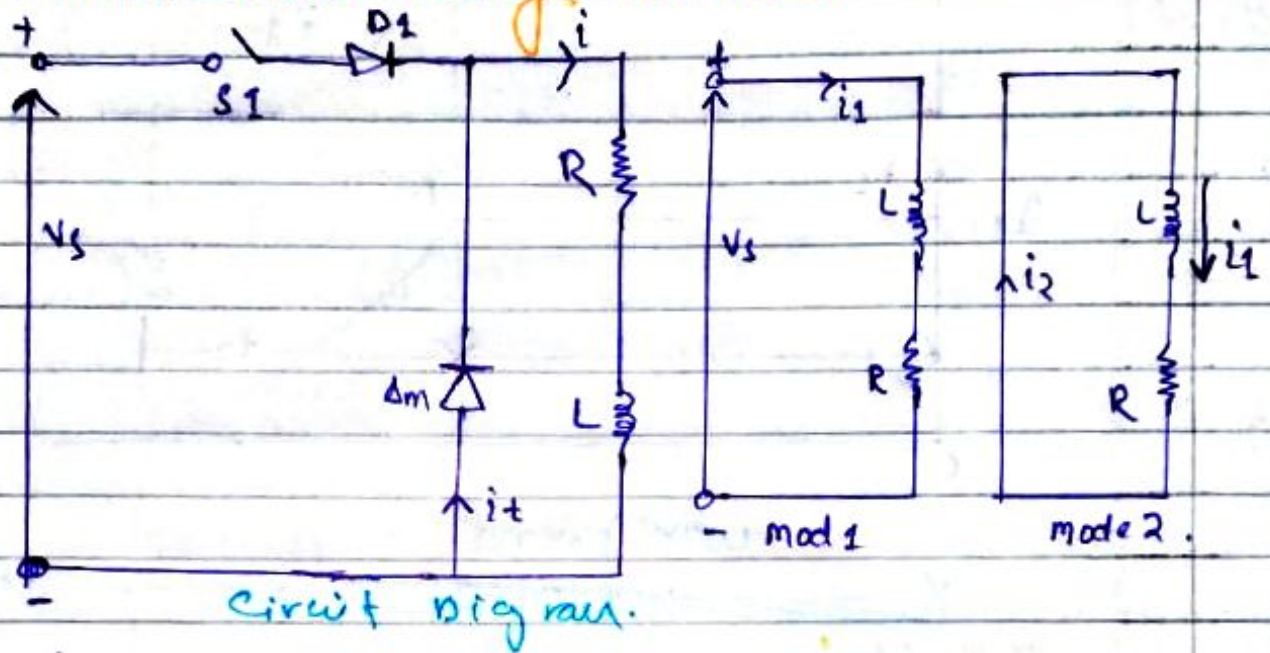∴ R-L circuit connected in parallel with freewheeling diode:



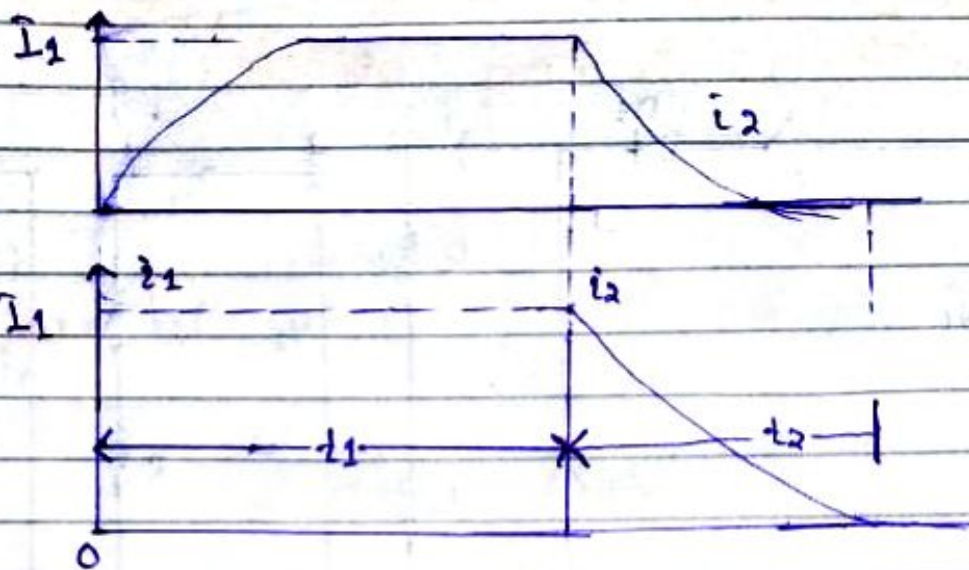- ⇒ The inductor has property to store energy.
- ⇒ In AC current during positive half cycle the inductor store energy.
- At negative half cycle the inductor de-energies.
- This may cause reverse damage to circuit.
- To avoid energy decription free wheeling diode is becomes forward bias so the current will flow through diode.



wave form

Q1 (b)

Solution:

ID: 13169.

$$V_{DS} = 69 \text{ V.}$$

$$V_T = 9 \text{ V.}$$

for solution.

$$V_{DS} \geq V_{GS} - V_T.$$

$$V_{DS} = V_{GS} - V_T.$$

$$\Rightarrow V_{GS} = V_{DS} + V_T.$$


$$V_{GS} = 69 + 9.$$

$$\begin{array}{r} 69 \\ + 9 \\ \hline 78 \end{array}$$

$$V_{GS} = 78 \text{ V}$$


Q#2 (a)

Answer.

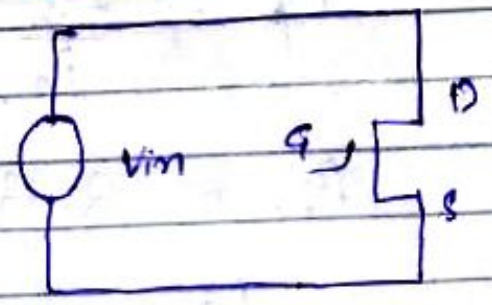

Whenever power MOSFET is connected to the power electronics circuit, it has high switching, high efficiency & less losses.

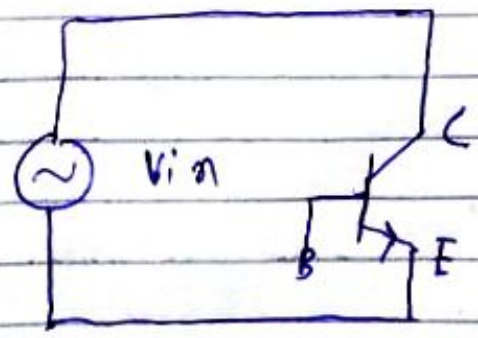=> When power MOSFET is replaced by power bipolar junction transistor, so, its switching speed decreases, efficiency decreases & its losses increase, as power bipolar junction transistor is mainly use for amplification.



X X X

Q#2 (b)

Answer

When power bipolar junction transistor is replaced by silicon controlled rectifier. So, an output we get controlled output voltage & switching.

=> In case of silicon controlled rectifier we get fast switching then power BJT but less their power MOSFET, variable efficiency & less losses.



Q#3 (a) Numerical.

Given data:

ID : 13169.

$R_C = 69 \Omega.$

$V_{CC} = 109 V.$

$V_B = 10 V.$

$V_{CE(sat)} = 1 V.$

$V_{BE(sat)} = 1.5 V.$

To find:

- a) mode of operation transistor.
- b) R_B
- c) β_{forced}
- d) power loss P_T .

Solution:

a). mode of operation transistor is

saturated mode.

(b)

$$\hat{I}_{CS} = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

$$\hat{I}_{CS} = \frac{10V - 9}{69}$$

$$\hat{I}_{CS} = 2.43 A. \quad \checkmark$$

$$\therefore I_{BS} = \frac{\hat{I}_{CS}}{\beta_{min}} \Rightarrow \frac{2.43}{8}$$

$$I_{BS} = 0.30 A. \quad \checkmark$$

$$\therefore I_B = ODF \times I_{BS}$$

$$I_B = 5 \times 0.30$$

$$I_B = 1.5 A. \quad \checkmark$$

$$\therefore I_B = \frac{V_B - V_{BE(sat)}}{R_B}$$

$$\Rightarrow R_B = \frac{V_B - V_{BE(sat)}}{I_B} \Rightarrow \frac{10 - 1.5}{1.5}$$

$$R_B = 5.66 \Omega$$

(c) β_{force} .

$$\beta_f = \frac{I_{cs}}{I_B}$$

$$\beta_f = 2.43 / 1.5$$

$$\beta_f = 1.62$$

(d) P_T

$$P_T = V_{BE} I_B + V_{CE} I_C$$

$$P_T = (4.5)(1.5) + 2(2.43)$$

$$P_T = 2.25 + 2.43$$

$$P_T = 4.68 \text{ W}$$

x ————— x ————— x

THE END.