

**Department of Electrical Engineering**  
**Sessional Assignment**  
**Course Details**

**Course Title:** Instrumentation and Measurement

**Module:** 6<sup>th</sup> (BE)

---

**Student Details**

**Name:** \_\_\_\_\_

**Student ID:** \_\_\_\_\_

---

**Q1:** A wattmeter has 2 current coils connected in parallel, each having a resistance of  $0.7\Omega$ . The wattmeter is connected in a circuit to measure power with its potential coil on the supply side. The reading on the wattmeter is 100W and the reading on the ammeter connected in series with the current coil is 3A. Calculate:

- a) Power loss in the wattmeter
  - b) True load power
  - c) Percentage error due to wattmeter connection
- 

**Q2:** Two voltmeters have the same range 0-500V. The internal resistances are  $30K\Omega$  and  $20K\Omega$  respectively. If they are connected in series and 700V be applied across them, what will be their readings?