 





**Program: BC (SE)**  
**Subject: Digital Logic Design (Theory)**  
**Assignment Number: 07**  
**Course Code: SEC-201**  
**EDP Code: 102002015**  
**Spring Semester 2020**

- Q.1** What is a register?
- Q.2** What is the storage capacity of a register that can retain one byte of data?
- Q.3** What does the “shift capacity” of a register mean?
- Q.4** The sequence 1011 is applied to the input of a 4-bit serial shift register that is initially cleared. What is the state of the shift register after three clock pulses?
- Q.5** For the data input and clock in Figure 01 (a), determine the states of each flip-flop in the shift register of Figure 01 (b) and show the  $Q$  waveforms. Assume that the register contains all 1s initially.




(a)

 

(b)


**FIGURE 01**

- Q.6** What is the state of the register in Figure 02 after each clock pulse if it starts in the 110001110000 state?

 


**FIGURE 02**

**Q.7** For the serial in/serial out shift register, determine the data-output waveform for the data-input and clock waveforms in Figure 03. Assume that the register is initially cleared.

 


**FIGURE 03**

**Q.8** A leading-edge clocked serial in/serial out shift register has a data-output waveform as shown in Figure 04. What binary number is stored in the 8-bit register if the first data bit out (left-most) is the LSB?

 


**FIGURE 04**

**Q.9** Show a complete timing diagram including the parallel outputs for the shift register in Figure 05. Use the waveforms in Figure 05 (c) with the register initially clear.

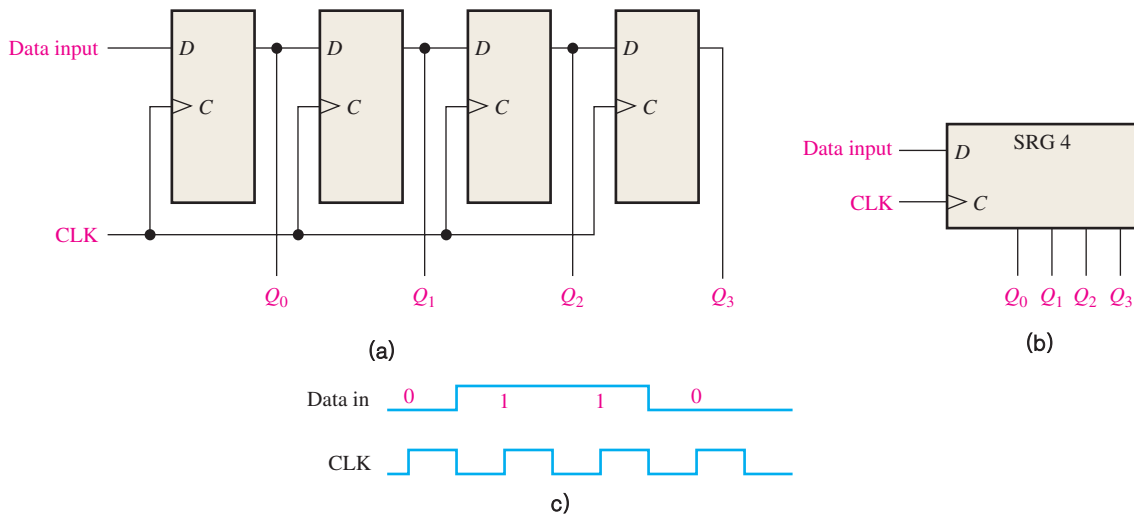

**FIGURE 05**

**Q.10** The shift register in Figure 06 (a) has  $\overline{SHIFT/LOAD}$  and CLK inputs as shown in part (b). The serial data input ( $SER$ ) is a 0. The parallel data inputs are  $D_0 = 1$ ,  $D_1 = 0$ ,  $D_2 = 1$ , and  $D_3 = 0$  as shown. Develop the data-output waveform in relation to the inputs.

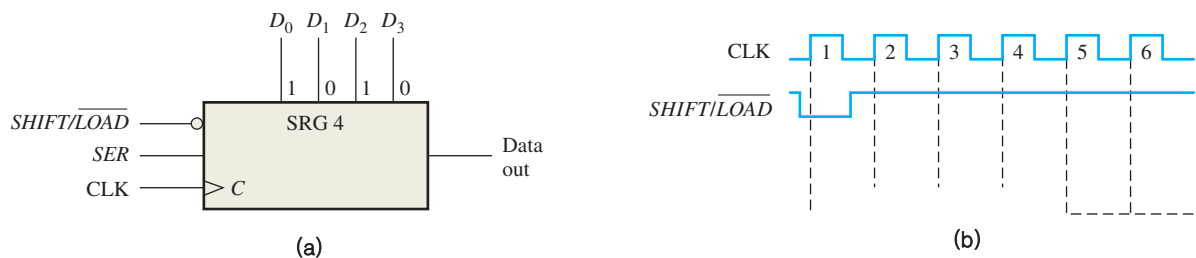

**FIGURE 06**