

Assignment

Lecture #08  
Power System Analysis

For the circuit shown below

Write the admittance matrix

Suppose the reactances in

the reactance diagram of

Your own choice.

