

Assignment

Power System Analysis

Lecture #09

⊛ Write in Matrix Form the node equations necessary to solve for the voltages of the numbered buses of figure. The network equivalent is as follows.

The emfs shown in figure are

$$E_g =$$

$$E_h = \text{all in Per unit.}$$

