

Assignment

① Convert a single line / one line diagram of Power System Network of your own choice to Impedance and Reactance diagram.