

---

## Example 13-4

A 2N5459 has  $V_{GS(\text{off})} = -8 \text{ V}$  and  $I_{DSS} = 16 \text{ mA}$ . What is the drain current at the half cutoff point?

**SOLUTION** The drain current is one quarter of the maximum, or:

$$I_D = 4 \text{ mA}$$

The gate-source voltage that produces this current is  $-4 \text{ V}$ , half of the cutoff voltage.

**PRACTICE PROBLEM 13-4** Repeat Example 13-4 using a JFET with  $V_{GS(\text{off})} = -6 \text{ V}$  and  $I_{DSS} = 12 \text{ mA}$ .

---

## 13-4 Biasing in the Ohmic Region

The JFET can be biased in the ohmic or in the active region. When biased in the ohmic region, the JFET is equivalent to a resistance. When biased in the active region, the JFET is equivalent to a current source. In this section, we discuss gate bias, the method used to bias a JFET in the ohmic region.

### Gate Bias

Figure 13-7a shows **gate bias**. A negative gate voltage of  $-V_{GG}$  is applied to the gate through biasing resistor  $R_G$ . This sets up a drain current that is less than  $I_{DSS}$ . When the drain current flows through  $R_D$ , it sets up a drain voltage of:

$$V_D = V_{DD} - I_D R_D \quad (13-4)$$

Gate bias is the worst way to bias a JFET in the active region because the  $Q$  point is too unstable.

For example, a 2N5459 has the following spreads between minimum and maximum:  $I_{DSS}$  varies from 4 to 16 mA, and  $V_{GS(\text{off})}$  varies from  $-2$  to  $-8 \text{ V}$ . Figure 13-7b shows the minimum and maximum transconductance curves. If a gate bias of  $-1 \text{ V}$  is used with this JFET, we get the minimum and maximum  $Q$  points shown.  $Q_1$  has a drain current of 12.3 mA, and  $Q_2$  has a drain current of only 1 mA.

### Hard Saturation


Although not suitable for active-region biasing, gate bias is perfect for ohmic-region biasing because stability of the  $Q$  point does not matter. Figure 13-7c shows how to bias a JFET in the ohmic region. The upper end of the dc load line has a drain saturation current of:

$$I_{D(\text{sat})} = \frac{V_{DD}}{R_D}$$

To ensure that a JFET is biased in the ohmic region, all we need to do is use  $V_{GS} = 0$  and:

$$I_{D(\text{sat})} \ll I_{DSS} \quad (13-5)$$

**Figure 13-7** (a) Gate bias; (b)  $Q$  point unstable in active region; (c) biased in ohmic region; (d) JFET is equivalent to resistance.

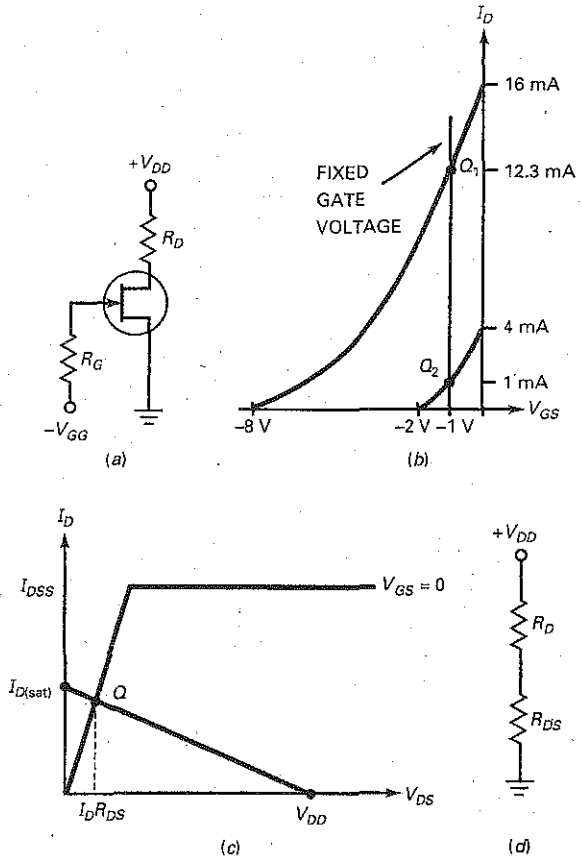

The symbol  $\ll$  means "much less than." This equation says that the drain saturation current must be much less than the maximum drain current. For instance, if a JFET has  $I_{DSS} = 10 \text{ mA}$ , hard saturation will occur if  $V_{GS} = 0$  and  $I_{D(sat)} = 1 \text{ mA}$ .

When a JFET is biased in the ohmic region, we can replace it by a resistance of  $R_{DS}$ , as shown in Fig. 13-7d. With this equivalent circuit, we can calculate the drain voltage. When  $R_{DS}$  is much smaller than  $R_D$ , the drain voltage is close to zero.


### Example 13-5

What is the drain voltage in Fig. 13-8a?

**SOLUTION** Since  $V_P = 4 \text{ V}$ ,  $V_{GS(\text{off})} = -4 \text{ V}$ . Before point A in time, the input voltage is  $-10 \text{ V}$  and the JFET is cut off. In this case, the drain voltage is:

$$V_D = 10 \text{ V}$$

Figure 13-8 Example.

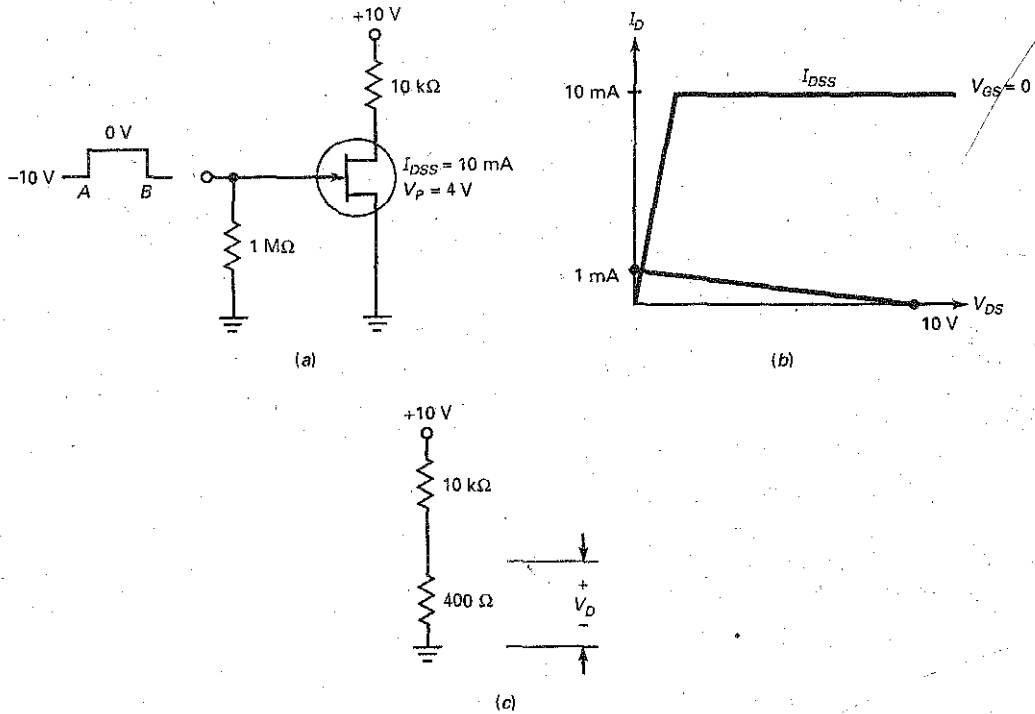

Between points A and B, the input voltage is 0 V. The upper end of the dc load line has a saturation current of:

$$I_{D(\text{sat})} = \frac{10 \text{ V}}{10 \text{ k}\Omega} = 1 \text{ mA}$$

Figure 13-8b shows the dc load line. Since  $I_{D(\text{sat})}$  is much less than  $I_{DSS}$ , the JFET is in hard saturation.

The ohmic resistance is:

$$R_{DS} = \frac{4 \text{ V}}{10 \text{ mA}} = 400 \Omega$$

In the equivalent circuit of Fig. 13-8c, the drain voltage is:

$$V_D = \frac{400 \Omega}{10 \text{ k}\Omega + 400 \Omega} 10 \text{ V} = 0.385 \text{ V}$$

**PRACTICE PROBLEM 13-5** Using Fig. 13-8a, find  $R_{DS}$  and  $V_D$  if  $V_p = 3 \text{ V}$ .