 


## Diode Clampers

A clamper adds a dc level to an ac voltage. **Clampers** are sometimes known as *dc restorers*. Figure 2–63 shows a diode clamper that inserts a positive dc level in the output waveform. The operation of this circuit can be seen by considering the first negative half-cycle of the input voltage. When the input voltage initially goes negative, the diode is forward-biased, allowing the capacitor to charge to near the peak of the input ( $V_{p(in)} - 0.7\text{ V}$ ), as shown in Figure 2–63(a). Just after the negative peak, the diode is reverse-biased. This is because the cathode is held near  $V_{p(in)} - 0.7\text{ V}$  by the charge on the capacitor. The capacitor can only discharge through the high resistance of  $R_L$ . So, from the peak of one negative half-cycle to the next, the capacitor discharges very little. The amount that is discharged, of course, depends on the value of  $R_L$ .




◀ FIGURE 2–63

Positive clamper operation.

If the capacitor discharges during the period of the input wave, clamping action is affected. If the  $RC$  time constant is 100 times the period, the clamping action is excellent. An  $RC$  time constant of ten times the period will have a small amount of distortion at the ground level due to the charging current.

The net effect of the clamping action is that the capacitor retains a charge approximately equal to the peak value of the input less the diode drop. The capacitor voltage acts essentially as a battery in series with the input voltage. The dc voltage of the capacitor adds to the input voltage by superposition, as in Figure 2–63(b).

 If the diode is turned around, a negative dc voltage is added to the input voltage to produce the output voltage as shown in Figure 2–64.




◀ FIGURE 2–64

Negative clamper.

**EXAMPLE 2-13**

What is the output voltage that you would expect to observe across  $R_L$  in the clamping circuit of Figure 2-65? Assume that  $RC$  is large enough to prevent significant capacitor discharge.

 ▶ **FIGURE 2-65**


**Solution** Ideally, a negative dc value equal to the input peak less the diode drop is inserted by the clamping circuit.

$$V_{DC} \cong -(V_{p(in)} - 0.7 \text{ V}) = -(24 \text{ V} - 0.7 \text{ V}) = -23.3 \text{ V}$$

Actually, the capacitor will discharge slightly between peaks, and, as a result, the output voltage will have an average value of slightly less than that calculated above. The output waveform goes to approximately +0.7 V, as shown in Figure 2-66.

▶ **FIGURE 2-66**

 Output waveform across  $R_L$  for Figure 2-65.



**Related Problem** What is the output voltage that you would observe across  $R_L$  in Figure 2-65 for  $C = 22 \mu\text{F}$  and  $R_L = 18 \text{ k}\Omega$ ?



Open the Multisim file E02-13 in the Examples folder on the companion website. For the specified input, measure the output waveform. Compare with the waveform shown in the example.

**SECTION 2-7  
CHECKUP**

1. Discuss how diode limiters and diode clammers differ in terms of their function.
2. What is the difference between a positive limiter and a negative limiter?
3. What is the maximum voltage across an unbiased positive silicon diode limiter during the positive alternation of the input voltage?
4. To limit the output voltage of a positive limiter to 5 V when a 10 V peak input is applied, what value must the bias voltage be?
5. What component in a clamping circuit effectively acts as a battery?