

# Digital Logic & Design (Theory)

Examination: Final-Term

Instructor: Muhammad Amin

Program: BS (SE)

Course Codes: SEC-201

EDP Codes: 102002015

Semester: Spring 2020

Total Marks: 50

Date: June 26, 2020

Timing: 12:00pm to 6:00pm

**Note: Attempt all questions. Use examples and diagrams where necessary.**

- Q.1** Draw and explain the logic diagram for each of the following:
- A circuit for adding or subtracting two 4-bit numbers
  - 4-bit active low decoder
  - Decimal to BCD encoder
  - Frequency divider (Use 3 J-K flip-flops and assume 16 kHz frequency of the initial wave-form.)
- Q.2** For the 4-input multiplexer, data inputs are given as:  
 $D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$   
Find the output Y if the select inputs are given as:
- $S_0 = 1, S_1 = 0$
  - $S_0 = 0, S_1 = 1$
  - $S_0 = 1, S_1 = 1$
  - $S_0 = 0, S_1 = 0$
- Q.3** Timing diagram in Figure 01 shows inputs to a 9-bit parity checker. Draw the  $\Sigma$  Even and  $\Sigma$  Odd output for the even parity checking.
- Q.4** The waveforms in Figure 02 are applied to the J, K, CLK,  $\overline{PRE}$ , and  $\overline{CLR}$  inputs as indicated. Determine the Q output, if the flip-flop is initially RESET.
- Q.5** Use the waveforms in Figure 03 to draw the timing diagram for the parallel outputs ( $Q_1, Q_2, Q_3, Q_4$ ) for the shift register. Assume that register is initially cleared.
- Q.6** Draw the logic diagram and timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

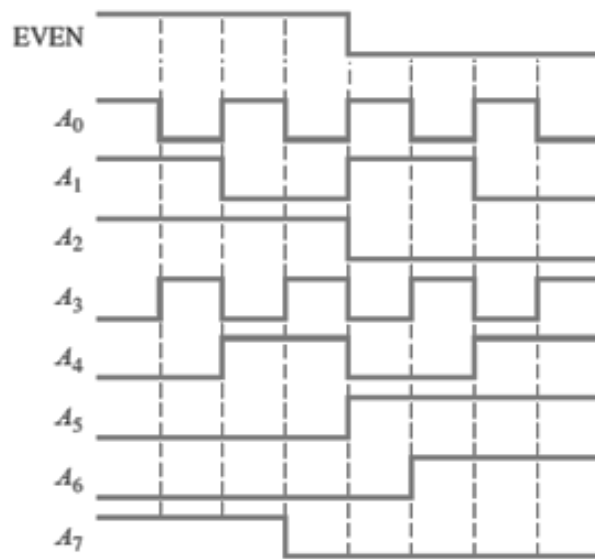


Figure 01

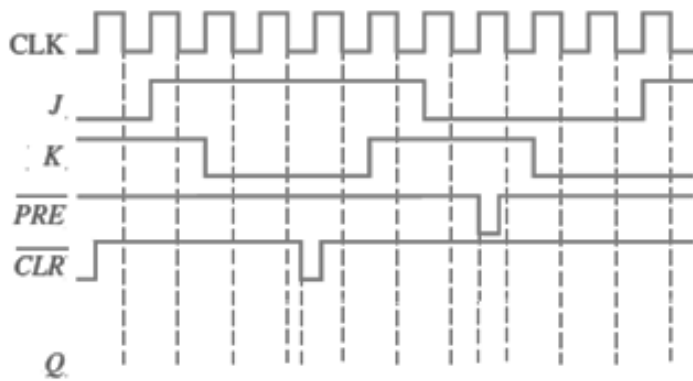


Figure 02

 
 


Figure 03