



## Digital Logic & Design/Digital Systems

Programs: BS (CS)/BS (SE)/BS (TELC)

Course Codes: CSC-201/ SEC-201/TSC-201

EDP Codes: 102007016

Instructor: Muhammad Amin

Examination: Final Term

Semester: Summer 2020

Date: Sep. 26, 2020

Timing: 3:00 pm - 7:00 pm

Question No.	Q.1	Q.2	Q.3	Q.4	Q.5	Q.6	Q.7	Q.8	Q.9	
Total Marks	5	5	5	5	6	6	6	6	6	50

Note: Attempt all questions.

Q.1 Draw the logic circuit using the input (A, B, C, D) and output (X) waveforms in Figure 01.

 


FIGURE 01

Q.2 For the 4-input multiplexer, data inputs are given as:

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

Find the output Y if the select inputs are given as:

a)  $S_0 = 1, S_1 = 0$

b)  $S_0 = 0, S_1 = 1$

c)  $S_0 = 1, S_1 = 1$

d)  $S_0 = 0, S_1 = 0$

Q.3 For the circuit in Figure 02, assume the inputs are  $\overline{Add/Subt.} = 1, A = 1010$ , and  $B = 1101$ . What is the output?


 



FIGURE 02

**Q.4** Determine the  $A = B$ ,  $A > B$ , and  $A < B$  outputs for the input numbers shown on the comparator in Figure 03.

 

**FIGURE 03**

- Q.5** Show the logic required to convert a 4-bit Gray code to binary and use that logic to convert the following Gray code words to binary: 1011
- Q.6** Draw and explain the logic diagram for 4-bit active low decoder.
- Q.7** Draw and explain the logic diagram for frequency divider (Use 3 J-K flip-flops and assume 16 kHz frequency of the initial wave-form.)
- Q.8** Determine the Q waveform relative to the clock if the signals shown in Figure 04 are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW.

 

**FIGURE 04**

**Q.9** Draw the logic diagram and timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

\*\*\*\*\**End of Exam*\*\*\*\*\*