



## Digital Logic & Design/Digital Systems

Programs: BS (CS)/BS (SE)/BS (TELC)

Course Codes: CSC-201/ SEC-201/TSC-201

EDP Codes: 102007016

Instructor: Muhammad Amin

Examination: Final Term

Semester: Summer 2020

Date: Sep. 26, 2020

Timing: 3:00 pm - 7:00 pm

Question No.	Q.1	Q.2	Q.3	Q.4	Q.5	Q.6	Q.7	Q.8	Q.9	Q.10	Q.11	Q.12	
Total Marks	7	7	7	7	6	6	6	6	7	7	7	7	80

**Note: Attempt all questions.**

**Q.1** Using Boolean algebra, simplify the following expression:

$$X = (A + B + C)(\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

**Q.2** Use a Karnaugh map to find the minimum SOP form for the following expression:

$$X = \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + AB\bar{C}\bar{D} + ABCD$$

**Q.3** Implement the expression  $X = \overline{(\bar{A} + \bar{B} + \bar{C})}DE$  by using NAND logic.

**Q.4** Draw the logic circuit using the input (A, B, C, D) and output (X) waveforms in Figure 01.

 


FIGURE 01

**Q.5** For the 4-input multiplexer, data inputs are given as:

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

Find the output Y if the select inputs are given as:

a)  $S_0 = 1, S_1 = 0$

b)  $S_0 = 0, S_1 = 1$

c)  $S_0 = 1, S_1 = 1$

d)  $S_0 = 0, S_1 = 0$

**Q.6** For the circuit in Figure 02, assume the inputs are  $\overline{Add/Subt.} = 1, A=1010$ , and  $B=1101$ . What is the output?

 


FIGURE 02

Q.7 Determine the  $A = B$ ,  $A > B$ , and  $A < B$  outputs for the input numbers shown on the comparator in Figure 03.

 


FIGURE 03

- Q.8 Show the logic required to convert a 4-bit Gray code to binary and use that logic to convert the following Gray code words to binary: 1011
- Q.9 Draw and explain the logic diagram for 4-bit active low decoder.
- Q.10 Draw and explain the logic diagram for frequency divider (Use 3 J-K flip-flops and assume 16 kHz frequency of the initial wave-form.)
- Q.11 Determine the Q waveform relative to the clock if the signals shown in Figure 04 are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW.

 


FIGURE 04

**Q.12** Draw the logic diagram and timing diagram for the 4-stage synchronous binary counter. Verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

\*\*\*\*\**End of Exam*\*\*\*\*\*