

★ Kirchhoff's Laws in Frequency Domain :-

- Both KCL and KVL can be expressed in freq. domain.
- For KVL, let v_1, v_2, \dots, v_n be voltages across closed loop. Then.

$$v_1 + v_2 + v_3 + \dots + v_n = 0 \quad \text{--- (9.51)}$$

In the sinusoidal steady state, each voltage above can be written as:

$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0 \quad \text{--- (9.52)}$$

This can be written as:

$$\text{Re}(V_{m1} e^{j\theta_1} e^{j\omega t}) + \text{Re}(V_{m2} e^{j\theta_2} e^{j\omega t}) + \dots + \text{Re}(V_{mn} e^{j\theta_n} e^{j\omega t}) = 0$$

$$\text{Re}[(V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2} + \dots + V_{mn} e^{j\theta_n}) e^{j\omega t}] = 0 \quad \text{--- (9.53)}$$

If we let $V_k = V_{mk} e^{j\theta_k}$, then (phasor part)

$$\text{Re}[(V_1 + V_2 + \dots + V_n) e^{j\omega t}] = 0 \quad \text{--- (9.54)}$$

time domain.
Phasor Part

Since $e^{j\omega t} \neq 0$,

$$V_1 + V_2 + \dots + V_n = 0 \quad \text{--- (9.55)}$$


- Similarly we can do same procedure for find KCL in phasor domain. For. $i_1 + i_2 + \dots + i_n = 0$ --- (9.56)
- ~~are~~ are currents entering and leaving in time t .

• Their phasor forms will be $I_1 + I_2 + \dots + I_n = 0$ --- (9.57)

A Impedance Combinations:-

→ Impedances in Series:-

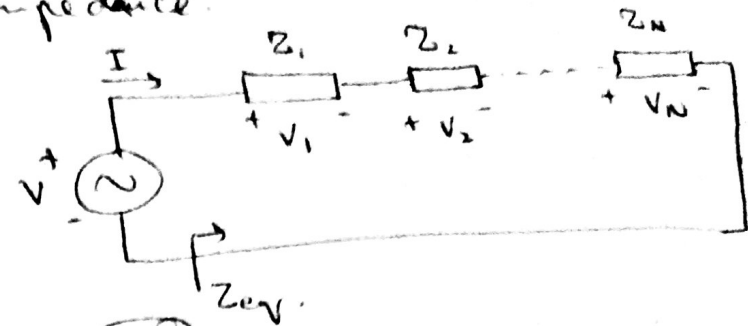- Consider N series-connected impedances.
- Current I is same through all impedances.
- Apply KVL around loop.




$$V = V_1 + V_2 + \dots + V_N$$

$$= I(Z_1 + Z_2 + \dots + Z_N) \quad \text{--- (9.58)}$$

$$\alpha \quad V = I(Z_{eq}) \Rightarrow \boxed{Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N} \quad \text{--- (9.59)}$$

• If N=2, then,
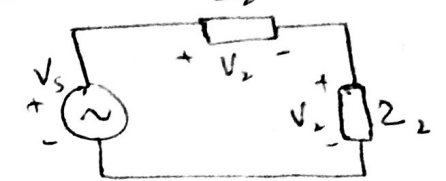
$$I = \frac{V}{Z_1 + Z_2} \quad \text{--- (9.60)}$$




Since, Voltage Division is V_1 and V_2 as below:

$$V_1 = I Z_1 \quad \text{and} \quad V_2 = I Z_2$$

$$\text{So, } \boxed{V_1 = \frac{Z_1}{Z_1 + Z_2} V \quad \text{and} \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V} \quad \text{--- (9.61)}$$

→ Impedances In Parallel:-

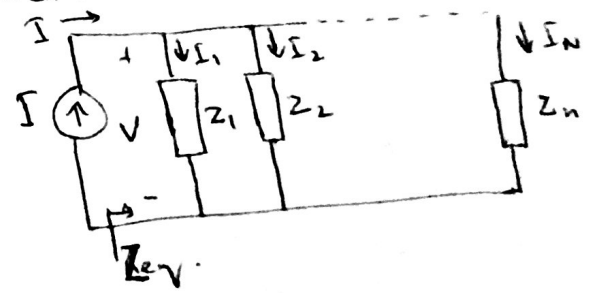- Consider N parallel-connected impedances.
- Voltage across each impedance is same.
- Apply KCL.




$$I = I_1 + I_2 + \dots + I_N = \frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_N}$$

$$= V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$I = \frac{V}{Z_{eq}} \Rightarrow I = V \cdot \frac{1}{Z_{eq}}$$

• The equivalent admittance is:

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

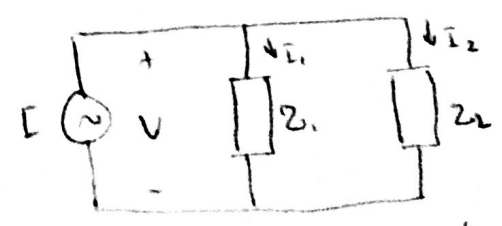


• when N=2, the equivalent admittance is:

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

• Since Current Division is I_1 and $I_2 \Rightarrow I_1 = \frac{V}{Z_1}, I_2 = \frac{V}{Z_2}$


$$I_1 = \frac{I Z_{eq}}{Z_1} = I \frac{Z_1 Z_2}{(Z_1 + Z_2) Z_1} = \frac{I Z_2}{Z_1 + Z_2}, \quad I_2 = \frac{I Z_{eq}}{Z_2} = \frac{I Z_1 Z_2}{(Z_1 + Z_2) Z_2} = \frac{I Z_1}{Z_1 + Z_2}$$

'Δ' Delta Circuit

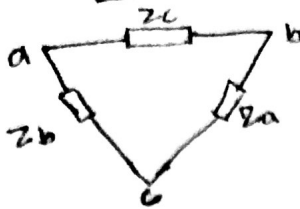

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

Star or Y Circuit

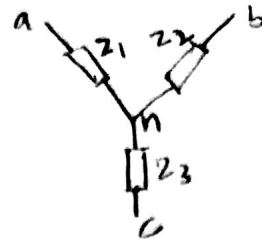

$$Z_1 = \frac{\text{Right} \times \text{Left}}{\text{Right} + \text{Left} + \text{Bottom}}$$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

* Impedances in Δ to Y and Y to Δ transformation :-


(2)

→ Y to Δ Conversion:

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$
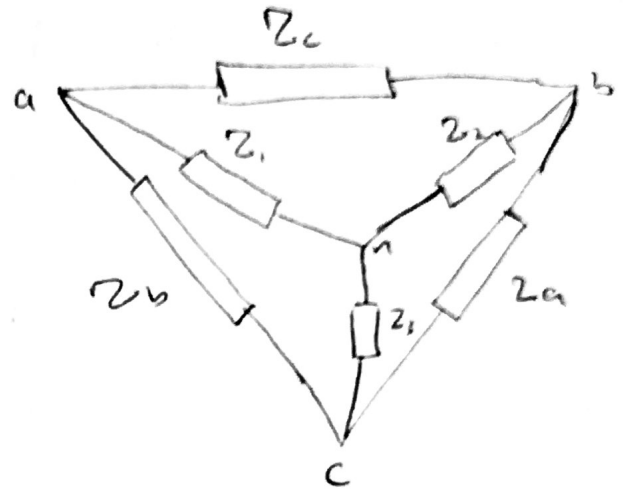
$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$



"Superimposed Y and Δ networks"

→ Δ to Y Conversion:

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

• A Δ or Y circuit is said to be 'balanced' if it has equal impedances in all branches. e.g.

• Consider each impedance is 1Ω then.

$$Z_a = 3Z_x \quad \text{or} \quad Z_x = \frac{1}{3} Z_a$$


and circuit is balanced.

Exp 9.10:- Find input impedance. Assume $\omega = 50 \text{ rad/s}$.

We set $Z_1 = \text{Impedance of } 2\text{mF}$

$Z_2 = \text{" " } 3\Omega \text{ and } 10\text{mF}$

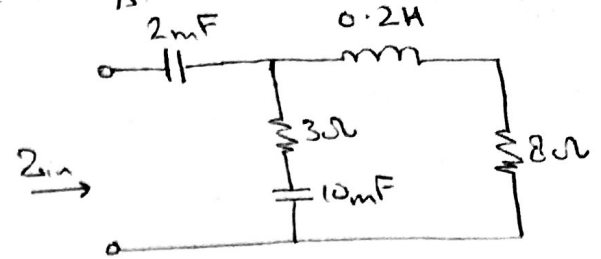$Z_3 = \text{" " } 0.2\text{H and } 8\Omega.$



Then, $Z_1 = \frac{1}{j\omega C} = \frac{1}{j 50 \times 2 \times 10^{-3}} = -j \frac{1}{100 \times 10^{-3}} = -j \frac{10 \cancel{\text{mF}}}{1 \cancel{\text{mF}}} = -j10 \Omega$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j(50)(10 \times 10^{-3})} = 3 + \frac{10 \cancel{\text{mF}}}{j 5 \cancel{\text{mF}}} = 3 + \frac{2}{j}$$

$$= \frac{-3j + 2}{j} = 3 - 2j \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j(50)(0.2) = 8 + j10 \Omega.$$

The input impedance is:

$$Z_{in} = Z_1 + Z_2 \parallel Z_3 = -j10 + \frac{(3-j2)(8+j10)}{3-2j+8+j10}$$

$$= -j10 + \frac{(24 + j30 - j16 - 20)}{11 + 8j} = -j10 + \frac{44 + 14j}{11 + 8j}$$

$$= -j10 + \frac{(44 + 14j)(11 - 8j)}{(11)^2 + (8)^2} = -j10 + \frac{484 - 352j + 154j + 112}{121 + 64}$$

$$= -j10 + \frac{596 - 198j}{185} = -j10 + 3.221 - 1.07j$$

$$Z_{in} = 3.221 - j11.07.$$


PP. 9.10: Find Z_{in} , $\omega = 10 \text{ rad/s}$
Book

Soln.:

$$Z_1 = 1 \text{ mF} \ \& \ 100 \ \Omega$$

$$Z_2 = 1 \text{ mF}$$
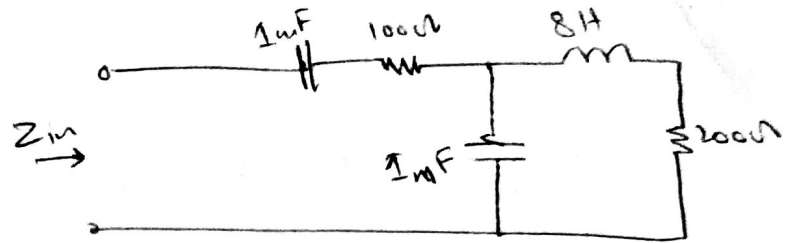
$$Z_3 = 8 \text{ H} \ \& \ 200 \ \Omega$$



$$\text{Then } Z_2 = \frac{1}{j\omega C} = \frac{1}{j(10)1 \times 10^{-3}} = \frac{1000}{j10} = -j100 \ \Omega$$

$$Z_1 = 100 + \frac{1}{j\omega C} = 100 + \frac{1}{j10 \times 10^{-3}} = 100 - j100 \ \Omega$$

$$Z_3 = 200 + j\omega L = 200 + j(10)(8) = 200 + j80.$$

$$\text{Then } Z_{in} = Z_1 + Z_2 \parallel Z_3$$

$$= 100 - j100 + \frac{(-j100)(200 + j80)}{-j100 + 200 + j80} = 100 - j100 + \frac{(-j20000 + 8000j)}{200 - 20j}$$

$$= 100 - j100 + \frac{(-j20000 + 8000j)(200 + 20j)}{(200)^2 + (20)^2} = 100 - j100 + 49.505 - 95.049j$$


$$Z_{in} = 149.5 - 195.049j \quad \checkmark$$

Pr 1.10: Determine Z_{in} and $\omega = 10 \text{ rad/s}$

Solution: - Let, $Z_1 =$ Impedance of 2 mF & 20Ω

$$Z_2 = \text{ " } = 4 \text{ mF}$$
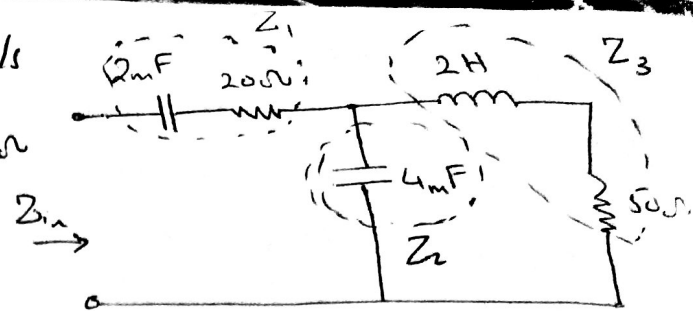
$$Z_3 = \text{ " } = 2 \text{ H} \text{ \& } 50 \Omega$$



$$Z_1 = 20 + \frac{1}{j\omega C} = 20 + \frac{1}{j(10)(2 \times 10^{-3})} = 20 - j50 \Omega$$

$$Z_2 = \frac{1}{j\omega C} = \frac{1}{j(10)(4 \times 10^{-3})} = -j25 \Omega$$

$$Z_3 = 50 + j\omega L = 50 + j(10)(2) = 50 + j20$$

$$Z_{in} = Z_1 + Z_2 \parallel Z_3 = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} = 20 - j50 + \frac{-j25 \times (50 + j20)}{-j25 + 50 + j20}$$

$$= 20 - j50 + \frac{5 - 1250j}{50 - 5j} = 20 - j50 + \frac{(5 - 1250j)(50 - 5j)}{(50)^2 + (5)^2}$$

$$= 20 - j50 + \frac{250 - 25j - 62500j - 6250}{2525} \quad (50 - 5j)(50 + 5j)$$

$$= 20 - j50 + \frac{-6000 - 62525j}{2525} \quad 2500 + 250j - 250j + 25$$

$$= 20 - j50 + \frac{500 - 1250j}{50 - 5j} = 20 - j50 + \frac{(500 - 1250j)(50 + 5j)}{2525}$$

$$= 20 - j50 + \frac{25000 + 2500j - 62500j + 6250}{2525}$$

$$= 20 - j50 + \frac{18750 - 60000j}{2525} + \frac{31250 - 6000j}{2525}$$

$$= 20 - j50 + 12.38 - 2130.76j$$

$$Z_{in} = 32.38 - j73.76 \Omega$$

Exp 9.11 Find $v_o(t)$

First we convert time domain terms to phasor domain.

$$V_s = 20 \cos(4t - 15^\circ)$$

$$V_s = 20 \angle -15^\circ, \omega = 4$$

$$10 \mu\text{F} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-6}}$$

$$5 \text{H} \Rightarrow j\omega L = j4 \times 5 = j20$$

Let $Z_1 =$ impedance of 60Ω , $Z_2 =$ Impedance $10 \mu\text{F}$ & 5H

Then $Z_1 = 60 \Omega$

and $Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20} = \frac{500}{-5j} = j100 \Omega$.

Use voltage division method.

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} \times (20 \angle -15^\circ)$$

$$= \frac{(j100)(60 - j100)}{3600 + 10000} \angle (20 \angle -15^\circ) = \frac{j6000 + 10000}{13600} \angle (20 \angle -15^\circ)$$


$$= (0.735 + 0.441j) (20 \angle -15^\circ) \quad 0.5402 + 0.1946$$

$$= (0.8575 \angle 30.96^\circ) (20 \angle -15^\circ)$$

$$= 17.15 \angle 15.96^\circ \text{ V}$$

We convert to time domain and get.
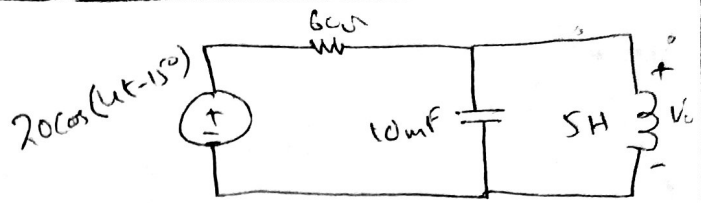
$$v_o(t) = 17.15 \cos(4t + 15.96^\circ)$$



Calculate V_o .

We convert time domain terms to freq. domain:


$$v_t = 10 \cos(10t + 75^\circ)$$

$$V_s = 10 \angle 75^\circ, \omega = 10$$

$$10 \Omega \Rightarrow 10 \Omega$$

$$0.5 \text{ H} \Rightarrow j\omega L = j \cdot 10 \cdot 0.5 = j5 \Omega$$
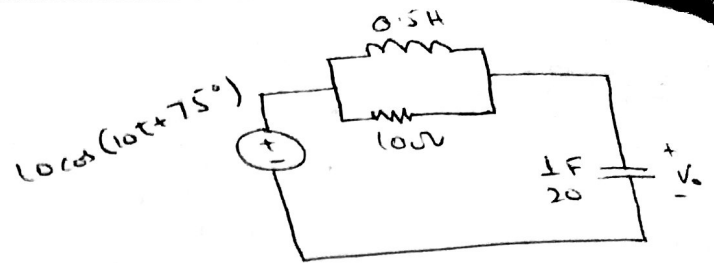
$$\frac{1}{2} \text{ F} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j \cdot 10 \cdot \frac{1}{20}} = \frac{20}{j10} = -2j \Omega$$



Assume. $Z_1 =$ impedance of 0.5 H and 10Ω

$$Z_2 = \frac{1}{20} \text{ F}$$

$$Z_1 = 10 \parallel j5 = \frac{10 \times j5}{10 + j5} = \frac{50j}{10 + j5} = 2 + j4 \Omega$$

$$Z_2 = -j2 \Omega$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{-j2}{2 + j4 - j2} (10 \angle 75^\circ)$$


$$= \frac{-j}{1 + j} (10 \angle 75^\circ) = \frac{-j(1-j)}{1+1} (10 \angle 75^\circ)$$

$$= \frac{-j-1}{2} (10 \angle 75^\circ) = -0.5 - 0.5j (10 \angle 75^\circ)$$





$$= (0.707 \angle -135^\circ) (10 \angle 75^\circ)$$

$$= 0.707 \angle -60^\circ$$

and $v(t) = 7.07 \cos(10t - 60^\circ) \text{ V}$

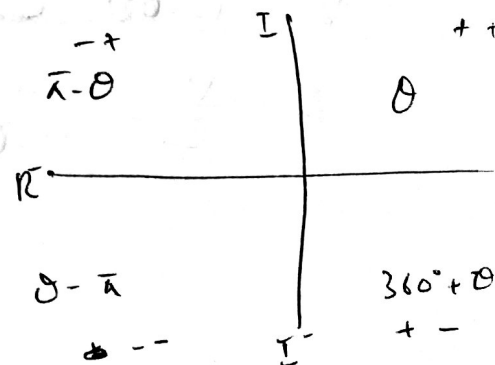

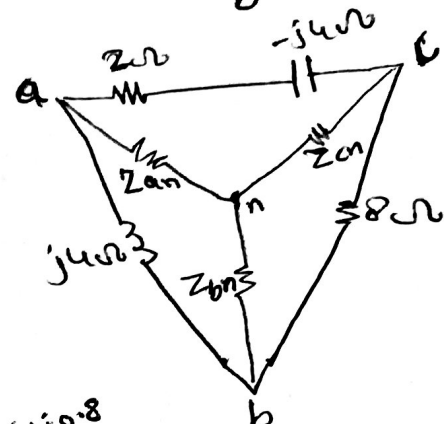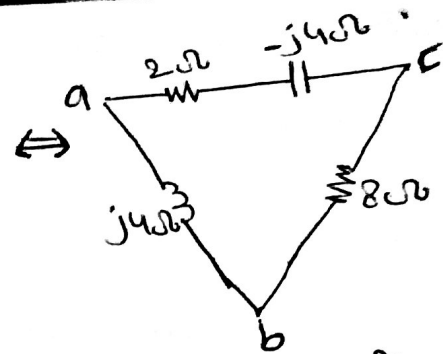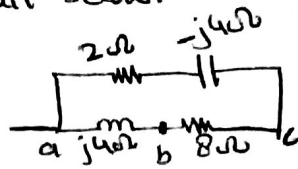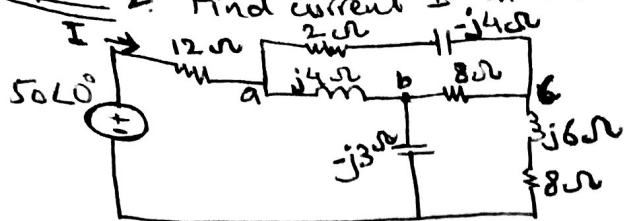Exp 9.12 Find current 'I' in the circuit below:-





Now we find Z_{an} , Z_{bn} , Z_{cn} as:

$$Z_{an} = \frac{(j4)(2-j4)}{j4+(2-j4)+8} = \frac{16+8j}{10} = 1.6+j0.8 \Omega$$

$$Z_{bn} = \frac{(j4)(8)}{j4+(2-j4)+8} = \frac{j32}{10} = j3.2 \Omega$$
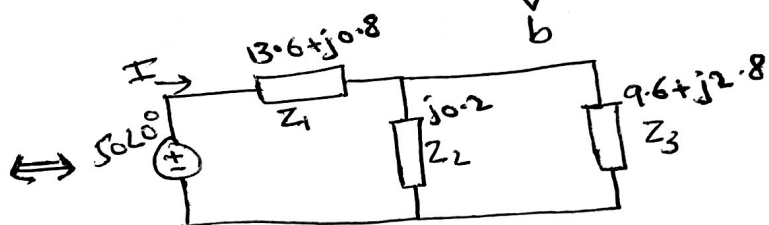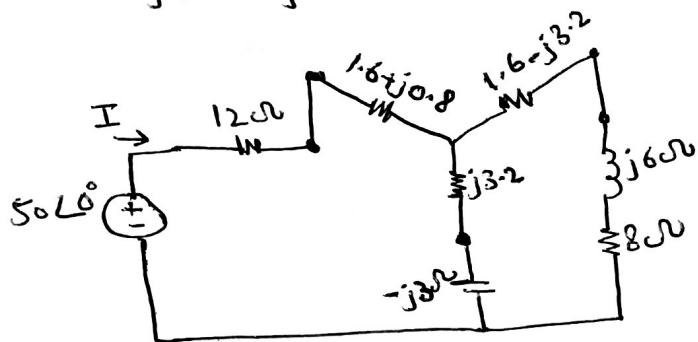
$$Z_{cn} = \frac{8(2-j4)}{j4+(2-j4)+8} = \frac{16-j32}{10} = 1.6-j3.2 \Omega$$



Now we calculate value of Z_1 , Z_2 , Z_3 .

$$Z_1 = 12 + 1.6 + j0.8 = 13.6 + j0.8$$

$$Z_2 = j3.2 - j3 = j0.2$$

$$Z_3 = 1.6 - j3.2 + j6 + 8 = 9.6 + j2.8$$

we can find Z as: $Z = Z_1 + Z_2 \parallel Z_3 = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3}$

$$Z = 13.6 + j0.8 + \frac{(j0.2)(9.6 + j2.8)}{(j0.2) + 9.6 + j2.8} = 13.6 + j0.8 + \frac{(j0.2)(9.6 + j2.8)}{9.6 + j3}$$

$$Z = 13.6 + j0.8 + \frac{(0.2 \angle 90^\circ)(10 \angle 16.26^\circ)}{10.058 \angle 17.35^\circ} = 13.6 + j0.8 + 0.1988 \angle 88.91^\circ$$

$$Z = 13.6 + j0.8 + j0.1988 + 0.0037 = 13.6037 + 0.998j$$

$$Z = 13.64 \angle 4.19^\circ$$

$$I = \frac{V}{Z} = \frac{50 \angle 0^\circ}{13.64 \angle 4.19^\circ} = 3.66 \angle -4.19^\circ \text{ Amp}$$