


⇒ Three Phase Circuits:

⇒ Wye-Wye Balanced Connections:

⇒ Key Concepts:

→ For voltage, look at the source.

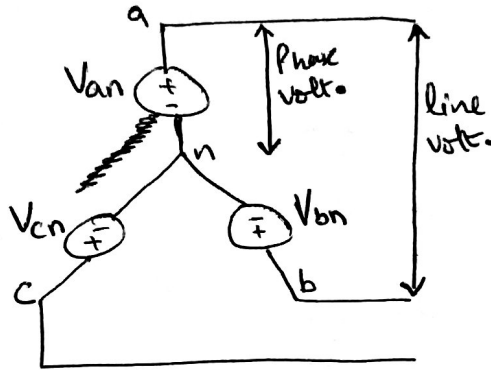
$V_L = \sqrt{3} V_p \angle 30^\circ$
 Remember $V_L > V_p$



line volt.: is line to line volt. as, here b/w a and b, b and c is line volt.

Phase volt.: is volt. across ~~across~~ source, e.g a and n, c and n, b and n. are three phase voltages.

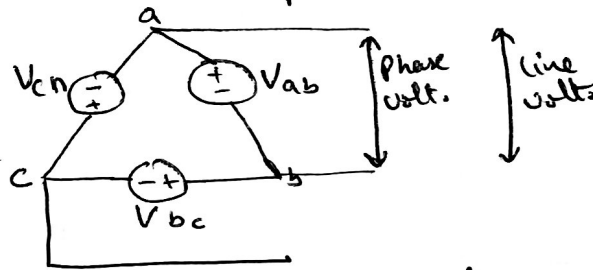* So here line volt. and phase volt. are not same.




* So here line and phase volt. are same.

→ For currents, look at the load:

* The current through any of line is line current, e.g I_a, I_b, I_c

* The current through any of impedance is phase current.

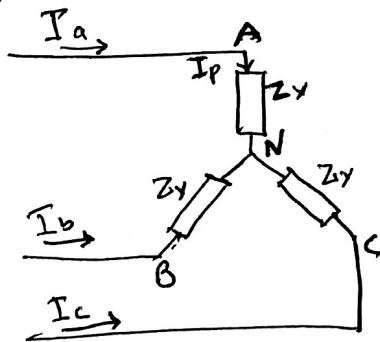* here line current and phase current are same. $I_L = I_p$.




* here current is dividing into two paths so $I_L \neq I_p$

Line current:

I_a, I_b, I_c

Phase current:


I_{AB}, I_{BC}, I_{CA}

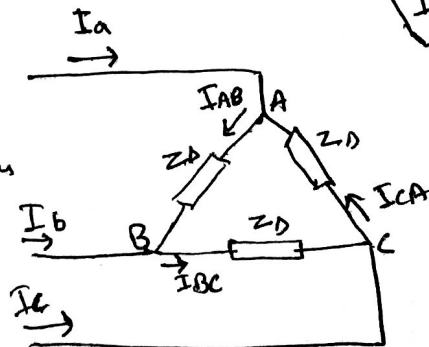

Remember.
 $I_L = \sqrt{3} I_p \angle -30^\circ$

⇒ Balanced Y-Y connection:-

(2)

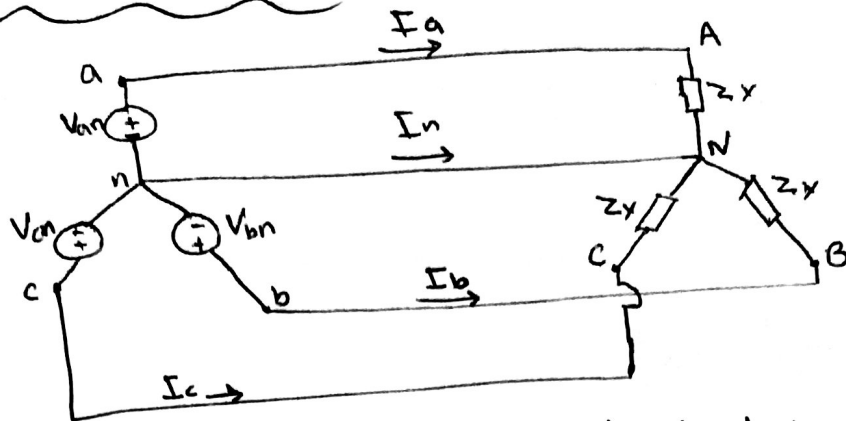

* Here we see source ~~impedance~~ and load impedance.

- Phase voltages: V_{an} , V_{bn} and V_{cn}

- Line conductors: $a \rightarrow A$, $b \rightarrow B$, $c \rightarrow C$ are called LINES.

- Line voltages: V_{ab} , V_{bc} , V_{ca} .

- The phase voltage is ($V_p = 230V$) V_{an} .
and line voltage is ($V_L = 400V$) V_{ab}

$$V_L = \sqrt{3} \times 230 = 400$$

So here $V_L \neq V_p$. i.e not same.

- The Line current and phase current are same.
see the phase current: (current through anyone load Z).

$$V_{an} = V_p \angle 0^\circ, \quad V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p (1 \angle 0^\circ - 1 \angle -120^\circ) = V_p (1 + 0.5 + j0.866) \\ &= V_p (1.5 + j0.866) = V_p (1.732 \angle 30^\circ) \end{aligned}$$

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$


$$\text{Similarly, } V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = V_{an} + V_{bn} = \sqrt{3} V_p \angle -210^\circ$$

Source side →

Load side →

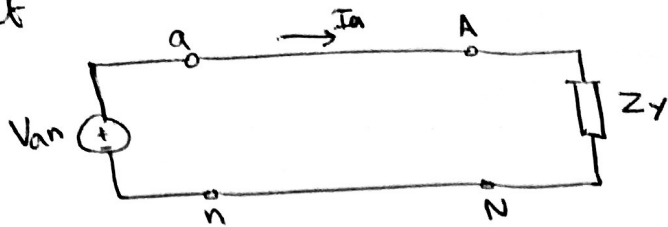=> Single Phase Equivalent
of Balanced Y-Y
connection



(3)

- * Balanced three phase circuits can be analyzed on per phase basis.
- * We look at one phase, say phase 'a' and analyze the single equivalent circuit.
- * Because the circuit is balanced, we can easily obtain other phase values using their phase relationships.

$$I_a = \frac{V_{an}}{Z_y}$$

Q-1. Calculate the line current in the three wire Y-Y system of figure below.

Soln. Here we have source in Y connection and have load in Y connection.

- we solve it for one phase and obtain I_a from the single phase analysis.

$$I_a = \frac{V_{an}}{Z_y}$$



where $Z_y = (5-j2) + (10+j8)$
 $= 15+j6 = 16.155 \angle 21.8^\circ$

So, $I_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$

Since the source voltages in Fig. are in positive sequence, the line current is in also positive sequence:

$$I_b = I_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$
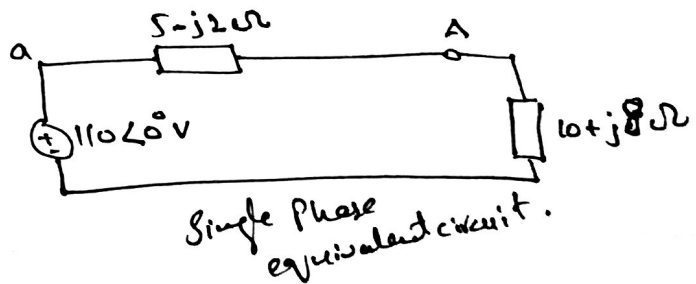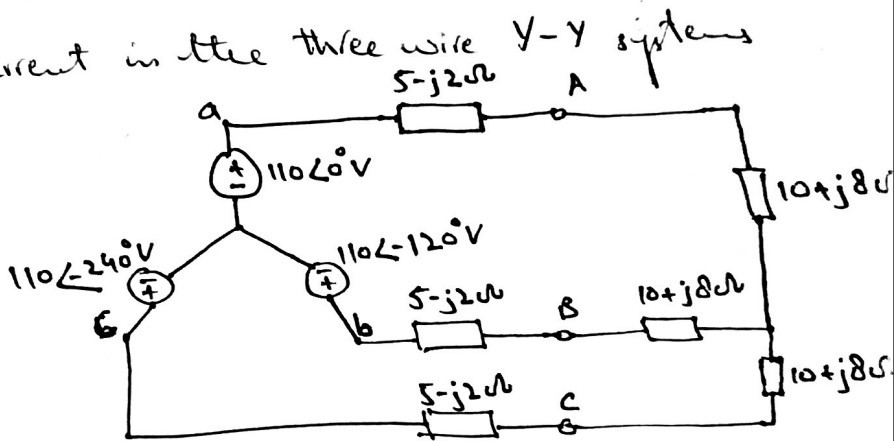
$$I_c = I_a \angle -240^\circ = 6.81 \angle -261.8^\circ \text{ A} = 6.81 \angle 98.2^\circ \text{ A}$$



Q.2 A Δ -connected balanced three-phase generator with an impedance of $0.4 + j0.3 \Omega$ per phase is connected to a Δ -connected balanced load with an impedance of $24 + j19 \Omega$ per phase. The line joining the generator and the load has an impedance of $0.6 + j0.7 \Omega$ per phase. Assuming a positive sequence for the source voltages and that $V_{an} = 120 \angle 30^\circ \text{ V}$, find
 (a) The line voltages, (b) the line currents.

Sol. (a) $V_L = \sqrt{3} V_p \angle 30^\circ$.


$$V_{ab} = \sqrt{3} \times 120 \angle 30^\circ \angle 30^\circ = 207.8 \angle 60^\circ$$

$$V_{bc} = 207.8 \angle -60^\circ \text{ V}$$

$$V_{ca} = 207.8 \angle -180^\circ \text{ V}$$

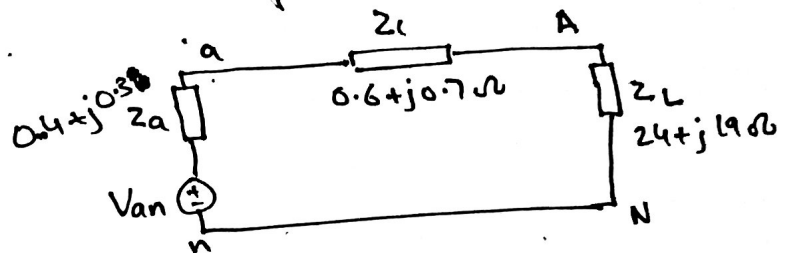(b) For line current just take one of the phase.

$$\begin{aligned} Z_Y &= 0.4 + j0.3 + 0.6 + j0.7 + 24 + j19 \\ &= 25 + j20 \Omega \\ &= 32.02 \angle 38.65^\circ \end{aligned}$$




$$\therefore I_a = \frac{120 \angle 30^\circ}{32.02 \angle 38.65^\circ} = 3.75 \angle -8.65^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 3.75 \angle -128.65^\circ \text{ A}$$

$$I_c = I_a \angle -240^\circ = 3.75 \angle 111.35^\circ \text{ A}$$


⇒ Balanced Wye - Delta (Y-Δ) Connections (5)

* key concepts:

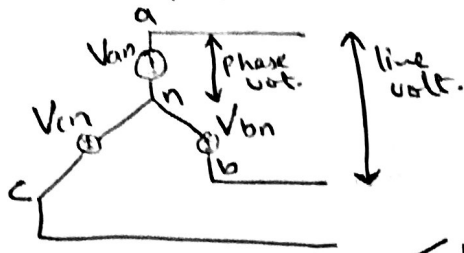


"for voltages look at source"

$$V_L = \sqrt{3} V_p \angle 30^\circ$$

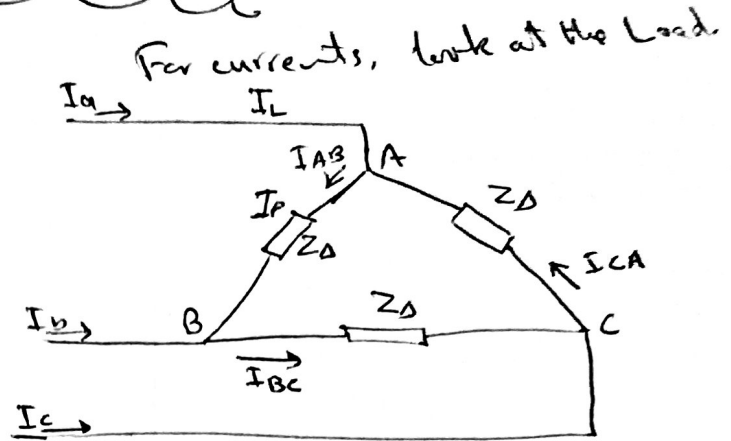

$$I_L = \sqrt{3} I_p \angle -30^\circ$$

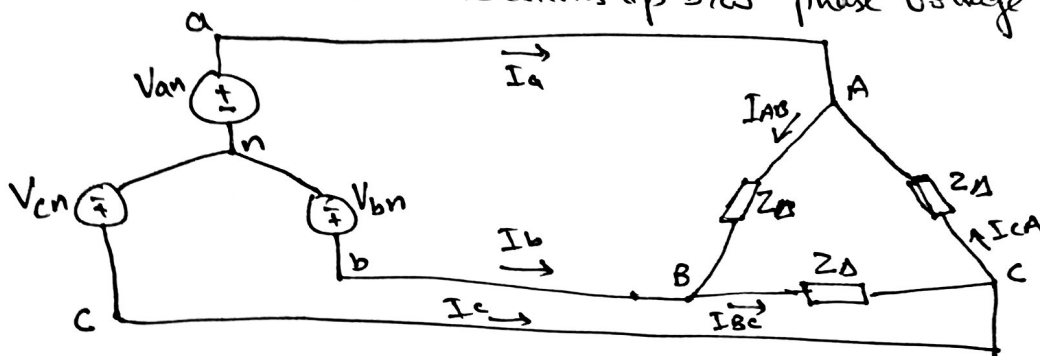STEP 1: Write down the relationship b/w phase voltage & line voltage.



For positive sequence.

Phase voltages:

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ$$

$$V_p = 230V$$

Line voltages:

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ = V_{AB}$$

$$V_{bc} = \sqrt{3} V_p \angle -90^\circ = V_{BC}$$

$$V_{ca} = \sqrt{3} V_p \angle -210^\circ = V_{CA}$$

STEP 2: Solve for phase currents I_{AB} , I_{BC} and I_{CA} .

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

Apply KCL at node A:

$$I_a + I_{CA} = I_{AB}$$

Line current:

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

We can write: $I_{CA} = I_{AB} \angle -240^\circ$.

$$\therefore I_a = I_{AB} - I_{CA} = I_{AB} - I_{AB} \angle -240^\circ$$

$$I_a = I_{AB} (1 + 0.5 - j0.866) = I_{AB} 1.732 \angle -30^\circ$$

$$\boxed{I_a = I_{AB} \sqrt{3} \angle -30^\circ}$$


Similarly, $I_b = I_{BC} \sqrt{3} \angle -30^\circ$

$$I_c = I_{CA} \sqrt{3} \angle -30^\circ$$


Alternate Way: To find current in γ - Δ connection ⑥ is to transfer the Δ connected load to an equivalent γ -connected load.

Using Δ - γ transform formula:
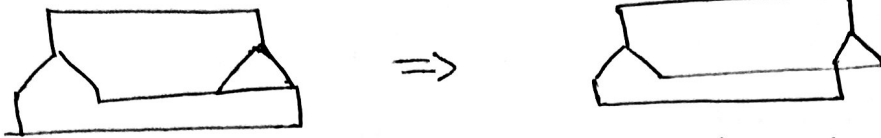
$$\boxed{Z_{\gamma} = \frac{Z_{\Delta}}{3}} \quad \gamma - \Delta$$



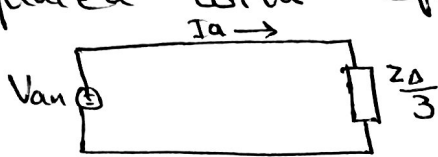So, the three phase γ - Δ system can be replaced with equivalent single phase circuit.



$$\boxed{I_a = \frac{V_{an}}{Z_{\gamma}} = \frac{V_{an}}{Z_{\Delta}/3}}$$

→ much easier to solve.

Q-1: A balanced abc sequence γ -connected source with $V_{an} = 100 \angle 10^\circ \text{V}$ is connected to a Δ -connected balanced load $8 + j4 \Omega$ per phase. Calculate the phase and line currents.

Sol: Convert Δ to γ at load side:

$$V_{an} = 100 \angle 10^\circ \text{V}, \quad Z_{\Delta} = 8 + j4 \Omega$$

$$Z_{\gamma} = \frac{Z_{\Delta}}{3} = \frac{8 + j4}{3} = \frac{8.944 \angle 26.57^\circ}{3} = 2.981 \angle 26.57^\circ \Omega$$

Line current:

$$I_a = \frac{V_{an}}{Z_{\Delta}/3} = \frac{100 \angle 10^\circ}{2.981 \angle 26.57^\circ}$$

$$I_a = 33.54 \angle -16.57^\circ \text{A} \checkmark$$

$$I_b = I_a \angle -120^\circ = (33.54 \angle -16.57^\circ) \angle -120^\circ$$

$$I_b = 33.54 \angle -136.57^\circ \text{A} \checkmark$$

$$I_c = I_a \angle +120^\circ = (33.54 \angle -16.57^\circ) \angle 120^\circ$$


$$I_c = 33.54 \angle 103.43^\circ \text{A} \checkmark$$

Phase Current: Line current = $\sqrt{3}$ Phase current $\angle -30^\circ$
Phase " = $\frac{\text{Line current}}{\sqrt{3}} \angle 30^\circ$

$$I_{AB} = \frac{33.54 \angle -16.57^\circ}{\sqrt{3}} \angle 30^\circ = 19.36 \angle 13.43^\circ \text{A} \checkmark$$

$$I_{BC} = I_{AB} \angle -120^\circ = 19.36 \angle -106.57^\circ \text{A} \checkmark$$
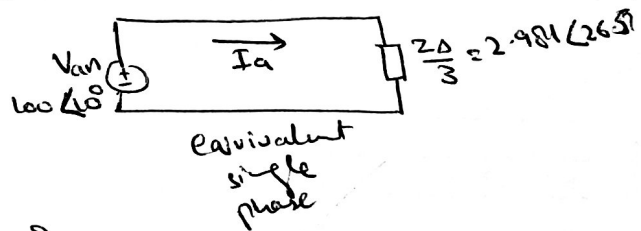
$$I_{CA} = I_{AB} \angle 120^\circ = 19.36 \angle 133.43^\circ \text{A} \checkmark$$



Q-2. One line voltage of the balanced Y-connected source is $V_{AB} = 180 \angle -20^\circ \text{V}$. If source is connected to a Δ -connected load of $20 \angle 40^\circ \Omega$, find the phase and line currents. Assume ABC sequence.

Sol: line voltage $V_{AB} = 180 \angle -20^\circ \text{V}$
 $Z_{\Delta} = 20 \angle 40^\circ \Omega$

using $V_L = \sqrt{3} V_p \angle 30^\circ \Rightarrow V_p = \frac{V_L}{\sqrt{3} \angle 30^\circ}$


Phase voltage:

$$V_{an} = \frac{180 \angle -20^\circ}{\sqrt{3}} \angle -30^\circ = 103.9 \angle -50^\circ \text{V} \checkmark$$

$$Z_y = \frac{Z_{\Delta}}{3} = \frac{20 \angle 40^\circ}{3} = 6.67 \angle 40^\circ \Omega. \checkmark$$

Line current:
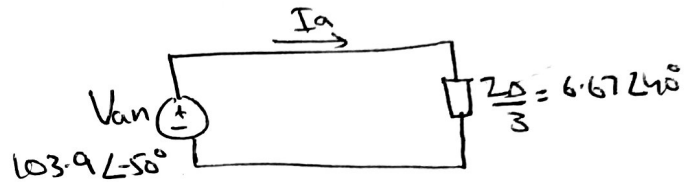
$$I_a = \frac{V_{an}}{Z_y/3} = \frac{103.9 \angle -50^\circ}{6.67 \angle 40^\circ}$$



$$I_a = 15.57 \angle -90^\circ \text{A} \checkmark$$

$$I_b = I_a \angle -120^\circ = 15.59 \angle +150^\circ \text{A} \checkmark$$

$$I_c = I_a \angle +120^\circ = 15.59 \angle 30^\circ \text{A} \checkmark$$

Phase current:

$$I_{AB} = \frac{15.57 \angle -90^\circ}{\sqrt{3}} \angle 30^\circ = 9 \angle -60^\circ \text{A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 9 \angle -180^\circ \text{A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 9 \angle 60^\circ \text{A}$$