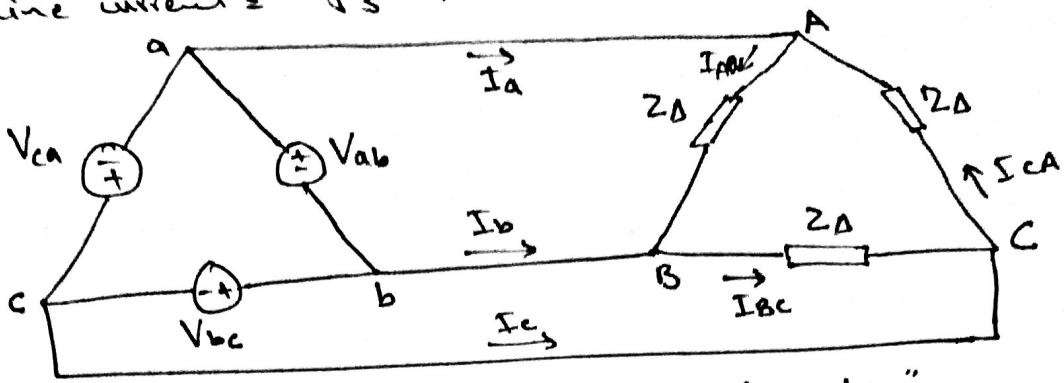


⇒ Balanced Delta-Delta (Δ-Δ) Connection:

- For Δ connection
- * Line voltage = phase voltage
 - * Line current = $\sqrt{3}$ Phase current. $\angle -30^\circ$



"Delta - Delta Connection"

* First of all the ~~find~~ voltage V_{AB} , ~~that~~ is ~~the~~ same as voltage V_{ab} . To find line current I_{AB} we can do it by $I_{AB} = \frac{V_{ab}}{Z_{\Delta}}$

* Other way is to convert both Δs to Ys and then find one of the phase and solve.

Q. 1. A balanced Δ connected load having an impedance $20 - j15 \Omega$ is connected to a Δ connected, positive sequence generator having $V_{ab} = 330 \angle 0^\circ V$. Find phase currents of load and line currents.

Sol: The load per phase is:
 $Z_{\Delta} = 20 - j15 = 25 \angle -36.87^\circ \Omega$.

Since $V_{AB} = V_{ab}$ the phase currents are:

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ A \checkmark$$

$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ A \checkmark$$

$$I_{CA} = I_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ A \checkmark$$

Line current: line current = $\sqrt{3}$ phase current. $\angle -30^\circ$.

$$I_a = I_{AB} \angle -30^\circ \cdot \sqrt{3} = (13.2 \angle 36.87^\circ)(\sqrt{3} \angle -30^\circ) = 22.86 \angle 6.87^\circ A \checkmark$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ A \checkmark$$

$$I_c = I_c \angle +120^\circ = 22.86 \angle 126.87^\circ A \checkmark$$

Q. 2.

A positive sequence, balanced Δ -connected source supplies a balanced Δ -connected load. If the impedance per phase of the load is $18 + j12 \Omega$ and $I_a = 9.609 \angle 35^\circ \text{ A}$, find I_{AB} and V_{AB} .

(9)

Sol:

we use formula: Line current = $\sqrt{3}$ phase current. $\angle -30^\circ$

$$I_{AB} = \frac{I_a}{\sqrt{3} \angle -30^\circ} = \frac{9.609 \angle 35^\circ}{\sqrt{3} \angle -30^\circ} = 5.57 \angle 65^\circ \checkmark$$

$$V_{AB} = I_{AB} \times Z_{\Delta} = 5.57 \angle 65^\circ \times (18 + j12)$$


$$= 5.57 \angle 65^\circ \times 21.6 \angle 33.69^\circ$$

$$V_{AB} = 120.3 \angle 98.69^\circ \checkmark$$

$\Delta \rightarrow Y$

Balanced Delta-Y Connection: A balanced Δ -Y system consists of balanced Δ connected source feeding a balanced Y connected load.

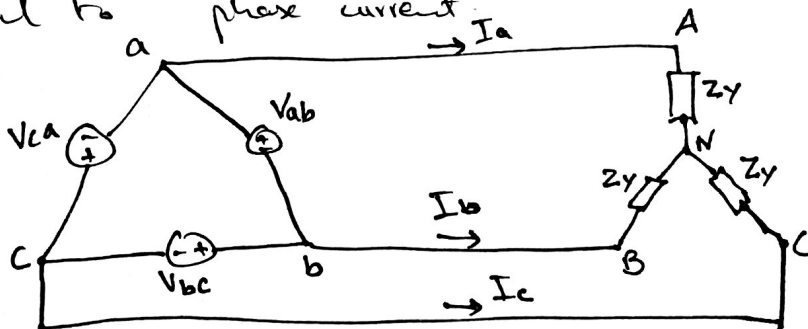- * The line voltage is equal to the phase voltage.
- * For load at Y-connection is: load current is equal to a phase current.




* First convert Δ source to Y source.

$$V_L = \sqrt{3} V_p \angle 30^\circ$$

$$V_p = \frac{V_L}{\sqrt{3} \angle 30^\circ}$$
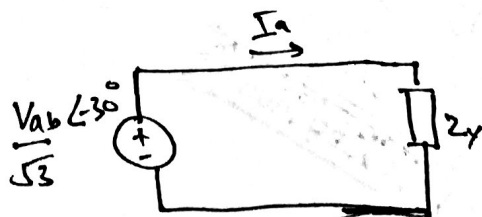
$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ$$



Equivalent single phase

Q-1: A balanced Y-connected load with a phase impedance of $40 + j25 \Omega$ is supplied by a balanced, positive sequence Δ -connected source with a line voltage of 210 V. Calculate the phase currents, use V_{ab} as a reference.


Sol:
 $Z_Y = 40 + j25 = 47.17 \angle 32^\circ \Omega$
 $V_{ab} = 210 \angle 0^\circ V$

When the Δ -connected source is transformed to a Y-connected source:

$$V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ = \frac{210 \angle 0^\circ}{\sqrt{3}} \angle -30^\circ$$

$$V_{an} = 121.2 \angle -30^\circ V$$

Now we can separate single phase network

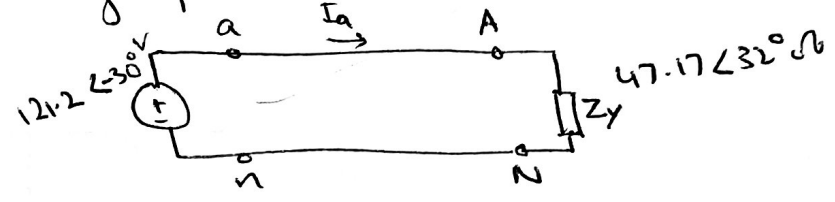

The line currents are:

$$I_a = \frac{V_{an}}{Z_Y} = \frac{121.2 \angle -30^\circ}{47.17 \angle 32^\circ}$$

$$I_a = 2.57 \angle -62^\circ A \checkmark$$

Similarly, $I_b = I_a \angle -120^\circ = 2.57 \angle -178^\circ A \checkmark$

$$I_c = I_a \angle 120^\circ = 2.57 \angle 58^\circ A \checkmark$$

The phase current: $I_P = I_L$

So, the phase current here will be same as line currents found above.


Q-2: In a balanced Δ -Y circuit, $V_{ab} = 240 \angle 15^\circ V$ and $Z_Y = (12 + j15) \Omega$. Calculate the line currents.

Sol: $Z_Y = (12 + j15) \Omega = 19.20 \angle 51.34^\circ \Omega$
 $V_{ab} = 240 \angle 15^\circ V$

Transform Δ source to Y source:
 $V_{an} = \frac{V_{ab}}{\sqrt{3}} \angle -30^\circ = \frac{240 \angle 15^\circ}{\sqrt{3}} \angle -30^\circ$

$$V_{an} = 138.56 \angle -15^\circ V$$

Now we separate single phase network:

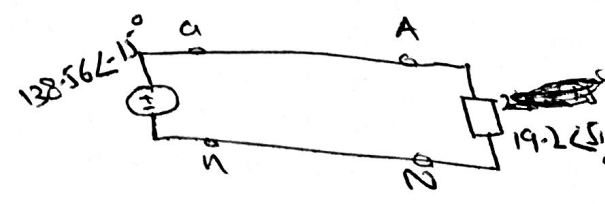

The line currents are:
 $I_a = \frac{V_{an}}{Z_Y} = \frac{138.56 \angle -15^\circ}{19.20 \angle 51.34^\circ} = 7.21 \angle -66.34^\circ A \checkmark$

$$I_b = I_a \angle -120^\circ = 7.21 \angle -186.34^\circ A \checkmark$$

$$I_c = I_a \angle 120^\circ = 7.21 \angle 53.66^\circ A \checkmark$$