

Chapter # 11.

⇒ AC Power Analysis:-

- ★ Instantaneous & Average Power
- ★ Max. Average Power Transfer
- ★ Effective or RMS value.
- ★ Apparent Power and Power Factor.
- ★ Complex Power.
- ★ Power Factor Correction.

→ Importance of Power:-

- * Electrical power is most efficiently generated, transmitted and distributed in ac form.
- * all electrical and electronic devices have certain power ratings
- * most common form of electric power is 50 or 60 Hz ac power

→ Instantaneous Power:-

- * "Instantaneous power (in watts) is the power at any instant of time"
- * "Instantaneous power $p(t)$ absorbed by an element is the product of the instantaneous voltage $v(t)$ across the element and the instantaneous current $i(t)$ through it". i.e.

$$p(t) = v(t)i(t)$$

- * Suppose the voltage and current at terminals of circuit be:
 $v(t) = V_m \cos(\omega t + \theta_v)$ → phase angles
 $i(t) = I_m \cos(\omega t + \theta_i)$ → amplitudes

- * The instantaneous power absorbed is:


$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\text{or } p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$p(t) =$ constant power + sinusoidal power (freq 2ω)

$$\because \cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

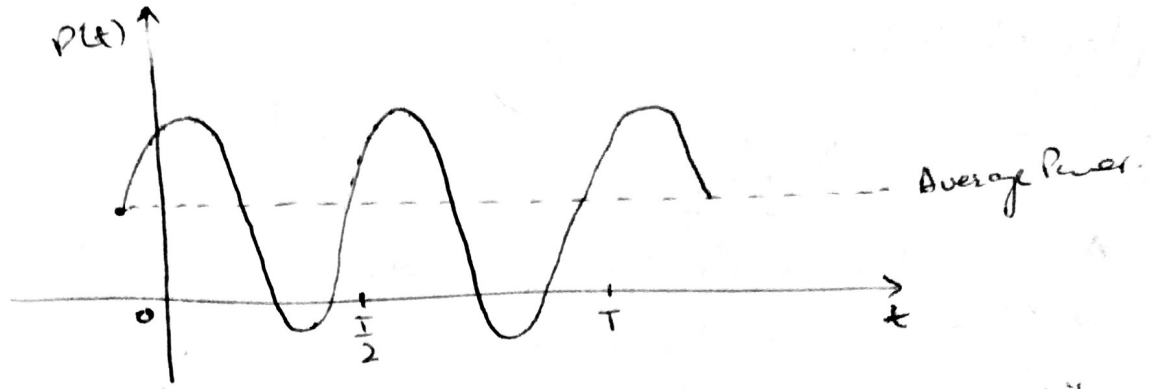- * when $P(t) > 0$ power is absorbed by circuit.
- * when $P(t) < 0$ " " " " source.



"instantaneous power $p(t)$ entering a circuit".

- * The instantaneous power changes with time, is therefore difficult to measure.

→ Average Power:-

- * "The average power (in watts) is the average of instantaneous power over one period".

$$p(t) = v(t) i(t) \quad \text{instantaneous power}$$

$$P = \frac{1}{T} \int_0^T p(t) dt \quad \text{Average power.}$$

$$v(t) = V_m \cos(\omega t + \theta_v) \quad , \quad i(t) = I_m \cos(\omega t + \theta_i)$$

$$\therefore P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt.$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + 0 \quad \text{--- } \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt = 0$$

$$\therefore P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

- * Now we take phasor forms of $v(t)$ and $i(t)$ as:

$$V(t) = V_m \cos(\omega t + \theta_v) \Rightarrow V = V_m \angle \theta_v$$

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow I = I_m \angle \theta_i$$

* Calculate P using phasor forms of v and i as: (2)

$$\frac{1}{2} VI^* = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i)$$

$$= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

* The real part above is same as we saw in P average power: S_0 ,

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

* Consider two cases: $\theta_v = \theta_i$ (voltage & current in phase)

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} I^2 R$$

means that for pure resistive load (circuit) absorbs power all the time.

* $\theta_v - \theta_i = \pm 90^\circ$. we have reactive load.

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

means a pure reactive load (circuit) absorbs no average power.

Exp 11.1: $v(t) = 120 \cos(377t + 45^\circ) \text{ V}$ and $i(t) = 10 \cos(377t - 10^\circ) \text{ A}$
find instantaneous and average power absorbed?

Soln: The instantaneous power is given by:

$$p = vi = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

$$p = 600 [\cos(754t + 35^\circ) + \cos 55^\circ]$$

$$\because \cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$$

$$p = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

\therefore find average power:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(10) \cos[45^\circ - (-10^\circ)]$$

$$P = 344.2 \text{ W}$$

is the constant part of 'p' instantaneous power.

PP 11.1
slide

$$v(t) = 80 \cos(10t + 20^\circ), \quad i(t) = 15 \sin(10t + 60^\circ)$$

find $p(t)$ and P ?

$$\begin{aligned} p(t) &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \\ &= \frac{1}{2} (80)(15) \cos(20^\circ - 60^\circ) + \frac{1}{2} (80)(15) \cos(20^\circ + 20^\circ + 60^\circ) \\ &= 600 \cos(-40^\circ) + 600 \sin(20^\circ + 80^\circ) \\ &= 600 \cos(40^\circ) + \end{aligned}$$

$$i(t) = 15 \sin(10t + 60^\circ)$$

$$= 15 \cos(10t - 30^\circ)$$

$$p(t) = \frac{1}{2} (80)(15) \cos(50^\circ) + \frac{1}{2} (80)(15) \cos(20t - 10^\circ)$$

$$= 600 \cos(50^\circ) + 600 \cos(20t - 10^\circ)$$

$$= 385.7 + 600 \cos(20t - 10^\circ) \text{ W}$$

Now we find instantaneous power as:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} (80)(15) \cos(20^\circ + 30^\circ)$$

$$= 600 \cos(50^\circ)$$

$$P = 385.7 \text{ W} \quad \text{average power.}$$

PP 11.1
Book

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V}, \quad i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

find $p(t) = ?$, $P = ?$

$$i(t) = 33 \sin(10t + 60^\circ) = 33 \cos(10t - 30^\circ)$$

$$p(t) = \frac{1}{2} (330)(33) \cos(-50^\circ) + \frac{1}{2} (330)(33) \cos(20t - 10^\circ)$$

$$= 5445 \cos(-50^\circ) + 5445 \cos(20t - 10^\circ)$$

$$= 3499.97 + 5445 \cos(20t - 10^\circ) \text{ W}$$

$$\text{Average power } P = \frac{1}{2} (330)(33) \cos(+50^\circ)$$

$$= 3499.97 \text{ W}$$

Exp 11.2: Calculate average power absorbed by an impedance $Z = 30 - j70 \Omega$ when voltage $V = 120 \angle 0^\circ$. (3)

Solution: The current through the impedance is:

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ}$$

$$I = 1.576 \angle 66.8^\circ \text{ A}$$

The average power is $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

$$P = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ)$$

$$P = 37.24 \text{ W}$$

Exp 11.2: Solve $I = 33 \angle 30^\circ$, $Z = 40 \angle -22^\circ \Omega$. Find P .

$$I = \frac{V}{Z} \Rightarrow V = IZ = 33 \angle 30^\circ \cdot 40 \angle -22^\circ$$

$$V = 1320 \angle 8^\circ$$

and avg. power $P = \frac{1}{2} (1320)(33) \cos(8^\circ - 30^\circ)$

$$= 21780 \cos(-22^\circ)$$

$$P = 20194.06 \text{ W}$$

Exp 11.3: Find avg. power supplied by source and average power absorbed by resistor.

Solution: Current I is given by:

$$I = \frac{5 \angle 30^\circ}{4 - j2} = \frac{5 \angle 30^\circ}{4.472 \angle -26.57^\circ}$$

$$I = 1.118 \angle 56.57^\circ \text{ A}$$

The average power supplied by source is:

$$P = \frac{1}{2} (5)(1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$

The current through resistor is:


$$I_R = I = 1.118 \angle 56.57^\circ \text{ A}$$

and voltage across it is

$$V_R = 4I_R = 4.472 \angle 56.57^\circ \text{ V}$$

The average power absorbed is
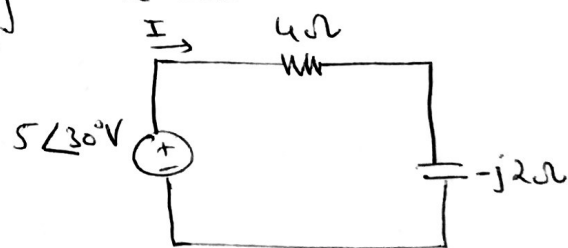
$$P = \frac{1}{2} V_m I_m = \frac{1}{2} (4.472)(1.118) = 2.5 \text{ W}$$




same

PP11.3: Find avg. power absorbed? by resistor and inductor? Find power supplied?

Solution:
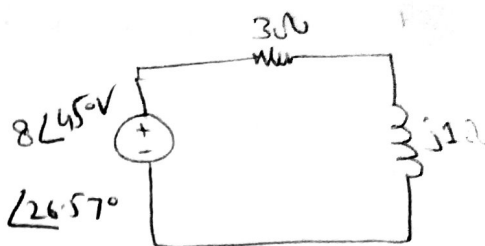
$$I = \frac{V}{Z} = \frac{8 \angle 45^\circ}{3 + j} = \frac{8 \angle 45^\circ}{3.16 \angle 18.43^\circ} = 2.53 \angle 26.57^\circ$$



Current I_R across the resistor is:

$$I_R = I = 2.53 \angle 26.57^\circ \text{ A}$$

Voltage V_R across the resistor is:

$$V_R = I_R R = (2.53 \angle 26.57^\circ) 3$$

$$V_R = 7.59 \angle 26.57^\circ$$

So power absorbed by resistor is:

$$P_R = \frac{1}{2} V_m I_m = \frac{1}{2} (7.59)(2.53) = 9.6 \text{ W}$$

Now we solve for current across inductor is:

$$I_L = I = 2.53 \angle 26.57^\circ \text{ A}$$

$$\begin{aligned} 0_v - 0_i \\ 26.57 - 26.57 \\ = 0 \end{aligned}$$

Voltage V_L across the inductor is:

$$V_L = I_L \cdot j = 2.53 \angle 26.57^\circ \cdot j$$

$$\therefore j = \angle 90^\circ$$

$$V_L = 2.53 \angle 26.57^\circ + 90^\circ$$

$$V_L = 2.53 \angle 116.57^\circ \text{ V}$$

So the power absorbed by inductor is:

$$\begin{aligned} P_L &= \frac{1}{2} V_m I_m \cos(0_v - 0_i) \\ &= \frac{1}{2} (2.53)^2 \cos(90^\circ) = 0 \text{ W} \end{aligned}$$

The average power supplied is:

$$P = \frac{1}{2} (8)(2.53) \cos(45^\circ - 26.57^\circ) = 9.6 \text{ W}$$

Exp 11.4 - Find average power generated by each source and the average power absorbed by each passive element.

Solution:

we apply mesh analysis.

For mesh 1,

$$I_1 = 4A$$

For mesh 2,

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0$$

$$j5I_2 = -60\angle 30^\circ + j10I_1$$

$$j5I_2 = -60\angle 30^\circ + j40$$

$$I_2 = \frac{-60\angle 30^\circ}{j5} + \frac{j40}{j5}$$

$$I_2 = -12\angle -60^\circ + 8 = -12(\cos(60^\circ) + j\sin(60^\circ)) + 8$$

$$= -12(0.5 + j(-0.866)) + 8 = -6 + j10.392 + 8$$

$$I_2 = -6 + 10.392j + 8 = 2 + 10.392j$$

$$I_2 = 10.58\angle 79.1^\circ A$$

For the voltage source, the current flowing from it is $I_2 = 10.58\angle 79.1^\circ A$ and the voltage across it is $60\angle 30^\circ V$.

So the average power is:

$$P_5 = \frac{1}{2} (60)(10.58)\cos(30^\circ - 79.1^\circ) = 207.8W$$

According to PSC this average power is absorbed by the source i.e circuit is delivering average power to source.

For the current source the current through it is

$I_1 = 4\angle 0^\circ$ and the voltage across it is:



$$V_1 = 20I_1 + j10(I_1 - I_2) = 80 + j10(4 - 2 - j10.392)$$

$$V_1 = 183.9 + j20 = 184.984\angle 6.21^\circ V$$

The average power supplied by current source is:

$$P_1 = -\frac{1}{2} (184.984)(4)\cos(6.21^\circ - 0^\circ) = -367.8W$$

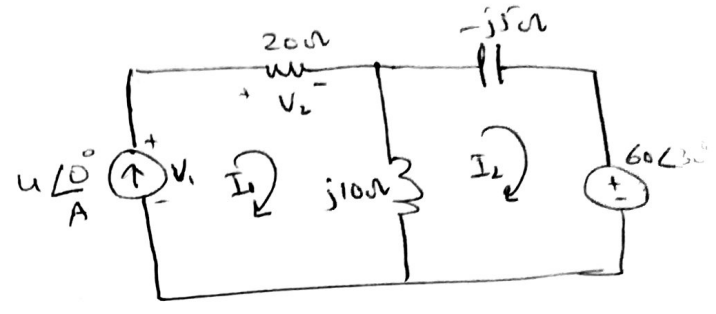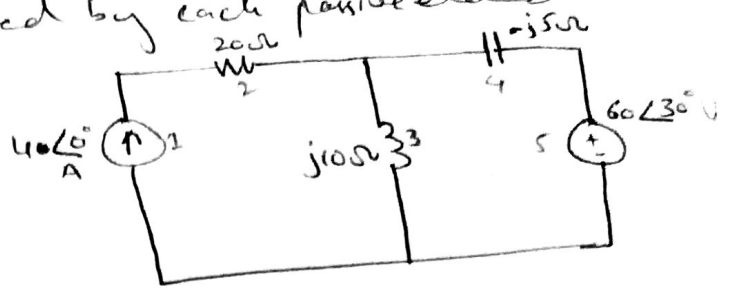It is -ve because the current source is supplying power to circuit.



For the resistor, the current through it is $I_1 = 4 \angle 0^\circ$
and the voltage across resistor is:

$$V_R = I_1 R = (20)(4 \angle 0^\circ) = 80 \angle 0^\circ \text{ V.}$$

average Power absorbed by resistor is:

$$P_2 = \frac{1}{2}(80)(4) = 160 \text{ W}$$

For the capacitor:

$$\text{current} = I_2 = 10.58 \angle 79.1^\circ \text{ A}$$

$$\begin{aligned} \text{voltage} = V_C &= I_2 (-j5) = (5 \angle -90^\circ)(10.58 \angle 79.1^\circ) \\ &= 52.9 \angle 79.1^\circ - 90^\circ \end{aligned}$$

average Power absorbed by Capacitor is:

$$P_4 = \frac{1}{2}(52.9)(10.58) \cos(-90^\circ) = 0$$

For the inductor:

$$\text{Current} = I_1 - I_2 = 4 - 2 - j10.39 = 2 - j10.39 \text{ A} = 10.58 \angle -79.1^\circ$$

$$\text{Voltage } V_L = (I_1 - I_2)j10 = (10.58 \angle -79.1^\circ)(j10)$$

$$V_L = 105.8 \angle -79.1^\circ + 90^\circ \text{ volt.}$$

Average power absorbed by inductor is:

$$P_3 = \frac{1}{2}(105.8)(10.58) \cos(90^\circ) = 0$$

So, finally we have noticed that capacitor and inductor have absorbed 0 W average power.

$$\text{Total Power supplied} + \text{Total power absorbed} = 0$$


$$0 + 0 + -367.8 + 160 + 207.8 = 0$$

PP 11.4
Solve

Find power absorbed by each element in circuit.

(5)

Solution.

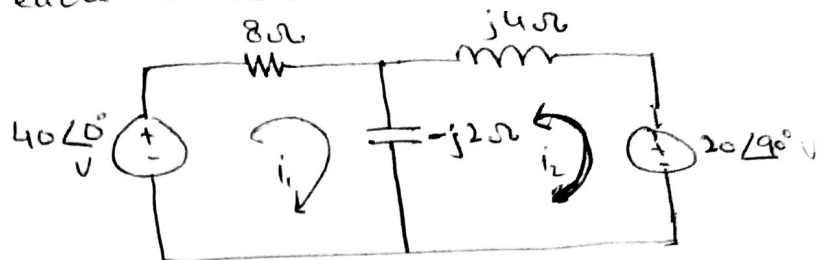

Mesh 1:

$$-40 + (8 - j2)I_1 + (-j2)I_2 = 0$$

$$-40 + 8I_1 - j2I_1 - j2I_2 = 0$$

$$-20 + 4I_1 - jI_1 - jI_2 = 0$$

$$(4 - j)I_1 - jI_2 = 20$$

Mesh 2:

$$-j20 + j4I_2 - j2(I_2 + I_1) = 0$$

$$-j20 + 4jI_2 - j2I_2 - j2I_1 = 0$$

$$-j20 + (4j - j2)I_2 - j2I_1 = 0$$

$$-j20 + 2jI_2 - j2I_1 = 0$$

$$-j10 + jI_2 - jI_1 = 0$$

$$-jI_1 + jI_2 = j10$$

Convert the above eq. to matrix form.

$$\begin{bmatrix} 4-j & -j \\ -j & +j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \\ j10 \end{bmatrix}$$

$$\Delta = 2 + j4, \quad \Delta_1 = -10 + j20, \quad \Delta_2 = 10 + j60$$

$$I_1 = \frac{\Delta_1}{\Delta} = 5 \angle 53.14^\circ \quad \text{and} \quad I_2 = \frac{\Delta_2}{\Delta} = 13.6 \angle 17.11^\circ$$

For $40 \angle 0^\circ$ source: $V_s = 40 \angle 0^\circ$ and $I_1 = 5 \angle 53.14^\circ$

$$P_s = -\frac{1}{2} (40)(5) \cos(-53.14^\circ) = -60 \text{ W}$$

For $20 \angle 90^\circ$ source: $V_s = 20 \angle 90^\circ$, $I_2 = 13.6 \angle 17.11^\circ$

$$P_s = -\frac{1}{2} (20)(13.6) \cos(90^\circ - 17.11^\circ) = -40 \text{ W}$$

For resistor: $I = I_1 = 5 \angle 53.14^\circ$
 $V = I \cdot R = 5 \angle 53.14^\circ \times 8 = 40 \angle 53.14^\circ$

The average power absorbed is:

$$P = \frac{1}{2} \operatorname{Re}\{V I^*\} = \frac{1}{2} 5 \times 40 = 100 \text{ W.}$$

The average power absorbed by inductor and capacitor is zero.