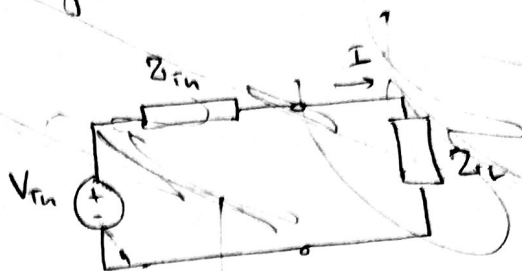


# ★ Max. Average Power Transfer

- \* We studied that to deliver max. power transfer to a load we use Thevenin theorem and that  $R_L = R_{Th}$ .
- \* now we see this concept for ac circuits.
- \* Consider below:



Circuit with ac load.



Thevenin equivalent circuit.

- \* load is represented by  $Z_L$ .
- \* Rectangular form of Thevenin Impedance and load impedance is  $Z_{Th}$  and  $Z_L$ .

$$Z_{Th} = R_{Th} + jX_{Th} \quad , \quad Z_L = R_L + jX_L$$

- \* The current through load is:

$$I = \frac{V_{Th}}{Z_{Th} + Z_L} = \frac{V_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$

- \* The average power delivered to load is:

$$P = \frac{1}{2} |I|^2 R_L$$

$$z = (R_{Th} + R_L) + j(X_{Th} + X_L)$$

$$|z| = \sqrt{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$|z|^2 = (R_{Th} + R_L)^2 + (X_{Th} + X_L)^2$$

$$P = \frac{R_L}{2} \cdot \frac{|V_{Th}|^2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \quad \text{--- (1)}$$

- \* ~~For~~ Objective is to adjust load parameters  $R_L$  and  $X_L$  to deliver max. P. So.

- \* So we take  $\frac{\partial P}{\partial X_L}$  and set it to zero.

$$\frac{\partial P}{\partial X_L} = \frac{|V_{Th}|^2}{2} \frac{\partial}{\partial R_L} \left( \frac{R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \right)$$

$$= \frac{|V_{Th}|^2}{2} \left( \frac{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 \cdot (0)) - (R_L)(2(0) + 2(X_{Th} + X_L)(1+0))}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \right)$$

$$= \frac{V_{Th}^2}{2} \left( - \frac{R_L (2X_{Th} + 2X_L)}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \right)$$

$$= \frac{-V_{Th}^2 R_L (X_{Th} + X_L)}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \quad \text{when set} = 0$$

So  $X_{Th} = -X_L$  — (a)

\* Solving  $\frac{\partial P}{\partial R_L}$  is:

$$\frac{\partial P}{\partial R_L} = \frac{V_{Th}^2}{2} \frac{\partial}{\partial R_L} \left( \frac{R_L}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2} \right)$$

$$= \frac{V_{Th}^2}{2} \left( \frac{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - R_L (2(R_{Th} + R_L)(0 + 1) + (0))}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \right)$$

$$= \frac{V_{Th}^2}{2} \left( \frac{R_{Th}^2 + R_L^2 + 2R_{Th}R_L + X_{Th}^2 + X_L^2 + 2X_{Th}X_L - 2R_L R_{Th} - 2R_L^2}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \right)$$

$$= \frac{V_{Th}^2}{2} \left( \frac{R_{Th}^2 - R_L^2 + (X_{Th} + X_L)^2}{((R_{Th} + R_L)^2 + (X_{Th} + X_L)^2)^2} \right) \quad \text{we set it} = 0$$

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2} \quad \text{--- (5)}$$

\* From selected

(a) and (5) we conclude <sup>for max. power transfer.</sup> that  $Z_L$  must be so that  $X_L = -X_{Th}$  and  $R_L = R_{Th}$  i.e.,

$$Z_L = R_L + jX_L = R_{Th} - jX_{Th} = Z_{Th}^*$$

\* So if we put  $R_L = R_{Th}$  and  $X_L = -X_{Th}$  in eq (1):

$$P_{max} = \frac{V_{Th}^2}{8R_{Th}} \quad \checkmark$$




\* Increase when load is purely real i.e.  $X_L = 0$  and eq (5)

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = |Z_{Th}| \quad \checkmark \quad \text{for resistive load.}$$

$R_L = |Z_{Th}|$

Exp-11.5: Find  $Z_L$  and  $P_{max}$ .

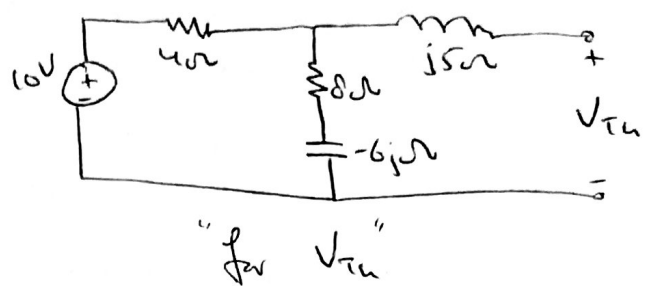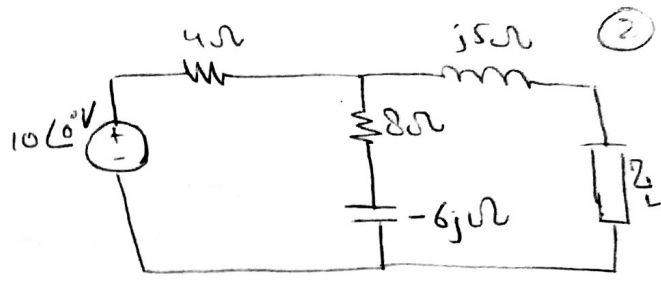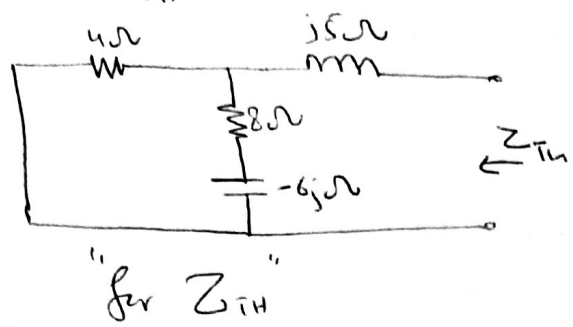Solution: First of all we find  $Z_{TH}$  and  $V_{TH}$ .



$Z_{TH}$ :

$$Z_{TH} = j5 + 4 \parallel (8 - j6)$$

$$= j5 + \frac{4(8 - j6)}{4 + 8 - j6} = j5 + \frac{32 - 24j}{12 - j6} = 2.933 + j4.467 \Omega$$


$V_{TH}$ :

$$V_{TH} = 10 \left( \frac{8 - j6}{4 + 8 - j6} \right)$$

by voltage division

$$= \left( \frac{8 - j6}{12 - j6} \right) 10$$
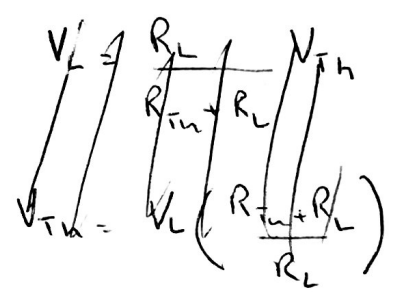
$$= \frac{80 - j60}{12 - j6} = 7.454 \angle -103^\circ V$$



As per conditions that for max. power transfer.  $Z_L = Z_{TH}^*$  so  $Z_L = 2.933 - j4.467 \Omega$ .

To find max. power transfer we use formula:

$$P_{max} = \frac{V_{TH}^2}{8R_{TH}} = \frac{(7.454)^2}{8(2.933)} = 2.368 W.$$

PP-11.5 slide: Find  $Z_L$  and  $P_{max}$ :



Soln: First  $Z_{TH}$  and  $V_{TH}$

$Z_{TH}$ :

$$Z_{TH} = 5 \parallel (8 - 4j + 10j)$$

$$= 5 \parallel (8 + 16j)$$
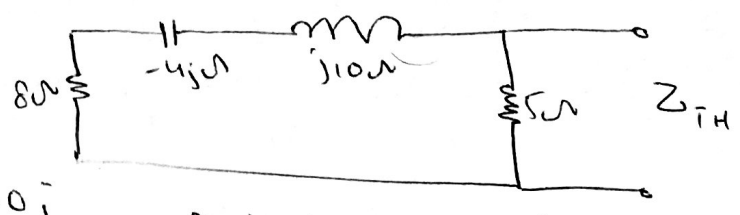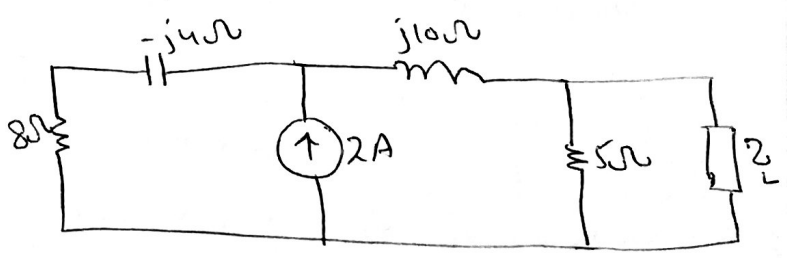
$$= \frac{(5)(8 + j6)}{5 + 8 + j6} = \frac{40 + 30j}{13 + j6} = 3.415 + j0.7317$$



For max Power transfer:  $Z_L = Z_{TH}^* = 3.415 - j0.7317$

$V_{TH}$  Apply mesh analysis to loop 1.

$$-2(8) + 2(j4) = 0$$

$$-2(8) + (-2+j2)i_1 = 0$$

$$-16 - 4i_1 + 2j i_1 = 0$$

$$i_1(8-j4) + i_2(5+j10) = 0 \Rightarrow 13 + j6 = 0$$

$$i_2 = i_1 + 2$$

$$i_1(8+j4) + (i_1+2)(5+j10) = 0$$

$$8i_1 + i_1j4 + 5i_1 + i_1j10 + 10 + 20j = 0$$

$$10 + 13i_1 + i_1j14 + 20j = 0 \Rightarrow i_1(13+j14) = -10 - 20j$$

$$i_1 = \frac{-10 - 20j}{13+j14}$$

Using current division

$$I = \frac{8-j4}{8-j4+j10+5} (2) = \frac{16-j8}{13+j6}$$


$$V_{TH} = 5I = 5 \left( \frac{16-j8}{13+j6} \right) = 6.25 \angle -51.34^\circ$$

$P_{max}$ :  $P_{max} = \frac{|V_{TH}|^2}{8R_{TH}} = \frac{(6.25)^2}{8(3.415)} = 1.429 \text{ W}$

Exp: 11.6 Find  $R_L$  and  $P_{max}$ .

Sol:  $Z_{TH}$ :  $Z_{TH} = (40-j30) \parallel j20$
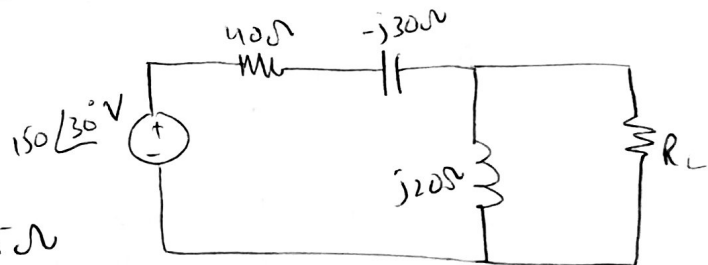
$$= \frac{j20(40-j30)}{j20+40-j30} = 9.412 + j22.35 \Omega$$



$V_{TH}$ : By voltage division.

$$V_{TH} = \frac{j20}{j20+40-j30} (150 \angle 30^\circ) = 72.76 \angle 134^\circ \text{ V}$$

purely resistive load

Value of  $R_L$  that will absorb max average power is:

$$R_L = |Z_{TH}| = \sqrt{(9.412)^2 + (22.35)^2} = 24.25 \Omega \quad R_L = \sqrt{R_{TH}^2 + X_{TH}^2}$$

The current through load is:


$$I = \frac{V_{TH}}{Z_{TH} + R_L} = \frac{72.76 \angle 134^\circ}{33.66 + j22.35} = 1.8 \angle 100.42^\circ \text{ A}$$

The max. average power absorbed by  $R_L$  is:

$$P_{max} = \frac{1}{2} |I|^2 R_L = \frac{1}{2} (1.8)^2 (24.25) = 39.29 \text{ W}$$

PP-116: Find  $R_L$  and  $P_{max}$

slide  
book

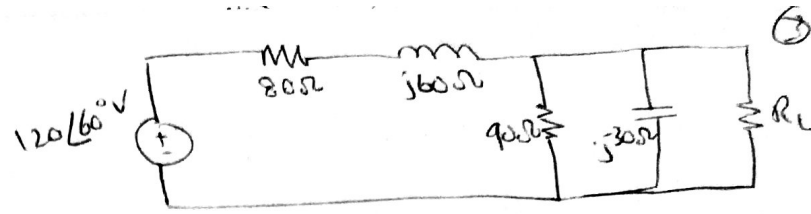

Sol:  $Z_{Th} = ?$

$$Z_1 = 80 + j60 \quad \text{and} \quad Z_2 = 90 \parallel -j30 = \frac{(90)(-j30)}{90 - j30} = 9 - j27$$

$$Z_{Th} = Z_1 \parallel Z_2 = \frac{(80 + j60)(9 - j27)}{80 + j60 + 9 - j27} = 17.181 - j24.57 \Omega$$

$V_{Th} = ?$

$$V_{Th} = \frac{Z_2 (120 \angle 60^\circ)}{Z_1 + Z_2} = \frac{9 - j27}{89 + j33} \angle 120 \angle 60^\circ$$

$$V_{Th} = 35.98 \angle -31.91^\circ$$

$$R_L = |Z_{Th}| = \sqrt{(17.181)^2 + (24.57)^2} = 30 \Omega$$

The current through load is:

$$I = \frac{V_{Th}}{Z_{Th} + R_L} = \frac{35.98 \angle -31.91^\circ}{30 + 17.181 - j24.57} = \frac{35.98 \angle -31.91^\circ}{47.181 - j24.57}$$

$$I = 0.6764 \angle -4.4^\circ \text{ A}$$

The max. average power absorbed by  $R_L$  is:

$$P_{max} = \frac{1}{2} |I|^2 R_L = \frac{1}{2} (0.6764)^2 (30) = 6.863 \text{ W}$$

Effective Value or RMS Value:-

\* We find effective value to measure the effectiveness of voltage or current source in delivering power to the a resistive load.

\* "Effective value of a periodic signal is its root mean square (rms) value".

\* Find  $I_{eff}$ ?

\* The average power absorbed by resistor in ac circuit is:



$$P = \frac{1}{T} \int_0^T i^2 R dt$$

∴ average Power  
⇒  $P = \frac{1}{T} \int_0^T P(t) dt$

$$P = \frac{R}{T} \int_0^T i^2 dt \quad \text{--- (a)}$$

\* Power absorbed by resistor in dc circuit.

$$P = I_{eff}^2 R \quad \text{--- (b)}$$

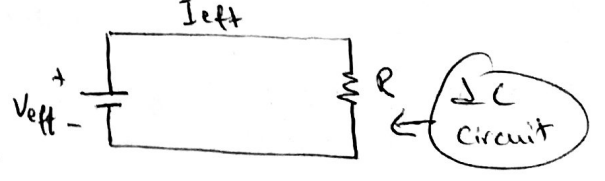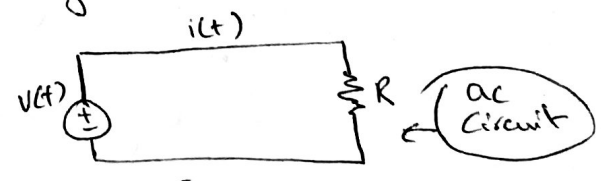

\* Equating both (a) and (b)

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

\* Similarly  $V_{\text{eff}}$  can be found as:

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

\* above means that "eff" value is the square root of the average of the periodic signal. So we can write:

$$I_{\text{eff}} = I_{\text{rms}} \quad , \quad V_{\text{eff}} = V_{\text{rms}}$$

\* Suppose sinusoidal signal  $i(t) = I_m \cos \omega t$ , so it's  $I_{\text{rms}}$ :

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt} \quad \text{"Double angle identity"}$$

$$= \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos 2\omega t) dt} \quad * \quad \because \cos^2(x) = \frac{1}{2} [1 + \cos(2x)]$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \quad (\text{for sinusoidal signals})$$

Similarly for  $v(t) = V_m \cos \omega t$ ,

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \quad (\text{for sinusoidal signal}).$$

\* So the average power can now be written as:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

\* Similarly average power absorbed by resistor  $R$  is

$$P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$

$$= \frac{I_{\text{rms}}^2 \int_0^T 1 dt + \int_0^T \cos 2\omega t dt}{2\pi} \quad *$$

$$= \frac{I_{\text{rms}}^2 t \Big|_0^{2\pi} + 0}{2(2\pi)}$$

$$= \frac{I_{\text{rms}}^2 (2\pi)}{4\pi}$$


$$= \frac{I_{\text{rms}}^2}{2}$$

Exp 11.7 Find  $I_{rms}$ ,  $R = 2\Omega$ .  
 $P = ?$

Soln:  $T = 4$ .

Current waveform  $i(t)$  is:
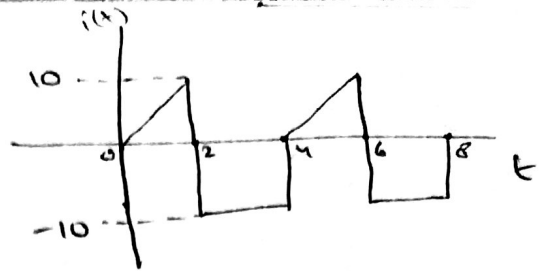
$$i(t) = \begin{cases} 5t & 0 < t < 2 \\ -10 & 2 < t < 4 \end{cases}$$



The rms value is:

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]}$$

$$= \sqrt{\frac{1}{4} \left[ 25 \frac{t^3}{3} \Big|_0^2 + 100t \Big|_2^4 \right]} = \sqrt{\frac{1}{4} \left( \frac{200}{3} + 200 \right)}$$

$$I_{rms} = 8.165 \text{ A}$$

The power absorbed by resistor ( $2\Omega$ ) is:


$$P = I_{rms}^2 R =$$

$$(8.165)^2 (2) = 133.3 \text{ W}$$

Pop 11.8 Find  $I_{rms} = ?$ ,  $P_R = ?$

Slide:  $R = 9\Omega$ ,  $T = 2$
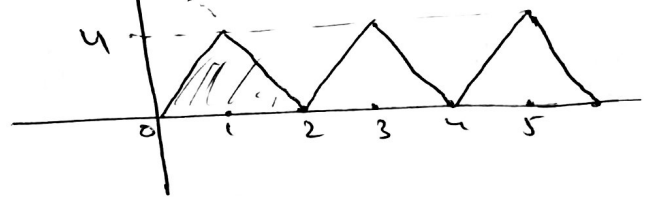
$$i(t) = \begin{cases} 4t & 0 < t < 1 \\ 8-4t & 1 < t < 2 \end{cases}$$



$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = \sqrt{\frac{1}{2} \left[ \int_0^1 (4t)^2 dt + \int_1^2 (8-4t)^2 dt \right]}$$

$$= \sqrt{\frac{16}{2} \left[ \int_0^1 t^2 dt + \int_1^2 (4-4t+t^2) dt \right]} = \sqrt{8 \left[ \frac{1}{3} t^3 \Big|_0^1 + (4t - 2t^2 + \frac{t^3}{3}) \Big|_1^2 \right]}$$

$$= \sqrt{\frac{16}{3}} = 2.309 \text{ A}$$

$$P = I_{rms}^2 R = 48 \text{ W}$$


$m = \frac{y_2 - y_1}{x_2 - x_1}$   
 $m = \frac{4 - 0}{1 - 0} = 4$   
 $y = mx + c \Rightarrow$  (line eq. formula)  
 $y = 4t$   $\rightarrow$  intersection.  
 $\rightarrow m = \frac{0 - 4}{2 - 1} = -\frac{4}{1} = -4$   
 $y = mx + c = -4t + c$   
 and  $c = 8$   
 So  $y = -4t + 8$

$$\begin{cases} 4t & 0 < t < 1 \\ -4t + 8 & 2 < t < 3 \end{cases}$$

Ex 11.8:  $V_{rms} = ?$ ,  $R = 10 \Omega$ ,  $P_R = ?$

$$T = 2\pi$$
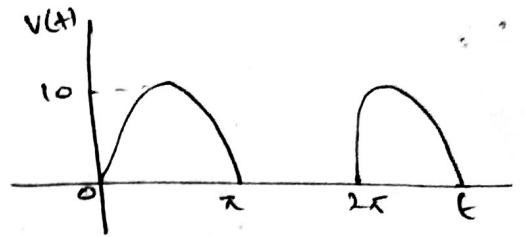
$$v(t) = \begin{cases} 10 \sin t, & 0 < t < \pi \\ 0, & \pi < t < 2\pi \end{cases}$$



$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2\pi} \left[ \int_0^{\pi} (10 \sin t)^2 dt + \int_{\pi}^{2\pi} 0^2 dt \right]$$

As,  $\sin^2 t = \frac{1}{2} (1 - \cos 2t)$ , Hence.

$$\begin{aligned} V_{rms}^2 &= \frac{1}{2\pi} \int_0^{\pi} \frac{100}{2} (1 - \cos 2t) dt = \frac{50}{2\pi} \left( t - \frac{\sin 2t}{2} \right) \Big|_0^{\pi} \\ &= \frac{50}{2\pi} \left( \pi - \frac{1}{2} \sin 2\pi - 0 \right) = 25 \text{ V} \end{aligned}$$


$$V_{rms} = 5 \text{ V}$$

$$\text{and } P = \frac{V_{rms}^2}{R} = \frac{(5)^2}{10} = 2.5 \text{ W.}$$

AP 11.8.  $V_{rms} = ?$ ,  $R = 6 \Omega$ ,  $P_R = ?$

$$T = \pi$$

$$v(t) = 8 \sin(t), \quad 0 < t < \pi$$

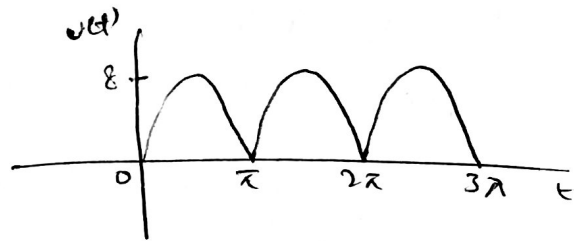

$$\begin{aligned} V_{rms}^2 &= \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^{\pi} (8 \sin(t))^2 dt \\ &= \frac{64}{\pi} \int_0^{\pi} \frac{1}{2} [1 - \cos 2t] dt = 32. \end{aligned}$$

$$V_{rms} = 5.657 \text{ V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{32}{6} = 5.333 \text{ W.}$$