

LAB NO: 02**IMPLEMENTATION OF A SERIES DC CIRCUIT****OBJECTIVE:**

THEORY:**KIRCHHOFF'S VOLTAGE LAW (KVL):**

Kirchhoff's Voltage Law (KVL) states that the algebraic sum of the voltages across any set of branches in a closed loop is zero.

$$\sum_{k=1}^n V_k = 0$$

SERIES DC CIRCUIT:

Series circuits are sometimes called *current-coupled* or *daisy chain-coupled*. The current in a series circuit goes through every component in the circuit. Therefore, all of the components in a series connection carry the same current. There is only one path in a series circuit in which the current can flow. The formula to search resistance in series is $R_s = R_1 + R_2 + R_3 \dots R_n$. The voltage across each of the components is the same, and the total current is the sum of the currents through each component.

CURRENT:

$$I = I_1 = I_2 = I_3 = \dots = I_r$$

In a series circuit the current is the same for all of elements.

RESISTOR:

The total resistance of resistors in series is equal to the sum of their individual resistances:

$$R_{\text{total}} = R_1 + R_2 + \dots + R_n$$

VOLTAGE:

The total voltage in the circuit is sum of all the voltages across each of the component.

$$V_{\text{total}} = V_1 + V_2 + V_3 + \dots + V_n$$

SCHEMATIC DIAGRAM

Figure 2.1: Series DC Circuit

PROCEDURE:

CALCULATIONS:

| Points | I Theoretical | I Measured |
|---------------|----------------------|-------------------|
| A. | | |
| B. | | |
| C. | | |

Table 2.1

| Points | V Theoretical | V Measured |
|---------------|----------------------|-------------------|
| V_{R1} | | |
| V_{R2} | | |
| V_{R3} | | |
| V_{AC} | | |

Table 2.2

CONCLUSION:

POST LAB QUESTIONS:

1. Is KVL verified in this experiment?

2. What is the relation between resistance and current in the circuit?

3. Why the value of current is same in a series circuit?

Teacher Remarks:

Obtained Marks: _____ / 10