

Department of Electrical Engineering
Sessional Assignment

Course Details

Course Title: Linear Circuit Analysis

Semester: Summer-20

Instructor: _____

Total Marks: 20

Student Details

Name: _____

Student ID: _____

Q1.	Briefly explain the following terms: a) Maximum Power Transfer Theorem b) Millman's Theorem c) Super Node d) RMS value e) Maximum Value f) Active and Passive elements	Marks 20
------------	---	-----------------