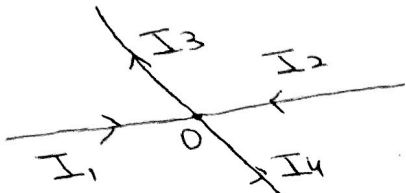


(5)

Kirchoff's Law:-

In 1847, a German Physicist, Kirchoff, formulated two fundamental laws of electricity. These laws are:-

i) Kirchoff's current Law (KCL):-



The algebraic sum of all the current meeting at a junction is always zero.

$$\sum I \text{ at junction point} = 0$$

"The total current flowing towards a junction point is equal to the total current flowing away from the junction point."

Sign convention:-
 currents flowing towards a junction is assumed to be +ve
 while currents flowing away from a junction point is assumed to be -ve

Consider the above junction point (O). At this junction point. Suppose $I_1 = 2A$, $I_2 = 4A$ and $I_3 = 1A$ and if we want to determine I_4 then applying KCL at O:-


$$I_1 + I_2 - I_3 - I_4 = 0$$

$$I_4 = I_1 + I_2 - I_3$$

$$I_4 = 2 + 4 - 1 = \boxed{5A}$$

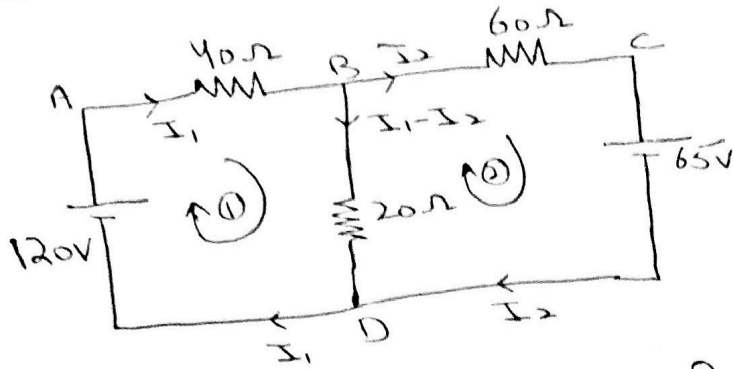Example 1:-

In the network shown below, Find the magnitude of current by KVL & KCL (mesh current method). ①



Applying KVL on mesh ABDA,

$$120 - 40I_1 - 20(I_1 - I_2) = 0$$

$$120 - 40I_1 - 20I_1 + 20I_2 = 0$$

$$120 = 60I_1 - 20I_2 \quad \text{--- ①}$$

Applying KVL on mesh BCDB:-

$$-60I_2 - 65 + 20(I_1 - I_2) = 0$$

$$-60I_2 - 65 + 20I_1 - 20I_2 = 0$$

$$-80I_2 - 65 + 20I_1 = 0$$

$$-65 = -20I_1 + 80I_2 \quad \text{--- ②}$$

Solving eqn ① & ② by determinant method:-

$$\text{determinant} = \begin{vmatrix} 60 & -20 \\ -20 & 80 \end{vmatrix}$$

$$= 4800 - 400 = \boxed{4400}$$


$$I_1 = \frac{\begin{vmatrix} 120 & -20 \\ -65 & 80 \end{vmatrix}}{4400} = \frac{(120)(80) - (-65)(-20)}{4400}$$

$$\boxed{I_1 = 1.886A}$$

$$I_2 = \frac{\begin{vmatrix} 60 & 120 \\ -20 & -65 \end{vmatrix}}{4400} = \frac{(60)(-65) - (-20)(120)}{4400}$$

$$I_2 = \frac{-1500}{4400} = \boxed{-0.341A}$$

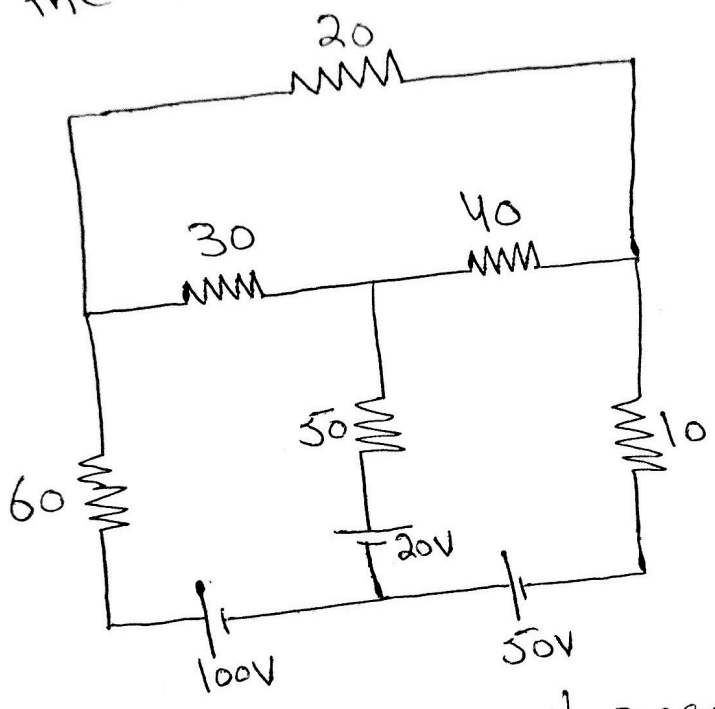
Example 2:- calculate the currents in each branch of the ckt shown below:-



(Solved on next page)

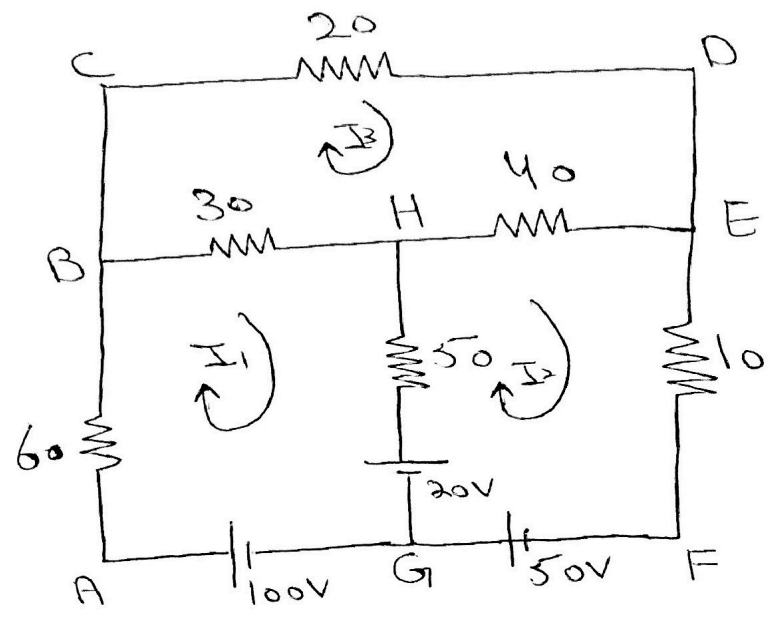Example 2:-

Calculate the current in each mesh of the ckt shown below:-



Solⁿ:- mesh ABHGA:-

Applying KVL, we have:-

$$-60I_1 - 30(I_1 - I_3) - 50(I_1 - I_2) - 20 + 100 = 0$$

$$140I_1 - 50I_2 - 30I_3 = 80$$

dividing by 10:-

$$14I_1 - 5I_2 - 3I_3 = 8 \quad \text{--- (1)}$$

mesh GHEFG:-

Applying KVL, we have,

$$20 - 50(I_2 - I_1) - 40(I_2 - I_3) - 10I_2 + 50 = 0$$

$$-50I_1 + 100I_2 - 40I_3 = 70 \quad \text{--- (2)}$$

$$-5I_1 + 10I_2 - 4I_3 = 7$$

Mesh BCDEHB:-

Applying KVL, we have:-

$$-20I_3 - 40(I_3 - I_2) - 30(I_3 - I_1) = 0$$

$$30I_1 + 40I_2 - 90I_3 = 0$$

$$3I_1 + 4I_2 - 9I_3 = 0$$

By determinant method:-


$$14I_1 - 5I_2 - 3I_3 = 8$$

$$-5I_1 + 10I_2 - 4I_3 = 7$$

$$3I_1 + 4I_2 - 9I_3 = 0$$

$$\Rightarrow I_1 = 1.65 \text{ A}, I_2 = 2.12 \text{ A}, I_3 = 1.5 \text{ A}$$

Example 3:-

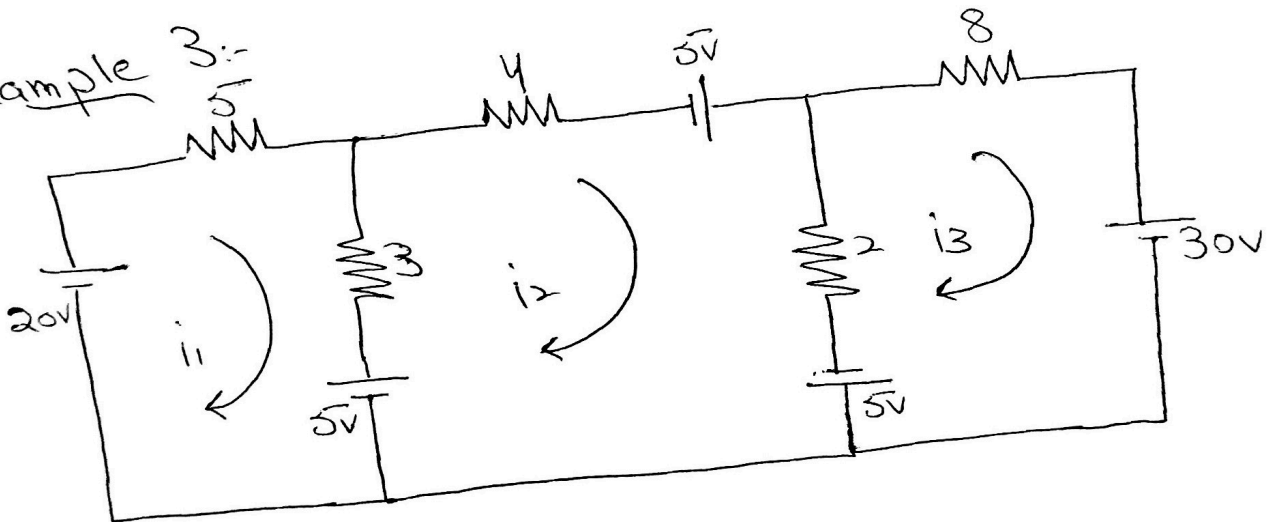

$$20 - 5I_1 - 3(I_1 - I_2) - 5 = 0$$

$$20 - 5I_1 - 3I_1 + 3I_2 - 5 = 0$$

$$-8I_1 + 3I_2 + 15 = 0 \quad \text{--- (1)}$$

on and mesh:-

$$-4I_2 + 5 - 2(I_2 - I_3) + 5 + 5 - 3(I_2 - I_1) = 0$$

$$-4I_2 + 15 - 2I_2 + 2I_3 - 3I_2 + 3I_1 = 0$$

$$3I_1 - 9I_2 + 2I_3 + 15 = 0$$

(P.T.O)

KVL on 3rd mesh:-

$$-5 - 2(I_3 - I_2) - 8I_3 - 30 = 0$$

$$-5 - 2I_3 + 2I_2 - 8I_3 - 30 = 0$$

$$+2I_2 - 10I_3 - 35 = 0$$

$$\Rightarrow -8I_1 + 3I_2 + 0I_3 = -15 \quad \text{--- (1)}$$

$$3I_1 - 9I_2 + 2I_3 = -15 \quad \text{--- (2)}$$

$$0I_1 + 2I_2 - 10I_3 = 35 \quad \text{--- (3)}$$

$$\boxed{I_1 = 2.56A}$$

$$\boxed{I_2 = 1.82A}$$

$$\boxed{I_3 = -3.13A}$$