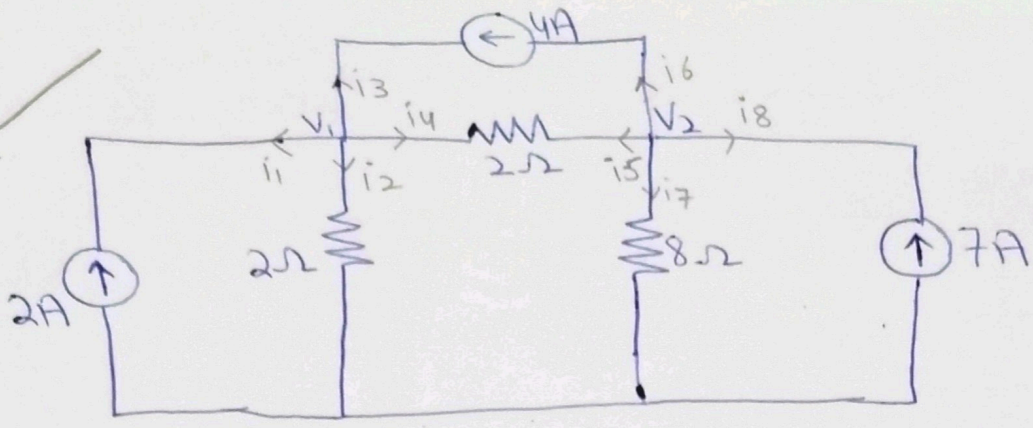


Q3:-



Soln:-  $i_1 + i_2 + i_3 + i_4 = 0$

$$(-2) + \left(\frac{V_1 - V_0}{2}\right) + (-4) + \left(\frac{V_1 - V_2}{2}\right) = 0$$

$$-2 + \frac{V_1}{2} - 4 + \frac{V_1 - V_2}{2} = 0$$

$$\frac{-4 + V_1 - 8 + V_1 - V_2}{2} = 0$$

$$2V_1 - V_2 = 12 \quad \text{--- (1)}$$

$i_5 + i_6 + i_7 + i_8 = 0$

$$\left(\frac{V_2 - V_1}{2}\right) + (4) + \left(\frac{V_2 - V_0}{8}\right) + (-7) = 0$$

$$\frac{V_2 - V_1}{2} + 4 + \frac{V_2}{8} - 7 = 0$$

$$\frac{4V_2 - 4V_1 + 32 + V_2 - 56}{8} = 0$$

$$-4V_1 + 5V_2 = 24 \quad \text{--- (2)}$$


$$-4V_1 + 5V_2 = 24 \quad \text{--- (2)}$$

$$4V_1 - 2V_2 = 24 \quad \text{--- (1)}$$

\*2

$$\frac{4V_1 - 2V_2 = 24}{3V_2 = 48} \Rightarrow V_2 = 16V \quad \text{put in (1)}$$
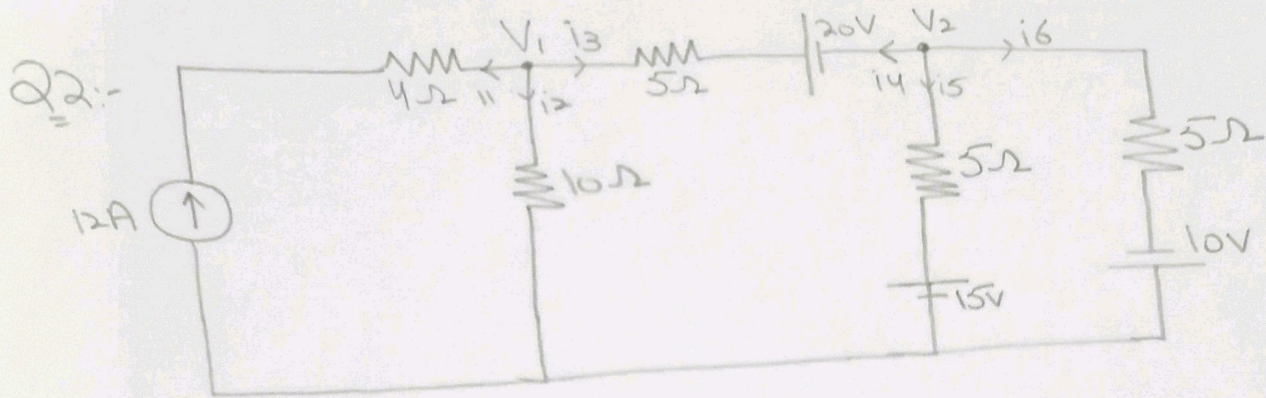
$$\text{(1)} \Rightarrow 2V_1 - 16 = 12 \Rightarrow 2V_1 = 28 \Rightarrow V_1 = 14V$$



Sol<sup>n</sup>:-

$$i_1 + i_2 + i_3 = 0$$

$$(-12) + \left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1 - 20 - V_2}{5}\right) = 0$$

$$\frac{-120 + V_1 + 2V_1 - 40 - 2V_2}{10} = 0$$

$$3V_1 - 2V_2 = 160 \quad \text{--- (1)}$$

$$i_4 + i_5 + i_6 = 0$$

$$\left(\frac{V_2 + 20 - V_1}{5}\right) + \left(\frac{V_2 - 15}{5}\right) + \left(\frac{V_2 + 10}{5}\right) = 0$$

$$V_2 + 20 - V_1 + V_2 - 15 + V_2 + 10 = 0$$

$$-V_1 + 3V_2 + 15 = 0$$

$$-V_1 + 3V_2 = -15 \quad \text{--- (2)}$$

$$3V_1 - 2V_2 = 160 \quad \text{--- (1)}$$

$$-3V_1 + 9V_2 = -45 \quad \text{--- (2) } \times 3$$

$$7V_2 = 115$$

$$V_2 = 16.42V \quad \text{put in (2)}$$

$$\text{(2)} \Rightarrow -V_1 + 49.28 = -15$$


$$-V_1 = -64.28$$

$$\Rightarrow V_1 = 64.28V$$

# Thevenin's Theorem :-



Find the current in  $8\Omega$  resistor using Thevenin's Theorem.

Step 1 :-

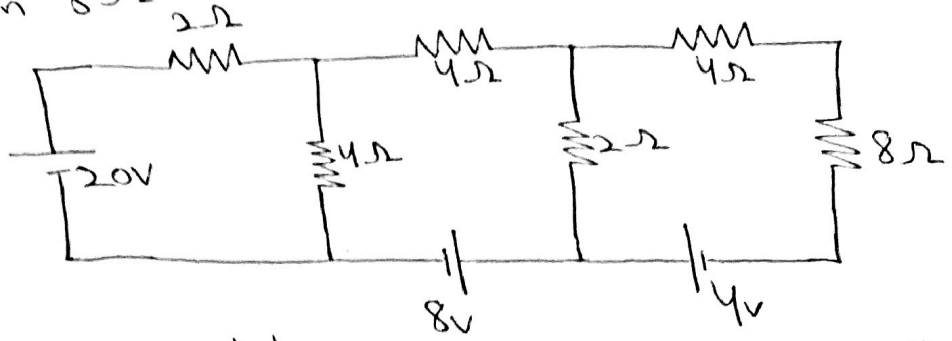


The resistor in which we want to find current is denoted by  $R_L$ . Remove  $R_L$  and mark the

terminals A & B.

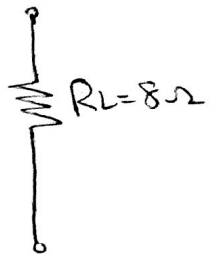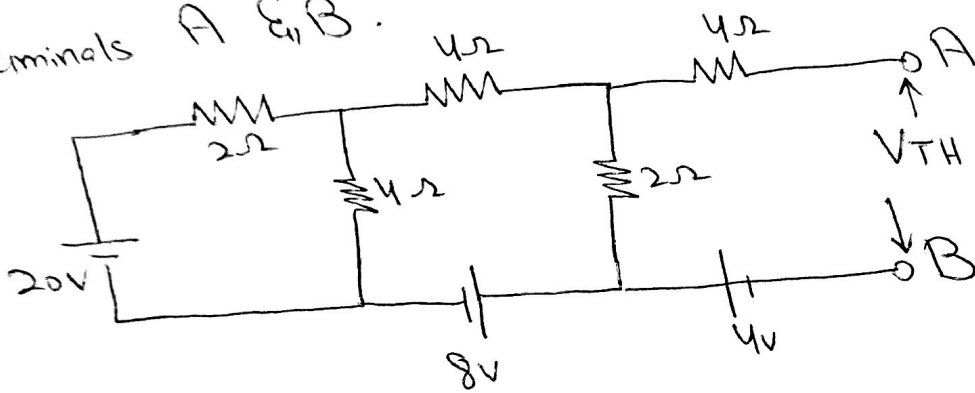

Step 2 :-

distribute currents in each mesh :-

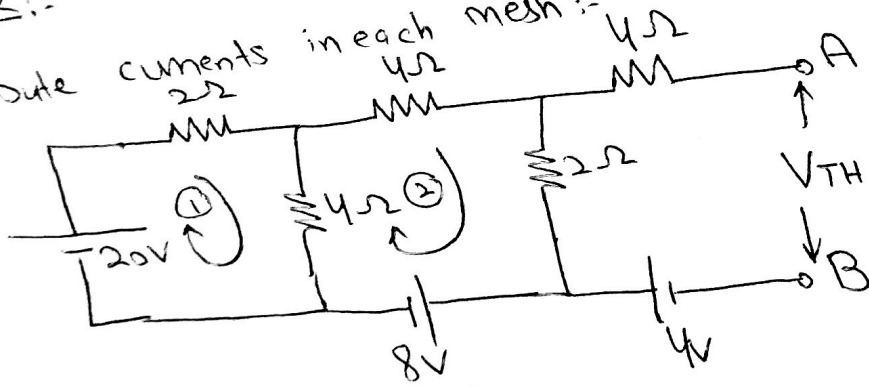

Applying KVL on mesh ① :-

$$20 - 2I_1 - 4(I_1 - I_2) = 0$$

$$20 - 2I_1 - 4I_1 + 4I_2 = 0 \Rightarrow -6I_1 + 4I_2 = -20 \quad \text{--- ①}$$

Applying KVL on mesh ② :-

$$-4I_2 - 2I_2 - 8 - 4(I_2 - I_1) = 0$$

$$-6I_2 - 8 - 4I_2 + 4I_1 = 0$$

$$4I_1 - 10I_2 = 8 \quad \text{--- ②}$$

$$\left\{ \begin{array}{l} I_1 = 3.81 \text{ A} \\ I_2 = 0.72 \text{ A} \end{array} \right.$$


by solving eq ① & ②:

$$I_1 = 3.81A \quad I_2 = 0.72A$$

Step 3:

Find  $V_{TH}$  (open ckt voltage across points A & B).

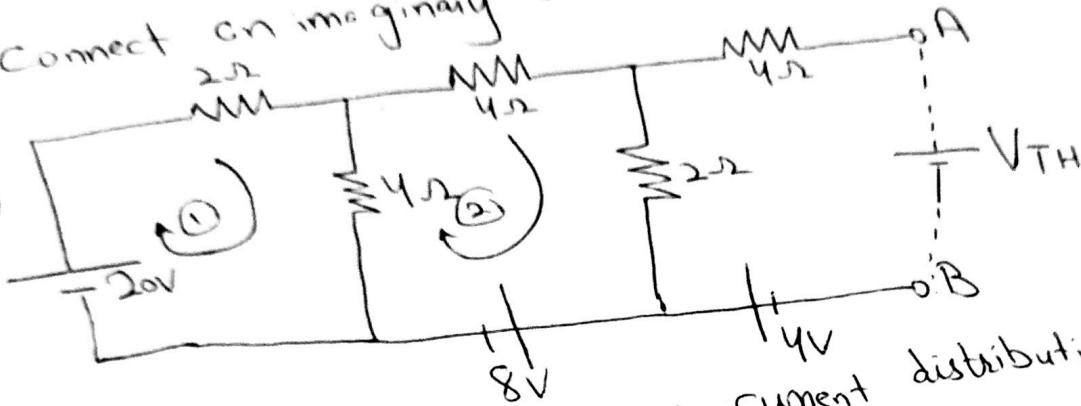Connect an imaginary source ( $V_{TH}$ ) to terminals A & B.



(Note: Take the previous current distribution):

$$-V_{TH} + 4 - 2I_2 = 0$$


$$V_{TH} = 4 - 2(0.72) \Rightarrow V_{TH} = 4 - 1.44$$



$$V_{TH} = 2.56V$$

Step 4:

Find  $R_{TH}$  (total resistance of the ckt)


→ Finish all the voltage sources.

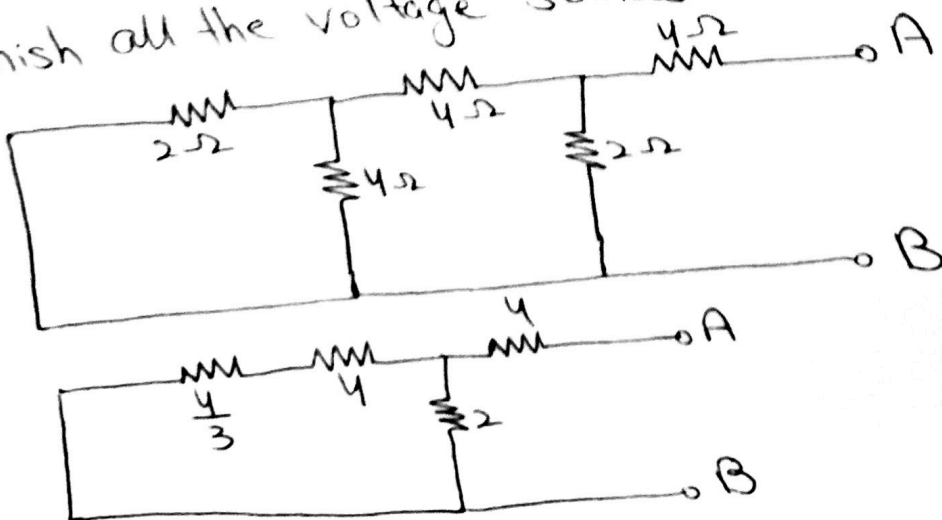

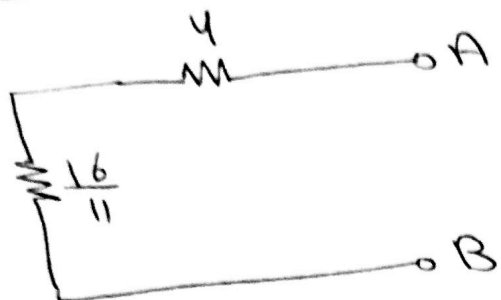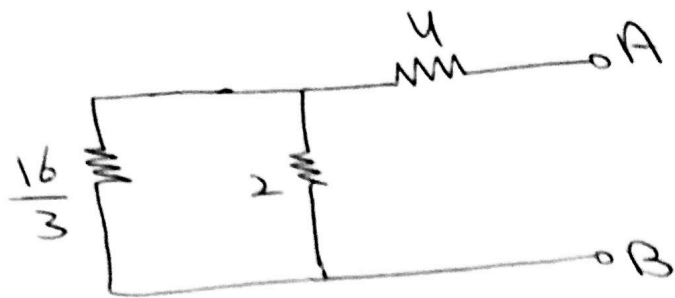

$$R_{TH} = 5.45 \Omega$$


Step 5:-

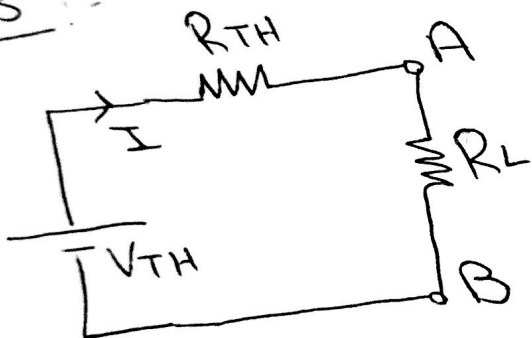



$$I = \frac{V_{TH}}{R_{TH} + R_L} = \frac{2.56}{5.45 + 8}$$

$$I = \frac{2.56}{13.45} = \boxed{0.19A}$$

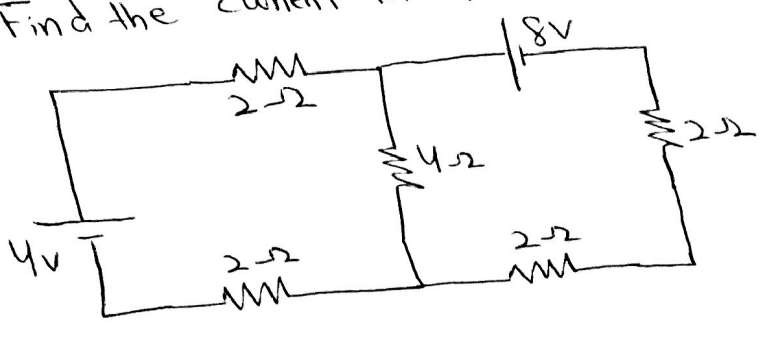
Q2:- Find the current in  $4\Omega$  resistor using Thevenin's Theorem:-



Step 1 :-

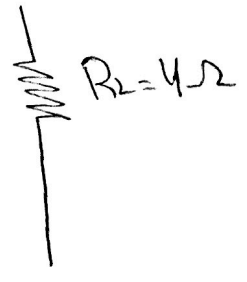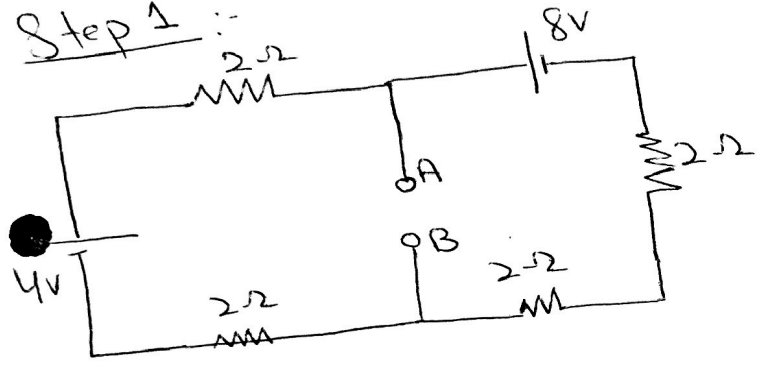

Step 2:-

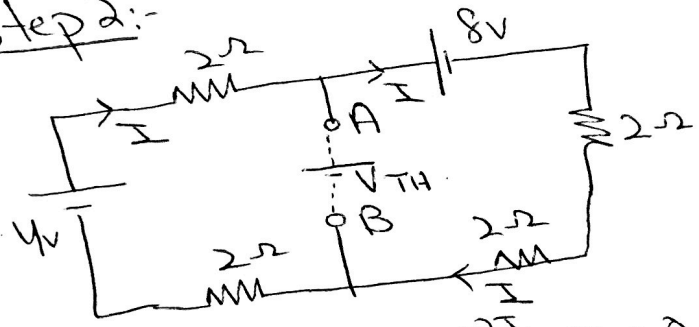


$$4 - 2I - 8 - 2I - 2I = 0$$

$$-8I - 4 = 0$$

$$I = -\frac{4}{8} \Rightarrow \boxed{I = -\frac{1}{2} \text{ A}}$$

Step 3 :-

Find  $V_{TH}$

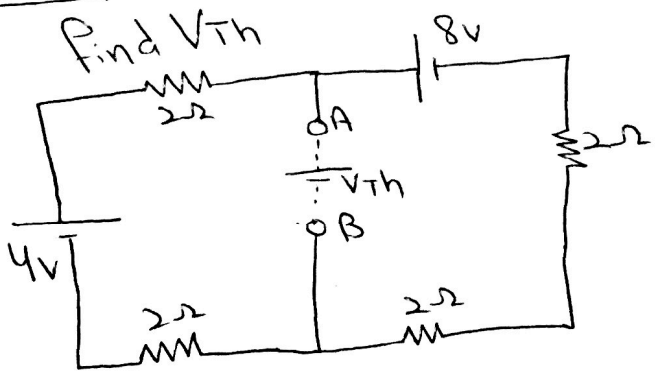

$$4 - 2I - V_{TH} - 2I = 0$$


$$V_{TH} = -4I + 4$$

$$V_{TH} = -4\left(-\frac{1}{2}\right) + 4$$

$$V_{TH} = 2 + 4 = 6 \text{ V}$$


Step 4:-

Finding  $R_{th}$

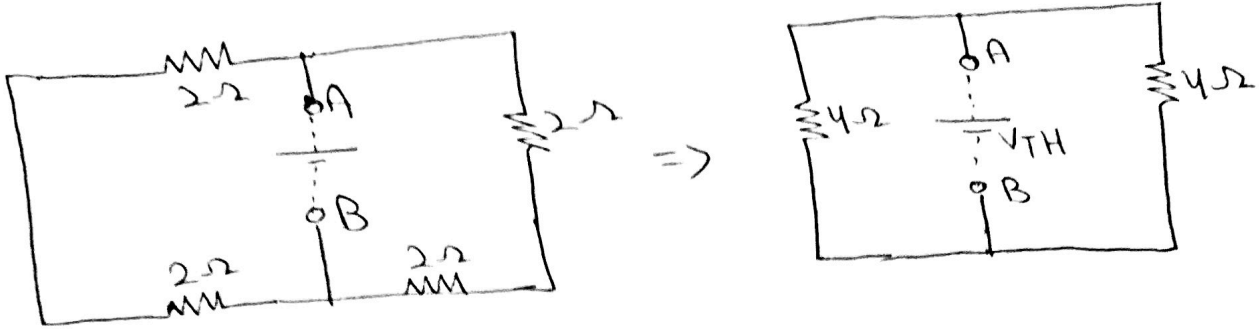

$$R_{TH} = \frac{4 \times 4}{4 + 4} = \frac{16}{8} \Rightarrow \boxed{R_{TH} = 2\Omega}$$

Step 5:-

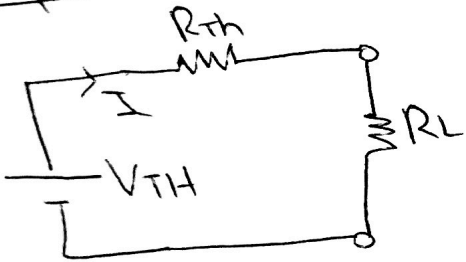

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{6}{2 + 4} = \boxed{1A} \quad \underline{\underline{\text{Ans:-}}}$$