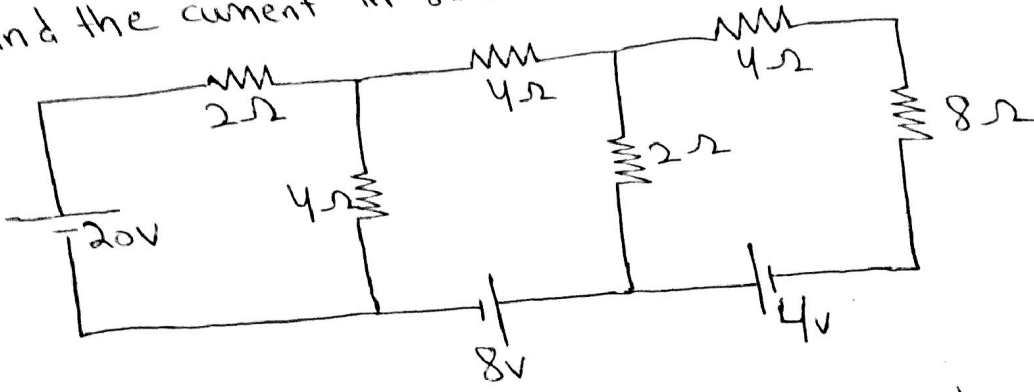




Norton's Theorem:-

Find the current in 8Ω resistor using Norton's Theorem.




Step No 1:-

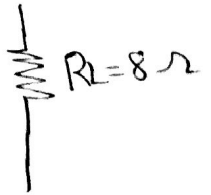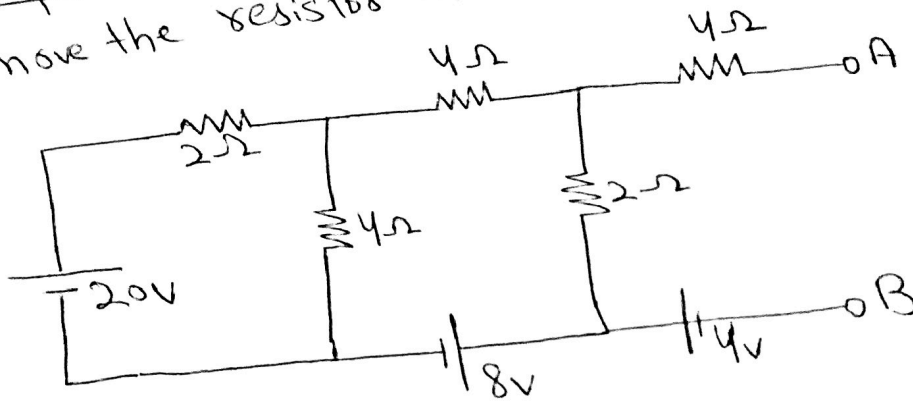Remove the resistor in which you want to find the current:-



Step 2:-

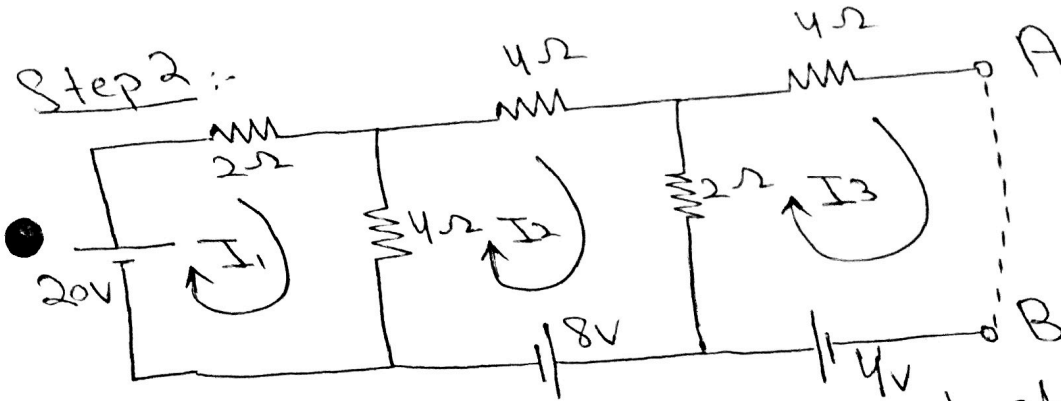

→ Place a temporary short circuit at points A & B and find current in that shorted path.

KVL on loop 1:-

$$20 - 2I_1 - 4(I_1 - I_2) = 0$$

$$20 - 2I_1 - 4I_1 + 4I_2 = 0$$

$$-6I_1 + 4I_2 = -20 \quad \text{--- (1)}$$

KVL on loop 2 :-

$$-4I_2 - 2(I_2 - I_3) - 8 - 4(I_2 - I_1) = 0$$

KVL on loop 3 :-

$$-4I_3 + 4 - 2(I_3 - I_2) = 0$$

$$-4I_3 + 4 - 2I_3 + 2I_2 = 0$$

$$2I_2 - 6I_3 = -4 \quad \text{--- (3)}$$

Solving by calculator :-



$$I_1 =$$



$$I_2 =$$

$$I_N = I_3 =$$


Step 3 :-
Find R_N (equivalent resistance)

→ Short all V sources :-

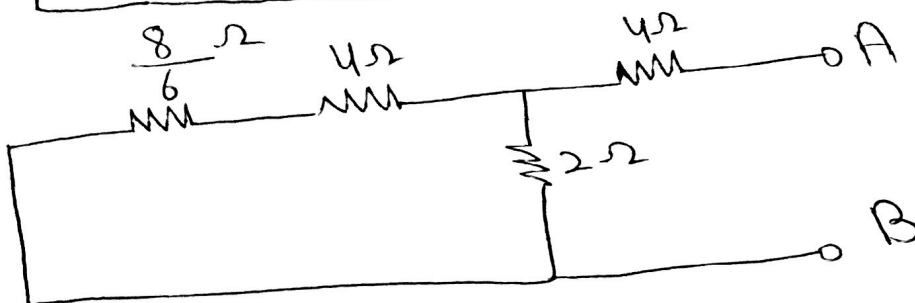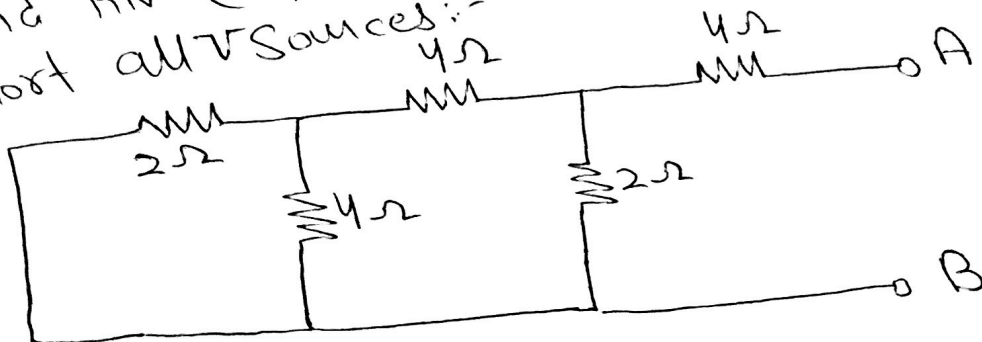

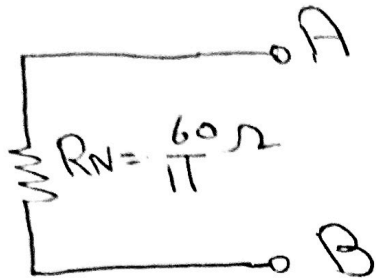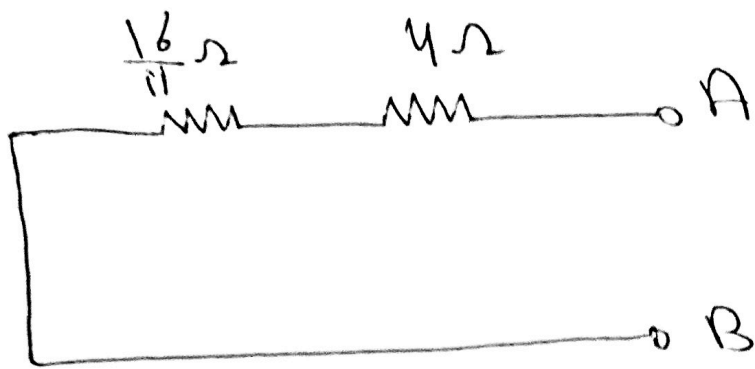

Step 4 :-

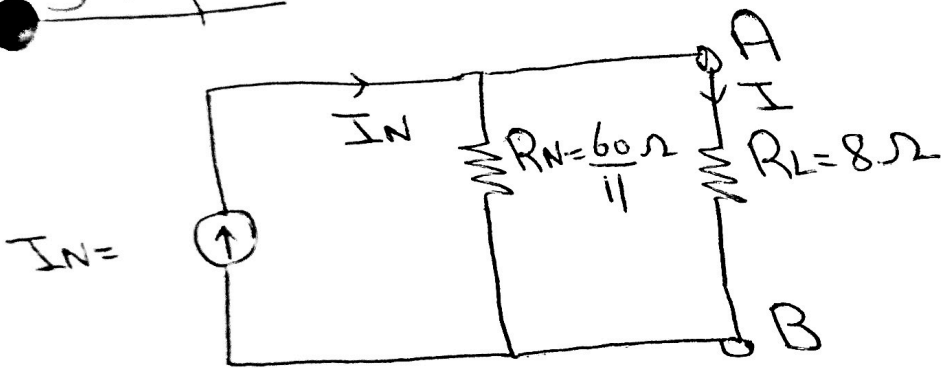

$$I = I_N \left(\frac{R_N}{R_N + R_L} \right)$$


Superposition Theorem:-

Steps:-

- 1) Identify the branch and quantity (V, I, P etc) calculated along with the presence of more than 1 active source.
- 2) Consider any 1 source and replace the remaining by their internal resistances.
- 3) Calculate the required electrical quantity for that particular source.
- 4) Repeat the last 2 steps for all the active sources.
- 5) Algebraic sum of all these individual source will be the final value of required electrical quantity for all the sources working together.

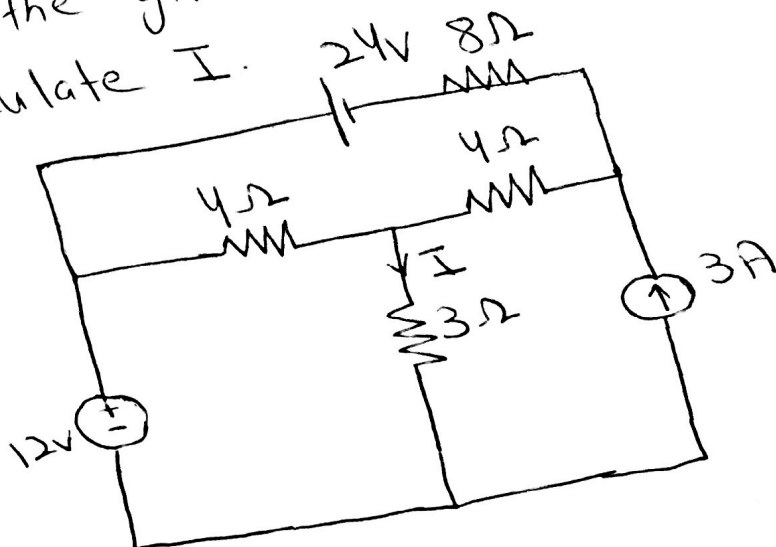
Example 1:-

For the given ckt, using the superposition theorem, calculate I .



Solution:-

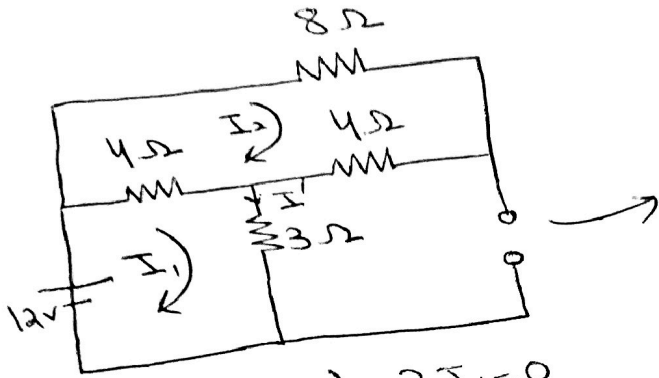There are 3 active sources in the given network.
 Taking 12V source and replacing all the other active sources by their internal resistances:-



{ The current source is replaced by an open circuit b/c its internal R is infinite }


1st mesh: $12 - 4(I_1 - I_2) - 3I_1 = 0$
 $-4I_1 + 4I_2 - 3I_1 = -12$
 $-7I_1 + 4I_2 = -12$ — (1)

2nd mesh:- $-8I_2 - 4I_2 - 4(I_2 - I_1) = 0$
 $-8I_2 - 4I_2 - 4I_2 + 4I_1 = 0$
 $4I_1 - 16I_2 = 0$ — (2)

By solving the above 2 eqs:-
 $I_1 = 2A$ & $I_2 = 0.5A$

As $I' = I_1$
 So $I'(12V) = 2A$

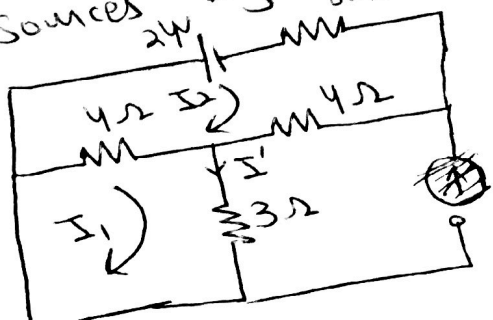Now taking 24V source and replacing all the other active sources by their internal resistances:-



For mesh ①:-

$$-4(I_1 - I_2) - 3I_1 = 0$$

$$-4I_1 + 4I_2 - 3I_1 = 0$$

$$-7I_1 + 4I_2 = 0 \quad \text{--- (1)}$$

For mesh ②:-

$$-24 - 8I_2 - 4I_2 - 4(I_2 - I_1) = 0$$

$$-24 - 8I_2 - 4I_2 - 4I_2 + 4I_1 = 0$$

$$4I_1 - 16I_2 = 24 \quad \text{--- (2)}$$

By solving eqⁿ ① & eqⁿ ②


$$I_1 = -1A$$

$$I_2 = -1.75A$$

As $I'(24V) = I_1$

Hence $I'(24V) = -1A$

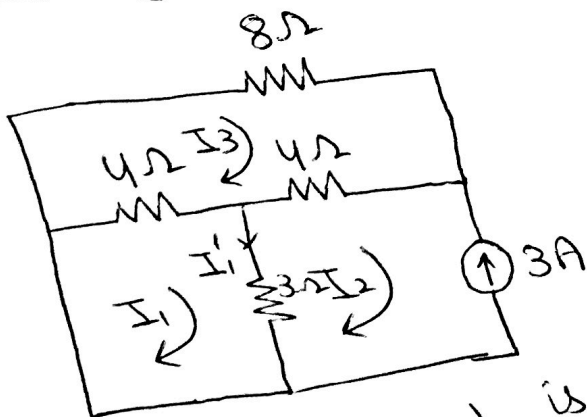Now 3A source E_1 replacing all the other active sources by their internal resistances:-



In mesh ②, current is given i.e. $I_2 = -3A$

now Applying KVL in mesh ①:-

$$-4(I_1 - I_3) - 3(I_1 - I_2) = 0$$

$$-4I_1 + 4I_3 - 3I_1 + 9 = 0$$

$$-7I_1 + 4I_3 = 9 \quad \text{--- (1)}$$

Now Applying in mesh (3)

$$-8I_3 - 4(I_3 - I_2) - 4(I_3 - I_1) = 0$$

$$-8I_3 - 4I_3 + 4I_2 - 4I_3 + 4I_1 = 0$$

$$4I_1 + 4I_2 - 16I_3 = 0$$

$$4I_1 + 4(-3) - 16I_3 = 0$$

$$4I_1 - 16I_3 = 12 \quad \text{--- (2)}$$

By solving eq (1) & (2)

$$\Rightarrow I_1 = -2A \quad \text{Eq.} \quad I_3 = -1.25A$$

As $I'_{(3A)}$ $I_1 - I_2$

(I_3 is written first b/c I' is in direction of I_1)


$$I'_{(3A)} = (-2 + 3) = \boxed{1A}$$

$$I_{\text{total}} = I'_1 + I'_2 + I'_3$$


$$= 2 - 1 + 1$$

$$\boxed{I_{\text{total}} = 2A} \quad \text{Ans:-}$$

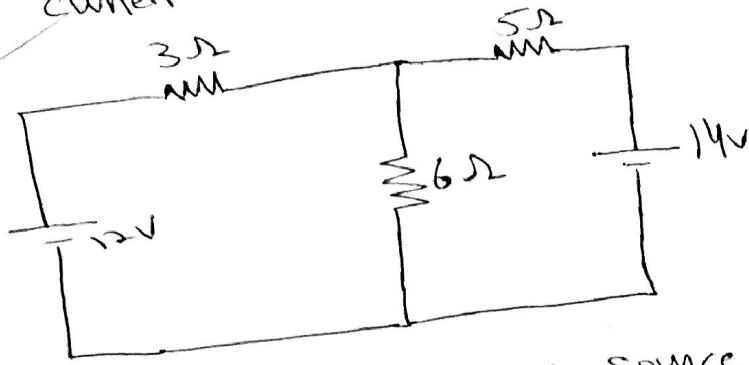Q:- Find current in 6Ω resistor using Superposition Theorem;



Soln:- First considering 12V source:-

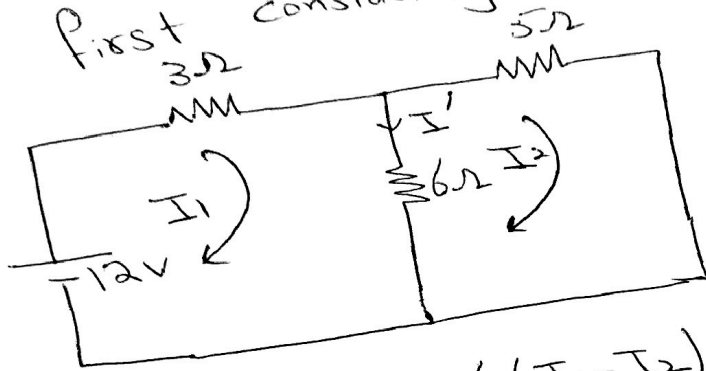

$$\begin{aligned} \text{mesh 1: } & 12 - 3I_1 - 6(I_1 - I_2) = 0 \\ & -3I_1 - 6I_1 + 6I_2 = -12 \\ & -9I_1 + 6I_2 = -12 \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{mesh 2: } & -6(I_2 - I_1) - 5I_2 = 0 \\ & -6I_2 + 6I_1 - 5I_2 = 0 \\ & 6I_1 - 11I_2 = 0 \quad \text{--- (2)} \end{aligned}$$

$$\begin{bmatrix} -9 & 6 \\ 6 & -11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -12 \\ 0 \end{bmatrix}$$


$$I_1 = 2.095 \text{ A}$$

$$I_2 = 1.14 \text{ A}$$

AS $I'_{(12V)} = I_1 - I_2$
 $I'_{(12V)} = 2.095 - 1.14$

$$I'_{(12V)} = 0.955 \text{ A}$$

Now taking 14V Source:-

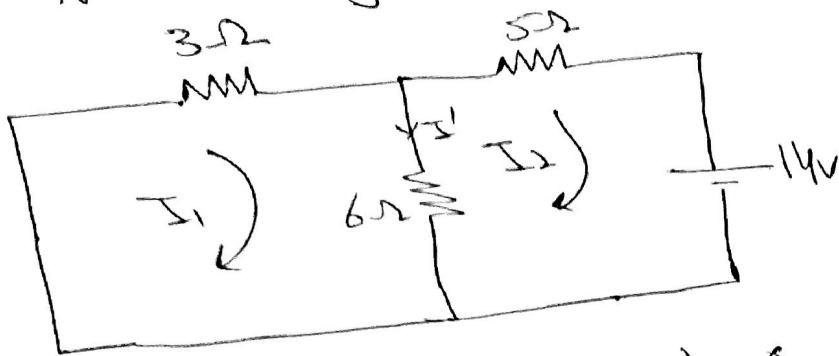

mesh (1):- $-3I_1 - 6(I_1 - I_2) = 0$
 $-3I_1 - 6I_1 + 6I_2 = 0$
 $-9I_1 + 6I_2 = 0$ — (1)

mesh (2):- $-5I_2 - 14 - 6(I_2 - I_1) = 0$
 $-5I_2 - 6I_2 + 6I_1 = 14$
 $6I_1 - 11I_2 = 14$ — (2)

$\Rightarrow I_1 = -1.33A, I_2 = -2A$

As $I'_{(14V)} = I_1 - I_2$
 $= -1.33 + 2$

$I'_{(14V)} = 0.67A$

Now $I = I'_{(12V)} + I'_{(14V)}$
 $= 0.955 + 0.67$

$I = 1.62A$