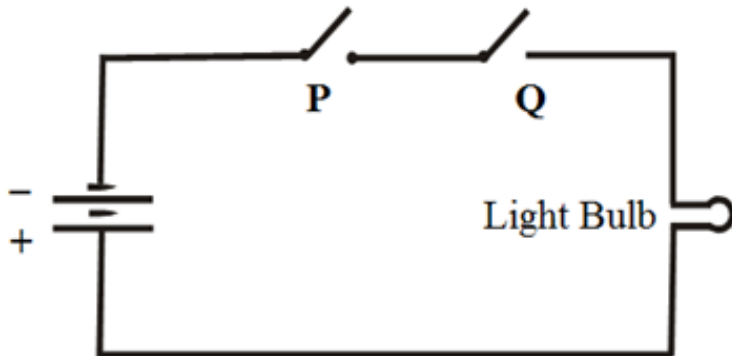


Lecture # 06
Discrete Structure

Switches in Series

- Circuit below consists of a battery, Light bulb, and two switches P and Q
- Both switches are open in both circuits
- An open switch means no current passes in the circuit
- A close switch means current passes in the circuit
- Switches are connected in series
- Light bulb is on only when both the switches are closed
- All the possibilities in the table below




| Switches | | Light Bulb |
|----------|--------|------------|
| P | Q | State |
| Closed | Closed | On |
| Closed | Open | Off |
| Open | Closed | Off |
| Open | Open | Off |

Switches in Series (Cont.)

- Replace **closed** and **on** by **T** and **open** and **off** by **F** then the table is same as truth table for conjunction ($P \wedge Q$)
- So both tables are equivalent

| Switches | | Light Bulb |
|----------|--------|------------|
| P | Q | State |
| Closed | Closed | On |
| Closed | Open | Off |
| Open | Closed | Off |
| Open | Open | Off |

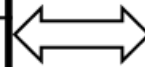


| P | Q | $P \wedge Q$ |
|---|---|--------------|
| T | T | T |
| T | F | F |
| F | T | F |
| F | F | F |

Switches in Parallel

- Now switches are connected in parallel
- Light bulb is on when at least one switch is closed
- All the possibilities in the table below

| Switches | | Light Bulb |
|----------|--------|------------|
| P | Q | State |
| Closed | Closed | On |
| Closed | Open | On |
| Open | Closed | On |
| Open | Open | Off |

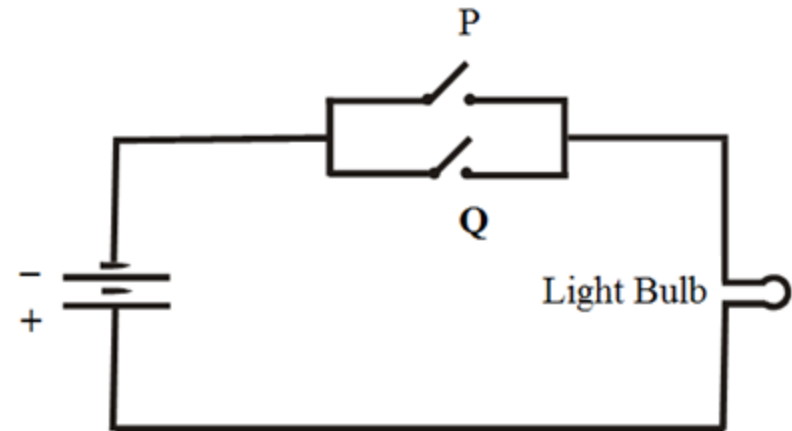

Switches in Parallel (Cont.)

- Replace **closed** and **on** by **T** and **open** and **off** by **F** then the table is same as truth table for disjunction ($P \vee Q$)
- So both tables are equivalent

| Switches | | Light Bulb |
|----------|--------|------------|
| P | Q | State |
| Closed | Closed | On |
| Closed | Open | On |
| Open | Closed | On |
| Open | Open | Off |



| P | Q | $P \vee Q$ |
|---|---|------------|
| T | T | T |
| T | F | T |
| F | T | T |
| F | F | F |

Digital Logic Gates


- Digital logic gates basic electronic components of a digital system
- Logic has important role in the digital circuits design
- Digital circuits process discrete, or separate, signals
- Generally bit 1 and bit 0 are used for T and F respectively

Basic Logic Gates

NOT Gate

- NOT gate is a circuit with one input & one output
- Also known as inverter
- If the input signal is 1, the output signal is 0
- Conversely, if the input signal is 0, then the output signal is 1

Symbolic Representation

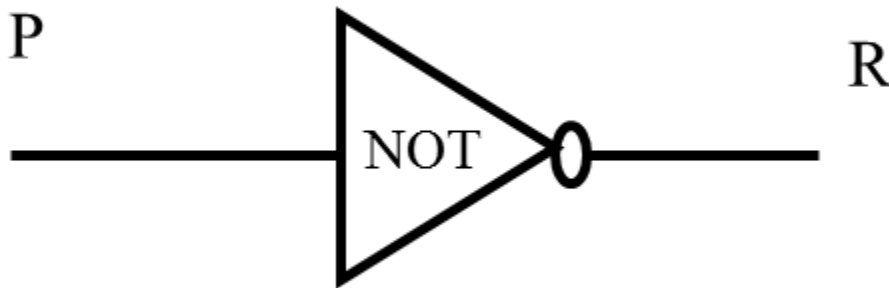

Input / Output Table


| Input | Output |
|-------|--------|
| P | R |
| 1 | 0 |
| 0 | 1 |

Basic Logic Gates (Cont.)

AND Gate

- AND gate is a circuit with two (or more) inputs and one output
- If both inputs are 1, the output is 1, else, the output is 0

Symbolic representation

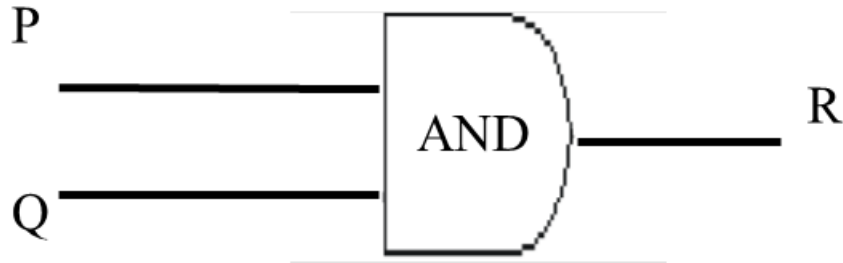

Input / Output Table


| Input | | Output |
|-------|---|--------|
| P | Q | R |
| 1 | 1 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 0 | 0 | 0 |

Basic Logic Gates (Cont.)

OR Gate

- OR gate is a circuit with two (or more) inputs and one output
- If both inputs are 0, then the output is 0, else, the output is 1

Symbolic representation

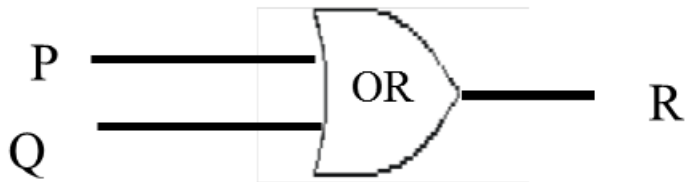


Input / Output Table

| Input | | Output |
|-------|---|--------|
| P | Q | R |
| 1 | 1 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 0 | 0 | 0 |

Combinational Circuit

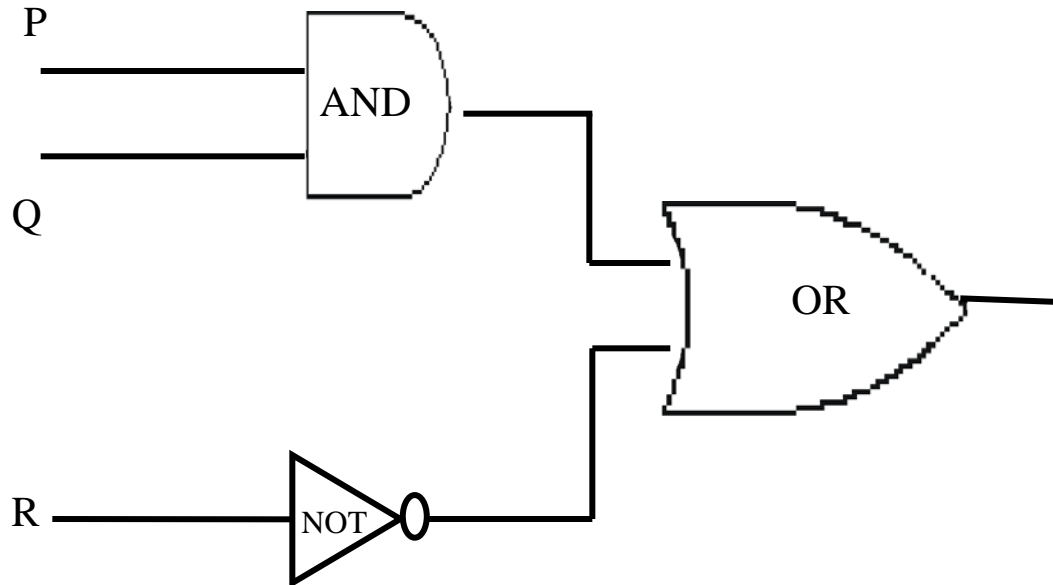- A Combinational Circuit is a compound circuit consisting of the basic logic gates such as NOT, AND, OR
- Figure shows a combinational logic circuit for logic expression $(P \wedge Q) \vee \sim R$



Rules of Forming Combinational Circuit


1. Inputs cannot be combined directly.
2. A single input can be split for two separate gates.
3. An output of a gate can be used as input for another gate.
4. No output of a gate can eventually feed back into that gate.

Determining Output for a Given Input

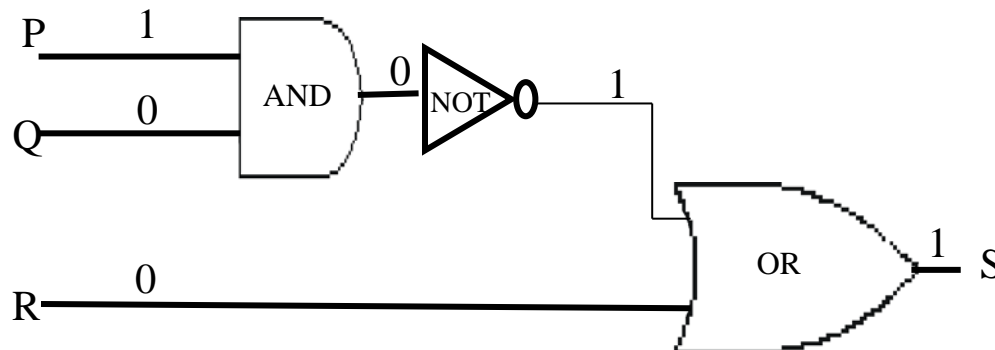Example: Indicate the output of the circuit below when the input signals are $P = 1$, $Q = 0$ and $R = 0$

Solution:


- Inputs are $P = 1$, $Q = 0$ and $R = 0$
- $P=1$ and $Q=0$ are Inputs to AND gate so the output will be 0
- This 0 output is the input to the NOT gate ,so output of the is 1
- This 1 output of NOT gate and $R = 0$ are input to OR gate thus producing a final output of 1



Output S = 1

Constructing the I/O Table for a Circuit

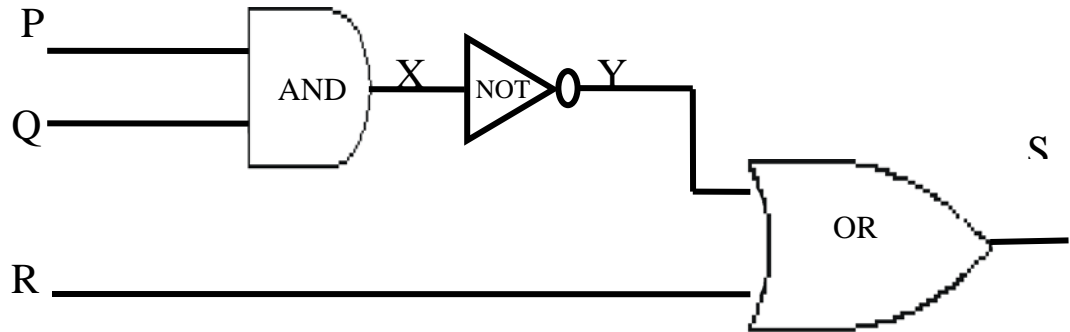- First label variables to inputs, intermediate outputs, and output as shown in figure
- There are 3 inputs P, Q and R, so I/O table have total $2^3 = 8$ rows
- First, fill the X column, which is the conjunction of P & Q
- Second, fill the Y column which is the negation of X
- Finally, fill the S column, which is the disjunction of Y and R




| P | Q | R | X | Y | S |
|---|---|---|---|---|---|
| 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 |

Boolean Expression

- Boolean expression is composed of Boolean variables and connectives \sim , \wedge , and \vee is called a Boolean expression
- Boolean variables that can take only two values i.e. 0 and 1
- In logic, variables such as p , q , and r represent statements, and a statement can have only two truth values
- input in a digital circuits, also take only one of the two values of 0 or 1
- So a statement variable or an input is treated as a Boolean variable

Finding a Boolean Expression for a Circuit

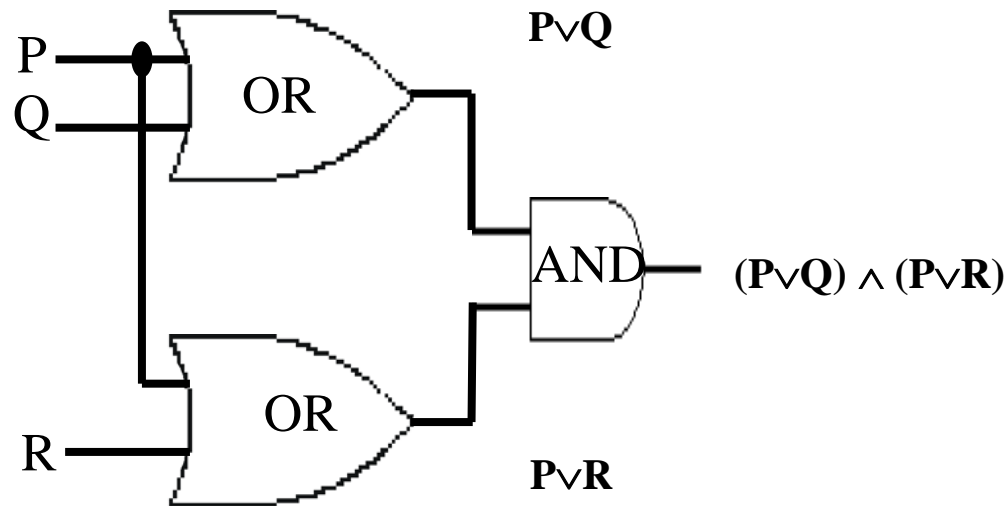- Trace through the circuit from left to right, writing down the output of each logic gate
- Hence $(P \vee Q) \wedge (P \vee R)$ is the Boolean expression for this circuit




Circuit Corresponding to a Boolean Expression

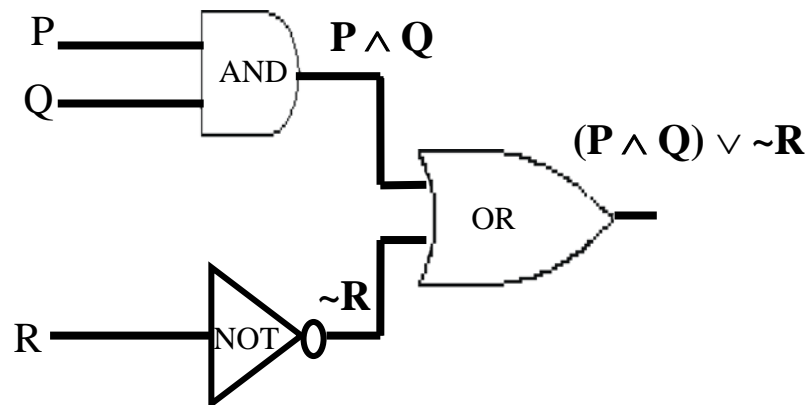Example: Construct circuit for the Boolean expression $(P \wedge Q) \vee \sim R$

Solution:

- There are three inputs P ,Q and R in the Boolean expression
- The conjunction b/w P & Q in the parenthesis tells that their must be an AND gate with inputs P and Q
- Then the negation of R gives information that we must have a “NOT gate” to convert the input R into $\sim R$
- Finally, the disjunction b/w $P \wedge Q$ and $\sim R$ can be implemented as OR gate with inputs $(P \wedge Q)$ and $\sim R$
- Circuit diagram below, is the implementation of the given Boolean expression




Circuit Corresponding to a Given I/O Table

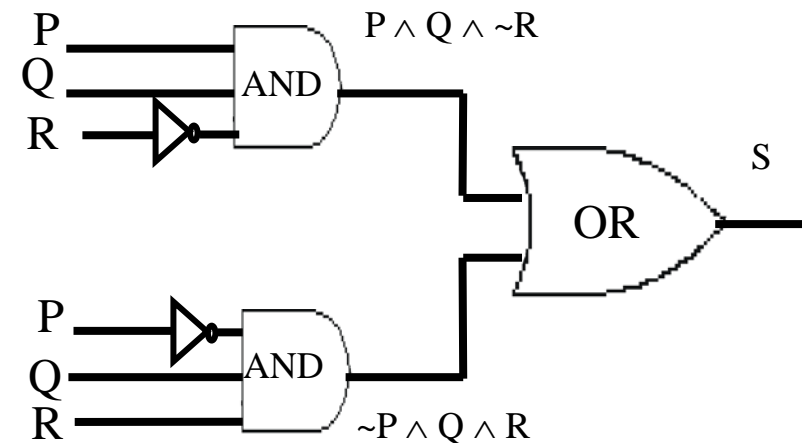Example: Design a circuit for the following input/output table.

Solution:

- First, find out the rows in the output columns where output is 1
- Second, write down the Boolean expression for these rows
- Finally, join these expressions using OR operator
- Hence the Boolean expression is $(P \wedge Q \wedge \sim R) \vee (\sim P \wedge Q \wedge R) = S$
- This Boolean expression can be implemented as logic circuit



| INPUTS | | | OUTPUT |
|--------|---|---|--------|
| P | Q | R | S |
| 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 |

$P \wedge Q \wedge \sim R$



$\sim P \wedge Q \wedge R$

Equivalent Circuits

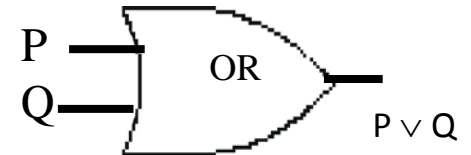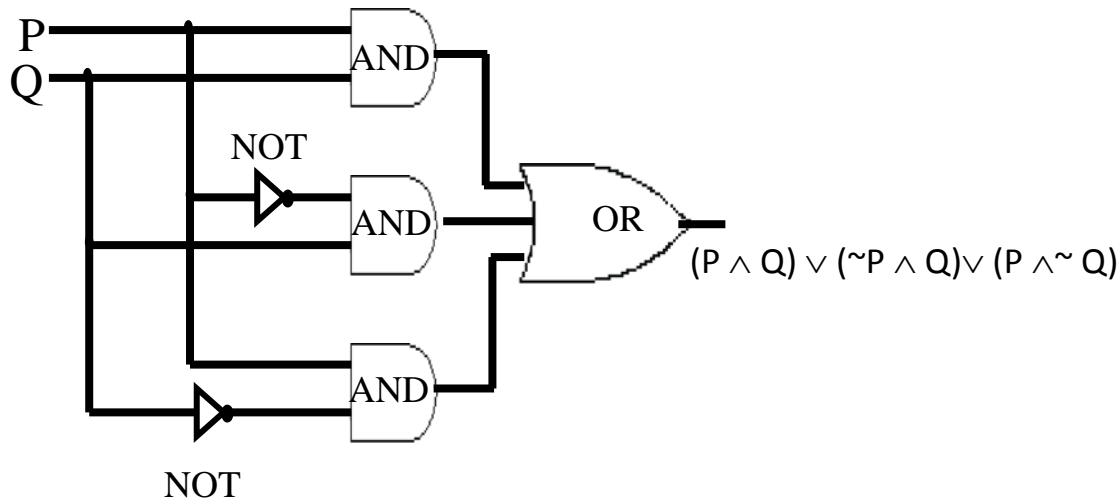Example: Show that the following pair of circuits are equivalent.

Solution:

- First, find the Boolean expressions for the circuits
- Then, show that they are logically equivalent using truth table or laws of logic



PTO

Equivalent Circuits (Cont.)

STATEMENT

REASON

$$(P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$$

$$\equiv (P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$$

$$\equiv (P \vee \sim P) \wedge Q \vee (P \wedge \sim Q)$$

Distributive law

$$\equiv t \wedge Q \vee (P \wedge \sim Q)$$

Negation law

$$\equiv Q \vee (P \wedge \sim Q)$$

Identity law

$$\equiv (Q \vee P) \wedge (Q \vee \sim Q)$$

Distributive law

$$\equiv (Q \vee P) \wedge t$$

Negation law

$$\equiv (Q \vee P) \wedge t$$

$$\equiv Q \vee P$$

Identity law

$$\equiv P \vee Q$$

Commutative law

$$\text{Thus } (P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q) \equiv P \vee Q$$

Accordingly, the two circuits are equivalent.