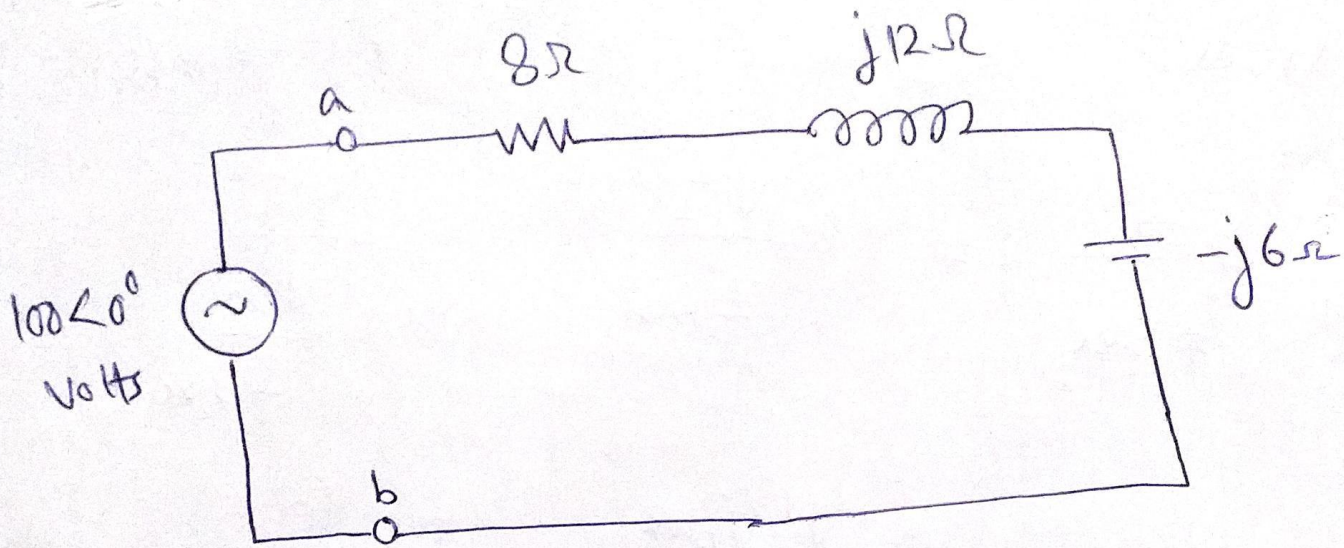


Assignment



From the following circuit:

(a) Solve for Z , I and S at point ab .

(b) Solve in P.U on basis of

$V_{base} = 100V$ and $S_{base} = 1000$