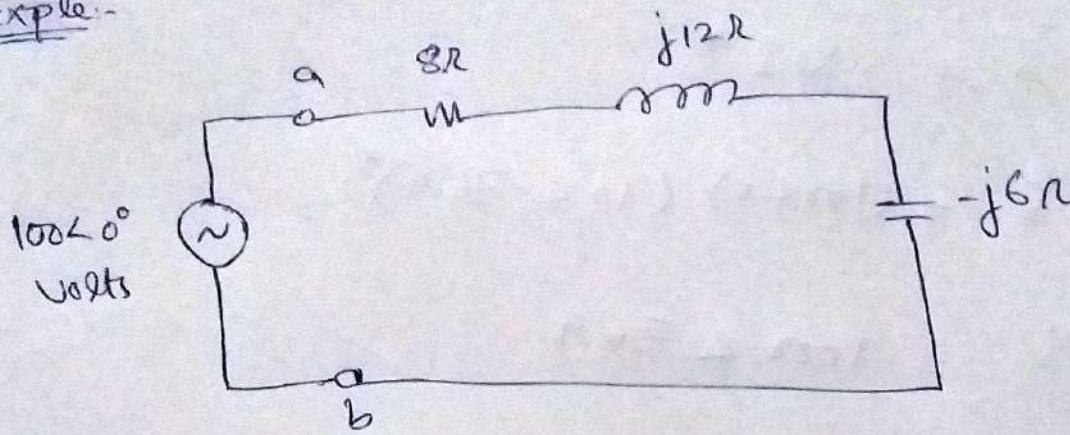


Exple:-



From the following circuit.

- (a) Solve for Z , I and S at port ab .
 (b) Solve in PU on basis of $V_{base} = 100V$
 and $S_{base} = 1000$.

Sol:-

$$\begin{aligned} \text{(a):- } Z_{ab} &= 8 + j12 - j6 \\ &= 8 + j6 \end{aligned}$$

$$Z_{ab} = 10 \angle 36.9^\circ \Omega$$

$$I = \frac{V_{ab}}{Z_{ab}}$$

$$I = \frac{100 \angle 0^\circ}{10 \angle 36.9^\circ}$$

$$I = 10 \angle -36.9^\circ \text{ A}$$

$$S = VI^*$$

$$S = (100 \angle 0) (10 \angle -36.9)^*$$

$$S = 1000 \angle 36.9$$

$$S = 800 + j600 \text{ VA}$$

\downarrow \downarrow \downarrow
 Apparent Power Real Power Reactive Power

$$P = 800 \text{ W} \quad ; \quad Q = 600 \text{ VAR}$$

(b) on the basis of V_{base} and S_{base}

$$Z_{\text{base}} = \frac{V_{\text{base}}^2}{S_{\text{base}}}$$

$$Z_{\text{base}} = \frac{(100)^2}{1000}$$

$$Z_{\text{base}} = 10 \Omega$$

$$I_{\text{base}} = \frac{S_{\text{base}}}{V_{\text{base}}} = \frac{1000}{100} = 10 \text{ A}$$

$$V_{p.u} = \frac{100 \angle 0}{100}$$

$$V_{p.u} = 1 \angle 0^\circ \text{ p.u.}$$

$$Z_{p.u} = \frac{10 \angle 36.9^\circ}{10}$$

$$Z_{p.u} = 1 \angle 36.9^\circ \text{ p.u.}$$

$$I_{p.u} = \frac{V_{p.u}}{Z_{p.u}}$$

$$I_{p.u} = \frac{1 \angle 0^\circ}{1 \angle 36.9^\circ}$$

$$I_{p.u} = 1 \angle -36.9^\circ \text{ p.u.}$$

$$S_{p.u} = V_{p.u} I_{p.u}^*$$

$$S_{p.u} = (1 \angle 0^\circ) (1 \angle -36.9^\circ)^*$$

$$S_{p.u} = 1 \angle 36.9^\circ \text{ p.u.}$$

Converting to SI Units:-

$$I = (I_{p.u}) (I_{base})$$

$$I = (1 \angle -36.9^\circ) (10)$$

$$I = 10 \angle -36.9^\circ \text{ A}$$

$$Z = (Z_{p.u}) (Z_{base})$$

$$Z = (1 \angle 36.9^\circ) (10)$$

$$Z = 10 \angle 36.9^\circ \Omega$$

OR

$$Z = 8 + j6 \Omega$$

$$S = (S_{p.u}) (S_{base})$$

$$S = (0.8 + j0.6) (1000)$$

$$S = 800 + j600 \text{ VA}$$

④ Equivalent Impedance of Transformer in P.U. :-

Let us consider a transformer having Z_1 and Z_2 , The equivalent impedance referred to primary and secondary. If V_p and V_s are the primary and secondary voltages and are taken as base. Similarly I_p and I_s are also taken as base.

Base impedance in primary circuit = V_p / I_p

Base impedance in secondary circuit = V_s / I_s

From transformer equation:

$$\text{Let } \boxed{V_p/V_s = I_s/I_p = N_p/N_s = K} \rightarrow \textcircled{1}$$

From eq ①:

$$V_p = K V_s \rightarrow \textcircled{2}$$

$$I_p = \frac{1}{K} I_s \rightarrow \textcircled{3}$$

Impedance of Primary:

$$Z_p = \frac{V_p}{I_p} = \frac{K V_s}{\frac{1}{K} I_s}$$

$$Z_p = K^2 \frac{V_s}{I_s}$$

$$Z_p = K^2 Z_s$$

$$\boxed{Z_p = Z_1 = K^2 Z_2} \rightarrow \textcircled{4}$$

Now in P.U

$$Z_{1, P.U} = \frac{Z_1}{Z_2} = Z_1 / VP/IP$$

$$Z_{1, P.U} = Z_1 * \frac{IP}{VP}$$

(Actual value)
Base value

$$Z_{2, P.U} = Z_2 * \frac{IS}{VS}$$

$$Z_{1, P.U} = K^2 Z_2 * \frac{\frac{1}{K} IS}{\frac{K VS}{1}}$$

$$Z_{1, P.U} = K^2 Z_2 * \frac{1}{K} IS * \frac{1}{K VS}$$

$$Z_{1, P.U} = Z_2 \cdot \frac{IS}{VS}$$


$$\boxed{Z_{1, P.U} = Z_{2, P.U}}$$

Hence P.U equivalent Impedence of T/F is
Same referred to primary or secondary

* Per Unit Impedance of Three Winding

Transformer :-

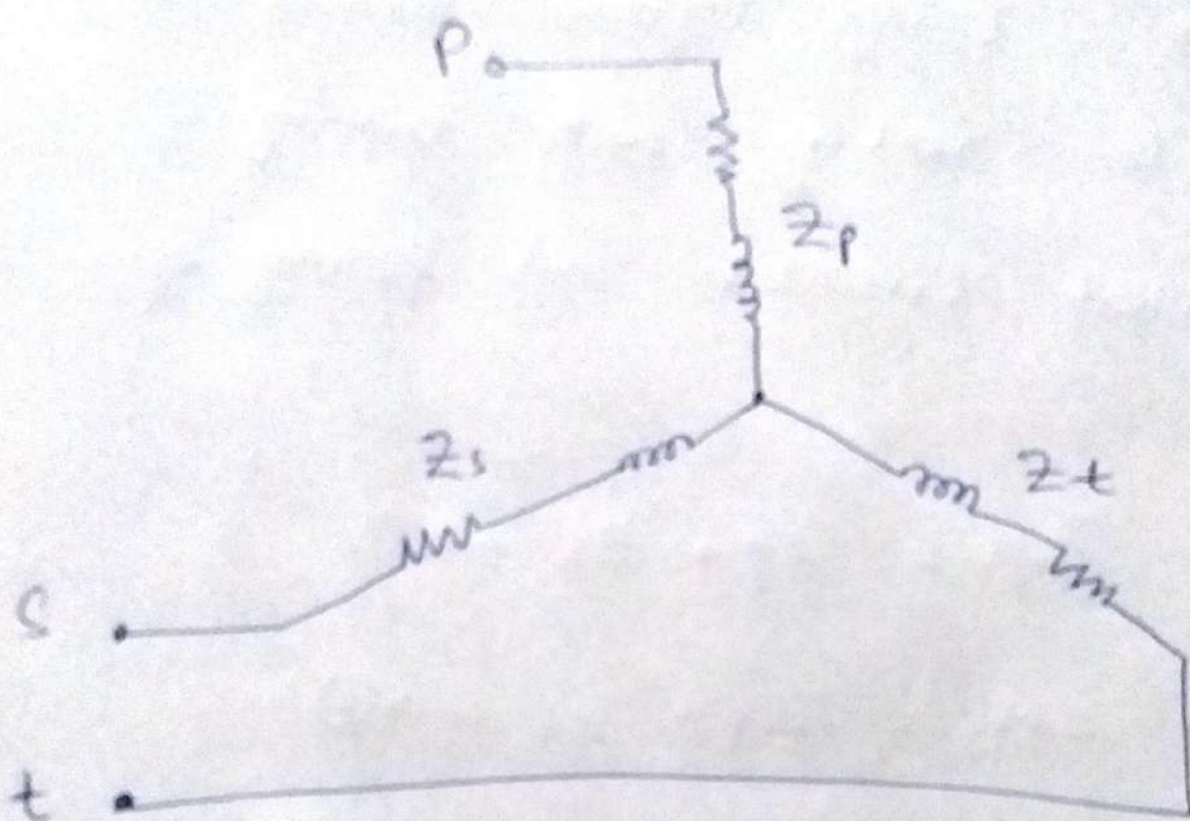Both the Primary and Secondary windings of a two-winding transformer have the same KVA ratings but all three windings of a three winding transformer may have different KVA ratings. The equivalent circuit of a three winding transformer is shown below :-



Let Z_{ps} = Leakage impedance measured in primary with secondary short circuited and tertiary open.

Z_{pt} = Leakage impedance measured in primary with tertiary short and secondary open.

Z_{st} = Leakage impedance measured
in secondary with tertiary
short circuited and primary open.

Then

$$Z_{ps} = Z_p + Z_s \rightarrow (1)$$

$$Z_{pt} = Z_p + Z_t \rightarrow (2)$$

$$Z_{st} = Z_s + Z_t \rightarrow (3)$$

Solving for Z_p , Z_s and Z_t

We get:-

for Z_p :- Adding eq (1) & eq (2)

$$Z_{ps} = Z_p + Z_s$$

$$Z_{pt} = Z_p + Z_t$$

$$Z_{ps} + Z_{pt} = 2Z_p + (Z_s + Z_t)$$

$$2z_p = z_{ps} + z_{pt} - (z_s + z_t)$$

$$\therefore z_s + z_t = z_{st}$$

$$z_p = \frac{1}{2} (z_{ps} + z_{pt} - z_{st})$$

Similarly for z_s

adding eq(1) and eq(3)

$$z_s = \frac{1}{2} (z_{ps} + z_{st} - z_{pt})$$

For

$$z_t = \frac{1}{2} (z_{pt} + z_{st} - z_{ps})$$