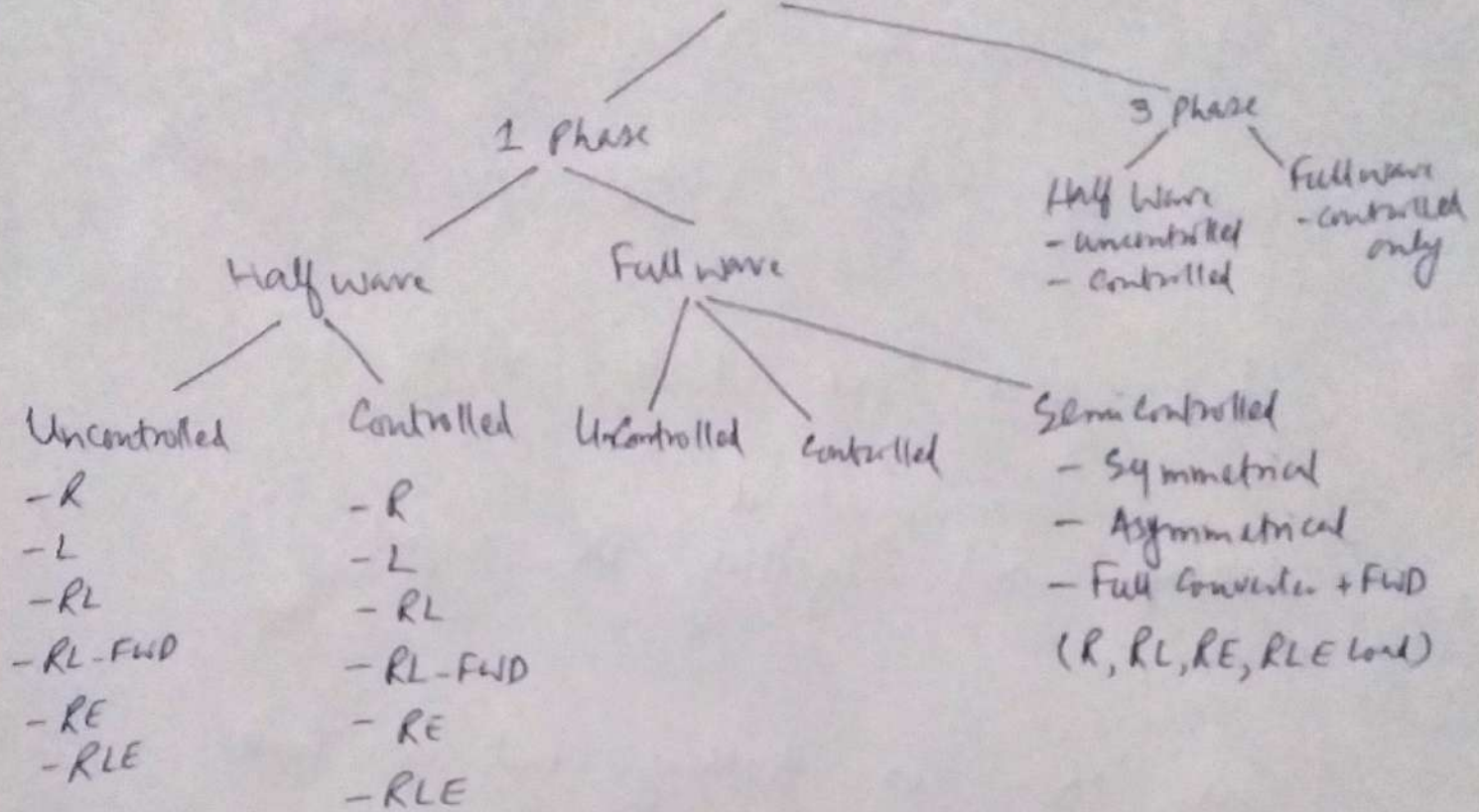



Rectifier Module



In this lecture we will cover 1-Phase

Half wave Diode Uncontrolled rectifier

with R and L load.

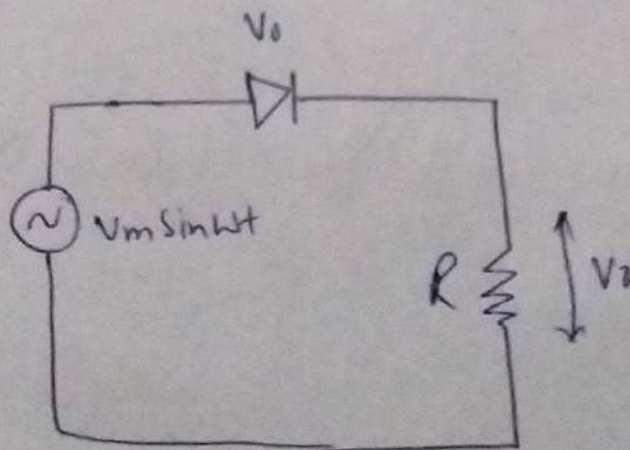


This is a single phase half wave uncontrolled rectifier.

Here we are given AC voltage
and get DC voltage on the output

I connect one diode with ac
source and ^{converting it} getting DC signal.

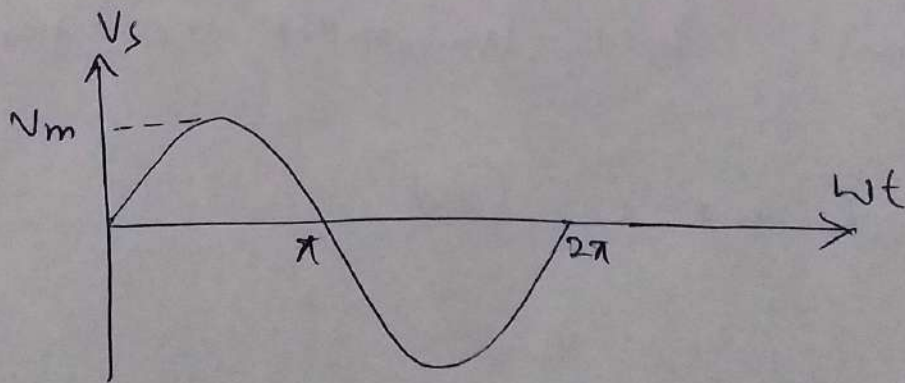See this is nothing but a diode
with R load.



$V_m \sin \omega t$ will be like this
shown above.

When anode potential is greater than cathode potential


$$V_A > V_K$$

This diode will act like conducting. i.e from 0 to π

this diode will conducting.


So,
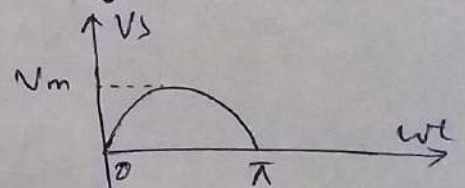
$$V_o = V_s \text{ (0 to } \pi \text{)}$$



Now when supply voltage get

reversed means

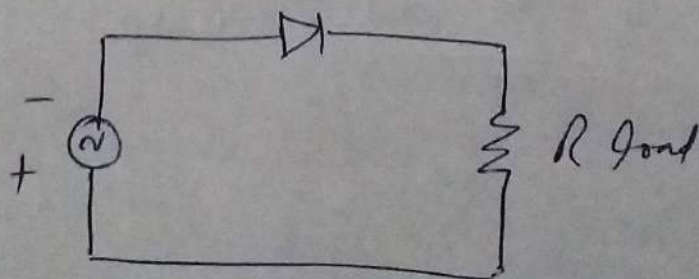

Now supply is reversed from π to 2π . Now diode is reversed bias and act as open circuit. Now Anode is -ive and Cathode is +ive.

$$V_o = I_o R$$

$$I_o = 0 \text{ so } \boxed{V_o = 0}$$

So we can say that

form


$$\underline{\underline{0 \text{ to } \pi}}$$

$$V_{\text{output}} = V_s = V_m \sin \omega t$$

$$\underline{\underline{\pi \text{ to } 2\pi}}$$

$$V_{\text{output}} = 0$$

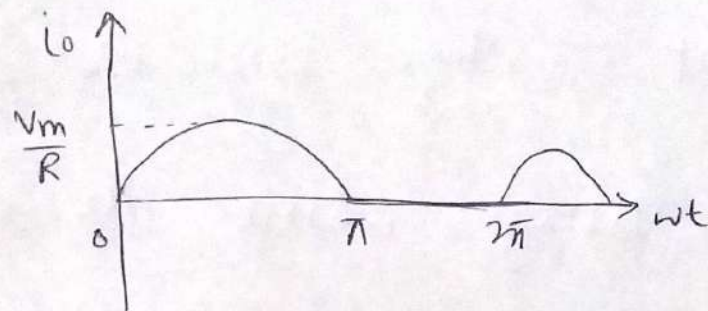
Here output current is equal
to output voltage S_o



$$S_o \quad I_o = \frac{V_m}{R}$$

Now see the voltage across the diode.

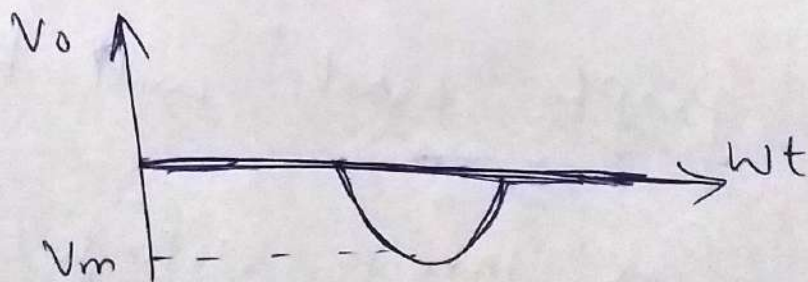From $0 - \pi$ Diode is conducting means it is shorted.



Means voltage across the diode

will be zero and from

$\pi - 2\pi$ it is acting like

open circuited.

Now applying KVL.

Output voltage will be zero

and voltage across the diode

V_D will be same as

the supply voltage.

So if I will ask from
you people what will be

the Peak inverse Voltage (PIV)

So $\boxed{PIV = V_m}$ and always +ive

So we are getting output
voltage only from 0 to π

means we are getting only one
pulse ^{in one cycle} \uparrow So ~~it~~ this type of

circuit is called one pulse
converter.

Now take a Note and This
type of note is important for
all type of rectifier.

Despite of changing of load.
i.e R, L, RL, RE etc.

Note:-

$$\textcircled{1} \quad V_{\text{avg}} = \frac{1}{T} \int_0^T V_0 dt$$

$$V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t d\omega t$$

$$V_{\text{avg}} = \frac{V_m}{\pi}$$

$$\textcircled{2} \quad I_{0 \text{ avg}} = \frac{V_{0 \text{ avg}}}{R}$$

$$I_{0 \text{ avg}} = \frac{V_m}{\pi R}$$

$$\textcircled{3} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V_0^2(t) dt}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} V_m^2 \int_0^{2\pi} (1 - \frac{\cos 2\omega t}{2}) d\omega t}$$

$$V_{rms} = \frac{V_m}{2}$$

$$(4) \quad I_{orms} = \frac{V_{orms}}{R}$$

$$(5) \quad P_o = \text{Output Power} = \frac{V_{orms}^2}{R} = I_{orms}^2 R$$

$$(6) \quad \text{Input Power Factor, IPF} \Rightarrow P_{in} = P_o$$

$$\text{Losses} = \text{zero}$$

$$P_{in} = P_{out}$$

$$V_s I_s \cos \phi = I_{orms}^2 R$$

Here source Rms current is equal to

output Rms current.

$$\therefore I_s = I_{orms}$$

So finally $\cos \phi = \frac{I_{or} R}{V_s} = \frac{V_{or}}{V_s}$ }

So If Input Power Factor is to be determined, no need to remember this whole formula but only remember

$$P_{in} = P_o$$

and see whether the source current is equal to the output RMS current or not.

If source current is equal to output RMS current then cut the source current = I_{or} and then find Power Factor.

$$\text{IPF} = \frac{V_{or}}{V_s}$$

⑦ Conduction angle of diode = γ (Gamma)
and Diode is conducting from $0 - \pi$

$$\gamma_D = \pi$$

⑧ Extension Angle, β = upto what angle diode is conducting. upto what angle you are getting current.

$$\beta = \pi$$

In this case $\gamma_D = \beta$ (In all the Diode rectifier)

⑨ Peak Inverse Voltage, $\text{PIV} = V_m$

⑩ Circuit turnoff time, t_c = The time for which the diode is in reverse bias.

$$W t_c = \pi$$

$$t_c = \pi / W$$

So these all points, I will derive for every type of converters for different types of load.

This is taken as a note, so that it will be easier to remember. And that's all about the R load.