

## Department of Electrical Engineering

### Assignment

Date: 22/08/2020

#### Course Details

Course Title: Network Analysis-I

Module: 4rth



Instructor: \_\_\_\_\_


Total Marks: 30

#### Student Details

Name: \_\_\_\_\_

Student ID: \_\_\_\_\_

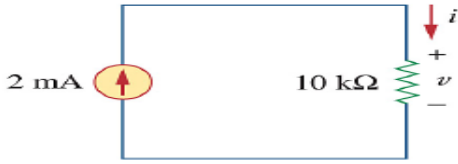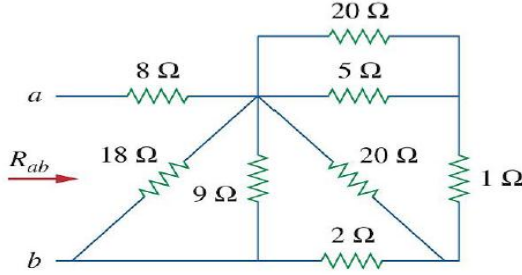Q1	(a)	For the circuit shown below, calculate the voltage $V$ , the conductance $G$ , and the power $P$ .	Marks 05 CLO 1
			
	(b)	A resistor absorbs an instantaneous power of $20 \cos^2(t) \text{ mW}$ when connected to a voltage source $V = 10 \cos(t) \text{ v}$ . Find $I$ and $R$ ?	Marks 05 CLO 1
Q2	(a)	Find $R_{ab}$ for the circuit given below.	Marks 10 CLO 1
			
Q3	(a)	Find $V_1$ and $V_2$ for the circuit shown below. Also calculate $i_1$ and $i_2$ and the power dissipated in the $12\Omega$ and $40\Omega$ resistors.	Marks 05 CLO 2

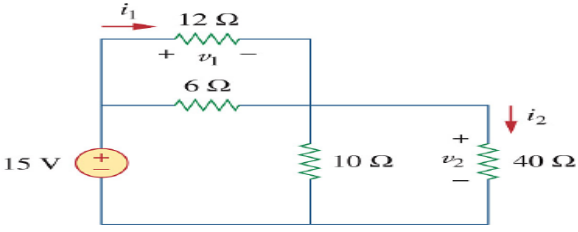		
(b)	<p>The essential component of a toaster is an electrical element (a resistor) that converts electrical energy to heat energy. How much current is drawn by a toaster with resistance <math>10\Omega</math> at <math>110V</math>?</p>	<p>Marks 05 CLO 2</p>

☺Good Luck☺