

### 13.5 Distributor Fed at Both Ends — Concentrated Loading

Whenever possible, it is desirable that a long distributor should be fed at both ends instead of at one end only, since total voltage drop can be considerably reduced without increasing the cross-section of the conductor. The two ends of the distributor may be supplied with (i) equal voltages (ii) unequal voltages.

- (i) **Two ends fed with equal voltages.** Consider a distributor  $AB$  fed at both ends with equal voltages  $V$  volts and having concentrated loads  $I_1, I_2, I_3, I_4$  and  $I_5$  at points  $C, D, E, F$  and  $G$  respectively as shown in Fig. 13.14. As we move away from one of the feeding points, say  $A$ , p.d. goes on decreasing till it reaches the minimum value at some load point, say  $E$ , and then again starts rising and becomes  $V$  volts as we reach the other feeding point  $B$ .

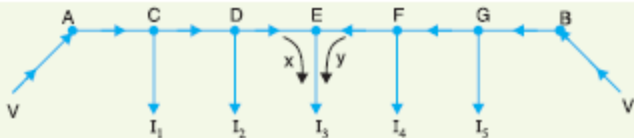


Fig. 13.14

All the currents tapped off between points  $A$  and  $E$  (minimum p.d. point) will be supplied from the feeding point  $A$  while those tapped off between  $B$  and  $E$  will be supplied from the feeding point  $B$ . The current tapped off at point  $E$  itself will be partly supplied from  $A$  and partly from  $B$ . If these currents are  $x$  and  $y$  respectively, then,

$$I_3 = x + y$$

Therefore, we arrive at a very important conclusion that at the point of minimum potential, current comes from both ends of the distributor.

**Point of minimum potential.** It is generally desired to locate the point of minimum potential. There is a simple method for it. Consider a distributor  $AB$  having three concentrated loads  $I_1, I_2$  and  $I_3$  at points  $C, D$  and  $E$  respectively. Suppose that current supplied by feeding end  $A$  is  $I_A$ . Then current distribution in the various sections of the distributor can be worked out as shown in Fig. 13.15 (i). Thus

$$I_{AC} = I_A;$$

$$I_{CD} = I_A - I_1$$

$$I_{DE} = I_A - I_1 - I_2;$$

$$I_{EB} = I_A - I_1 - I_2 - I_3$$

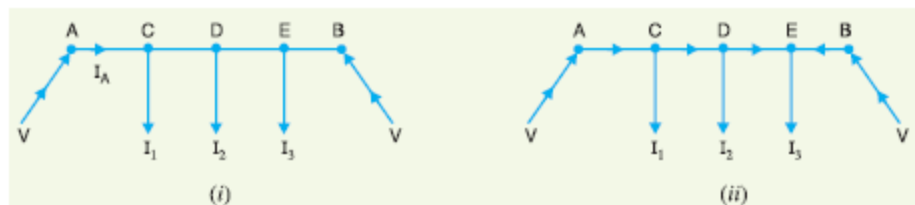


Fig. 13.15

Voltage drop between  $A$  and  $B$  = Voltage drop over  $AB$

$$\text{or } V - V = I_A R_{AC} + (I_A - I_1) R_{CD} + (I_A - I_1 - I_2) R_{DE} + (I_A - I_1 - I_2 - I_3) R_{EB}$$

From this equation, the unknown  $I_A$  can be calculated as the values of other quantities are generally given. Suppose *actual* directions of currents in the various sections of the distributor are indicated as shown in Fig. 13.15 (ii). The load point where the currents are coming from both sides of the distributor is the point of minimum potential *i.e.* point  $E$  in this case

**(ii) Two ends fed with unequal voltages.** Fig. 13.16 shows the distributor  $AB$  fed with unequal voltages; end  $A$  being fed at  $V_1$  volts and end  $B$  at  $V_2$  volts. The point of minimum potential can be found by following the same procedure as discussed above. Thus in this case,

Voltage drop between  $A$  and  $B$  = Voltage drop over  $AB$

$$\text{or } V_1 - V_2 = \text{Voltage drop over } AB$$

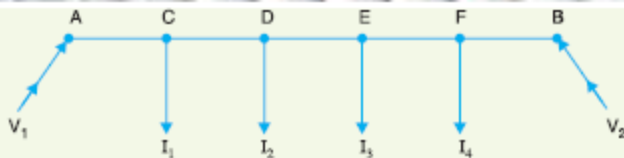


Fig. 13.16

**Example 13.10.** A 2-wire d.c. street mains AB, 600 m long is fed from both ends at 220 V. Loads of 20 A, 40 A, 50 A and 30 A are tapped at distances of 100 m, 250 m, 400 m and 500 m from the end A respectively. If the area of X-section of distributor conductor is  $1 \text{ cm}^2$ , find the minimum consumer voltage. Take  $\rho = 1.7 \times 10^{-6} \Omega \text{ cm}$ .

**Solution.** Fig. 13.17 shows the distributor with its tapped currents. Let  $I_A$  amperes be the current supplied from the feeding end A. Then currents in the various sections of the distributor are as shown in Fig. 13.17.

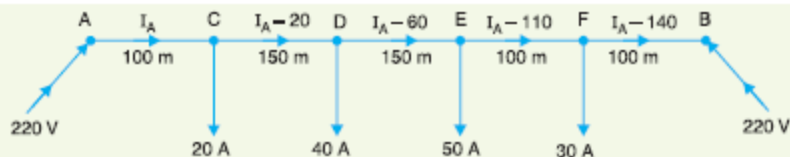


Fig. 13.17

Resistance of 1 m length of distributor

$$= 2 \times \frac{1.7 \times 10^{-6} \times 100}{1} = 3.4 \times 10^{-4} \Omega$$

Resistance of section AC,  $R_{AC} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section CD,  $R_{CD} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section DE,  $R_{DE} = (3.4 \times 10^{-4}) \times 150 = 0.051 \Omega$

Resistance of section EF,  $R_{EF} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Resistance of section FB,  $R_{FB} = (3.4 \times 10^{-4}) \times 100 = 0.034 \Omega$

Voltage at B = Voltage at A - Drop over length AB

$$\text{or } V_B = V_A - [I_A R_{AC} + (I_A - 20) R_{CD} + (I_A - 60) R_{DE} + (I_A - 110) R_{EF} + (I_A - 140) R_{FB}]$$

$$\text{or } 220 = 220 - [0.034 I_A + 0.051 (I_A - 20) + 0.051 (I_A - 60) + 0.034 (I_A - 110) + 0.034 (I_A - 140)]$$

$$= 220 - [0.204 I_A - 12.58]$$

$$\text{or } 0.204 I_A = 12.58$$

$$\therefore I_A = 12.58 / 0.204 = 61.7 \text{ A}$$

The \*actual distribution of currents in the various sections of the distributor is shown in Fig. 13.18. It is clear that currents are coming to load point E from both sides i.e. from point D and point F. Hence, E is the point of minimum potential.

$\therefore$  Minimum consumer voltage,

$$V_E = V_A - [I_{AC} R_{AC} + I_{CD} R_{CD} + I_{DE} R_{DE}]$$

**Example 13.11.** A 2-wire d.c. distributor AB is fed from both ends. At feeding point A, the voltage is maintained as at 230 V and at B 235 V. The total length of the distributor is 200 metres and loads are tapped off as under :

25 A at 50 metres from A ; 50 A at 75 metres from A

30 A at 100 metres from A ; 40 A at 150 metres from A

The resistance per kilometre of one conductor is 0.3  $\Omega$ . Calculate :

- currents in various sections of the distributor
- minimum voltage and the point at which it occurs

**Solution.** Fig. 13.19 shows the distributor with its tapped currents. Let  $I_A$  amperes be the current supplied from the feeding point A. Then currents in the various sections of the distributor are as shown in Fig. 13.19.

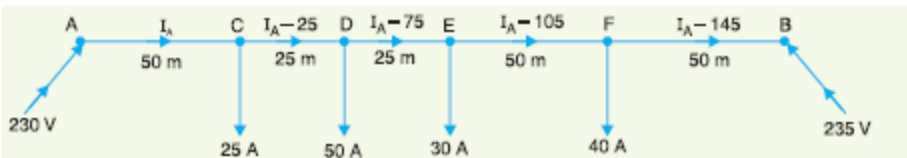


Fig. 13.19

Resistance of 1000 m length of distributor (both wires)

$$= 2 \times 0.3 = 0.6 \Omega$$

Resistance of section AC,  $R_{AC} = 0.6 \times 50/1000 = 0.03 \Omega$

Resistance of section CD,  $R_{CD} = 0.6 \times 25/1000 = 0.015 \Omega$

Resistance of section DE,  $R_{DE} = 0.6 \times 25/1000 = 0.015 \Omega$

Resistance of section EF,  $R_{EF} = 0.6 \times 50/1000 = 0.03 \Omega$

Resistance of section FB,  $R_{FB} = 0.6 \times 50/1000 = 0.03 \Omega$

Voltage at B = Voltage at A - Drop over AB

$$\text{or } V_B = V_A - [I_A R_{AC} + (I_A - 25)R_{CD} + (I_A - 75)R_{DE} + (I_A - 105)R_{EF} + (I_A - 145)R_{FB}]$$

$$\text{or } 235 = 230 - [0.03 I_A + 0.015 (I_A - 25) + 0.015 (I_A - 75) + 0.03 (I_A - 105) + 0.03 (I_A - 145)]$$

$$\text{or } 235 = 230 - [0.12 I_A - 9]$$

$$\therefore I_A = \frac{239 - 235}{0.12} = 33.34 \text{ A}$$

- (i)  $\therefore$  Current in section AC,  $I_{AC} = I_A = 33.34 \text{ A}$   
 Current in section CD,  $I_{CD} = I_A - 25 = 33.34 - 25 = 8.34 \text{ A}$